

Using the principle similar to those used in the bit-serial adder and the shift-and-add multiplier presented in class, design the data-path for a *bit-serial 4-bit unsigned multiplier*. Your circuit should use one flip-flop, several shift registers, and only one full-adder cell. Draw the circuit diagram and write down the control algorithm. How many cycles does your circuit take to perform 4-bit multiplication?