

**University of California at Berkeley**  
**College of Engineering**  
**Department of Electrical Engineering and Computer Sciences**

EECS150  
Spring 2000

J. Wawrzynek  
E. Caspi

Quiz #9 – Solution

- (a) The 1-bit subtractor computes:  $d = x - y - b_{in}$ , passing a borrow  $b_{out}$  to the right. The truth table for  $d$  and  $b_{out}$  follows:

x	y	$b_{in}$	d	$b_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

The difference output  $d$  is identical to the sum output of a full adder. It is expressed most simply using XORs:  $d = x \oplus y \oplus b_{in}$ .

The borrow output  $b_{out}$  is not so familiar. We derive its reduced expression using a Karnaugh map:  $b_{out} = x'b_{in} + x'y + yb_{in}$ .

		$b_{in}$	
		0	1
$x\ y$	00	0	1
	01	1	1
	11	0	1
	10	0	0

- (b) A ripple subtractor can be formed by cascading several 1-bit subtractors with a *borrow-chain*. This construction is similar to a ripple adder with a *carry-chain*.

