

Outline


- Last time:
 - Introduction to Computer Organization
 - Control
 - Datapath
 - I/O Interface
 - Bussing Strategies
- This lecture:
 - Deriving the State Diagram & Datapath (Cont.)
 - Mapping the Datapath onto Control

Finite State Machines for Simple CPUs

State Diagram and Datapath Derivation

Processor Specification:

Instruction Format:

 

Op 00 = LD
 Code 01 = ST
 10 = ADD
 11 = BRN


Load from memory: Mem[XXX] @ AC;

Store to memory: AC @ Mem[XXX];

Add from memory: AC + Mem[XXX] @ AC;

Branch if accumulator is negative: AC < 0 ? XXX @ PC;


Memory Interface:

 

Finite State Machines for Simple CPUs

Deriving the State Diagram and Datapath

First pass state diagram:

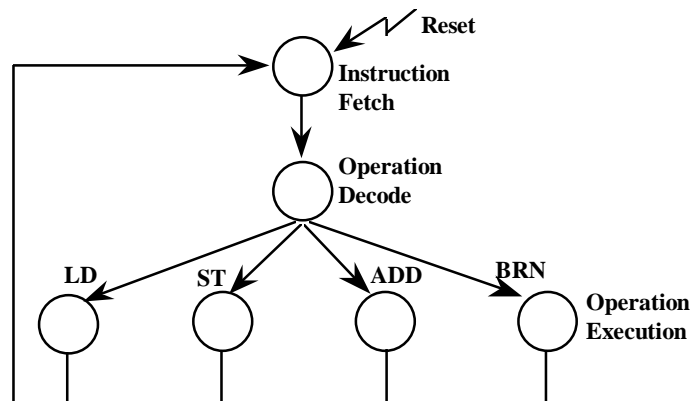


CS150 Newton/Pister

11.2.3

Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:
Transitions associated with arcs rather than states

 **Reset State (State 0)
and Instruction Fetch
Sequence**



On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal

CS150 Newton/Pister

11.2.4


Deriving the State Diagram and Datapath

Assume Synchronous Mealy Machine:
Transitions associated with arcs rather than states

Reset State (State 0) and Instruction Fetch Sequence

On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal

 Instruction Fetch:
issue read request
4 cycle handshake on Wait signal



Deriving the State Diagram and Datapath


Assume Synchronous Mealy Machine:
Transitions associated with arcs rather than states

Reset State (State 0) and Instruction Fetch Sequence

On Reset:
zero the PC
Mem Request unasserted
Mem asserts Wait signal


Instruction Fetch:
issue read request
4 cycle handshake on Wait signal

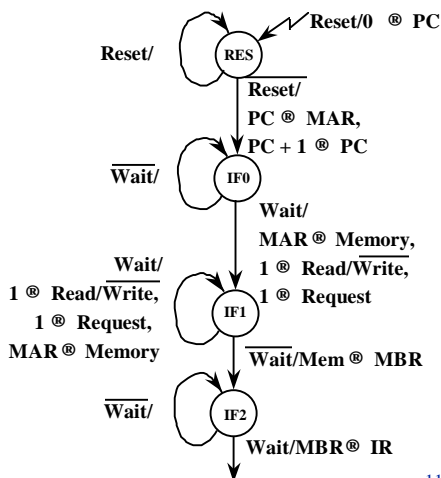Note: No explicit mention of the
busses being used to implement
register transfers!



Deriving the State Diagram and Datapath

Operation Decode State

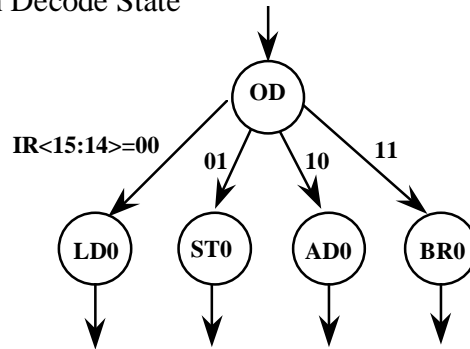


Four Way Next State Branch based on opcode bits

Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

 like IFetch, except that
operand address comes
from IR and data should
be loaded into AC




Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

 like IFetch, except that operand address comes from IR and data should be loaded into AC




Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

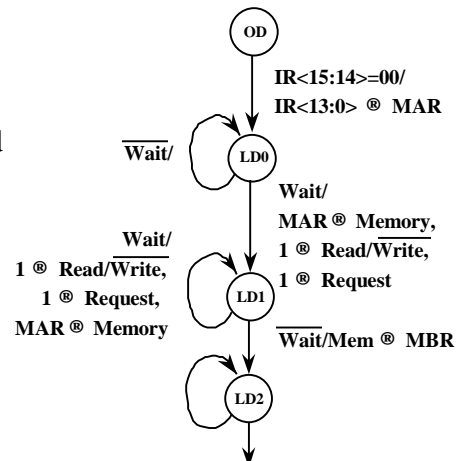like IFetch, except that operand address comes from IR and data should be loaded into AC




Deriving the State Diagram and Datapath

Execution Sequences

Load Sequence

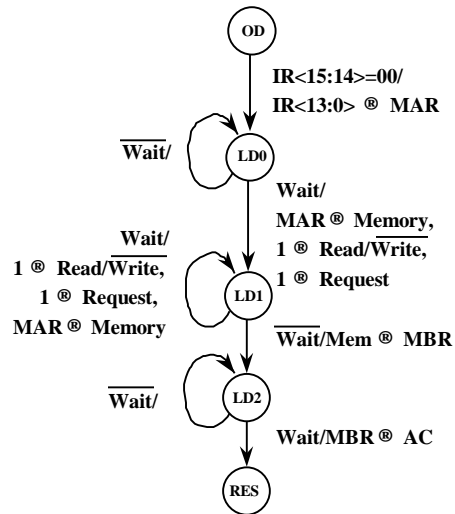like IFetch, except that operand address comes from IR and data should be loaded into AC




CS150 Newton/Pister

11.2.11

Deriving the State Diagram and Datapath

Store Execution Sequence

Memory write sequence

 


CS150 Newton/Pister

11.2.12

Deriving the State Diagram and Datapath

Store Execution Sequence


Memory write sequence

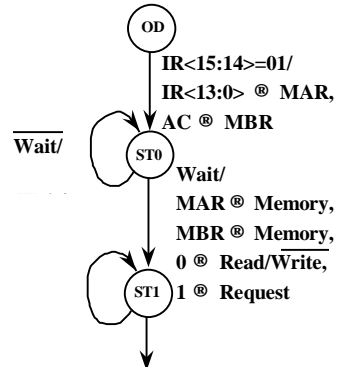

Deriving the State Diagram and Datapath

Store Execution Sequence


Memory write sequence

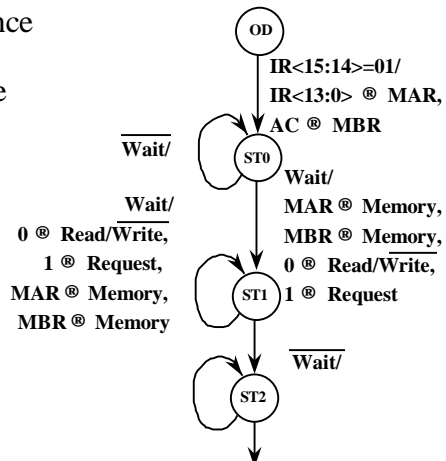

Deriving the State Diagram and Datapath

Add Execution Sequence

 
Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC



Deriving the State Diagram and Datapath


Add Execution Sequence

 Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC



Deriving the State Diagram and Datapath

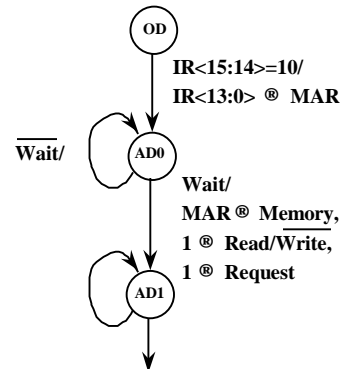
Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC



Deriving the State Diagram and Datapath

Add Execution Sequence

 
Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC



Deriving the State Diagram and Datapath

Add Execution Sequence

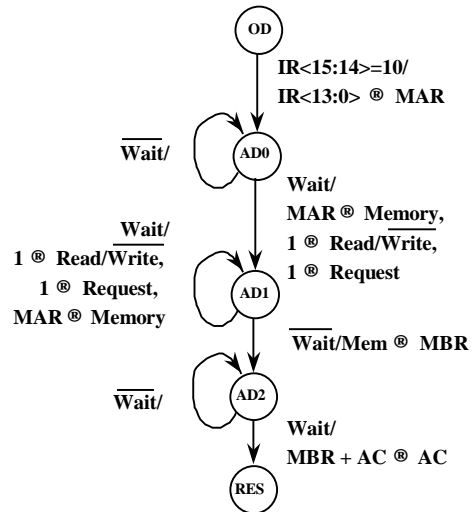Similar to Load sequence
Add MBR, AC rather than
simply transfer MBR to AC




CS150 Newton/Pister

11.2.19

Deriving the State Diagram and Datapath

Branch Execution Sequence

 


CS150 Newton/Pister

11.2.20

Deriving the State Diagram and Datapath

Branch Execution Sequence

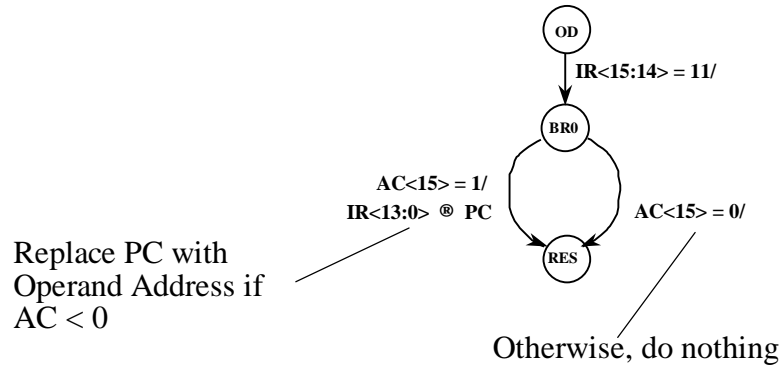

Deriving the State Diagram and Datapath


Revised/Complete State Diagram

Simplify Wait Looping

Eliminate some Wait states

At this point, Wait must be asserted, so why loop on Wait?

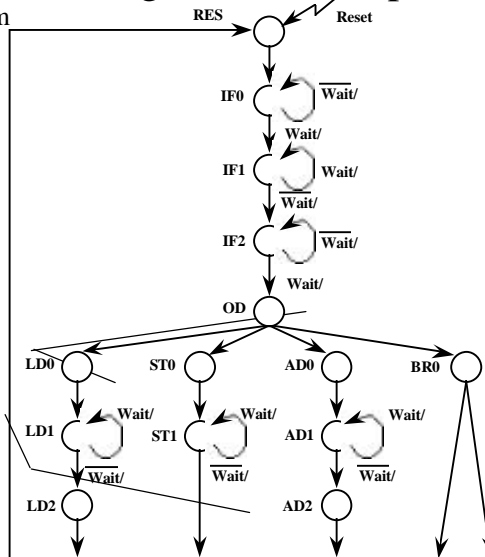Why loop on Wait when resync will take place at state IF0?



Deriving the State Diagram and Datapath

State Machine Inputs and Outputs so far:


Inputs:

Reset
Wait
IR<15:14>
AC<15>

Outputs:

0 → PC
PC + 1 → PC
PC → MAR
MAR → Memory Address Bus
Memory Data Bus → MBR
MBR → Memory Data Bus
MBR → IR
MBR → AC
AC → MBR
AC + MBR → AC
IR<13:0> → MAR
IR<13:0> → PC
1 → Read/Write
0 → Read/Write
1 → Request


Processor Signal Flow

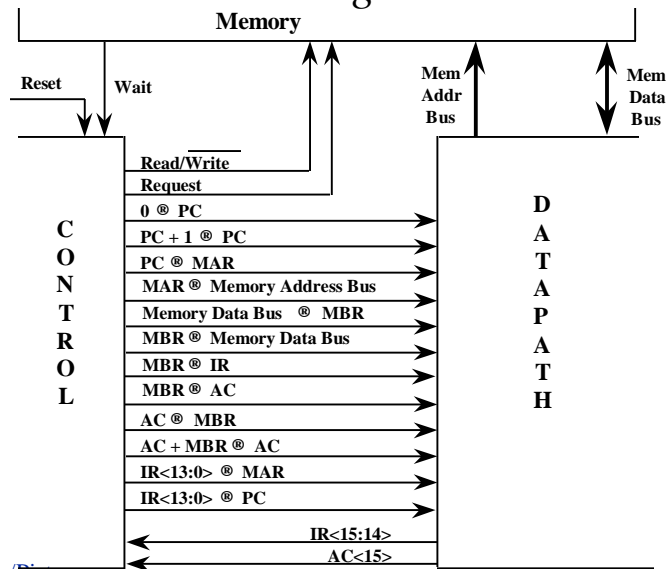

Mapping onto Datapath Control

Specification so far is independent of bussing strategy

Implied transfers:

 

This is the point-to-point connection scheme

CS150 Newton/Pister

11.2.25

Mapping onto Datapath Control

Observe that instruction fetch and operand fetch take place at different times

This implies that IR, PC, and MAR transfers can be implemented by single bus (Address Bus)

Combine MBR, IR, ALU B, and AC connections (Memory Bus)

Combine ALU, AC, and MBR connections (Result Bus)


Three bus architecture:

AC + MBR → AC implemented in single state

CS150 Newton/Pister

11.2.26

Mapping onto Datapath Control

 

AC has two inputs, RBUS and MBUS
(Other registers except MBR have single input and output)

Dual ported configuration is more complex

Better idea: reuse existing paths were possible
MBR → AC transfer implemented by PASS B ALU operation

Mapping onto Datapath Control

Detailed implementation of register transfer operations

More detailed control operations are called *microoperations*

One register transfer operation = several microoperations


Some operations directly implemented by functional units:

e.g., ADD, Pass B, 0 @ PC, PC + 1 @ PC

Some operations require multiple control operations:

e.g., PC → MAR implemented as
PC → ABUS and ABUS → MAR

Mapping onto Datapath Control

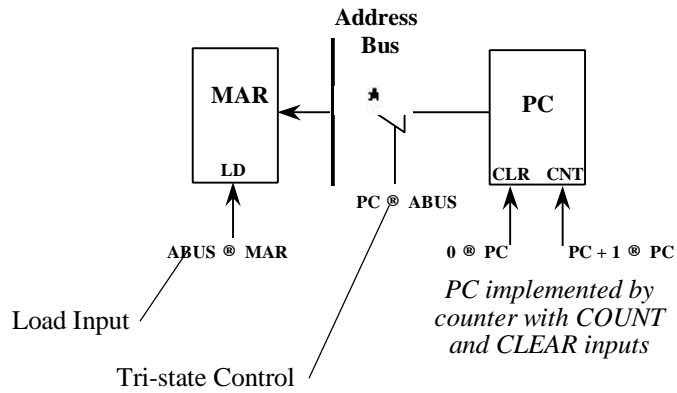


CS150 Newton/Pister

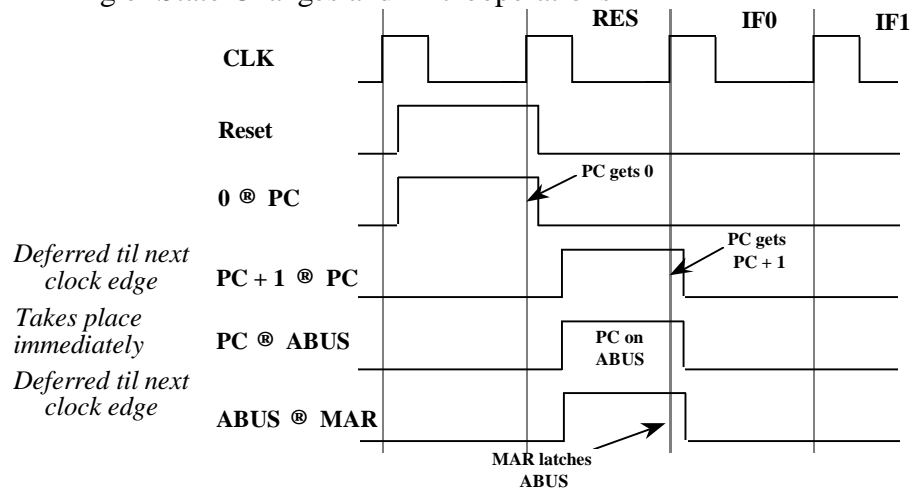11.2.29

Mapping onto Datapath Control

Timing of State Changes and Microoperations



CS150 Newton/Pister

11.2.30

Mapping onto Datapath Control

Relationship between register transfer and microoperations:

<u>Register Transfer</u>	<u>Microoperations</u>
0 @ PC	0 @ PC (delayed);
PC + 1 @ PC	PC + 1 @ PC (delayed);
PC @ MAR	PC @ ABUS (immediate), ABUS @ MAR (delayed);
MAR @ Address Bus	MAR @ Address Bus (immediate);
Data Bus @ MBR	Data Bus @ MBR (delayed);
MBR @ Data Bus	MBR @ Data Bus (immediate);
MBR @ IR	MBR @ ABUS (immediate), ABUS @ IR (delayed);
MBR @ AC	MBR @ MBUS (immediate), MBUS @ ALU B (immediate), ALU PASS B (immediate), ALU Result @ RBUS (immediate), RBUS @ AC (delayed);

CS150 Newton/Pister

11.2.31

Mapping onto Datapath Control

Relationship between register transfer and microoperations:


<u>Register Transfer</u>	<u>Microoperations</u>
AC → MBR	AC → RBUS (immediate), RBUS → MBR (delayed);
AC + MBR → AC	AC → ALU A (immediate), MBR → MBUS (immediate), MBUS → ALU B (immediate), ALU ADD (immediate), ALU Result → RBUS (immediate), RBUS → AC (delayed);
IR<13:0> → MAR	IR → ABUS (immediate), ABUS → IR (delayed);
IR<13:0> → PC	IR → ABUS (immediate), ABUS → PC (delayed);
1 → Read/Write	Read (immediate);
0 → Read/Write	Write (immediate);
1 → Request	Request (immediate);

Special microoperations for AC → ALU and ALU Result → RBUS not strictly necessary since these connections can be hardwired

CS150 Newton/Pister

11.2.32

Mapping onto Datapath Control

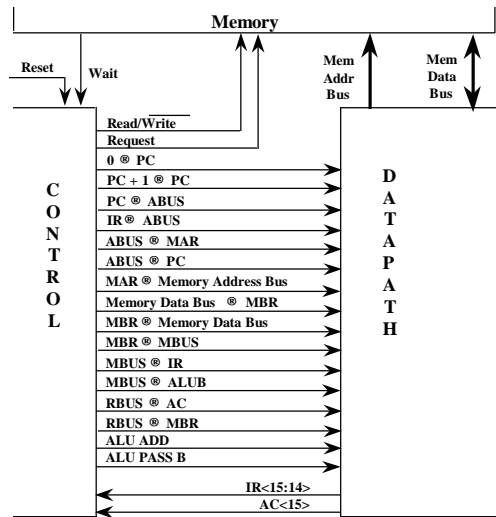

Revised microoperation signal flow

5 inputs

make sure that Reset and Wait are synchronized

16 datapath control lines

2 memory control lines