

Outline

- Last time:
 - Combinational Testability and Test-pattern Generation
 - Faults in digital circuits
 - What is a test?: Controllability & Observability
 - Redundancy & testability
 - Test coverage & simple PODEM ATPG
 - Sequential Test: What are sequential faults?
 - SCAN Design
- This lecture:
 - Asynchronous Circuits
 - Moore and Mealy Standard Forms
 - Design Example: Word Problem

CS150 Newton/Pister

13.1.1

Asynchronous Circuits (Feedback Sequential Circuits)

- Clocked Synchronous Circuits:
 - Change of state only occurs in response to a clock pulse
 - When this change of state requires that a number of flip-flops change their values, they do so simultaneously because they are synchronized by the common clock pulse.
 - Input changes are assumed to occur in between clock pulses and outputs may be read during or immediately before a clock pulse.
- Conditions where this model is too restrictive:
 - The network has inputs which may change at any time and cannot be synchronized by a clock.
 - Signal travel time down wires is significant and wire lengths in the circuit cannot be controlled
 - We want the network to operate as fast as possible
 - The power dissipation overhead of clocking signals that do not change is unacceptable (we need "event-driven" circuits).

CS150 Newton/Pister

13.1.2


Asynchronous Circuits

- Asynchronous Circuits:
 - Operation is not synchronized by a clock.
 - When an input change occurs, the state of the network can change almost immediately.
 - If several storage elements must change state, there is no guarantee they will do so at the same time.
- To simplify this challenging problem we consider only *fundamental mode* asynchronous circuits:
 - The input signals will only change when the circuit is in a stable condition (i.e. no internal signals are changing).
 - All of the input signals are considered to be levels, rather than pulses or edges.
 - Inputs may not change simultaneously
 - Asynchronous circuits may be structured as Mealy and Moore forms, as before, but delays in the feedback path are not clocked and may be different!

CS150 Newton/Pister

13.1.3

D Latch Example

 

Excitation Equation for Y^* :

$$Y^* = CD + (CD' + Y)' = CD + C'Y + DY$$

CS150 Newton/Pister

13.1.4

D Latch Example: Transition Table

Y	CD			
	00	01	11	10
0	0	0	1	0
1	1	1	1	0

Y^*

CS150 Newton/Pister

13.1.5

D Latch Example: State Table

S	CD			
	00	01	11	10
S0	S0	S0	S1	S0
S1	S1	S1	S1	S0

S^*

○ = stable state

CS150 Newton/Pister

13.1.6

Transition Table

- A transition table has one row for each possible combination of the state variables.
 - If the circuit has n feedback loops, it has 2^n rows in its transition table
- The table has one column for each input combination
 - A circuit with m inputs has 2^m columns in its transition table.
- The circuit is monitoring its inputs continuously

Total State

- The total state of a circuit is a particular combination of the internal state (values stored in the feedback loops) and input state (the current values of the circuit inputs).
- A *stable total state* is a combination of *internal state* and *input state* such that the next internal state predicted by the transition table is the same as the current internal state.
- If the next internal state is different, then the combination is an *unstable total state*.

D Latch Example: Output Equations

- $Q = CD + C'Y + DY$
 $Q' = CD' + Y'$
- Y is the only internal state variable
- Combined state and output table:


S	CD			
	00	01	11	10
S0	S0,01	S0,01	S1,11	S0,01
S1	S1,10	S1,10	S1,10	S0,01

S*, Q /Q

Races

- In a feedback sequential circuit, a *race* is said to occur when multiple internal variables change state as a result of a single input variable changing state.
- If the final state depends on the order in which the variables change, the race is said to be *critical*.

 Analysis Example: Positive Edge-Triggered D Flip-Flop



Transition Table for D Flip-Flop

Y1Y2Y3	CLK D			
	00	01	11	10
000	010	010	000	000
001	011	011	000	000
010	010	110	110	000
011	011	111	111	000
100	010	010	111	111
101	011	011	111	111
110	010	110	111	111
111	011	111	111	111

$Y1 * Y2 * Y3*$

State and Output Table for D Flip-Flop

S	CLK D			
	00	01	11	10
S0	S2,01	S2,01	S0,01	S0,01
S1	S3,10	S3,10	S0,01	S0,01
S2	S2,01	S6,01	S6,01	S0,01
S3	S3,10	S7,10	S7,10	S0,01
S4	S2,01	S2,01	S7,11	S7,11
S5	S3,10	S3,10	S7,10	S7,10
S6	S2,01	S6,01	S7,11	S7,11
S7	S3,10	S7,10	S7,10	S7,10

S*

CS150 Newton/Pister

13.1.13

Flow and Output Table for the D Flip-Flop

S	CLK D			
	00	01	11	10
S0	S2,01	S6,01	S0,01	S0,01
S2	S2,01	S6,01	-,-	S0,01
S3	S3,10	S7,10	-,-	S0,01
S6	S2,01	S6,01	S7,11	-,-
S7	S3,10	S7,10	S7,10	S7,10

S*

CS150 Newton/Pister

13.1.14

Steps to Asynchronous FSM Design

- Construct a *Primitive Flow Table* from the word statement of the problem.
- Derive a minimum-row primitive flow table or *Reduced Primitive Flow Table* by eliminating redundant, stable total-states.
- Convert the resulting table to Mealy form, if necessary, so that the output value is associated with the total state rather than the internal state.
- Derive a minimum-row flow table, or *Merged Flow Table*, by merging compatible rows of the reduced primitive flow table using a merger diagram. (Note: solution not necessarily unique)
- Perform race-free, or critical-race-free, state assignment, adding additional states if necessary.
- Complete the *Output Table* to avoid momentary false outputs when switching between stable total states.
- Draw *logic diagram* that shows ideal combinational next-state and output functions as well as necessary delay elements.

CS150 Newton/Pister

13.1.15

Design Example 1: Word Problem

- An asynchronous network has two inputs and one output. The input sequence $X_1X_2 = 00, 01, 11$ causes the output, Z, to become 1. The next input change then causes the output to return to 0. No other input sequence will produce a 1 output.

	X ₁ X ₂				Z
	00	01	11	10	
(reset) 1	1	2	3	0	
(00,01) 2		2		0	
(00,10) 3			3	0	

Fundamental mode, single input changes, so input can only change in stable total state and only one bit can change, so this total-state is impossible, since only stable total state is inputs 00 in this row.

CS150 Newton/Pister

13.1.16

Derivation of Primitive Flow Table: Cont.

	X ₁ X ₂				Z
	00	01	11	10	
(reset) 1	1	2	-	3	0
(00,01) 2	1	2	4	-	0
(00,10) 3	1	-	5	3	0
(00,01,11) 4	-	-	4	-	1
(00,10,11) 5	-	-	5	-	0

CS150 Newton/Pister

13.1.17

Derivation of Primitive Flow Table: Cont.

- *Primitive Flow Table*: Only one stable state per row is permitted, so every change in input must result in an internal state change as well as a total state change (by definition).

	X ₁ X ₂				Z
	00	01	11	10	
(reset) 1	1	2	-	3	0
(00,01) 2	1	2	4	-	0
(00,10) 3	1	-	5	3	0
(00,01,11) 4	-	6	4	3	1
* 5	-	6	5	3	0
* 6	1	6	5	-	0


States marked * cannot lead to a 1 output without first resetting.

CS150 Newton/Pister

 13.1.18

Design Example 2: Word Problem

- A clock signal (C) is to be gated on and off by another signal (S). The gating network must be such that only complete clock pulses appear at the output (Z) even though S may change in the middle of a clock pulse. S will always be on or off for at least two clock pulses.



CS150 Newton/Pister

13.1.19

Derivation of Primitive Flow Table: Cont.

	CS				Z
	00	01	11	10	
1	1	3	-	2	0
2	1	-	6	2	0
3	-	3	4	-	0
4	-	3	4	-	1

CS150 Newton/Pister

13.1.20

Derivation of Primitive Flow Table: Cont.

	CS				Z
	00	01	11	10	
1	1	3	-	2	0
2	1	-	6	2	0
3	1	3	4	-	0
4	-	3	4	5	1
5	1	-	5	5	1
6	-	3	6	-	0

10->11 cannot occur in State 5 since S is assumed to be off for at least two clock pulses. Same for 11->10 in State 6.

CS150 Newton/Pister

13.1.21

Steps to Asynchronous FSM Design

- Construct a *Primitive Flow Table* from the word statement of the problem.
- Derive a minimum-row primitive flow table or *Reduced Primitive Flow Table* by eliminating redundant, stable total-states.
- Convert the resulting table to Mealy form, if necessary, so that the output value is associated with the total state rather than the internal state.
- Derive a minimum-row flow table, or *Merged Flow Table*, by merging compatible rows of the reduced primitive flow table using a merger diagram. (Note: solution not necessarily unique)
- Perform race-free, or critical-race-free, state assignment, adding additional states if necessary.
- Complete the *Output Table* to avoid momentary false outputs when switching between stable total states.
- Draw *logic diagram* that shows ideal combinational next-state and output functions as well as necessary delay elements.

CS150 Newton/Pister

13.1.22

Minimum-Row Primitive Flow Table: Eliminate Redundant Stable Total States

- Redundant States:** Two stable total states are equivalent if:
 - Their inputs are the same and
 - Their outputs are the same and
 - Their next-states are equivalent for each possible next input

In Example 1, possible candidates for combining are:
 {4,5} - no, because outputs not the same
 {2,6} - no, because next-states not equivalent under 11 input (states 4 and 5)

so no redundant states here.
 In Example 2, possible candidates are:
 {4,6} - no, different outputs
 {2,5} - no, different outputs
 so no redundant states here either.

CS150 Newton/Pister

13.1.23

Removal of Redundant States: Example

	X1X2				Z1Z2	
	00	01	11	10	Z1	Z2
1	1	7	-	4	1	1
2	2	5	-	4	0	1
3	-	7	3	11	1	0
4	2	-	3	4	0	0
5	6	5	9	-	1	1
6	6	7	-	11	0	1
7	1	7	14	-	1	0
8	8	12	-	4	0	1
9	-	7	9	13	0	1
10	-	7	10	4	1	0
11	8	-	10	11	0	0
12	6	12	9	-	1	1
13	8	-	14	13	1	1
14	-	12	14	11	0	0

Examine stable states in same column (same input) that have same output:
 00: {2,6,8} - under input 01, {2,6} go to different, not-equivalent next states. Similarly for {6,8}, {2,8} equiv. iff {5,12} equiv.
 01: {5,12} - yes
 11: {3,10} iff {4,11}
 10: {4,11} iff {3,10} and {5,12}. leads to:
 {2,8}, {5,12}, {3,10}, {4,11} so eliminate 8, 10, 11, 12

CS150 Newton/Pister

13.1.24

Removal of Redundant States: Example

	X1X2				Z1Z2	
	00	01	11	10		
1	①	7	-	4	1	1
2	②	5	-	4	0	1
3	-	7	③	4	1	0
4	2	-	3	④	0	0
5	⑥	⑤	9	-	1	1
6	⑥	7	-	4	0	1
7	1	⑦	14	-	1	0
9	-	7	⑨	13	0	1
13	2	-	14	⑬	1	1
14	-	5	⑭	4	0	0