

Outline

- Last time:
 - Asynchronous Circuits
 - Moore and Mealy Standard Forms
 - Design Example: Word Problem
- This lecture:
 - Race-free State Assignment
 - Excitation Equations
 - Design Example: Implementation
 - Summary of Asynchronous Design Process

Steps to Asynchronous FSM Design

- Construct a *Primitive Flow Table* from the word statement of the problem.
- ✓ Derive a minimum-row primitive flow table or *Reduced Primitive Flow Table* by eliminating redundant, stable total-states.
 - Convert the resulting table to Mealy form, if necessary, so that the output value is associated with the total state rather than the internal state.
 - Derive a minimum-row flow table, or *Merged Flow Table*, by merging compatible rows of the reduced primitive flow table using a merger diagram. (Note: solution not necessarily unique)
 - Perform race-free, or critical-race-free, state assignment, adding additional states if necessary.
 - Complete the *Output Table* to avoid momentary false outputs when switching between stable total states.
 - Draw *logic diagram* that shows ideal combinational next-state and output functions as well as necessary delay elements.

Conversion to Mealy Form for Merging: Example 1

	X_1X_2				Z			
	00	01	11	10	00	01	11	10
1	1	2	-	3	0	-	-	-
2	1	2	4	-	-	0	-	-
3	1	-	5	3	-	-	-	0
4	-	6	4	3	-	-	1	-
5	-	6	5	3	-	-	0	-
6	1	6	5	-	-	0	-	-

CS150 Newton/Pister

13.2.3


Create Merger Diagram

What we are doing is choosing *internal* states that can have the *same* code, though the *total* states will still be different (since they will not have the same code for the same inputs; if that were possible they would have been redundant).

Two rows of a reduced primitive Mealy flow table are *compatible* and can be merged into a single row iff there are no state or output conflicts in any column.

Draw a line between any pair of rows (states) which are compatible and can be merged.

 Choose the sub-groups of fully-connected rows that will result in the maximum reduction. In this case, {1,2} and {3,5,6} are best. We could also have chosen {1,3} and {5,6}, or just {3,6} in which case no others would be permitted.



CS150 Newton/Pister

13.2.4


Example 1: After Merging

	X1X2							
	00	01	11	10	00	01	11	10
a(1,2)	①	②	④	③	0	0	-	-
b(3,5,6)	1	⑥	⑤	3	-	0	0	0
c(4)	-	6	4	3	-	-	1	-

Conversion to Mealy Form for Merging: Example 2

	CS				Z			
	00	01	11	10	00	01	11	10
1	①	3	-	2	0	-	-	-
2	1	-	6	②	-	-	-	0
3	1	③	4	-	-	0	-	-
4	-	3	④	5	-	-	1	-
5	1	-	-	⑤	-	-	-	1
6	-	3	⑥	-	-	-	0	-

Create Merger Diagram: Example 2

 

Choose {1,2,6} and {4,5}

Steps to Asynchronous FSM Design

Construct a *Primitive Flow Table* from the word statement of the problem.

- ✓ Derive a minimum-row primitive flow table or *Reduced Primitive Flow Table* by eliminating redundant, stable total-states.
- ✓ Convert the resulting table to Mealy form, if necessary, so that the output value is associated with the total state rather than the internal state.
- ✓ Derive a minimum-row flow table, or *Merged Flow Table*, by merging compatible rows of the reduced primitive flow table using a merger diagram. (Note: solution not necessarily unique)
- Perform race-free, or critical-race-free, state assignment, adding additional states if necessary.
- Complete the *Output Table* to avoid momentary false outputs when switching between stable total states.
- Draw *logic diagram* that shows ideal combinational next-state and output functions as well as necessary delay elements.


Example: After State Reduction and Merging

	X1X2							
	00	01	11	10	00	01	11	10
a(1,2)	①	②	4	3	0	0	-	-
b(3,5,6)	1	⑥	⑤	③	-	0	0	0
c(4)	-	6	④	3	-	-	1	-


Example 1: States Labelled in Terms of Internal States

	X1X2							
	00	01	11	10	00	01	11	10
a	Ⓐ	Ⓐ	c	b	0	0	-	-
b	a	Ⓑ	Ⓑ	Ⓑ	-	0	0	0
c	-	b	Ⓒ	b	-	-	1	-

Example: Race-Free State Assignment

 

 - Line between states indicates required transition.
- Need assignment such that only one state variable changes during each state transition



Example: Critical-Race-Free State Assignment

	X1X2							
	00	01	11	10	00	01	11	10
a 00	00	00	10	01	0	0	-	0v
b 01	00	01	01	01	0u	0	0	0
d 11	-	01	-	-	-	-s	-	-
c 10	-	11	10	00	-	1t	1	-

- In col. 01, row C, 10->11->01: critical race avoided
- In col 10, could have directed transition via row d but already have transition to b in row a, so use it.
- Fill in outputs corresponding to unstable states to avoid momentary false outputs during transitions

Critical-Race-Free State Assignment via Shared-Row Assignments

	00	01	11	10
a	①	2	5	4
b	⑦	②	3	⑩
c	1	8	③	4
d	7	⑧	5	④
e	1	⑨	⑤	6
f	⑪	8	3	⑥

- **Required transitions:**
 - col 00: e,c → a; d→b
 - col 01: a→b; c,f→d
 - col 11: b,f→c; a,d→e
 - col 10: a,c→d; e→f

Shared Row Assignment

- Consider required transitions: e,c → a
- Could implement as: e→a, c→a; or e→c→a; or c→e→a; or any of the above going through an intermediate state (or states).
- To avoid critical races, must ensure that {a,c,e} are placed in adjacent squares on the assignment map. Similar for other constraints. Must satisfy:
 - {a,c,e}, {b,d}, {a,b}, {c,d,f}, {b,c,f}, {a,d,e}, {a,c,d}, {e,f}

a	e
b	d
x	c
y	f

Completion of the Output Table

		X1X2							
		00	01	11	10	00	01	11	10
a	00	00	00	10	01	0	0	-	0v
b	01	00	01	01	01	0u	0	0	0
d	11	-	01	-	-	-	-s	-	-
c	10	-	11	10	00	-	1t	1	-

From State 00, input change 00->10 causes transition to stable state 01. To avoid glitch if logic synthesis assigns "don't care" in output to 1 for input value 10, make it a 0 (labelled v above).

From State 01, input change 01->00 causes transition to State 00, so avoid possible glitch by assigning output in State 01 for input 00 to 0 (u above)

From State 10, input change 11->01 causes transition to stable state 01, via 11. Since output goes from 1 to 0, choose output at t above to be 1, consistent with the starting value, but leave output at s a "don't care" since must make the transition somewhere and either before or after State 11 is the same.

Steps to Asynchronous FSM Design

- Construct a *Primitive Flow Table* from the word statement of the problem.
- ✓ Derive a minimum-row primitive flow table or *Reduced Primitive Flow Table* by eliminating redundant, stable total-states.
- ✓ Convert the resulting table to Mealy form, if necessary, so that the output value is associated with the total state rather than the internal state.
- ✓ Derive a minimum-row flow table, or *Merged Flow Table*, by merging compatible rows of the reduced primitive flow table using a merger diagram. (Note: solution not necessarily unique)
- ✓ Perform race-free, or critical-race-free, state assignment, adding additional states if necessary.
- ✓ Complete the *Output Table* to avoid momentary false outputs when switching between stable total states.
- Draw *logic diagram* that shows ideal combinational next-state and output functions as well as necessary delay elements.