

Outline

- Last time:
 - Introduction to number systems: sign/magnitude, ones complement, twos complement
 - Review of latches, flip flops, counters
- This lecture:
 - Review State Tables & State Transition Diagrams
 - Implementation Using D Flip-Flops
 - Machine Equivalence
 - Incompletely Specified Machines
 - State Assignment & State Coding Schemes
 - Design Example: Assign Codes to States
 - Design Example: Implement Using D flip-flops
 - Design Example: Implement Using T flip-flops

CS150 Newton/Pister

8.1.1

Clocked Synchronous Finite-State Machines


○ Example:

Consider the student association coffee vending machine which sells coffee at 15¢/cup. The machine will accept nickles, dimes, and quarters, one at a time. The coffee release line will be set to true when 15¢ or more has been put into the machine and the machine will return the correct change.

CS150 Newton/Pister

8.1.2

Definition: Mealy Machine

 


- A sequential machine or *Mealy Machine* can be characterized by the quintuple: $M = (S, Q, Z, \mathbf{d}, \mathbf{I})$ where
 - S = finite non-empty set of input symbols $\sigma_1, \sigma_2, \dots, \sigma_i$
 - Q = finite non-empty set of states q_1, q_2, \dots, q_n
 - Z = finite non-empty set of output symbols z_1, z_2, \dots, z_m
 - \mathbf{d} = *next-state* function, which maps $Q \times S \rightarrow Q$
 - \mathbf{I} = the *output* function, which maps $Q \times S \rightarrow Z$

CS150 Newton/Pister

8.1.3

Definition: Moore Machine

 

- A sequential machine is said to be of the *Moore type (Moore Machine)* if its output function is a function only of its states (i.e. $\mathbf{I} : Q \rightarrow Z$)
- Every Mealy Machine can be converted to a Moore Machine and vice versa.
- If the State Memory is clocked, the machines are Clocked, Synchronous Mealy and Moore machines respectively.

CS150 Newton/Pister


8.1.4

Design Example: Inputs, Outputs and States

○ Example:

Consider the student association coffee vending machine which sells coffee at 15¢/cup. The machine will accept nickles, dimes, and quarters, one at a time. The coffee release line will be set to true when 15¢ or more has been put into the machine and the machine will return the correct change.

$$M_1 = (S_1, Q_1, Z_1, d, I_1)$$

 

CS150 Newton/Pister

8.1.5

Next-State and Output Functions


○ State/Output table (¢ symbol dropped for clarity):

| q\i | 5 | 10 | 25 |
|-----|--------|--------|--------|
| q0 | q5,D0 | q10,D0 | q0,R10 |
| q5 | q10,D0 | q0,R0 | q0,R15 |
| q10 | q0,R0 | q0,R5 | q0,R20 |

Present State

Next State, Present Output

Present Input

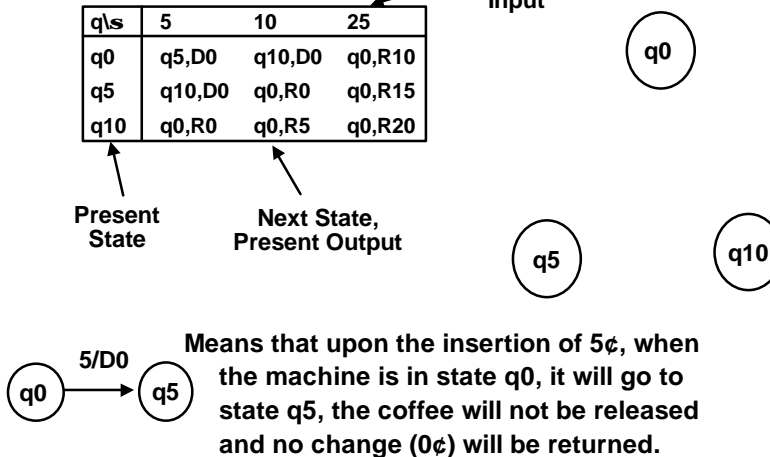


Means that upon the insertion of 5¢, when the machine is in state q0, it will go to state q5, the coffee will not be released and no change (0¢) will be returned.

CS150 Newton/Pister

8.1.6

How About a Moore Machine?

Input
 $S_1 = \{ 5¢, 10¢, 25¢ \}$

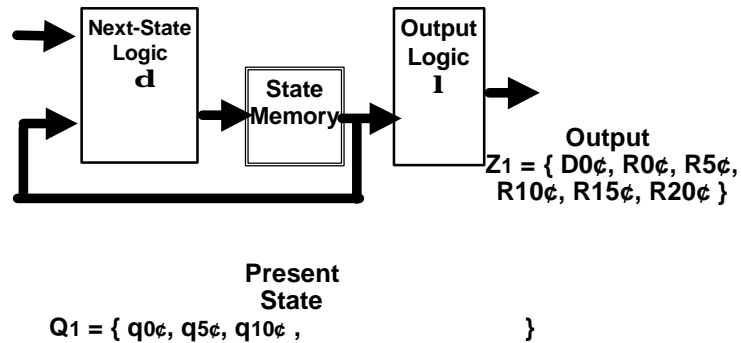


CS150 Newton/Pister

8.1.7

State/Output Transition Table and Transition Diagram: Moore Machine

Present Input

| q\s | 5 | 10 | 25 | z |
|-----|-----|-----|-----|-----|
| q0 | q5 | q10 | q25 | D0 |
| q5 | q10 | q15 | q30 | D0 |
| q10 | q15 | q20 | q35 | D0 |
| q15 | q5 | q10 | q25 | R0 |
| q20 | q5 | q10 | q25 | R5 |
| q25 | q5 | q10 | q25 | R10 |
| q30 | q5 | q10 | q25 | R15 |
| q35 | q5 | q10 | q25 | R20 |

 

Present State

Next State

Present Output

CS150 Newton/Pister

8.1.8

Conversion to Mealy Machine

| q\i | Present Input | | |
|-----|---------------|--------|---------|
| | 5 | 10 | 25 |
| q0 | q5,D0 | q10,D0 | q25,R10 |
| q5 | q10,D0 | q15,R0 | q30,R15 |
| q10 | q15,R0 | q20,R5 | q35,R20 |
| q15 | q5,D0 | q10,D0 | q25,R10 |
| q20 | q5,D0 | q10,D0 | q25,R10 |
| q25 | q5,D0 | q10,D0 | q25,R10 |
| q30 | q5,D0 | q10,D0 | q25,R10 |
| q35 | q5,D0 | q10,D0 | q25,R10 |

Present State

Next State, Present Output

CS150 Newton/Pister

8.1.9

Machine Equivalence

- Let qa and qb be two states of machines Ma and Mb respectively. States qa and qb are said to be *equivalent* iff, starting with qa and qb , for *any* sequence of input symbols applied to the two machines, the output sequences are identical. If qa and qb are not identical, they are said to be *distinguishable*.
- Let Ma and Mb be two sequential machines. Ma and Mb are said to be *equivalent* iff for every state of Ma there exists at least one equivalent state in Mb , and vice versa. Similarly, if Ma and Mb are not equivalent we say they are *distinguishable*.
- Two states qa and qb are equivalent if:
 - (1) qa and qb produce the same output values (for Mealy machines, they must produce the same outputs for all legal input conditions).
 - (2) For each input combination, qa and qb must have the same next state, or equivalent next states.

CS150 Newton/Pister

8.1.10

State Minimization of Completely-Specified Machines

- Two states are said to be *k-equivalent* if, when excited by an input sequence of *k* symbols, yield identical output sequences. The machine can be partitioned by this *k-equivalence* relation into *k-equivalence classes*.
- For any *n*-state machine, there can be at most (*n*-1) successive, distinct partitions.
- For any *n*-state machine, these equivalence classes contain one and only one unique state.

- To minimize a completely-specified machine:
 - (1) Find the 1-equivalence classes, 2-equivalence classes, etc. until the *k*+1 equivalence classes are the same as the *K* equivalence classes, then stop.
 - (2) Combine all the states in the same class into a single state. If the machine has *m* equivalence classes, the machine has *m* states.

CS150 Newton/Pister

8.1.11

Design Example: State Minimization

| q \ s | 5 | 10 | 25 | 1-partition |
|-------|--------|--------|---------|-------------|
| q0 | q5,D0 | q10,D0 | q25,R10 | I |
| q5 | q10,D0 | q15,R0 | q30,R15 | II |
| q10 | q15,R0 | q20,R5 | q35,R20 | III |
| q15 | q5,D0 | q10,D0 | q25,R10 | I |
| q20 | q5,D0 | q10,D0 | q25,R10 | I |
| q25 | q5,D0 | q10,D0 | q25,R10 | I |
| q30 | q5,D0 | q10,D0 | q25,R10 | I |
| q35 | q5,D0 | q10,D0 | q25,R10 | I |

CS150 Newton/Pister

8.1.12

Design Example: State Minimization

| 1-partition | q \ s | 5 | 10 | 25 | 2-partition |
|-------------|-------|--------|--------|---------|-------------|
| I | q0 | q5,D0 | q10,D0 | q25,R10 | |
| | q15 | q5,D0 | q10,D0 | q25,R10 | |
| | q20 | q5,D0 | q10,D0 | q25,R10 | |
| | q25 | q5,D0 | q10,D0 | q25,R10 | |
| | q30 | q5,D0 | q10,D0 | q25,R10 | |
| | q35 | q5,D0 | q10,D0 | q25,R10 | |
| II | q5 | q10,D0 | q15,R0 | q30,R15 | |
| III | q10 | q15,R0 | q20,R5 | q35,R20 | |

CS150 Newton/Pister

8.1.13

State Assignment

| q \ s | 5 | 10 | 25 |
|-------|--------|--------|--------|
| q0 | q5,D0 | q10,D0 | q0,R10 |
| q5 | q10,D0 | q0,R0 | q0,R15 |
| q10 | q0,R0 | q0,R5 | q0,R20 |

- We must assign codes to symbolic values. Codes for input and output symbols are usually "given" so we must determine codes for the state symbols. This process is called state assignment or state coding. If binary storage elements are used we need:

$$\lceil \log_2(N_s) \rceil \leq N_m < N_s$$

CS150 Newton/Pister

8.1.14

Design Example: State Assignment Minimum-Length Code

- For this example, $2 < N_m < 3$. If we choose $N_m = 2$, and assign codes randomly, then we have the state table:

| $q \setminus \sigma$ | 5 | 10 | 25 |
|----------------------|-------|-------|--------|
| 00 | 01,D0 | 11,D0 | 00,R10 |
| 01 | 11,D0 | 00,R0 | 00,R15 |
| 11 | 00,R0 | 00,R5 | 00,R20 |
| 10 | ??,?? | ??,?? | ??,?? |


unused
state

CS150 Newton/Pister

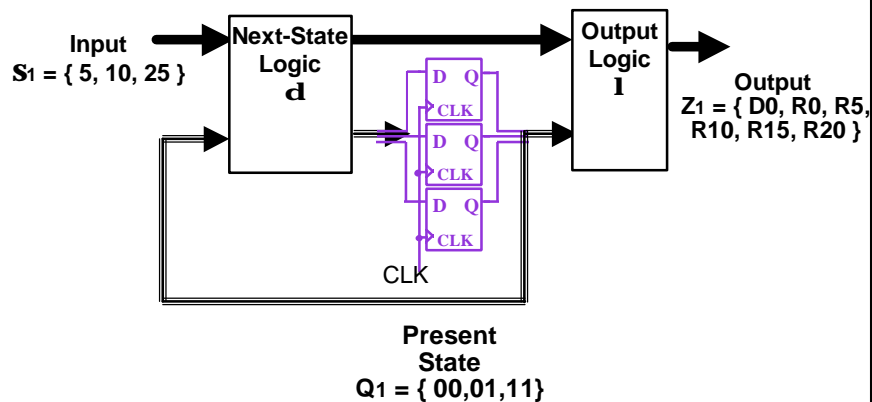8.1.15

Implementation Using D Flip-Flops

- Can use positive-edge-triggered D flop-flop directly to implement storage element:



CS150 Newton/Pister

8.1.16

Design Example: State Assignment One-Hot Code

- For this example, $2 < N_m < 3$. If we choose $N_m = 3$, and assign codes randomly but where exactly one bit of the code is "1" for each valid state, then we have the state table:

| q/s | 5 | 10 | 25 |
|-----|--------|--------|---------|
| 001 | 010,D0 | 100,D0 | 001,R10 |
| 010 | 100,D0 | 001,R0 | 001,R15 |
| 100 | 001,R0 | 001,R5 | 001,R20 |
| 000 | ???,?? | ???,?? | ???,?? |
| 011 | ???,?? | ???,?? | ???,?? |
| 101 | ???,?? | ???,?? | ???,?? |
| 110 | ???,?? | ???,?? | ???,?? |
| 111 | ???,?? | ???,?? | ???,?? |

unused
states

CS150 Newton/Pister

8.1.17

Steps to FSM Design

- Construct a state/output table from the word description (or a state graph).
- State Minimization: Minimize the number of states (usually helps).
- State Assignment: Choose a set of state variables and assign codes to named states.
- Substitute the state-variable combinations into the state/output table to create a transition/output table that shows the desired next-state variable combination for each state/input combination.
- Choose a flip-flop type (e.g. D, J-K, T) for the state memory.
- Construct an excitation table that shows the excitation values required to obtain the desired next-state value for each state/input combination.
- Derive excitation equations from excitation table.
- Derive output equations from transition/output table.
- Draw logic diagram that shows combinational next-state and output functions as well as flip-flops.


CS150 Newton/Pister

8.1.18

State Minimization Using an Implication Table

- Build a compatibility checking table in a ladder shape, as shown, and label each row q_2, q_3, \dots, q_n and column q_1, q_2, \dots, q_{n-1} (no need for diagonal).

| q\s | 0 | 1 | z |
|-----|---|---|---|
| a | d | c | 0 |
| b | f | h | 0 |
| c | e | d | 1 |
| d | a | e | 0 |
| e | c | a | 1 |
| f | f | b | 1 |
| g | b | h | 0 |
| h | c | g | 1 |

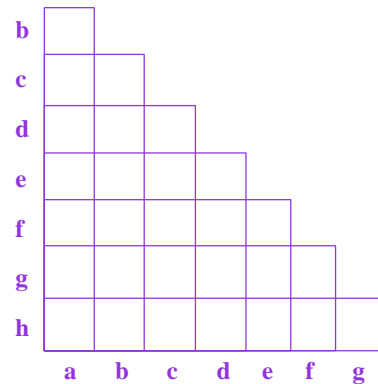

CS150 Newton/Pister

8.1.19

State Minimization Using an Implication Table: Summary of Approach

- Construct an implication table which contains a square for each pair of states. Label each row q_2, q_3, \dots, q_n and column q_1, q_2, \dots, q_{n-1} (no need for diagonal).
- Compare each pair of rows in the state table. If the outputs associated with states i and j are different, put an X in square $i-j$ to indicate that $i \not\equiv j$ (trivial non-equivalence). If the outputs and the next states are the same, put a \checkmark in square $i-j$ to indicate $i \equiv j$ (trivial equivalence).
- In all other squares, put state-pairs that must be equivalent if states $i-j$ are to be equivalent (if the next states of i and j are m and n for some input σ , then $m-n$ is an implied pair and goes in square $i-j$).
- Go through the non- \checkmark and non- X squares, one at a time. If square $i-j$ contains an implied pair and square $m-n$ contains an X , then $i \equiv j$ so put an X in $i-j$ as well.
- If any X 's were added in the last step, repeat it until no more X 's are added. For each square $i-j$ which not containing an X , $i \not\equiv j$.

CS150 Newton/Pister

8.1.20

Implication Table Example: Pass 0

| q\s | 0 | 1 | z |
|-----|---|---|---|
| a | d | c | 0 |
| b | f | h | 0 |
| c | e | d | 1 |
| d | a | e | 0 |
| e | c | a | 1 |
| f | f | b | 1 |
| g | b | h | 0 |
| h | c | g | 1 |

| | | | | | | | |
|---|------------|------------|------------|------------|------------|------------|---|
| b | d-f c-h | | | | | | |
| c | × | × | | | | | |
| d | c-e | a-f e-h | × | | | | |
| e | × | × | a-d | × | | | |
| f | × | × | e-f b-d | × | c-f a-b | | |
| g | b-d c-h | b-f | × | a-b e-h | × | × | |
| h | × | × | c-e d-g | × | a-g | c-f b-g | × |
| | a | b | c | d | e | f | g |

CS150 Newton/Pister

8.1.21

Implication Table Example: Pass 1 and Pass 2

| | | | | | | | |
|---|--|----------------------------------|----------------------------------|----------------------------------|----------------------------------|----------------------------------|---|
| b | × d-f c-h | | | | | | |
| c | × | × | | | | | |
| d | c-e | a-f e-h | × | | | | |
| e | × | × | a-d | × | | | |
| f | × | × | b-f b-d | × | a-b a-h | | |
| g | b-d c-h | b-f | × | a-b e-h | × | × | |
| h | × | × | c-e d-g | × | a-g | c-f b-g | × |
| | a | b | c | d | e | f | g |

CS150 Newton/Pister

8.1.22

Implication Table Example: Final State Table

| q\s | 0 | 1 | z |
|-----|---|---|---|
| a | d | c | 0 |
| b | f | h | 0 |
| c | c | a | 1 |
| f | f | b | 1 |
| g | b | h | 0 |
| h | c | g | 1 |

CS150 Newton/Pister

8.1.23

Steps to FSM Design


- ✓ Construct a state/output table from the word description (or a state graph).
- ✓ *State Minimization*: Minimize the number of states (usually helps a bit).
- *State Assignment*: Choose a set of state variables and assign codes to named states.
- Substitute the state-variable combinations into the state/output table to create a *transition/output table* (next-state table) that shows the desired next-state variable combination for each state/input combination. Construct next-state K-maps as needed.
- Choose a flip-flop type (e.g. D, J-K, T) for the state memory.
- Construct an *excitation table* that shows the flip-flop input excitation values required to obtain the desired next-state value for each state/input combination.
- Derive flip-flop *excitation equations* from excitation table.
- Derive *output equations* from transition/output table.
- Draw *logic diagram* that shows combinational next-state and output functions as well as flip-flops.

CS150 Newton/Pister

 8.1.24

Guidelines for State Assignment

- The idea of the following heuristics is to try to get the 1's together (in the same implicant) on the flip-flop input maps. This method does not apply to all problems and even when it is applicable it does not guarantee a minimum solution.
- States which have the same next state, for a given input, should be given adjacent assignments ("fan-out oriented").
- States which are the next states of the same state should be given adjacent assignments ("fan-in oriented").
- Third priority, to simplify the output function, states which have the same output for a given input should be given adjacent assignments (this will help put the 1's together in the output K-maps; "output oriented").



CS150 Newton/Pister

8.1.25

But How Do You Actually Do It?

- Write down all of the states that should be given adjacent assignments according to the criteria above ("assignment constraints", or "face embedding constraints.") Then, using a Karnaugh-map, try to satisfy as many of them as possible (or use a computer program which does it: Kiss, Nova, Mustang, Jedi). Some guidelines to help are:
 - Assign the starting state to the "0" square on the map (picking a different square doesn't help, since all squares have the same number of adjacencies and it's easier to reset to "0").
 - Fanout-oriented guidelines and adjacency conditions required more than once should be satisfied first.
 - When guidelines require that 3 or 4 states be adjacent, these states should be placed within a group of 4 on the assignment map.
 - If there are only a few outputs, the output guideline should be applied last. If there are lots of outputs and only a few states, then give more weight to the third guideline.

CS150 Newton/Pister

8.1.26

State Assignment: Design Example

| q \ s | 0 | 1 |
|-------|------|------|
| q0 | q1,0 | q2,0 |
| q1 | q3,0 | q2,0 |
| q2 | q1,0 | q4,0 |
| q3 | q5,0 | q2,0 |
| q4 | q1,0 | q6,0 |
| q5 | q5,1 | q2,0 |
| q6 | q1,0 | q6,1 |

- Consider the state table opposite:
 - **Guideline 1:** {q0,q2,q4,q6} since all have q1 as next-state with input 0. Similarly {q0,q1,q3,q5}; {q3,q5}; {q4,q6}.
 - **Guideline 2:** {q1,q2} since next-states of q0. Similarly {q2,q3}; {q1,q4}; {q2,q5} twice; {q1,q6} twice.
 - **Guideline 3:** would not be worth using here. We already have a lot of constraints and their is only one output, mostly 0.

CS150 Newton/Pister

8.1.27

State Assignment: Design Example

- Given the adjacency constraints:

1: {q0,q2,q4,q6}; {q0,q1,q3,q5}; {q3,q5}; {q4,q6}.

2: {q1,q2}; {q2,q3}; {q1,q4}; {q2,q5} twice; {q1,q6} twice.

- Choose number of flip-flops: 6 states so need at least 3 and no more than 6. Try with 3 -A, B, C say.
- Task is now to choose assignment of 3-bit (ABC) state codes to q1-q6 so that as many of the above constraints as possible are satisfied, in the order stated earlier.

| | | AB | | A | |
|---|---|-----------------|-----------------|-----------------|-----------------|
| | | 00 | 01 | 11 | 10 |
| C | 0 | q0 ₀ | q6 ₂ | q1 ₆ | 4 |
| | 1 | q2 ₁ | q4 ₃ | q3 ₇ | q5 ₅ |

B

| | | AB | | A | |
|---|---|-----------------|-----------------|-----------------|-----------------|
| | | 00 | 01 | 11 | 10 |
| C | 0 | q0 ₀ | q5 ₂ | q2 ₆ | 4 |
| | 1 | q1 ₁ | q3 ₃ | q4 ₇ | q6 ₅ |


B

CS150 Newton/Pister

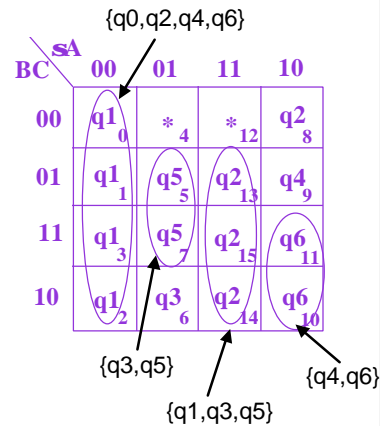8.1.28

State Assignment: Design Example

- Assignments achieved by trial-and-error (question: would we have been able to satisfy more constraints using 4 flip-flops instead of 3?).
- Top assignment leads to codes:
 $q_0 = 000$, $q_1 = 110$, $q_2 = 001$, $q_3 = 111$,
 $q_4 = 011$, $q_5 = 101$, $q_6 = 010$
- Now we can construct the next-state maps for the assignment.



CS150 Newton/Pister

8.1.29

Steps to FSM Design

- ✓ Construct a state/output table from the word description (or a state graph).
- ✓ *State Minimization*: Minimize the number of states (usually helps a bit).
- ✓ *State Assignment*: Choose a set of state variables and assign codes to named states.
- ✓ Substitute the state-variable combinations into the state/output table to create a *transition/output table* (next-state table) that shows the desired next-state variable combination for each state/input combination. Construct next-state K-maps as needed.
 - Choose a flip-flop type (e.g. D, J-K, T) for the state memory.
 - Construct an *excitation table* that shows the flip-flop input excitation values required to obtain the desired next-state value for each state/input combination.
 - Derive flip-flop *excitation equations* from excitation table.
 - Derive *output equations* from transition/output table.
 - Draw *logic diagram* that shows combinational next-state and output functions as well as flip-flops.

CS150 Newton/Pister

8.1.30

Guidelines for Determining Flip-Flop Input Equations from Next-State Map

| | | Q _n = 0 | | Q _n = 1 | | Rules for forming input map from next-state map (2) | |
|------|-------|---------------------|---------------------|---------------------|---------------------|---|------------------------|
| Type | Input | Q _{n+1} =0 | Q _{n+1} =1 | Q _{n+1} =0 | Q _{n+1} =1 | Q _n =0 half | Q _n =1 half |
| D | | 0 | 1 | 0 | 1 | no change | no change |
| T | EN | 0 | 1 | 1 | 0 | no change | complement |
| S-R | S | 0 | 1 | 0 | * | no change | replace 1s with *s |
| | R | * | 0 | 1 | 0 | replace 0s with *s | complement |
| J-K | J | 0 | 1 | * | * | no change | fill in with *s |
| | K | * | * | 1 | 0 | fill in with *s | complement |


Notes:

- (1) * = "don't care"
- (2) Always copy *s from next-state map to input map first
- (3) For S, Q_n=1 half and R, Q_n=0 half, fill remaining entries with 0s.

CS150 Newton/Pister

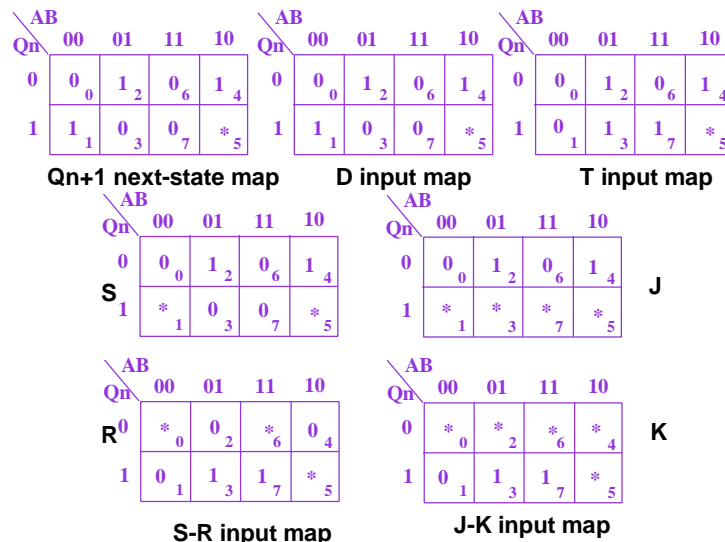8.1.31

Flip-Flop Input Equations From Next-State Map: Example




CS150 Newton/Pister

 8.1.32

Next-State Maps: Design Example

- Choose flip-flop types: D flip-flops
- Recall assignments:
 - q0 = 000, q1 = 110, q2 = 001, q3 = 111, q4 = 011, q5 = 101, q6 = 010
- Construct D input maps from next-state map, substituting state codes.



CS150 Newton/Pister

8.1.33

Steps to FSM Design

- ✓ Construct a state/output table from the word description (or a state graph).
- ✓ *State Minimization*: Minimize the number of states (usually helps a bit).
- ✓ *State Assignment*: Choose a set of state variables and assign codes to named states.
- ✓ Substitute the state-variable combinations into the state/output table to create a *transition/output table* (next-state table) that shows the desired next-state variable combination for each state/input combination. Construct next-state K-maps as needed.
- ✓ Choose a flip-flop type (e.g. D, J-K, T) for the state memory.
- ✓ Construct an *excitation table* that shows the flip-flop input excitation values required to obtain the desired next-state value for each state/input combination.
 - Derive flip-flop *excitation equations* from excitation table.
 - Derive *output equations* from transition/output table.
 - Draw *logic diagram* that shows combinational next-state and output functions as well as flip-flops.

CS150 Newton/Pister

8.1.34

Next-State Maps: Summary of Example

- Need 6 gates and 13 gate-inputs to implement the machine using this assignment.
- Straight binary assignment (q0=000, q1=001, etc.) would yield 10 gates and 39 gate-inputs.
- The approach gave good results in this example, but that is not always the case.

CS150 Newton/Pister

8.1.35

Derive Output Equations from Output Maps

| | | | | | |
|----|---|--------|--------|---------|---------|
| | A | 00 | 01 | 11 | 10 |
| BC | | 00 | 01 | 11 | 10 |
| 00 | | 0 0 | * 4 | * 12 | 0 8 |
| 01 | | 0 1 | 1 5 | 0 13 | 0 9 |
| 11 | | 0 3 | 0 7 | 0 15 | 0 11 |
| 10 | | 0 2 | 0 6 | 0 14 | 1 10 |

Output map from Transition/Output Table

CS150 Newton/Pister

8.1.36

Steps to FSM Design

- ✓ Construct a state/output table from the word description (or a state graph).
- ✓ *State Minimization*: Minimize the number of states (usually helps a bit).
- ✓ *State Assignment*: Choose a set of state variables and assign codes to named states.
- ✓ Substitute the state-variable combinations into the state/output table to create a *transition/output table* (next-state table) that shows the desired next-state variable combination for each state/input combination. Construct next-state K-maps as needed.
- ✓ Choose a flip-flop type (e.g. D, J-K, T) for the state memory.
- ✓ Construct an *excitation table* that shows the flip-flop input excitation values required to obtain the desired next-state value for each state/input combination.
- ✓ Derive flip-flop *excitation equations* from excitation table.
- ✓ Derive *output equations* from transition/output table.
- Draw *logic diagram* that shows combinational next-state and output functions as well as flip-flops.