



(1)	/30
(2)	/30
(3)	/40
TOTAL	/100

Quiz 2 Solutions

Room 10 Evans Hall, 2:10pm Tuesday April 7th

(Open Katz only, Calculators OK, 1hr 20mins)

Include all final answers in locations indicated on these pages and in pen. Use space provided for all working. If necessary, attach additional sheets by staple at the end. BE SURE TO WRITE YOUR NAME ON EVERY SHEET.

1. (30pts) (a) A digital system is required to amplify a binary-encoded audio signal. The user should be able to control the signal amplitude **from minimum to maximum in 100 increments**. What is the **minimum number of binary bits** required to encode the user-specified amplitude?

(b) *Excess-3 code* (Katz page 499) is a variation of binary-coded decimal (BCD) code. Each decimal digit is represented by a 4-bit code that is **three more than the associated BCD code**. For example, 0_{10} is encoded in excess-3 as 0011_2 , 1_{10} is encoded in excess-3 as 0100_2 , etc. Design a **single-output combinational logic circuit that outputs a 1 when the input to the circuit in 4-bit excess-3 code is a prime number**. For all other (non-prime) legal 4-bit excess-3 numbers applied to the inputs, the output is a 0. Assume **complement inputs are available** and implement the circuit using:


- (i) One **16-input, four control-line** multiplexer **only**.
- (ii) One **8-input, three control-line** multiplexer **only**.
- (iii) One **4-input, two control-line** multiplexer and a **minimum number of simple logic gates** (INV, NAND, NOR, AND, OR, XOR, XNOR)

1. (a) (5pts)

Number of bits = $2^6=64$ and $2^7=128$ so seven bits are required _____


1. (b) (i) (5pts) One 16-input MUX

Decimal	A	B	C	D	Prime
	0	0	0	0	-
	0	0	0	1	-
	0	0	1	0	-
0	0	0	1	1	1
1	0	1	0	0	1
2	0	1	0	1	1
3	0	1	1	0	1
4	0	1	1	1	0
5	1	0	0	0	1
6	1	0	0	1	0
7	1	0	1	0	1
8	1	0	1	1	0
9	1	1	0	0	0
	1	1	0	1	-
	1	1	1	0	-
	1	1	1	1	-

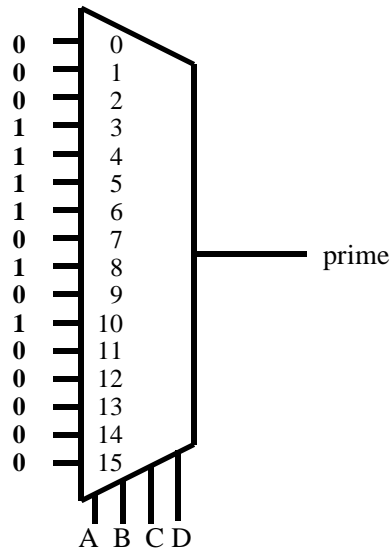


(additional space for solutions on reverse)

1. (b) (ii) (10pts) One 8-input MUX

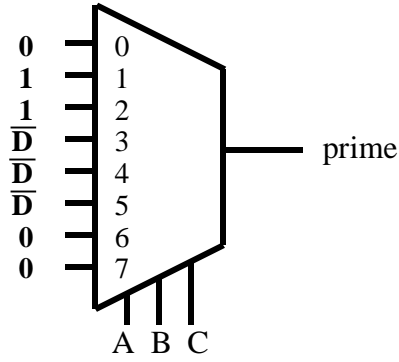

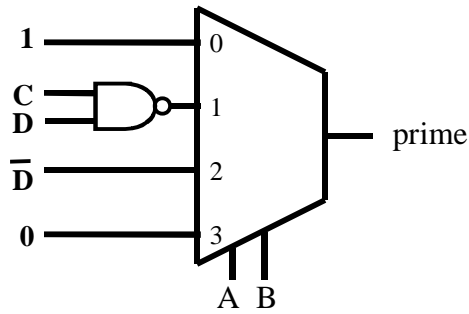1. (b) (iii) (10pts) One 4-input MUX and logic gates




Additional space for Problem 1

Your Name: _____

(2) (30 points)

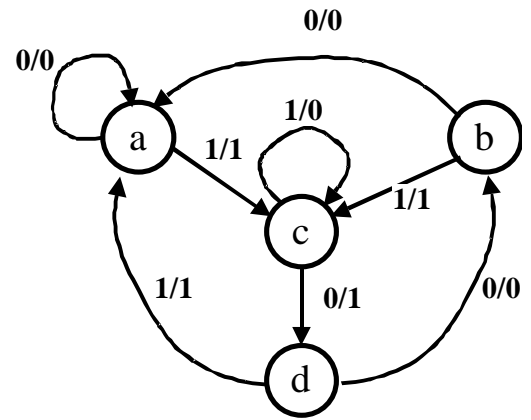- (a) What is the better way to implement arithmetic in a binary computer: **one's-complement** or **two's-complement**? Why? **Include all of the arguments you can think of for and against your answer.**
- (b) Does the state-machine opposite have any **equivalent states**? If so, **which states are equivalent**? Show all working.
- (c) Design a **4-bit ripple up-counter using positive edge-triggered D flip flops** and a minimum number of combinational logic gates. Show the schematic diagram.




(a) (10pts) One's or two's complement? Why?

2's complement
 + easier to do addition and subtraction (sum of -ve #s) (can be done in one byte-serial pass)
 + single representation for 0
 - must add 1 for making -ve #s

(continue on reverse if necessary)


(b) (10pts)

Equivalent states: a = b

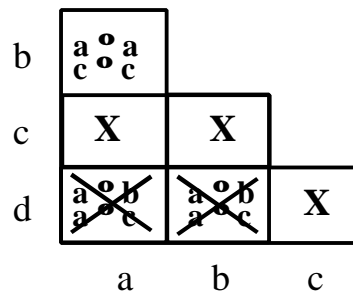

(additional space for solutions on reverse)

2.(c) (10pts) 4-bit ripple up-counter

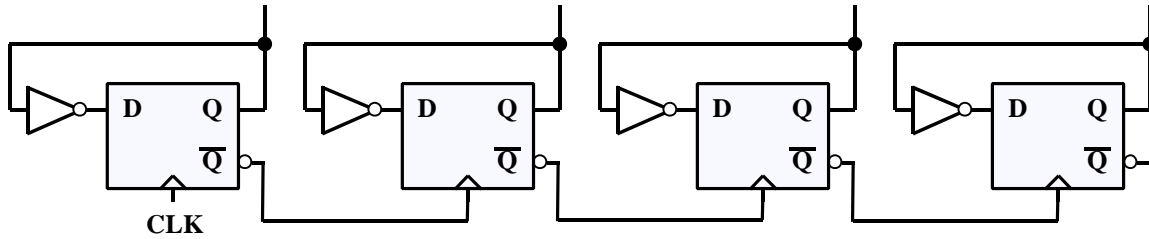

Additional space for Problem 2


Your Name: _____

3. (40 pts) Design a Moore machine that detects the number 9_{10} encoded in binary (1001_2) and in excess-3 (1100_2). The machine should reset after each detection (i.e. overlapping sequences are ignored). Sample input (X) and output (Z) sequences are given below:

X=1001100011001...
Z=0001000000010...

- (a) Draw a state transition diagram for the Moore machine.
- (b) Use an implication table to determine if any states are equivalent. If so, list the equivalent states and then re-draw your (now minimized) state diagram.
- (c) Using D flip-flops and the state-assignment rules discussed in class, indicate all adjacency constraints for an optimal state encoding and determine an optimal encoding, listing the state codes for each state in the machine.
- (d) Write equations for the next-state logic only (not the output logic) using a minimal NOR-NOR two-level representation.

3. (a) (10pts) State transition graph:

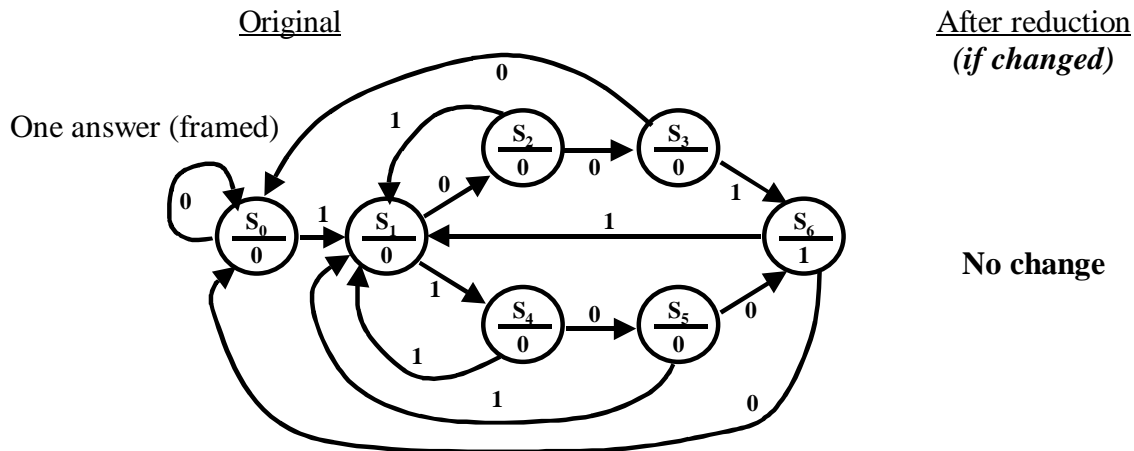

3. (b) (5pts) Implication table:

normal table with no equivalent states

(5pts) Equivalent States: _____ None _____

(additional space for solutions on reverse)

3. (c) (5pts) Adjacency constraints:

Rule 1: _____ {S₀, S₃, S₆}, {S₂, S₄, S₅}, {S₀, S₆} _____

Rule 2 _____ {S₀, S₁}, {S₂, S₄}, {S₀, S₃}, {S₀, S₆}, {S₀, S₅} _____

Rule 3: _____ {S₀, S₁, S₂, S₃, S₄, S₅} _____

(5 pts) Optimal state assignment (show Karnaugh map)

		Q_B			
	Q_C	00	01	11	10
Q_A	0	S ₀ ₀	S ₆ ₁	S ₅ ₃	S ₁ ₂
	1	S ₃ ₄	S ₂ ₅	S ₄ ₇	6
			└───┬───┘		
			Q_C		

State codes: ___ S₀=000, S₁=010, S₂=101, S₃=100, S₄=111, S₅=011, S₆=001 _____

3. (d) (10pts) Next-state logic in NOR-NOR form (equations only!):

— $D_A = \overline{(\overline{Q_B + Q_C}) + (\overline{Q_C + X}) + (\overline{Q_B + Q_C}) + (\overline{Q_A + Q_C})}$ —

— $D_B = \overline{(\overline{Q_A + X}) + (\overline{Q_A + Q_B}) + (\overline{Q_A + X}) + (\overline{Q_A + Q_B + Q_C})}$ —

— $D_C = \overline{(\overline{Q_A + Q_B}) + (\overline{Q_B + X}) + (\overline{Q_C + X})}$ —

Additional space for Problem 3