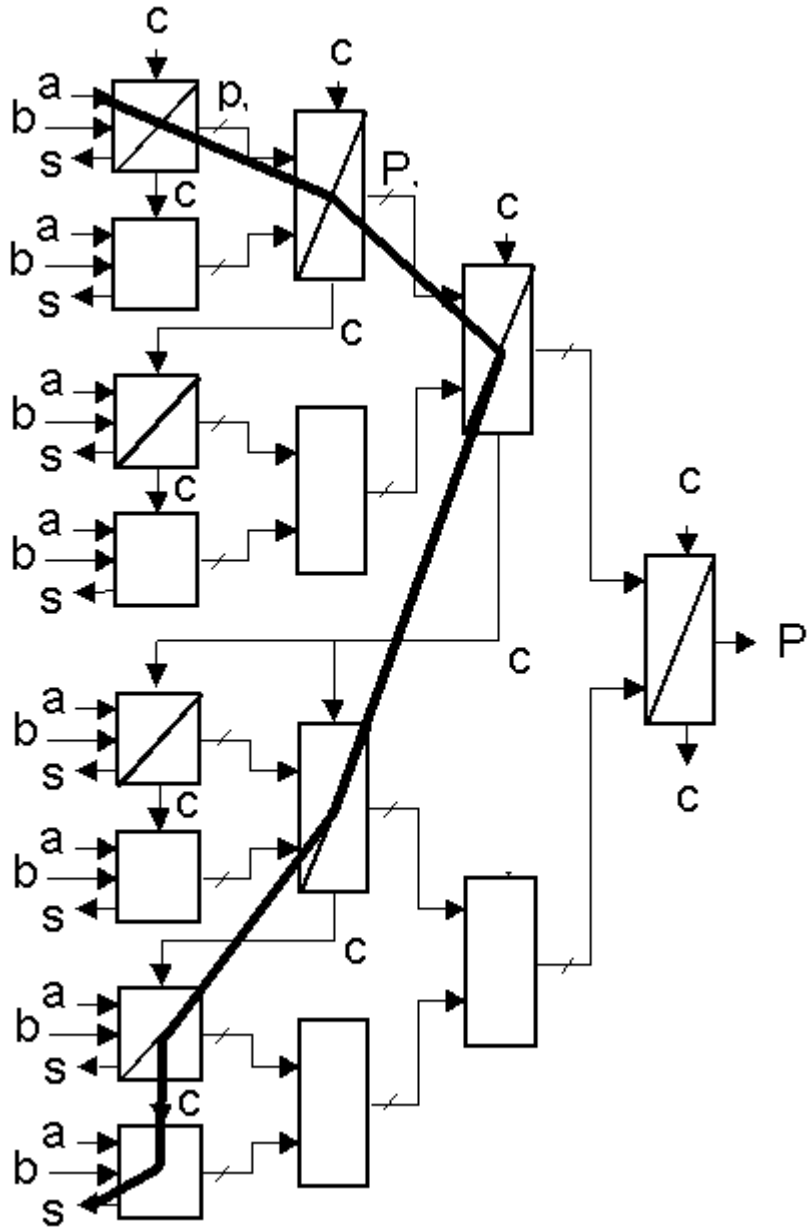


EECS150 Homework #5 Solutions:

1)



Delay: $O(\log n)$

Cost: $O(n)$

2)

30 4-LUTs.

3)

a) 3, 4, 5, 6, 7, 7

b) Delay = $O(\log n)$
Cost = $O(3^{\log n})$

4)

| | Cost | Delay |
|-----------------|------|-------|
| Carry-ripple | 384 | 130 |
| Carry-select A | 970 | 40 |
| Carry-select B | 5240 | 31 |
| Carry-propagate | 506 | 34 |

5)

a) $D = 0.05 * r + 0.4 (n / r - 1)$

b) $d / dr (0.05 * r + 0.4 (n / r - 1)) = 0$
 $0.05 - 0.4 * nr^{-2} = 0$
 $r^2 = 8n$
 $r = (8n)^{0.5}$

c) $n = 64; r = 21, 21, 22$
 $n = 128; r = 32$

6)

4-10)

$$O_0 = I_0$$


$$O_1 = I_1 \oplus I_0$$

$$O_2 = I_2 \oplus (I_1 + I_0)$$

$$O_3 = I_3 \oplus (I_2 + I_1 + I_0)$$

$$O_4 = I_4 \oplus (I_3 + I_2 + I_1 + I_0)$$

4-11)

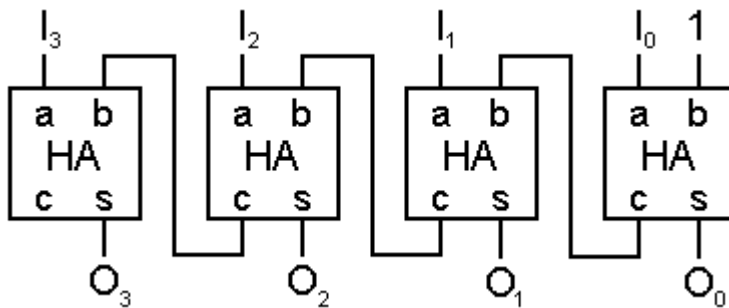

4-13)

a) SUM = 1101 C = 0 V = 1

b) SUM = 0001 C = 1 V = 1

c) SUM = 0100 C = 1 V = 0

d) SUM = 1011 C = 0 V = 1

e) SUM = 1111 C = 0 V = 0

4-15)

$$C_4 = G_3 + P_3 C_3$$

4-21)

