



EECS 150 - Components and Design Techniques for Digital Systems

Lec 03 – Field Programmable Gate Arrays 9-4-07

David Culler

Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://inst.eecs.berkeley.edu/~cs150>



Review

- Building blocks of computer systems
 - ICs (Chips), PCBs, Chassis, Cables & Connectors
- CMOS Transistors
 - Voltage controlled switches
 - Complementary forms (nmos, pmos)
- Logic gates from CMOS transistors
 - Logic gates implement particular boolean functions
 - » N inputs, 1 output
 - Serial and parallel switches
 - Dual structure
 - P-type “pull up” transmit 1
 - N-type
- Complex gates: mux
- Synchronous Sequential Elements [today]
 - D FlipFlops

9/4/2007

EECS 150, Fa07, Lec 03-fpga


2



 Question from Thurs

Transmission Gate

- Transmission gates are the way to build “switches” in CMOS.
- Both transistor types are needed:
 - nFET to pass zeros.
 - pFET to pass ones.
- The transmission gate is bi-directional (unlike logic gates and tri-state buffers).
- Functionally it is similar to the tri-state buffer, but does not connect to Vdd and GND, so must be combined with logic gates or buffers.



Together they go
Rail-to-Rail 😊

How does nFET behave

- when EN is Hi, S = D = Hi?
- when EN is Hi, S = D = lo?

Is it self restoring?

8/30/2007

© UC Berkeley

EECS150-F05 CMOS lec02

How does nFET behave

- when EN is Hi, S = D = lo?
- when EN is Hi, S = D = Hi?


9/4/2007

EECS 150, Fa07, Lec 03-fpga



Combinational vs. Sequential Digital Circuits

 - Simple model of a digital system is a unit with inputs and outputs:



- Combinational means "memory-less"
 - Digital circuit is combinational if its output values only depend on its inputs

9/4/2007

EECS 150, Fa07, Lec 03-fpga

4



Sequential logic

- **Sequential systems**
 - Exhibit behaviors (output values) that depend on current as *well* as previous inputs
- **All real circuits are sequential**
 - Outputs do not change instantaneously after an input change
 - Why not, and why is it then sequential?
- **Fundamental abstraction of digital design is to reason (mostly) about steady-state behaviors**
 - Examine outputs only after sufficient time has elapsed for the system to make its required changes and settle down




Synchronous sequential digital systems


- **Combinational circuit outputs depend *only* on current inputs**
 - After sufficient time has elapsed
- **Sequential circuits have *memory***
 - Even after waiting for transient activity to finish
- **Steady-state abstraction: most designers use it when constructing sequential circuits:**
 - Memory of system is its state
 - Changes in system state only allowed at specific times controlled by an external periodic signal (the *clock*)
 - Clock period is elapsed time between state changes sufficiently long so that system reaches steady-state before next state change at end of period




Recall: What makes Digital Systems tick?

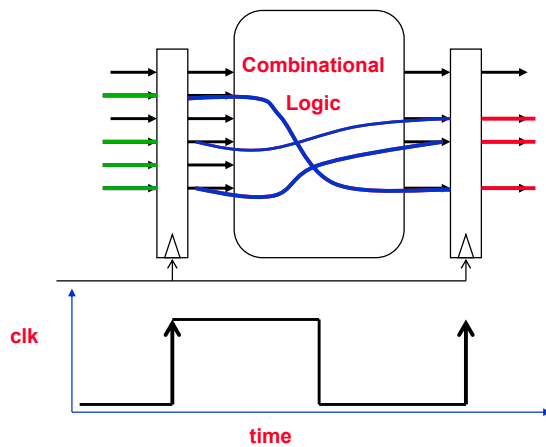

D-type edge-triggered flip-flop

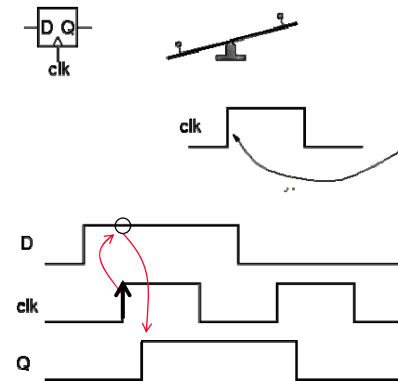


 - The edge of the clock is used to *sample* the "D" input & send it to "Q" (positive edge triggering).
 - At all other times the output Q is independent of the input D (just stores previously sampled value).
 - The input must be stable for a short time before the clock edge.





D-type edge-triggered flip-flop

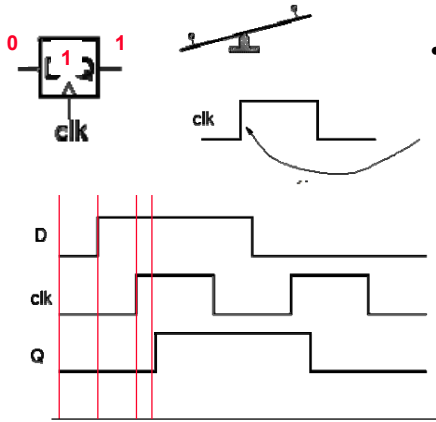


- The edge of the clock is used to *sample* the "D" input & send it to "Q" (positive edge triggering).
 - At all other times the output Q is independent of the input D (just stores previously sampled value).
 - The input must be stable for a short time before the clock edge.





Parallel to Serial Converter Example


LD X = [xn-1, xn-2, ..., x1, x0]

 

  
- Operation:
 - cycle 1: load x, output x₀
 - cycle i: output x_i



Parallel to Serial Converter Example



 


- timing:

 

Transistor-level Logic Circuits - Latch


- Positive Level-sensitive latch

   

D FlipFlop



Positive Edge-triggered Flip-flop

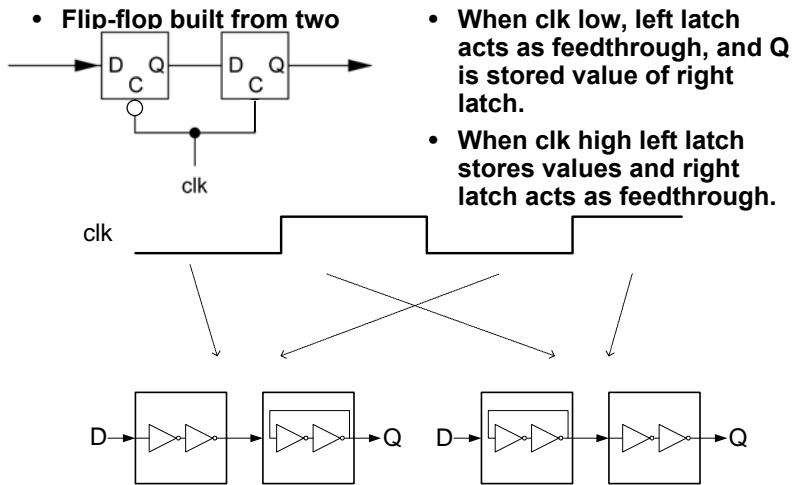

Summary: Representation of digital designs

- Physical devices (transistors, relays)
 - **Switches**
 - **Truth tables**
 - **Boolean algebra**
 - **Gates**
 - Waveforms
 - Finite state behavior
 - Register-transfer behavior
 - **Concurrent abstract specifications**
- scope of CS 150
more depth than 61C
focus on building systems



Outline

- Review
- What are FPGAs?
- Why use FPGAs (a short history lesson).
- Canonical Forms => Programmable Logic
- FPGA variations
- Internal logic blocks.
- Designing with FPGAs.
- Specifics of Xilinx Virtex-E series.


Today's reading

- Katz: 9.4 pp 428-447 (especially 9.4.4)
- XILINX Virtex-E FPGA data sheet (first 10 pages)



FPGA Overview

 - Basic idea: two-dimensional array of logic blocks and flip-flops with a means for the user to configure:
 1. the interconnection between the logic blocks,
 2. the function of each block.




Simplified version of FPGA internal architecture:



Why FPGAs?

- By the early 1980's most of the logic circuits in typical systems were absorbed by a handful of standard large scale integrated circuits (LSI).
 - Microprocessors, bus/IO controllers, system timers, ...
- Every system still had the need for random "glue logic" to help connect the large ICs:
 - generating global control signals (for resets etc.)
 - data formatting (serial to parallel, multiplexing, etc.)
- Systems had a few LSI components and lots of small low density SSI (small scale IC) and MSI (medium scale IC) components.

 

9/4/2007


EECS 150, Fa07, Lec 03-fpga

17



Why FPGAs?

- Custom ICs sometimes designed to replace the large amount of glue logic:
 - reduced system complexity and manufacturing cost, improved performance.
 - However, custom ICs are very expensive to develop, and delay introduction of product to market (time to market) because of increased design time.
- Note: need to worry about two kinds of costs:
 1. cost of development, sometimes called non-recurring engineering (NRE)
 2. cost of manufacture
 - A tradeoff usually exists between NRE cost and manufacturing costs

 

9/4/2007

EECS 150, Fa07, Lec 03-fpga

18



Why FPGAs?

- Custom IC approach viable for products that are ...
 - very high volume (where NRE could be amortized),
 - not time-to-market sensitive.
- FPGAs introduced as an alternative to custom ICs for implementing glue logic:
 - improved density relative to discrete SSI/MSI components (within around 10x of custom ICs)
 - with the aid of computer aided design (CAD) tools circuits could be implemented in a short amount of time (no physical layout process, no mask making, no IC manufacturing), relative to ASICs.
 - » lowers NREs
 - » shortens TTM
- Because of Moore's law the density (gates/area) of FPGAs continued to grow through the 80's and 90's to the point where major data processing functions can be implemented on a single FPGA.


9/4/2007

EECS 150, Fa07, Lec 03-fpga


19

Programmable Logic

 - Regular logic
 - Programmable Logic Arrays
 - Multiplexers/Decoders
 - ROMs
- Field Programmable Gate Arrays
 - Xilinx Vertex



"Random Logic"
Full Custom Design

 

"Regular Logic"
Structured Design

9/4/2007

EECS 150, Fa07, Lec 03-fpga





Canonical Forms

- Truth table is the unique signature of a Boolean function
- Many alternative gate realizations may have the same truth table
- Canonical forms
 - Standard forms for a Boolean expression
 - Provides a unique algebraic signature



Sum-of-Products Canonical Forms

- Also known as disjunctive normal form
- Also known as minterm expansion

$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$
 $F = A'B'C + A'BC + AB'C + ABC' + ABC$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F' = A'B'C' + A'BC' + AB'C'$



Sum-of-Products Canonical Form (cont'd)

- Product term (or minterm)
 - ANDed product of literals – input combination for which output is true
 - Each variable appears exactly once, in true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

short-hand notation for minterms of 3 variables

F in canonical form:

$$F(A, B, C) = \Sigma m(1,3,5,6,7)$$

$$= m1 + m3 + m5 + m6 + m7$$

$$= A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form ≠ minimal form

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC + ABC'$$

$$= (A'B' + A'B + AB' + AB)C + ABC'$$

$$= ((A' + A)(B' + B))C + ABC'$$

$$= C + ABC'$$

$$= ABC' + C$$

$$= AB + C$$



Product-of-Sums Canonical Form

- Also known as conjunctive normal form
- Also known as maxterm expansion

$F = 000 \quad 010 \quad 100$
 $F = (A + B + C) (A + B' + C) (A' + B + C)$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$

Product-of-Sums Canonical Form (cont'd)

- **Sum term (or maxterm)**

- ORed sum of literals – input combination for which output is false
- Each variable appears exactly once, in true or inverted form (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

F in canonical form:

$$F(A, B, C) = \Pi M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A + B + C)(A + B' + C)(A' + B + C)$$

canonical form \neq minimal form

$$F(A, B, C) = (A + B + C)(A + B' + C)(A' + B + C)$$

$$= (A + B + C)(A + B' + C)$$

$$(A + B + C)(A' + B + C)$$

$$= (A + C)(B + C)$$

short-hand notation for maxterms of 3 variables
9/4/2007

S-o-P, P-o-S, and deMorgan's Theorem

- **Sum-of-products**

- $F' = A'B'C' + A'BC' + AB'C'$

- **Apply de Morgan's**

- $(F')' = (A'B'C' + A'BC' + AB'C')'$

- $F = (A + B + C)(A + B' + C)(A' + B + C)$

- **Product-of-sums**


- $F' = (A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C')$

- **Apply de Morgan's**

- $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$

- $F = A'B'C' + A'BC' + AB'C' + ABC' + ABC$

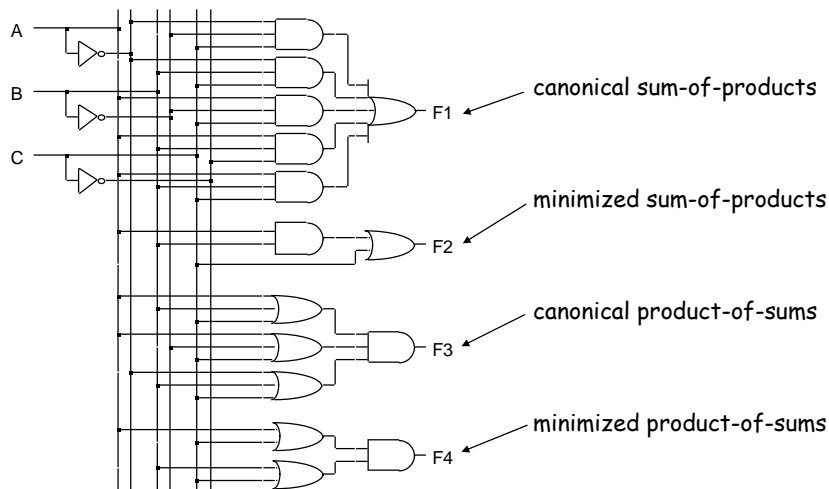
Four Alternative Two-level Implementations of $F = AB + C$



Waveforms for the Four Alternatives

- **Waveforms are essentially identical**

 - Except for timing hazards (glitches)
- Delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)





Mapping Between Canonical Forms

- **Minterm to maxterm conversion**
 - Use maxterms whose indices do not appear in minterm expansion
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7) = \Pi M(0,2,4)$
- **Maxterm to minterm conversion**
 - Use minterms whose indices do not appear in maxterm expansion
 - e.g., $F(A,B,C) = \Pi M(0,2,4) = \Sigma m(1,3,5,6,7)$
- **Minterm expansion of F to minterm expansion of F'**
 - Use minterms whose indices do not appear
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7)$ $F'(A,B,C) = \Sigma m(0,2,4)$
- **Maxterm expansion of F to maxterm expansion of F'**
 - Use maxterms whose indices do not appear
 - e.g., $F(A,B,C) = \Pi M(0,2,4)$ $F'(A,B,C) = \Pi M(1,3,5,6,7)$

9/4/2007

EECS 150, Fa07, Lec 03-fpga

29



Incompletely Specified Functions

- **Example: binary coded decimal increment by 1**
 - BCD digits encode decimal digits 0 – 9 in bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	1	0	
0	0	1	0	0	1	1	
0	0	1	1	1	0	0	
0	1	0	0	1	1	0	1
0	1	0	1	1	1	1	0
0	1	1	0	1	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Annotations:

- off-set of W (rows 1, 2, 3, 4)
- on-set of W (rows 5, 6, 7, 8)
- don't care (DC) set of W (rows 9, 10, 11, 12, 13, 14, 15, 16)
- these inputs patterns should never be encountered in practice - "don't care" about associated output values, can be exploited in minimization

9/4/2007

EECS 150, Fa07, Lec 03-fpga

30



Notation for Incompletely Specified Functions

- **Don't cares and canonical forms**
 - So far, only represented on-set
 - Also represent don't-care-set
 - Need two of the three sets (on-set, off-set, dc-set)
- **Canonical representations of the BCD increment by 1 function:**
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$

9/4/2007

EECS 150, Fa07, Lec 03-fpga

31



Simplification of Two-level Combinational Logic

- **Finding a minimal sum of products or product of sums realization**
 - Exploit don't care information in the process
- **Algebraic simplification**
 - Not an algorithmic/systematic procedure
 - How do you know when the minimum realization has been found?
- **Computer-aided design tools**
 - Precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - Heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- **Hand methods still relevant**
 - Understand automatic tools and their strengths and weaknesses
 - Ability to check results (on small examples)

9/4/2007


EECS 150, Fa07, Lec 03-fpga

32



Programmable Logic Arrays (PLAs)

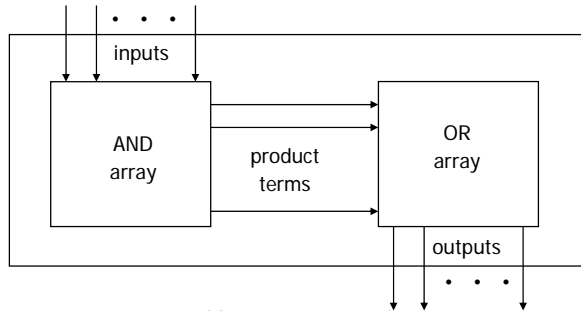- Pre-fabricated building block of many AND/OR gates
 - Actually NOR or NAND
 - "Personalized" by making or breaking connections among gates
 - Programmable array block diagram for sum of products form



9/4/2007

EECS 150, Fa07, Lec 03-fpga

33



Enabling Concept

- Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

input side:
 1 = uncomplemented in term
 0 = complemented in term
 - = does not participate

output side:
 1 = term connected to output
 0 = no connection to output

reuse of terms

9/4/2007


EECS 150, Fa07, Lec 03-fpga

34



Before Programming

 - All possible connections available before "programming"
 - In reality, all AND and OR gates are NANDs



9/4/2007


EECS 150, Fa07, Lec 03-fpga

35



After Programming

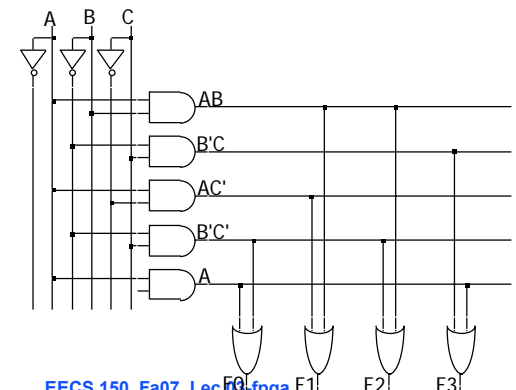- Unwanted connections are "blown"
 - Fuse (normally connected, break unwanted ones)
 - Anti-fuse (normally disconnected, make wanted connections)



9/4/2007

EECS 150, Fa07, Lec 03-fpga

36



Announcements

- Homework #1 due Friday 2pm. (#2 out thurs)
- Please do the reading (the earlier the better).
- Attend discussions!
 - Held this week. Propose Fridays 11-12 and 1-2, Take vote
- Homework is an important part of the class:
 - It goes beyond what is covered in class.
 - High correlation to exam questions.
 - Work on it seriously.
 - We'll try to post it early.
 - Discussion is a good place to get hints about homework.
- Unlike some of our lower division classes we will not necessarily tell you everything you need to know. Some of it will come from readings and homework.

9/4/2007

EECS 150, Fa07, Lec 03-fpga

37



Why FPGAs?

- Much more general form of programmable logic
- FPGAs continue to compete with custom ICs for special processing functions (and glue logic) but now also compete with microprocessors in dedicated and embedded applications.
 - Performance advantage over microprocessors because circuits can be customized for the task at hand. Microprocessors must provide special functions in software (many cycles).

- Summary:

	performance	NREs	Unit cost	TTM
↑	ASIC	ASIC	FPGA	ASIC
	FPGA	FPGA	MICRO	FPGA
	MICRO	MICRO	ASIC	MICRO

ASIC = custom IC, MICRO = microprocessor + SW

9/4/2007

EECS 150, Fa07, Lec 03-fpga


38




FPGA Variations

- Families of FPGA's differ in:
 - physical means of implementing user programmability,
 - arrangement of interconnection wires, and
 - the basic functionality of the logic blocks.
- Most significant difference is in the method for providing flexible blocks and connections:

- Anti-fuse based (ex: Actel)

 

 - + Non-volatile, relatively small
- fixed (non-reprogrammable)



9/4/2007


EECS 150, Fa07, Lec 03-fpga

39



User Programmability

 - Latch-based (Xilinx, Altera, ...)
- Latches are used to:
 1. make or break cross-point connections in the interconnect
 2. define the function of the logic blocks
 3. set user options:
 - » within the logic blocks
 - » in the input/output blocks
 - » global reset/clock
- "Configuration bit stream" can be loaded under user control:
 - All latches are strung together in a shift chain:



- + reconfigurable
- volatile
- relatively large.


9/4/2007

EECS 150, Fa07, Lec 03-fpga

40



Idealized FPGA Logic Block

 

- **4-input look up table (LUT)**
 - implements combinational logic functions
- **Register**
 - optionally stores output of LUT

what's a LUT?



Boolean Functions: 1 variable

A	False	A	\bar{A}	A	A	A	TRUE
0	0	0	1	0	0	0	1
1	0	1	0	1	1	1	1

A	False	\bar{A}	A	True
0	0	1	0	1
1	0	0	1	1

- What are the possible boolean functions of two variable?




Interactive Quiz: Boolean Functions of 2 variables?

A	B	False ??	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB	True
0	0	0 1	0 1	0 1	0 1	0 1	1
0	1	0 0	1 1	0 0	0 1	0 1	1
1	0	0 0	0 0	1 1	1 1	1 1	1
1	1	0 0	0 0	0 0	0 0	0 0	1

- What are the possible boolean functions of 3, 4 variables?



 
How could you build a generic boolean logic circuit?



- 1-bit memory to hold boolean value
- Address is vector of boolean input values
- Contents encode a boolean function
- Read out logical value (col) for associated row

Recall: Multiplexer/Demultiplexer

 - **Multiplexer:** route one of many inputs to a single output
- **Demultiplexer:** route single input to one of many outputs




9/4/2007

EECS 150, Fa07, Lec 03-fpga

45

Multiplexers/Selectors – a logical function

 - **Multiplexers/Selectors: general concept**
 - 2^n data inputs, n control inputs (called "selects"), 1 output
 - Used to connect 2^n points to a single point
 - Control signal pattern forms binary index of input connected to output




9/4/2007

EECS 150, Fa07, Lec 03-fpga

46

Multiplexers/Selectors: to implement logic

 - 2:1 mux: $Z = A' I_0 + A I_1$
- 4:1 mux: $Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$
- 8:1 mux: $Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$
- In general, $Z = \sum_{k=0}^{2^n-1} (m_k I_k)$
 - in minterm shorthand form for a $2^n:1$ Mux




9/4/2007

EECS 150, Fa07, Lec 03-fpga

47

Cascading Multiplexers

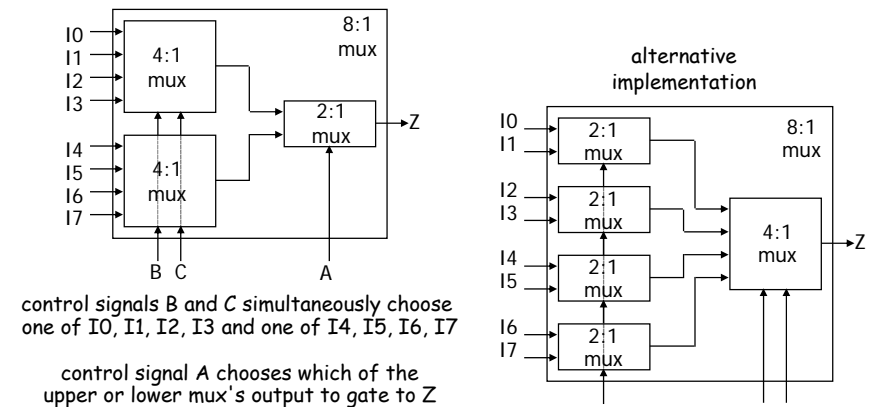- Large multiplexers implemented by cascading smaller ones



9/4/2007

EECS 150, Fa07, Lec 03-fpga

48




Multiplexers as Lookup Tables (LUTs)

• 2ⁿ:1 multiplexer implements any function of n variables

- With the variables used as control inputs and
- Data inputs tied to 0 or 1
- In essence, a *lookup table*

 • Example:

- $F(A,B,C) = m_0 + m_2 + m_6 + m_7$
 $= A'B'C' + A'BC' + ABC' + ABC$
 $= A'B'(C') + A'B(C') + AB'(0) + AB(1)$



9/4/2007

EECS 150, Fa07, Lec 03-fpga




Multiplexers as LUTs (cont'd)

• 2ⁿ⁻¹:1 mux can implement any function of n variables

- With n-1 variables used as control inputs and
- Data inputs tied to the last variable or its complement

 • Example:


- $F(A,B,C) = m_0 + m_2 + m_6 + m_7$
 $= A'B'C' + A'BC' + ABC' + ABC$
 $= A'B'(C') + A'B(C') + AB'(0) + AB(1)$



9/4/2007

EECS 150, Fa07, Lec 03-fpga

4-LUT Implementation

 

• n-bit LUT is implemented as a 2ⁿ x 1 memory:

- inputs choose one of 2ⁿ memory locations.
- memory locations (latches) are normally loaded with values from user's configuration bit stream.
- Inputs to mux control are the CLB inputs.

- Result is a general purpose "logic gate".
- n-LUT can implement any function of n inputs!

EECS 150, Fa07, Lec 03-fpga



LUT as general logic gate

Example: 4-lut

- An n-lut as a direct implementation of a function truth-table.
- Each latch location holds the value of the function corresponding to one input combination.

Example: 2-lut

INPUTS	AND	OR
00	0	0
01	0	1
10	0	1
11	1	1

Implements any function of 2 inputs.

How many of these are there?


How many functions of n inputs?

INPUTS	Function	Notes
0000	F(0,0,0,0)	store in 1st latch
0001	F(0,0,0,1)	store in 2nd latch
0010	F(0,0,1,0)	
0011	F(0,0,1,1)	
0100		
0101		
0110		
0111		
1000		
1001		
1010		
1011		
1100		
1101		
1110		
1111		

9/4/2007


EECS 150, Fa07, Lec 03-fpga

FPGA Generic Design Flow

 

- **Design Entry:**
 - Create your design files using:
 - » schematic editor or
 - » hardware description language (Verilog, VHDL)
- **Design "implementation" on FPGA:**
 - Partition, place, and route to create bit-stream file
- **Design verification:**
 - Use Simulator to check function,
 - other software determines max clock frequency.
 - Load onto FPGA device (cable connects PC to development board)
 - » check operation at full speed in real environment.

Example Partition, Placement, and Route

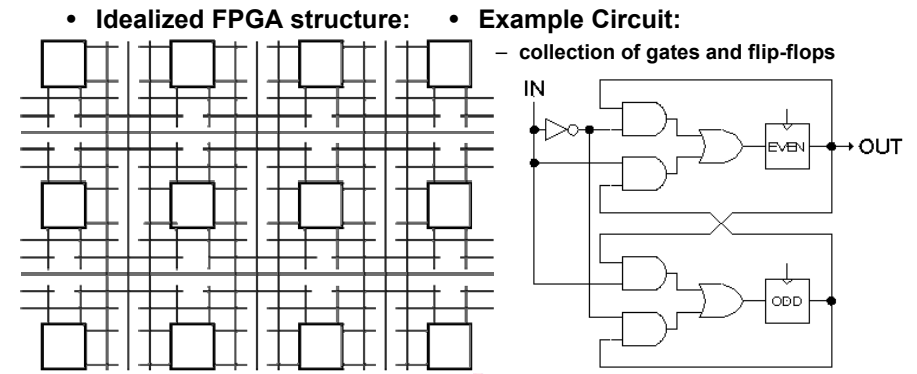


Circuit combinational logic must be "covered" by 4-input 1-output "gates".
 Flip-flops from circuit must map to FPGA flip-flops.
 (Best to preserve "closeness" to CL to minimize wiring.)
 Placement in general attempts to minimize wiring.

Xilinx Virtex-E Floorplan

Configurable Logic Blocks

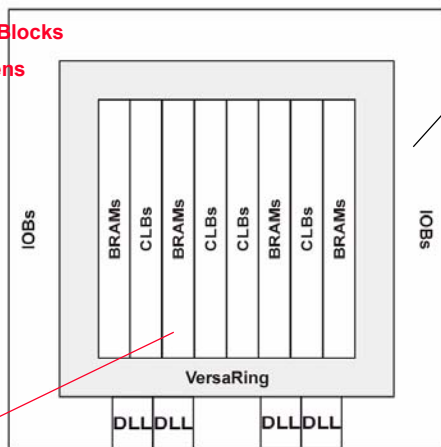- 4-input function gens
- buffers
- flipflop



- Input/Output Blocks**
- combinational, latch, and flipflop output
 - sampled inputs

Block RAM


- 4096 bits each
- every 12 CLB columns

Virtex-E Configurable Logic Block (CLB)

CLB = 4 logic cells (LC) in two slices


LC: 4-input function generator, carry logic, storage ele't

80 x 120 CLB array on 2000E

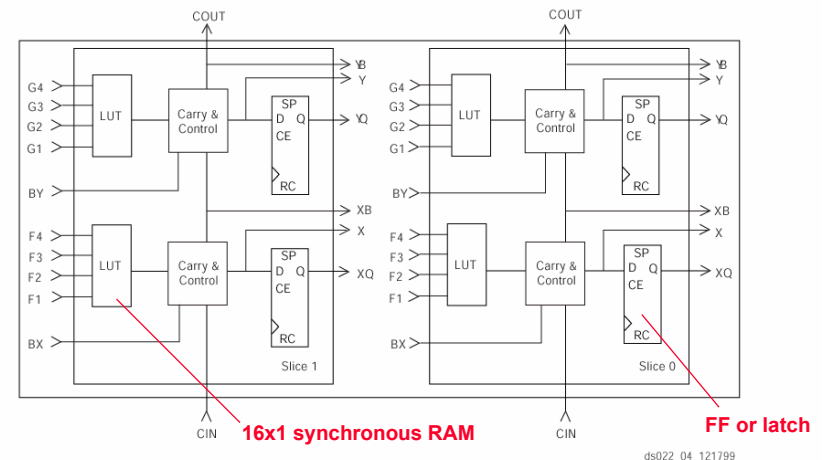



Details of Virtex-E Slice

 

- LUT**
- 4-input fun
- 16x1 sram
- 32x1 or 16x2 in slice
- 16 bit shift register
- Storage element**
- D flipflip
- latch
- Combinational outputs**
- 5 and 6 input functions**
- Carry chain**
- arithmetic along row or col


9/4/2007

EECS 150, Fa07, Lec 03-fpga

57



Xilinx FPGAs (interconnect detail)

 


9/4/2007

58



Virtex-E Input/Output block (IOB) detail

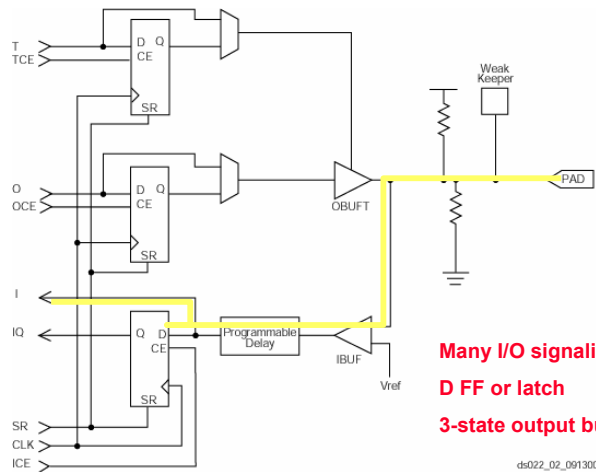

- Many I/O signaling stds**
- D FF or latch**
- 3-state output buf**

9/4/2007

EECS 150, Fa07, Lec 03-fpga

59



Virtex-E Family of Parts

Table 1: Virtex-E Field-Programmable Gate Array Family Members

Device	System Gates	Logic Gates	CLB Array	Logic Cells	Differential I/O Pairs	User I/O	BlockRAM Bits	Distributed RAM Bits
XCV50E	71,693	20,736	16 x 24	1,728	83	176	65,536	24,576
XCV100E	128,236	32,400	20 x 30	2,700	83	196	81,920	38,400
XCV200E	306,393	63,504	28 x 42	5,292	119	284	114,688	75,264
XCV300E	411,955	82,944	32 x 48	6,912	137	316	131,072	98,304
XCV400E	569,952	129,600	40 x 60	10,800	183	404	163,840	153,600
XCV600E	985,882	186,624	48 x 72	15,552	247	512	294,912	221,184
XCV1000E	1,569,178	331,776	64 x 96	27,648	281	660	393,216	393,216
XCV1600E	2,188,742	419,904	72 x 108	34,992	344	724	589,824	497,664
XCV2000E	2,541,952	518,400	80 x 120	43,200	344	804	655,360	614,400
XCV2600E	3,263,755	685,584	92 x 138	57,132	344	804	753,664	812,544
XCV3200E	4,074,387	876,096	104 x 156	73,008	344	804	851,968	1,038,336

9/4/2007

EECS 150, Fa07, Lec 03-fpga

60



Xilinx FPGAs

- **How they differ from idealized array:**
 - In addition to their use as general logic “gates”, LUTs can alternatively be used as general purpose RAM.
 - » Each 4-lut can become a 16x1-bit RAM array.
 - Special circuitry to speed up “ripple carry” in adders and counters.
 - » Therefore adders assembled by the CAD tools operate much faster than adders built from gates and luts alone.
 - Many more wires, including tri-state capabilities.



Summary

- **Logic design process influenced by available technology AND economic drivers**
 - Volume, Time to Market, Costs, Power
- **Fundamental understanding of digital design techniques carry over**
 - Specifics on design trade-offs and implementation differ
- **FPGA offer a valuable new sweet spot**
 - Low TTM, medium cost, tremendous flexibility
- **Fundamentally tied to powerful CAD tools**
- **Build everything (simple or complex) from one set of building blocks**
 - LUTs + FF + routing + storage + IOs