



# EECS 150 - Components and Design Techniques for Digital Systems

## Lec 04 – Hardware Description Languages / Verilog

9/6/2007

David Culler

Electrical Engineering and Computer Sciences  
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>  
<http://inst.eecs.berkeley.edu/~cs150>



## Review

- Advancing technology changes the trade-offs and design techniques
  - 2x transistors per chip every 18 months
- ASIC, Programmable Logic, Microprocessor
- Programmable logic invests chip real-estate to reduce design time & time to market
  - Canonical Forms, Logic Minimization, PLAs, →
- FPGA:
  - programmable interconnect,
  - configurable logic blocks
    - » LUT + storage
  - Block RAM
  - IO Blocks



## Outline

- Netlists
- Design flow
- What is a HDL?
- Verilog
- Announcements
- Structural models
- Behavioral models
- Elements of the language
- Lots of examples

**Firehose Day!**




## Remember: to design is to represent

- How do we represent digital designs?
- Components
  - Logic symbol, truth table
  - Storage symbol, timing diagram
- Connections
  - Schematics

Human readable or machine readable???




## Design Flow

 

## Netlist

- A key data structure (or representation) in the design process is the “netlist”:
  - Network List
- A netlist lists components and connects them with nodes:

ex:

 

```

g1 "and" n1 n2 n5
g2 "and" n3 n4 n6
g3 "or" n5 n6 n7
  
```

Alternative format:


```

n1 g1.in1
n2 g1.in2
n3 g2.in1
n4 g2.in2
n5 g1.out g3.in1
n6 g2.out g3.in2
n7 g3.out
g1 "and"
g2 "and"
g3 "or"
  
```

- Netlist is needed for simulation and implementation.
- Could be at the transistor level, gate level, ...
- Could be hierarchical or flat.
- How do we generate a netlist?




## Design Flow

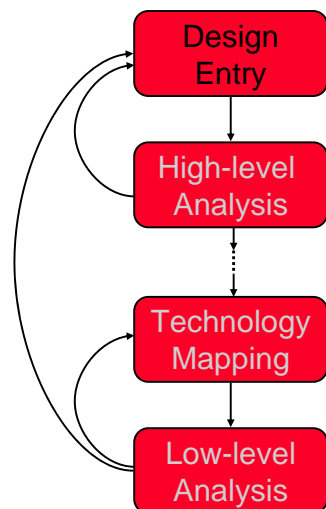

- Circuit is described and represented:
  - Graphically (Schematics)
  - Textually (HDL)
- Result of circuit specification (and compilation) is a netlist of:
  - generic primitives - logic gates, flip-flops, or
  - technology specific primitives - LUTs/CLBs, transistors, discrete gates, or
  - higher level library elements - adders, ALUs, register files, decoders, etc.




## Design Flow

 


- High-level Analysis is used to verify:
  - correct function
  - rough:
    - » timing
    - » power
    - » cost
- Common tools used are:
  - simulator - check functional correctness, and
  - static timing analyzer
    - » estimates circuit delays based on timing model and delay parameters for library elements (or primitives).

## Design Flow

 


- **Technology Mapping:**
  - Converts netlist to implementation technology dependent details
    - » Expands library elements,
    - » performs:
      - partitioning,
      - placement,
      - routing
- **Low-level Analysis**
  - Simulation and Analysis Tools perform low-level checks with:
    - » accurate timing models,
    - » wire delay
  - For FPGAs this step could also use the actual device.

## Design Flow

 
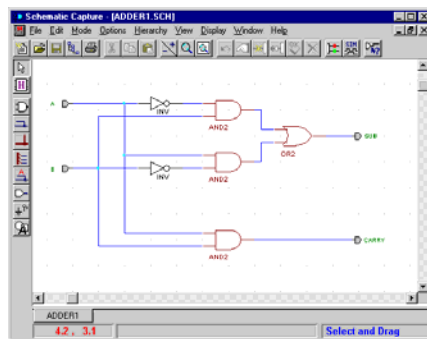
## Design Entry

- Schematic entry/editing used to be the standard method in industry
- Used in EECS150 until recently
- ☺ Schematics are intuitive. They match our use of gate-level or block diagrams.
- ☺ Somewhat physical. They imply a physical implementation.
- ☹ Require a special tool (editor).
- ☹ Unless hierarchy is carefully designed, schematics can be confusing and difficult to follow.



- **Hardware Description Languages (HDLs) are the new standard**
  - except for PC board design, where schematics are still used.

## HDLs

- **Basic Idea:**
  - Language constructs describe circuits with two basic forms:
    - *Structural descriptions* similar to hierarchical netlist.
    - *Behavioral descriptions* use higher-level constructs (similar to conventional programming).
- **Originally designed to help in abstraction and simulation.**
  - Now “logic synthesis” tools exist to automatically convert from behavioral descriptions to gate netlist.
  - Greatly improves designer productivity.
  - However, this may lead you to falsely believe that hardware design can be reduced to writing programs!

### “Structural” example:

```

Decoder(output x0,x1,x2,x3;
         inputs a,b)
{
  wire abar, bbar;
  inv(bbar, b);
  inv(abar, a);
  nand(x0, abar, bbar);
  nand(x1, abar, b );
  nand(x2, a, bbar);
  nand(x3, a, b );
}
  
```

### “Behavioral” example:


```

Decoder(output x0,x1,x2,x3;
         inputs a,b)
{
  case [a b]
    00: [x0 x1 x2 x3] = 0x0;
    01: [x0 x1 x2 x3] = 0x2;
    10: [x0 x1 x2 x3] = 0x4;
    11: [x0 x1 x2 x3] = 0x8;
  endcase;
}
  
```


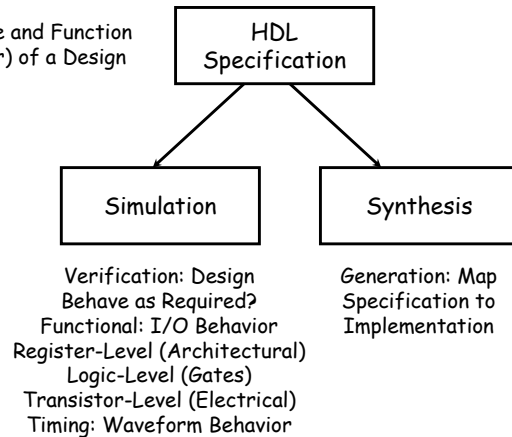
## Design Methodology

Structure and Function  
(Behavior) of a Design



## Quick History of HDLs

- **ISP (circa 1977) - research project at CMU**
  - Simulation, but no synthesis
- **Abel (circa 1983) - developed by Data-I/O**
  - Targeted to programmable logic devices
  - Not good for much more than state machines
- **Verilog (circa 1985) - developed by Gateway (now Cadence)**
  - Similar to Pascal and C, originally developed for simulation
  - Fairly efficient and easy to write
  - 80s Berkeley develops synthesis tools
  - IEEE standard
- **VHDL (circa 1987) - DoD sponsored standard**
  - Similar to Ada (emphasis on re-use and maintainability)
  - Simulation semantics visible
  - Very general but verbose
  - IEEE standard



## Verilog

- **Supports structural and behavioral descriptions**
- **Structural**
  - Explicit structure of the circuit
  - How a module is composed as an interconnection of more primitive modules/components
  - E.g., each logic gate instantiated and connected to others
- **Behavioral**
  - Program describes input/output behavior of circuit
  - Many structural implementations could have same behavior
  - E.g., different implementations of one Boolean function



## Verilog Introduction

- **the module describes a component in the circuit**
- **Two ways to describe:**
  - **Structural Verilog**
    - » List of components and how they are connected
    - » Just like schematics, but using text
      - A net list
    - » tedious to write, hard to decode
    - » Essential without integrated design tools
  - **Behavioral Verilog**
    - » Describe *what* a component does, not *how* it does it
    - » Synthesized into a circuit that has this behavior
    - » Result is only as good as the tools
- **Build up a hierarchy of modules**




# Structural Model - XOR

```

module xor_gate (out, a, b);
  input  a, b;
  output out;
  wire  abar, bbar, t1, t2;
  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);
endmodule

```

 Annotations: **module name** (xor\_gate), **port list** (out, a, b), **declarations** (input, output, wire), **statements** (inverter, and\_gate, or\_gate), **interconnections** (wires connecting gates).



- Composition of primitive gates to form more complex module
- Note use of wire declaration!

By default, identifiers are wires




# Structural Model: 2-to1 mux

```

//2-input multiplexor in gates
module mux2 (in0, in1, select, out);
  input in0,in1,select;
  output out;
  wire s0,w0,w1;
  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or (out, w0, w1);
endmodule // mux2

```

 - Notes:
  - comments
  - "module"
  - port list
  - declarations
  - wire type
  - primitive gates
  - Instance names?
  - List per type



# Simple Behavioral Model

- Combinational logic
  - Describe output as a function of inputs
  - Note use of assign keyword: *continuous* assignment

```

module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  assign out = in1 & in2;
endmodule

```

Annotations: **Output port of a primitive must be first in the list of ports** (pointing to 'out'), **Restriction does not apply to modules in general** (pointing to 'assign out = in1 & in2;').

When is this "evaluated"?



# 2-to-1 mux behavioral description

```

// Behavioral model of 2-to-1
// multiplexor.
module mux2 (in0,in1,select,out);
  input in0,in1,select;
  output out;
  //
  reg out;
  always @ (in0 or in1 or select)
    if (select) out=in1;
    else out=in0;
endmodule // mux2

```

- Notes:
  - behavioral descriptions using keyword *always* followed by blocking *procedural* assignments
  - Target output of procedural assignments must of of type *reg* (not a real register)
  - Unlike wire types where the target output of an assignment may be continuously updated, a *reg* type retains it value until a new value is assigned (the assigning statement is executed).
  - Optional initial statement

Sensitivity list



## Behavioral 4-to1 mux

```
//Does not assume that we have
// defined a 2-input mux.
```

```
//4-input mux behavioral description
```

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  reg out;

  always @ (in0 in1 in2 in3 select)
    case (select)
      2'b00: out=in0;
      2'b01: out=in1;
      2'b10: out=in2;
      2'b11: out=in3;
    endcase
endmodule // mux4
```

### Notes:

- No instantiation
- Case construct equivalent to nested if constructs.
- **Definition:** A structural description is one where the function of the module is defined by the instantiation and interconnection of sub-modules.
- A behavioral description uses higher level language constructs and operators.
- Verilog allows modules to mix both behavioral constructs and sub-module instantiation.



## Mixed Structural/Behavioral Model

### Example 4-bit ripple adder

```
module full_addr (S,Cout,A, B, Cin );
  input A, B, Cin;
  output S, Cout;
```

```
  assign {Cout, S} = A + B + Cin;
endmodule
```

Behavior

```
module adder4 (S,Cout,A, B, Cin);
  input [3:0] A, B;
  input Cin;
  output [3:0] S;
  output Cout;
  wire C1, C2, C3;
```

Structural

```
  full_addr fa0 (S[0], C1, A[0], B[0], Cin);
  full_addr fa1 (S[1], C2, A[1], B[1], C1);
  full_addr fa2 (S[2], C3, A[2], B[2], C2);
  full_addr fa3 (S[3], Cout, A[3], B[3], C3);
endmodule
```



## Announcements

Office hours will be posted on [schedule.php](#)  
 Homework 1 due tomorrow (2 pm outside 125)  
 Homework 2 out today  
 Feedback on labs, Lab lectures

### Reading:

- these notes
- verilog code you see in lab



## Verilog Help

- The lecture notes only cover the basics of Verilog and mostly the conceptual issues.
  - Lab Lectures have more detail focused on lab material
- Textbook has examples.
- Bhasker book is a good tutorial.
- <http://www.doe.carleton.ca/~shams/97350/PetervrIK.pdf> pretty good
- The complete language specification from the IEEE is available on the class website under "Refs/Links"
- <http://toolbox.xilinx.com/docsan/xilinx4/data/docs/xst/verilog2.html>





# Verilog Data Types and Values

- **Bits - value on a wire**
  - 0, 1
  - X - don't care/don't know
  - Z - undriven, tri-state
- **Vectors of bits**
  - A[3:0] - vector of 4 bits: A[3], A[2], A[1], A[0]
  - Treated as an *unsigned* integer value
    - » e.g., A < 0 ??
  - Concatenating bits/vectors into a vector
    - » e.g., sign extend
    - » B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};
    - » B[7:0] = {3{A[3]}, A[3:0]};
  - **Style: Use** a[7:0] = b[7:0] + c;  
**Not:** a = b + c; // need to look at declaration



# Verilog Numbers

- 14 - ordinary decimal number
- -14 - 2's complement representation
- 12'b0000\_0100\_0110 - binary number with 12 bits (\_ is ignored)
- 12'h046 - hexadecimal number with 12 bits
- **Verilog values are *unsigned***
  - e.g., C[4:0] = A[3:0] + B[3:0];
  - if A = 0110 (6) and B = 1010(-6)  
 C = 10000 not 00000  
 i.e., B is zero-padded, not sign-extended



# Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ &   ~& ~  ^ ~^ or ^~	logical negation negation AND reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{() }	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

>	greater than	Relational
>=	greater than or equal to	Relational
<	less than	Relational
<=	less than or equal to	Relational
==	logical equality	Equality
!=	logical inequality	Equality
===	case equality	Equality
!==	case inequality	Equality
&	bit-wise AND	Bit-wise
^	bit-wise XOR	Bit-wise
^~ or ~^	bit-wise XNOR	Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional



# Verilog Variables


- **wire**
  - Variable used simply to connect components together
- **reg**
  - Variable that saves a value as part of a behavioral description
  - Usually corresponds to a wire in the circuit
  - Is *NOT* necessarily a register in the circuit
- **usage:**
  - Don't confuse reg assignments with the combinational continuous assign statement! (more soon)
  - Reg should only be used with always blocks (sequential logic, to be presented ...)


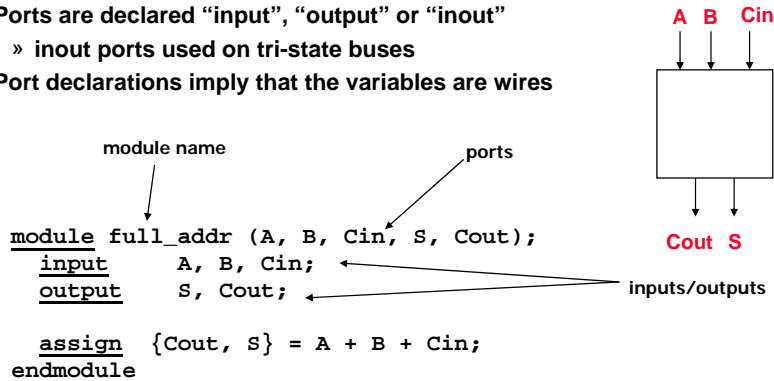
## Verilog Module

- Corresponds to a circuit component

- "Parameter list" is the list of external connections, aka "ports"
- Ports are declared "input", "output" or "inout"
  - » inout ports used on tri-state buses
- Port declarations imply that the variables are wires



## Verilog Continuous Assignment

- Assignment is continuously evaluated
- `assign` corresponds to a connection or a simple component with the described function
- Target is *NEVER* a reg variable
- Dataflow style

```

assign A = X | (Y & ~Z);
assign B[3:0] = 4'b01XX;
assign C[15:0] = 4'h00ff;
assign #3 {Cout, S[3:0]} = A[3:0] + B[3:0] + Cin;

```



## Comparator Example

```

module Compare1 (A, B, Equal, Alarger, Blarger);
  input  A, B;
  output Equal, Alarger, Blarger;

  assign Equal = (A & B) | (~A & ~B);
  assign Alarger = (A & ~B);
  assign Blarger = (~A & B);
endmodule

```

When evaluated?

What is synthesized?



## Comparator Example

```

// Make a 4-bit comparator from 4 1-bit comparators
module Compare4(A4, B4, Equal, Alarger, Blarger);
  input [3:0] A4, B4;
  output Equal, Alarger, Blarger;
  wire e0, e1, e2, e3, A10, A11, A12, A13, B10, B11, B12, B13;

  Compare1 cp0(A4[0], B4[0], e0, A10, B10);
  Compare1 cp1(A4[1], B4[1], e1, A11, B11);
  Compare1 cp2(A4[2], B4[2], e2, A12, B12);
  Compare1 cp3(A4[3], B4[3], e3, A13, B13);

  assign Equal = (e0 & e1 & e2 & e3);
  assign Alarger = (A13 | (A12 & e3) |
                   (A11 & e3 & e2) |
                   (A10 & e3 & e2 & e1));
  assign Blarger = (~Alarger & ~Equal);
endmodule

```

What would be a "better" behavioral version?



## Simple Behavioral Model - the always block



- **always block**

- Always waiting for a change to a trigger signal
- Then executes the body

```
module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  reg    out;

  always @(in1 or in2) begin
    out = in1 & in2;
  end
endmodule
```

Not a real register!!  
A Verilog register  
Needed because of  
assignment in always  
block

Specifies when block is executed  
I.e., triggered by which signals

## always Block



- A procedure that describes the function of a circuit

- Can contain many statements including *if*, *for*, *while*, *case*
  - Statements in the `always` block are executed *sequentially*
    - » “*blocking*” assignment
    - » Continuous assignments `<=` are executed in *parallel*
      - Non-blocking
  - The entire block is executed ‘at once’
    - » But the meaning is established by sequential interpretation
      - Simulation micro time vs macro time
      - synthesis
  - The *final* result describes the function of the circuit for current set of inputs
    - » intermediate assignments don’t matter, only the final result
- `begin/end` used to group statements

## What Verilog generates storage elements?




- Expressions produce combinational logic
  - Map inputs to outputs
- Storage elements carries same values forward in time
 
## State Example



```
module shifter (in, A,B,C,clk);
  input in, clk;
  input A,B,C;
  reg A, B, C;
  always @ (posedge clk) begin
    C = B;
    B = A;
    A = in;
  end
endmodule
```



- Block interpreted sequentially, but action happens “at once”




## State Example2 – Non blocking

```

module shifter (in, A,B,C,clk);
  input in, clk;
  input A,B,C;
  reg A, B, C;
  always @ (posedge clk) begin
    B <= A;
    A <= in;
    C <= B;
  end
endmodule

```

 

- **Non-blocking: all statements interpreted in parallel**
  - Everything on the RHS evaluated,
  - Then all assignments performed




## State Example2 – interactive quiz

```

module shifter (in, A,B,C,clk);
  input in, clk;
  input A,B,C;
  reg A, B, C;
  always @ (posedge clk) begin
    A = in;
    B = A;
    C = B;
  end
endmodule

```

 

- Variable becomes a storage element if its value is preserved (carried forward in time) despite changes in variables the produce it.
- Not whether it is declared as a wire or a reg!



## “Complete” Assignments

- If an `always` block executes, and a variable is *not* assigned
  - Variable keeps its old value (think implicit state!)
  - *NOT* combinational logic  $\Rightarrow$  latch is inserted (implied memory)
  - This is usually *not* what you want: dangerous for the novice!
- Any variable assigned in an `always` block should be assigned for any (and every!) execution of the block.



## Incomplete Triggers

- Leaving out an input trigger usually results in a sequential circuit
- Example: The output of this “and” gate depends on the input history

```

module and_gate (out, in1, in2);
  input    in1, in2;
  output   out;
  reg     out;

  always @(in1) begin
    out = in1 & in2;
  end

endmodule

```

What Hardware would this generate?



## Behavioral with Bit Vectors

//Behavioral model of 32-bitwide 2-to-1 multiplexor.

```

module mux32 (in0,in1,select,out);
  input [31:0] in0,in1;
  input      select;
  output [31:0] out;
  //
  reg [31:0] out;
  always @ (in0 or in1 or select)
    if (select) out=in1;
    else out=in0;
endmodule // Mux

```

- Notes:
  - inputs, outputs 32-bits wide

//Behavioral model of 32-bit adder.

```

module add32 (S,A,B);
  input [31:0] A,B;
  output [31:0] S;
  reg [31:0] S;
  always @ (A or B)
    S = A + B;
endmodule // Add

```



## Hierarchy & Bit Vectors

- Notes:
  - instantiation similar to primitives
  - select is 2-bits wide
  - named port assignment

```

//Assuming we have already
// defined a 2-input mux (either
// structurally or behaviorally,

```

//4-input mux built from 3 2-input muxes

```

module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output      out;
  wire      w0,w1;

```

```

  mux2
  m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
  m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
  m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
endmodule // mux4

```

Which select?



## Verilog if

- Same syntax as C if statement
- Sequential meaning, action “at once”

```

// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;

endmodule

```



## Verilog if

```

// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel[0] == 0)
      if (sel[1] == 0) Y = A;
      else Y = B;
    else
      if (sel[1] == 0) Y = C;
      else Y = D;
endmodule

```



## Verilog case

- Sequential execution of cases
  - Only first case that matches is executed (no break)
  - Default case can be used

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel; // 2-bit control signal
input A, B, C, D;
output Y;
reg Y; // target of assignment

always @(sel or A or B or C or D)
case (sel)
2'b00: Y = A;
2'b01: Y = B;
2'b10: Y = C;
2'b11: Y = D;
endcase
endmodule
```

↓  
Conditions tested in  
top to bottom order  
↓



## Verilog case

- Without the default case, this example would create a latch for Y!
  - your generating hardware, not programming
- Assigning X to a variable means synthesis is free to assign any value

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
case (A)
8'b00000001: Y = 0;
8'b00000010: Y = 1;
8'b00000100: Y = 2;
8'b00001000: Y = 3;
8'b00010000: Y = 4;
8'b00100000: Y = 5;
8'b01000000: Y = 6;
8'b10000000: Y = 7;
default: Y = 3'bX; // Don't care when input is not 1-hot
endcase
endmodule
```

## Verilog case (cont)

- Cases are executed sequentially
  - The following implements a *priority* encoder

```
// Priority encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
case (1'b1)
A[0]: Y = 0;
A[1]: Y = 1;
A[2]: Y = 2;
A[3]: Y = 3;
A[4]: Y = 4;
A[5]: Y = 5;
A[6]: Y = 6;
A[7]: Y = 7;
default: Y = 3'bX; // Don't care when input is all 0's
endcase
endmodule
```



## Parallel Case

- A priority encoder is more expensive than a simple encoder
  - If we know the input is 1-hot, we can tell the synthesis tools
  - "parallel-case" pragma says the order of cases does not matter

```
// simple encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
case (1'b1) // synthesis parallel-case
A[0]: Y = 0;
A[1]: Y = 1;
A[2]: Y = 2;
A[3]: Y = 3;
A[4]: Y = 4;
A[5]: Y = 5;
A[6]: Y = 6;
A[7]: Y = 7;
default: Y = 3'bX; // Don't care when input is all 0's
endcase
endmodule
```





## Verilog casex

- Like case, but cases can include 'X'
  - X bits not used when evaluating the cases
  - In other words, you don't care about those bits!



## casex Example

```
// Priority encoder
module encode (A, valid, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
output valid;             // Asserted when an input is not all 0's
reg    [2:0] Y;           // target of assignment
reg    valid;

always @(A) begin
    valid = 1;
    casex (A)
        8'bXXXXXXXX1: Y = 0;
        8'bXXXXXXXX10: Y = 1;
        8'bXXXXXXXX100: Y = 2;
        8'bXXXXX1000: Y = 3;
        8'bXXXX10000: Y = 4;
        8'bXXX100000: Y = 5;
        8'bX1000000: Y = 6;
        8'b10000000: Y = 7;
        default: begin
            valid = 0;
            Y = 3'bX; // Don't care when input is all 0's
        end
    endcase
end
endmodule
```



## Verilog for

- for is similar to C
- for statement is executed at compile time (like macro expansion)
  - Result is all that matters, not how result is calculated
  - Use in testbenches only!

```
// simple encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment

integer i;                // Temporary variables for program only
reg [7:0] test;

always @(A) begin
    test = 8b'00000001;
    Y = 3'bX;
    for (i = 0; i < 8; i = i + 1) begin
        if (A == test) Y = i;
        test = test << 1;
    end
end
endmodule
```



## Another Behavioral Example

- Computing Conway's Game of Life rule
  - Cell with no neighbors or 4 neighbors dies; with 2-3 neighbors lives

```
module life (neighbors, self, out);
input      self;
input [7:0] neighbors;
output    out;
reg       out;
integer   count;
integer   i;

always @(neighbors or self) begin
    count = 0;
    for (i = 0; i < 8; i = i + 1) count = count + neighbors[i];
    out = out | (count == 3);
    out = out | ((self == 1) & (count == 2));
end
endmodule
```

integers are temporary compiler variables

always block is executed instantaneously,  
if there are no delays only the final result is used



## Verilog while/repeat/forever

- **while (expression) statement**
  - Execute statement while expression is true
- **repeat (expression) statement**
  - Execute statement a fixed number of times
- **forever statement**
  - Execute statement forever



## full-case and parallel-case

- `// synthesis parallel_case`
  - Tells compiler that ordering of cases is not important
  - That is, cases do not overlap
    - » e. g., state machine - can't be in multiple states
  - Gives cheaper implementation
- `// synthesis full_case`
  - Tells compiler that cases left out can be treated as don't cares
  - Avoids incomplete specification and resulting latches




## Sequential Logic

`//Parallel to Serial converter`

```

module ParToSer(LD, X, out, CLK);
  input [3:0] X;
  input LD, CLK;
  output out;
  reg out;
  reg [3:0] Q;
  assign out = Q[0];
  always @ (posedge CLK)
    if (LD) Q=X;
    else Q = Q>>1;
endmodule // mux2

```

 

### Notes:

- “always @ (posedge CLK)” forces Q register to be rewritten every simulation cycle.
- “>>” operator does right shift (shifts in a zero on the left).
- Shifts on non-reg variables can be done with concatenation:
 

```
wire [3:0] A, B;
      assign B = {1'b0, A[3:1]}
```

```

module FF (CLK,Q,D);
  input D, CLK;
  output Q; reg Q;
  always @ (posedge CLK) Q=D;
endmodule

```



## Testbench

Top-level modules written specifically to test sub-modules.

Generally no ports.

```

module testmux;
  reg a, b, s;
  wire f;
  reg expected;

```

```

mux2 myMux (.select(s), .in0(a), .in1(b), .out(f));

```

```

initial
  begin
    s=0; a=0; b=1; expected=0;
    #10 a=1; b=0; expected=1;
    #10 s=1; a=0; b=1; expected=1;
  end
initial
  $monitor(
    "select=%b in0=%b in1=%b out=%b, expected out=%b time=%d",
    s, a, b, f, expected, $time);
endmodule // testmux

```

### Notes:

- initial block similar to always except only executes once (at beginning of simulation)
- #n's needed to advance time
- \$monitor - prints output
- A variety of other “system functions”, similar to monitor exist for displaying output and controlling the simulation.



## Final thoughts

---

- **Verilog looks like C, but it describes hardware**
  - Multiple physical elements, Parallel activities
  - Temporal relationships
  - Basis for simulation and synthesis
  - figure out the circuit you want, then figure out how to express it in Verilog
- **Understand the elements of the language**
  - Modules, ports, wires, reg, primitive, continuous assignment, blocking statements, sensitivity lists, hierarchy
  - Best done through experience
- **Behavioral constructs hide a lot of the circuit details but you as the designer must still manage the structure, data-communication, parallelism, and timing of your design.**