



EECS 150 - Components and Design Techniques for Digital Systems

Lec 8 – Timing Intro, KMAP, Synthesis

David Culler

Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://inst.eecs.berkeley.edu/~cs150>


Outline

- Timing Methodology for Synchronous Circuits
- Boolean Logic minimization (Kmaps)
- Synthesis – what else the tools do [to the extent time permits]




Review: Fundamental Design Principle

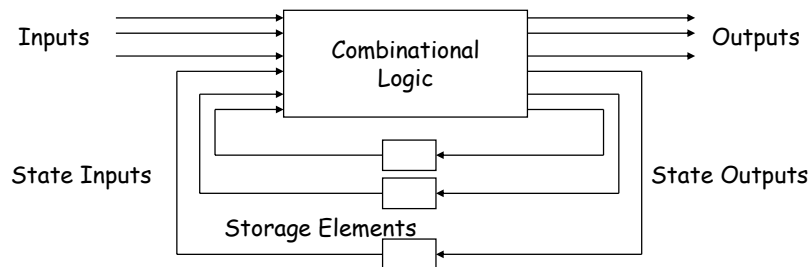- Divide circuit into combinational logic and state
- Localize feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic



Recall: What makes Digital Systems tick?

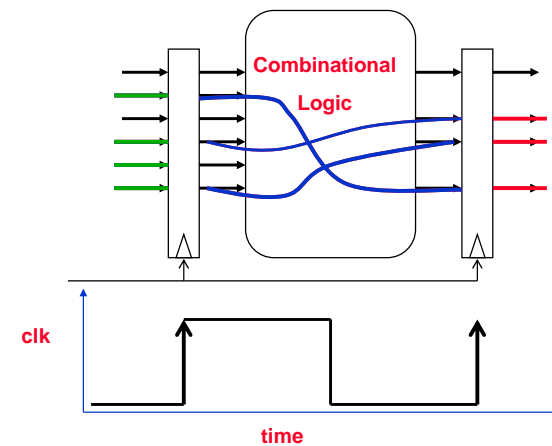




Timing Methodology

- Rules for interconnecting components and clocks
 - Guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for storage elements
 - Focus on systems with edge-triggered flip-flops
 - » Found in programmable logic devices
 - Many custom integrated circuits focus on level-sensitive latches
- Basic rules for correct timing:
 - (1) Correct inputs, with respect to time, are provided to the flip-flops
 - » Everything is stable when the clock ticks
 - (2) No flip-flop changes state more than once per clocking event




Timing Methodologies (cont'd)


 
- Definition of terms
 - clock: periodic event, causes state of storage element to change; can be rising or falling edge, or high or low level
 - setup time: minimum time before the clocking event by which the input **must be stable** (Tsu)
 - hold time: minimum time after the clocking event until which the input **must remain stable** (Th)



 
there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized



Comparison of Latches and Flip-Flops

  


 behavior is the same unless input changes while the clock is high



Typical Timing Specifications

 - Positive edge-triggered D flip-flop
 - Setup and hold times
 - Minimum clock width
 - Propagation delays (low to high, high to low, max and typical)




all measurements are made from the clocking event, i.e. the rising edge of the clock




Cascading Edge-triggered Flip-Flops

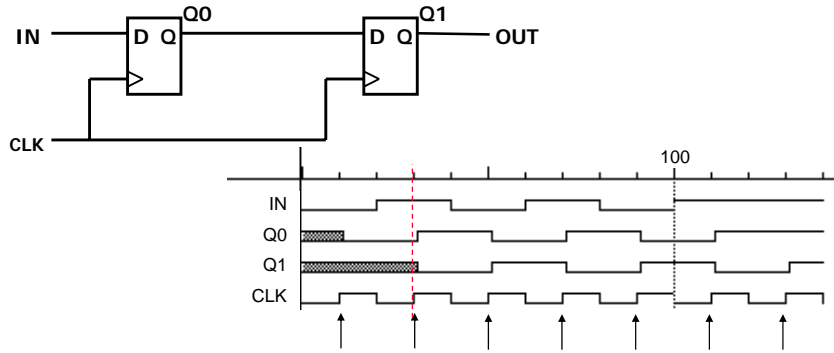- Shift register
 - New value goes into first stage
 - While previous value of first stage goes into second stage
 - Consider setup/hold/propagation delays (*prop must be > hold*)




Cascading Edge-triggered Flip-Flops

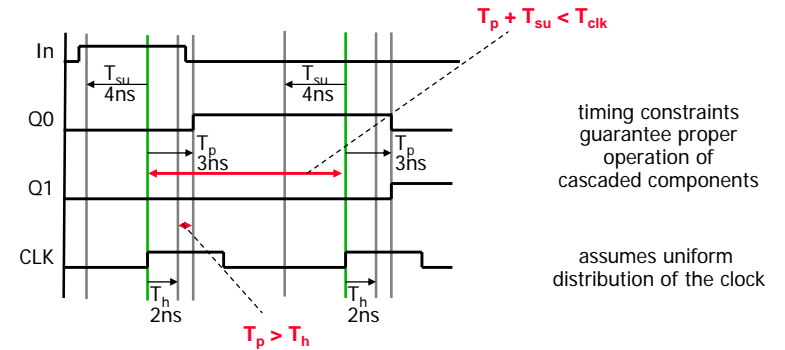- Why this works
 - Propagation delays exceed hold times
 - Clock width constraint exceeds setup time
 - This guarantees following stage will latch current value before it changes to new value




Cascading Edge-triggered Flip-Flops

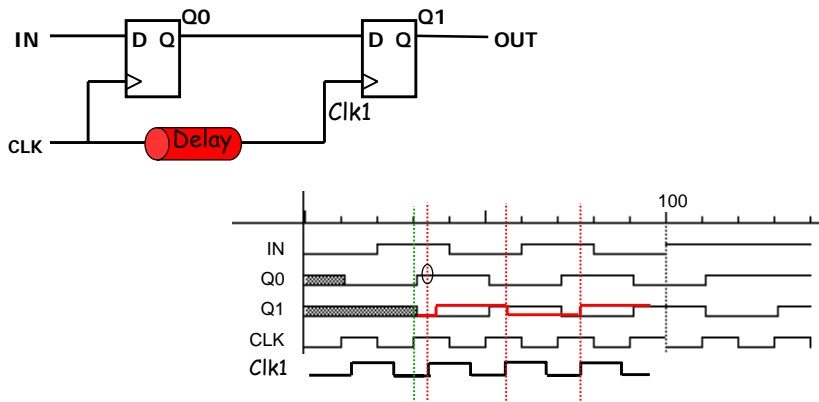- Shift register
 - New value goes into first stage
 - While previous value of first stage goes into second stage
 - Consider setup/hold/propagation delays (*prop must be > hold*)



Clock Skew

 - The problem
 - Correct behavior assumes next state of all storage elements determined by all storage elements at the same time
 - Difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic (and will soon become greater than logic delay)
 - Effect of skew on cascaded flip-flops:




original state: IN = 0, Q0 = 1, Q1 = 1
 due to skew, next state becomes: Q0 = 0, Q1 = 0, and not Q0 = 0, Q1 = 1



Cascading Edge-triggered Flip-Flops

 - Why this works (redux)
 - Propagation delays exceed hold times
 - Clock width constraint exceeds setup time
 - This guarantees following stage will latch current value before it changes to new value



Comparison of Latches and Flip-Flops

Type	When inputs are sampled	When output is valid
unclocked latch	always	propagation delay from input change
level-sensitive latch	clock high (Tsu/Th around falling edge of clock)	propagation delay from input change or clock edge (whichever is later)
master-slave flip-flop	clock high (Tsu/Th around falling edge of clock)	propagation delay from falling edge of clock
negative edge-triggered flip-flop	clock hi-to-lo transition (Tsu/Th around falling edge of clock)	propagation delay from falling edge of clock



Summary of Latches and Flip-Flops

- Development of D-FF
 - Level-sensitive used in custom integrated circuits
 - » can be made with 4 switches
 - Edge-triggered used in programmable logic devices
 - Good choice for data storage register
- Historically J-K FF was popular but now never used
 - Similar to R-S but with 1-1 being used to toggle output (complement state)
 - Good in days of TTL/SSI (more complex input function: $D = JQ' + K'Q$)
 - Not a good choice for PLAs as it requires two inputs
 - Can always be implemented using D-FF
- Preset and clear inputs are highly desirable on flip-flops
 - Used at start-up or to reset system to a known state



Logic Minimization

- One piece of synthesis



Quick Review: Canonical Forms

- Standard form for a Boolean expression - *unique* algebraic expression directly from a true table (TT) description.
- Two Types:
 - * Sum of Products (SOP)
 - * Product of Sums (POS)
- Sum of Products (disjunctive normal form, minterm expansion).

Example:

minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'bc'	0	1	0	0	1
a'bc	0	1	1	0	1
ab'c'	1	0	0	0	1
ab'c	1	0	1	0	1
abc'	1	1	0	0	1
abc	1	1	1	0	1

One product (and) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$



Quick Review: Sum of Products (cont.)

Canonical Forms are usually not minimal:

Our Example:

$$f = a'bc + ab'c' + ab'c + abc' + abc \quad (xy' + xy = x)$$

$$= a'bc + ab' + ab$$

$$= a'bc + a \quad (x'y + x = y + x)$$

$$= a + bc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

$$= a'b' + a'bc'$$

$$= a' (b' + bc')$$

$$= a' (b' + c')$$

$$= a'b' + a'c'$$



Quick Review: Canonical Forms

- Product of Sums (conjunctive normal form, maxterm expansion).

Example:

maxterms	a	b	c	f	f'
a+b+c	0	0	0	0	1
a+b+c'	0	0	1	0	1
a+b'+c	0	1	0	0	1
a+b'+c'	0	1	1	0	1
a'+b+c	1	0	0	0	1
a'+b+c'	1	0	1	0	1
a'+b'+c	1	1	0	0	1
a'+b'+c'	1	1	1	0	1

One sum (or) term for each 0 in f:

$$f = (a+b+c)(a+b+c')(a+b'+c)$$

$$f' = (a+b'+c')(a'+b+c)(a'+b+c')(a'+b'+c)(a+b+c')$$

Mapping from SOP to POS (or POS to SOP): *Derive truth table then proceed.*



Incompletely specified functions

- Example: binary coded decimal increment by 1

- BCD digits encode decimal digits 0 - 9 in bit patterns 0000 - 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Annotations:

- off-set of W (rows 1-4)
- on-set of W (rows 5-8)
- don't care (DC) set of W (rows 9-12)
- these inputs patterns should never be encountered in practice - "don't care" about associated output values, can be exploited in minimization



Implementing the TT

- Circuit must “cover the 1s” and “none of the 0s”.
- Don’t care can go either way

A	B	f
0	0	0
0	1	1
1	0	1
1	1	1

A	B	f
0	0	0
0	1	1
1	1	1
1	0	1

9/20/07

EECS 150, Fa07, Lec 08-timing-synth


21



The Uniting Theorem

- Key tool to simplification: $A(B' + B) = A$
- Essence of simplification of two-level logic
 - Find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$

 

9/20/07


EECS 150, Fa07, Lec 08-timing-synth

22



Boolean cubes

 - Visual technique for identifying when the uniting theorem can be applied
- n input variables = n-dimensional “cube”
- Neighbors “address” differs by one bit flip



9/20/07

EECS 150, Fa07, Lec 08-timing-synth


23



Mapping truth tables onto Boolean cubes

- Uniting theorem combines two “faces” of a cube into a larger “face”
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 

9/20/07

EECS 150, Fa07, Lec 08-timing-synth


24



Three variable example

- Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$Cout = BCin + AB + ACin$$

9/20/07


EECS 150, Fa07, Lec 08-timing-synth

25



Higher dimensional cubes

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2

represents an expression in one variable
i.e., 3 dimensions - 2 dimensions

A is asserted (true) and unchanged
B and C vary

This subcube represents the literal A

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

26



m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
 - 0-cube, i.e., a single node, yields a term in 3 literals
 - 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

27



Announcements

- Typo corrected on HW3, prob. 1
- P3, yes there is an input to each controller described in the text that is not shown in the picture.
- HW4 out tonight – it is a mid term review
- Review session Tues
- Mid term next Thurs in 125 Cory
 - Everything you want to know at hkn/student/online/cs/150 ...

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

28



Karnaugh maps

- Flat map of Boolean cube
 - Wrap-around at edges
 - Hard to draw and visualize for more than 4 dimensions
 - Virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
 - Guide to applying the uniting theorem
 - On-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

	A	0	1
B	0	1	1
1	1	0	0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

9/20/07


EECS 150, Fa07, Lec 08-timing-synth

29



Karnaugh maps (cont'd)

 - Numbering scheme based on **Gray-code**
 - e.g., 00, 01, 11, 10
 - 2^n values of n bits where each differs from next by one bit flip
 - » Hamiltonian circuit through n-cube
 - Only a single bit changes in code for adjacent map cells



9/20/07


EECS 150, Fa07, Lec 08-timing-synth

30



Adjacencies in Karnaugh maps

 - Wrap from first to last column
- Wrap top row to bottom row



9/20/07

EECS 150, Fa07, Lec 08-timing-synth

31



Karnaugh map examples

- $F =$
- $C_{out} =$
- $f(A,B,C) = \sum m(0,4,6,7)$

$AB + AC_{in} + BC_{in}$

$AC + B'C + AB$ (crossed out)

obtain the complement of the function by covering 0s with subcubes

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

32



More Karnaugh map examples

		A	
	0	0	1
	0	0	1
C	0	0	1
		B	

$G(A,B,C) = A$

		A	
	1	0	0
	0	0	1
C	0	0	1
		B	

$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$

		A	
	0	1	1
	1	1	0
C	1	1	0
		B	


F' simply replace 1's with 0's and vice versa
 $F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$



K-map: 4-variable interactive quiz

- $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$
F =

		A	
	1	0	0
	0	1	0
C	1	1	1
	1	1	1
		B	

 


find the smallest number of the largest possible subcubes to cover the ON-set (fewer terms with fewer inputs per term)



Karnaugh map: 4-variable example

- $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$
F =
 $C + A'BD + B'D'$

		A	
	1	0	0
	0	1	0
C	1	1	1
	1	1	1
		B	

 

find the smallest number of the largest possible subcubes to cover the ON-set (fewer terms with fewer inputs per term)




Karnaugh maps: don't cares

- $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$
- without don't cares
» f =
 $A'D + B'CD$

		A	
	0	0	X
	1	1	X
C	1	1	0
	0	X	0
		B	

Karnaugh maps: don't cares (cont'd)

 - $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$
 - $f = A'D + B'C'D$ without don't cares
 - $f = A'D + C'D$ with don't cares



by using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node


don't cares can be treated as 1s or 0s depending on which is more advantageous

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

37

Design example: two-bit comparator

 

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	1	0	0
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	1	0	0
		1	1	1	0	0
1	0	0	0	0	0	1
		0	1	0	0	1
		1	0	0	1	0
		1	1	1	0	0
1	1	0	0	0	0	1
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	1	0

block diagram and truth table


we'll need a 4-variable Karnaugh map for each of the 3 output functions

9/20/07


EECS 150, Fa07, Lec 08-timing-synth

38

 
Design example: two-bit comparator (cont'd)



K-map for LT

 

K-map for EQ

 

K-map for GT

$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + ABCD + AB' C D' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$

$$GT = B C' D' + A C' + A B D'$$

Canonical PofS vs minimal?

LT and GT are similar (flip A/C and B/D)

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

39

Definition of terms for two-level simplification



- **Implicant**
 - Single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- **Prime implicant**
 - Implicant that can't be combined with another to form a larger subcube
- **Essential prime implicant**
 - Prime implicant is essential if it alone covers an element of ON-set
 - Will participate in ALL possible covers of the ON-set
 - DC-set used to form prime implicants but not to make implicant essential
- **Objective:**
 - Grow implicant into prime implicants (minimize literals per term)
 - Cover the ON-set with as few prime implicants as possible (minimize number of product terms)

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

40

Examples to illustrate terms

  

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

41

Algorithm for two-level simplification


- **Algorithm: minimum sum-of-products expression from a Karnaugh map**
 - **Step 1:** choose an element of the ON-set
 - **Step 2:** find "maximal" groupings of 1s and Xs adjacent to that element
 - » consider top/bottom row, left/right column, and corner adjacencies
 - » this forms prime implicants (number of elements always a power of 2)
 - Repeat Steps 1 and 2 to find all prime implicants
 - **Step 3:** revisit the 1s in the K-map
 - » if covered by single prime implicant, it is essential, and participates in final cover
 - » 1s covered by essential prime implicant do not need to be revisited
 - **Step 4:** if there remain 1s not covered by essential prime implicants
 - » select the smallest number of prime implicants that cover the remaining 1s

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

42

 Algorithm for two-level simplification (example)




9/20/07

EECS 150, Fa07, Lec 08-timing-synth

43

Recall: Design Methodology

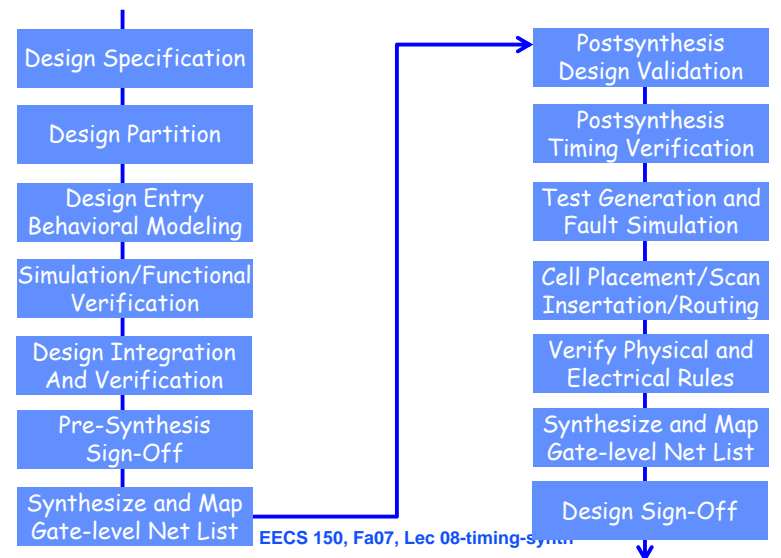

EECS 150, Fa07, Lec 08-timing-synth

44



Design Specification

- Written statement of functionality, timing, area, power, testability, fault coverage, etc.
- Functional specification methods:
 - State Transition Graphs
 - Timing Charts
 - Algorithm State Machines (like flowcharts)
 - HDLs (Verilog and VHDL)



Design Partition

- Partition to form an Architecture
 - Interacting functional units
 - » Control vs. datapath separation
 - » Interconnection structures within datapath
 - » Structural design descriptions
 - Components described by their behaviors
 - » Register-transfer descriptions
 - Top-down design method exploiting hierarchy and reuse of design effort



Design Entry

- Primary modern method: hardware description language
 - Higher productivity than schematic entry
 - Inherently easy to document
 - Easier to debug and correct
 - Easy to change/extend and hence experiment with alternative architectures
- **Synthesis tools map description into generic technology description**
 - E.g., logic equations or gates that will subsequently be mapped into detailed target technology
 - Allows this stage to be technology independent (e.g., FPGA LUTs or ASIC standard cell libraries)
- **Behavioral descriptions are how it is done in industry today**



Simulation and Functional Verification

- Simulation vs. Formal Methods
- Test Plan Development
 - What functions are to be tested and how
 - Testbench Development
 - » Testing of independent modules
 - » Testing of composed modules
 - Test Execution and Model Verification
 - » Errors in design
 - » Errors in description syntax
 - » Ensure that the design can be synthesized
 - The model must be VERIFIED before the design methodology can proceed



Design Integration and Verification

- Integrate and test the individual components that have been independently verified
- Appropriate testbench development and integration
- Extremely important step and one that is often the source of the biggest problems
 - Individual modules thoroughly tested
 - Integration not as carefully tested
 - Bugs lurking in the interface behavior among modules!



Presynthesis Sign-off

- Demonstrate full functionality of the design
- Make sure that the behavior specification meets the design specification
 - Does the demonstrated input/output behavior of the HDL description represent that which is expected from the original design specification
- Sign-off only when all functional errors have been eliminated




Gate-Level Synthesis and Technology Mapping

- Once all syntax and functional errors have been eliminated, synthesize the design from the behavior description
 - Optimized Boolean description
 - Map onto target technology
- Optimizations include
 - Minimize logic
 - Reduce area
 - Reduce power
 - Balance speed vs. other resources consumed
- Produces netlist of standard cells or database to configure target FPGA



Design Methodology in Detail

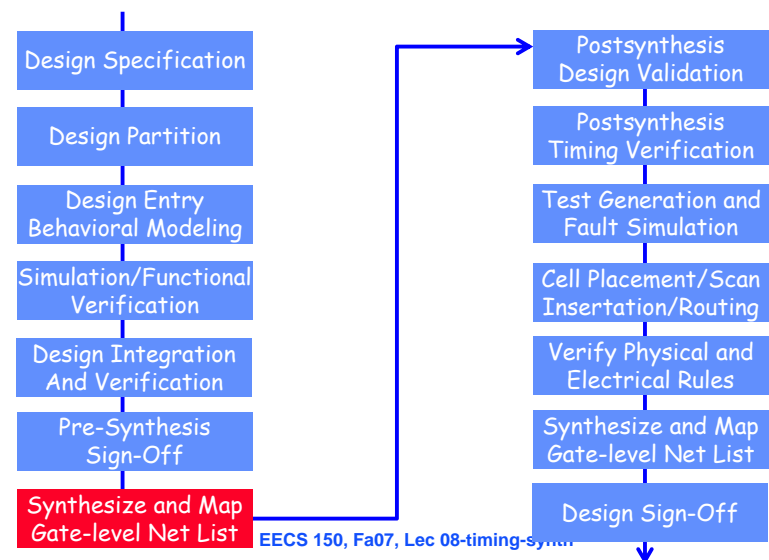



Logic Synthesis

- Verilog and VHDL started out as simulation languages, but quickly people wrote programs to automatically convert Verilog code into low-level circuit descriptions (netlists).



- Synthesis converts Verilog (or other HDL) descriptions to implementation technology specific primitives:**
 - For FPGAs: LUTs, flip-flops, and RAM blocks
 - For ASICs: standard cell gate and flip-flop libraries, and memory blocks.


9/20/07

EECS 150, Fa07, Lec 08-timing-synth

53



Die Photos: Vertex vs. Pentium IV

 

- FPGA Vertex chip looks remarkably structured**
 - Very dense, very regular structure
 - Lots of volume, low NRE, high silicon overhead
- Full Custom Pentium chip somewhat more random in structure**
 - Large on-chip memories (caches) are visible
- Logic Synthesis essential for both**

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

54



Logic Synthesis – where EE and CS meet



9/20/07

EECS 150, Fa07, Lec 08-timing-synth

55



Why Logic Synthesis?

- Automatically manages many details of the design process:**
 - ⇒ Fewer bugs
 - ⇒ Improved productivity
- Abstracts the design data (HDL description) from any particular implementation technology.**
 - Designs can be re-synthesized targeting different chip technologies.
Ex: first implement in FPGA then later in ASIC.
- In some cases, leads to a more optimal design than could be achieved by manual means (ex: logic optimization)**

Why Not Logic Synthesis?

- May lead to non-optimal designs in some cases.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

56




How does it work?

- A variety of general and ad-hoc (special case) methods:
 - **Instantiation:** maintains a library of primitive modules (AND, OR, etc.) and user defined modules.
 - **“macro expansion” / substitution:** a large set of language operators (+, -, Boolean operators, etc.) and constructs (if-else, case) expand into special circuits.
 - **Inference:** special patterns are detected in the language description and treated specially (ex: inferring memory blocks from variable declaration and read/write statements, FSM detection and generation from “always @ (posedge clk)” blocks).
 - **Logic optimization:** Boolean operations are grouped and optimized with logic minimization techniques.
 - **Structural reorganization:** advanced techniques including sharing of operators, and retiming of circuits (moving FFs), and others?



Synthesis vs Compilation

Levels of Representation

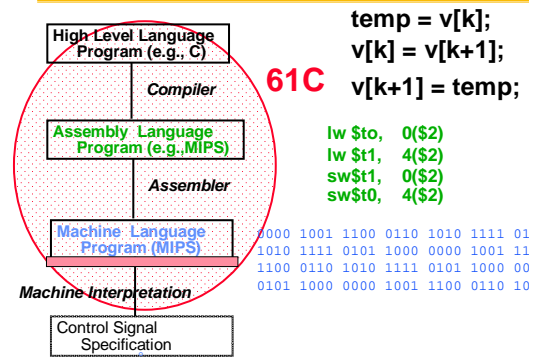

- **Compiler**
 - recognizes all possible constructs in a formally defined program language
 - translates them to a machine language representation of execution process
- **Synthesis**
 - Recognizes a target dependent subset of a hardware description language
 - Maps to collection of concrete hardware resources
 - Iterative tool in the design flow




Simple Example


```

module foo (a,b,s0,s1,f);
input [3:0] a;
input [3:0] b;
input s0,s1;
output [3:0] f;
reg f;
always @ (a or b or s0 or s1)
  if (`s0 && s1 || s0) f=a; else f=b;
endmodule
  
```

 - Should expand if-else into 4-bit wide multiplexor and optimize the control logic:



Mapping

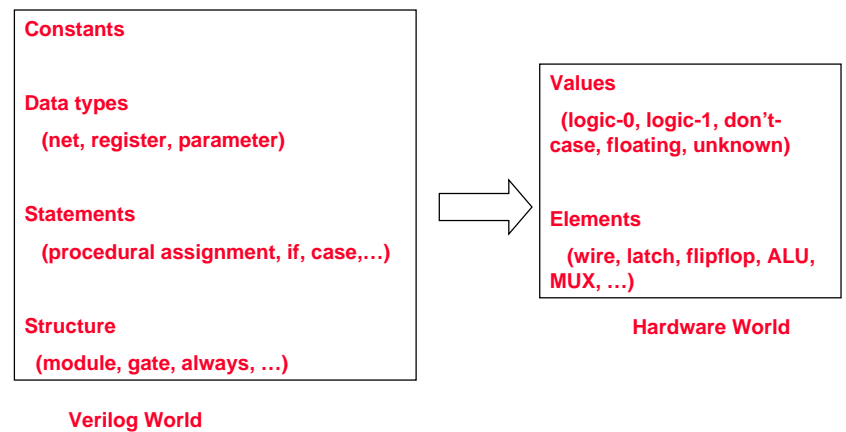



Module Template

Synthesis tools expects to find modules in this format.

```

module <top_module_name>(<port list>);
/* Port declarations. followed by wire, reg, integer, task and function declarations */
/* Describe hardware with one or more continuous assignments, always blocks, module
instantiations and gate instantiations */
// Continuous assignment
wire <result_signal_name>;
assign <result_signal_name> = <expression>;
// always block
always @( <event expression> )
begin
// Procedural assignments
// if statements
// case, casez, and casez statements
// while, repeat and for loops
// user task and user function calls
end
// Module instantiation
<module_name> <instance_name> (<port list>);
// Instantiation of built-in gate primitive
gate_type_keyword (<port list>);
endmodule

```

- The order of these statements is irrelevant, all execute concurrently.
- The statements between the **begin** and **end** in an always block execute sequentially from top to bottom. (However, beware of blocking versus non-blocking assignment)
- Statements within a fork-join statement in an always block execute concurrently.



Supported Verilog Constructs

- **Net types:**
 - wire, tri, supply1, supply0;
 - register types: reg, integer, time (64 bit reg); arrays of reg.
- **Continuous assignments.**
- **Gate primitive and module instantiations.**
- **always blocks, user tasks, user functions.**
- **inputs, outputs, and inout to a module.**
- **All operators**
 - +, -, *, /, %, <, >, <=, >=, ==, !=, ===, !==, &&, ||, !, ~, &, ~&, |, ~|, ^, ~^, ^, <<, >>, ?:, { }, {{ }}
 - Note: / and % are supported for compile-time constants and constant powers of 2.
- **Procedural statements:**
 - if-else-if, case, casez, casez, for, repeat, while, forever, begin, end, fork, join.
- **Procedural assignments:**
 - blocking assignments =,
 - nonblocking assignments <=
 - Note: <= cannot be mixed with = for the same register.
- **Compiler directives:** `define, `ifdef, `else, `endif, `include, `undef
- **Miscellaneous:**
 - Integer ranges and parameter ranges.
 - Local declarations to begin-end block.
 - Variable indexing of bit vectors on the left and right sides of assignments.



Unsupported Language Constructs

Generate error and halt synthesis

- Net types: trireg, wor, trior, wand, triand, tri0, tri1, and charge strength;
- register type: real.
- Built-in unidirectional and bidirectional switches, and pull-up, pull-down.
- Procedural statements: assign (different from the “continuous assignment”), deassign, wait.
- Named events and event triggers.
- UDPs (user defined primitives) and specify blocks.
- force, release, and hierarchical net names (for simulation only).

Simply ignored

- delay, delay control, and drive strength.
- scalared, vectored.
- initial block.
- Compiler directives (except for `define, `ifdef, `else, `endif, `include, and `undef, which are supported).
- Calls to system tasks and system functions (they are only for simulation).



Net Data Type

- Variable of NET type maps into a wire
- wire → wire
- supply0 → wire connected to logic-0
- supply1 → wire connected to logic-1
- tri → like a wire
- wor
- wand




Register Data Type

- Reg declaration specifies size in bits
- Integer type – max size is 32 bits, synthesis may determine size by analysis
 - Wire [1:5] Brq, Rbu
 - Integer Arb
 - ...
 - Arb = Brq + Rbu “Arb is 6 bits”
- Variable of reg type maps into wire, latch or flip-flop *depending on context*



Operators

- Logical operators map into primitive logic gates
- Arithmetic operators map into adders, subtractors, ...
 - Unsigned 2s complement
 - Model carry: target is one-bit wider than source
 - Watch out for *, %, and /
- Relational operators generate comparators
- Shifts by constant amount are just wire connections
 - No logic involved
- Variable shift amounts a whole different story --- shifter
- Conditional expression generates logic or MUX

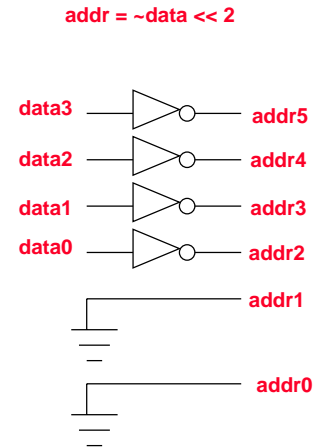

Procedural Assignments

- Verilog has two types of assignments within always blocks:
- Blocking procedural assignment “=”
 - The RHS is executed and the assignment is completed before the next statement is executed. Example:
 - Assume A holds the value 1 ... A=2; B=A; A is left with 2, B with 2.
- Non-blocking procedural assignment “<=”
 - The RHS is executed and assignment takes place at the end of the current time step (not clock cycle). Example:
 - Assume A holds the value 1 ... A<=2; B<=A; A is left with 2, B with 1.
- The notion of the “current time step” is tricky in synthesis, so to guarantee that your simulation matches the behavior of the synthesized circuit, follow these rules:

- Use blocking assignments to model combinational logic within an always block.
- Use non-blocking assignments to implement sequential logic.
- Do not mix blocking and non-blocking assignments in the same always block.
- Do not make assignments to the same variable from more than one always block.



Combinational Logic

CL can be generated using:

1. primitive gate instantiation:
 - AND, OR, etc.
2. continuous assignment (assign keyword), example:


```
Module adder_8 (cout, sum, a, b, cin);
output cout;
output [7:0] sum;
input cin;
input [7:0] a, b;
assign {cout, sum} = a + b + cin;
endmodule
```
3. Always block:


```
always @ (event_expression)
begin
// procedural assignment statements, if statements,
// case statements, while, repeat, and for loops.
// Task and function calls
end
```



Combinational logic always blocks

- **Make sure all signals assigned in a combinational always block are explicitly assigned values every time that the always block executes. Otherwise latches will be generated to hold the last value for the signals not assigned values.**

- Example:
 - Sel case value 2'd2 omitted.
 - Out is not updated when select line has 2'd2.
 - Latch is added by tool to hold the last value of out under this condition.

```

module mux4to1 (out, a, b, c, d, sel);
output out;
input a, b, c, d;
input [1:0] sel;
reg out;
always @(sel or a or b or c or d)
begin
    case (sel)
        2'd0: out = a;
        2'd1: out = b;
        2'd3: out = d;
    endcase
end
endmodule

```

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

69



Fixes to the avoid creating latch

```

module mux4to1 (out, a, b, c, d, sel);
output out;
input a, b, c, d;
input [1:0] sel;
reg out;
always @(sel or a or b or c or d)
begin
    case (sel)
        2'd0: out = a;
        2'd1: out = b;
        2'd2: out = c;
        2'd3: out = d;
    endcase
end
endmodule

```

- add the missing select line
- Or, in general, use the “default” case:


```
default: out = foo;
```

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

70



Example (cont)

```

module funnymux4to1 (out, a, b, c, d, sel);
output out;
input a, b, c, d;
input [1:0] sel;
reg out;
always @(sel or a or b or c or d)
begin
    case (sel)
        2'd0: out = a;
        2'd1: out = b;
        2'd3: out = d;
        default: out = 1'bx;
    endcase
end
endmodule

```

- If you don't care about the assignment in a case (for instance you know that it will never come up) then assign the value “x” to the variable.
- The x is treated as a “don't care” for synthesis and will simplify the logic. (The synthesis directive “full_case” will accomplish the same, but can lead to differences between simulation and synthesis.)

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

71



Latch rule

- If a variable is not assigned in all possible executions of an always statement then a latch is inferred
 - E.g., when not assigned in all branches of an if or case
 - Even a variable declared locally within an always is inferred as a latch if incompletely assigned in a conditional statement

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

72




Assign before use ordering

```

module onelatch (clock, curState, nxtState);
input clock;
input curState;
output nxtState;
reg nxtState

```

 

```

always @(Clock or CurrentState)
begin: L1
integer temp
if (clock) begin
temp = CurState;
NxtState = temp;
end
end
end module
9/20/07

```




Use before Assign ordering

```

module twolatch (clock, curState, nxtState);
input clock;
input curState;
output nxtState;
reg nxtState

```

 

```

always @(Clock or CurrentState)
begin: L1
integer temp
if (clock) begin
NxtState = temp;
temp = CurState;
end
end
end module
9/20/07

```




Combinational Logic (cont.)

- Be careful with nested IF-ELSE. They can lead to "priority logic"
 - Example: 4-to-2 encoder

```

always @(x)
begin : encode
if (x[0] == 1'b1) y = 2'b00;
else if (x[1] == 1'b1) y = 2'b01;
else if (x[2] == 1'b1) y = 2'b10;
else if (x[3] == 1'b1) y = 2'b11;
else y = 2'bxxx;
end


```

 

```

always @(x)
begin : encode
case (x)
4'b0001: y = 2'b00;
4'b0010: y = 2'b01;
4'b0100: y = 2'b10;
4'b1000: y = 2'b11;
default: y = 2'bxxx;
endcase
end
end

```

 

Sequential Logic

- Example: D flip-flop with synchronous set/reset:


```

module dff(q, d, clk, set, rst);
input d, clk, set, rst;
output q;
reg q;
always @(posedge clk)
if (reset)
q <= 0;
else if (set) begin
q <= 1;
end
else begin
q <= d;
end
endmodule

```

- "@(posedge clk)" key to flip-flop generation.
- Note in this case, priority logic is appropriate.
- For Xilinx Virtex FPGAs, the tool infers a native flip-flop (no extra logic is needed for the set/reset).

 We prefer *synchronous* set/reset, but how would you specify *asynchronous* preset/clear?





Procedural Assignment

- Target of proc. Assignment is synthesized into a wire, a flip-flop or a latch, depending on the context under which the assignment appears.
- A target cannot be assigned using a blocking assignment and a non-blocking assignment.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

77



Finite State Machines

```
module FSM1(clk,rst, enable, data_in, data_out);
input clk, rst, enable;
input [2:0] data_in;
output data_out;
```

```
/* Defined state encoding;
this style preferred over 'defines*/
parameter default=2'bxx;
parameter idle=2'b00;
parameter read=2'b01;
parameter write=2'b10;
reg data_out;
reg [1:0] state, next_state;

/* always block for sequential logic*/
always @(posedge clk)
    if (!rst) state <= idle;
    else state <= next_state;
```

- Style guidelines (some of these are to get the right result, and some just for readability)
 - Must have reset.
 - Use separate always blocks for sequential and combination logic parts.
 - Represent states with defined labels or enumerated types.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

78



FSMs (cont.)

```
/* always block for CL */
always @(state or enable or data_in)
begin
case (state)
/* For each state def output and next */
idle : begin
    data_out = 1'b0;
    if (enable && data_in)
        next_state = read;
    else next_state = idle;
    end
read : begin ... end
write : begin ... end

default : begin
    next_state = default;
    data_out = 1'bx;
    end
endcase
end
endmodule
```

- Use a CASE statement in an always to implement next state and output logic.
- Always use a default case and assign the state variable and output to 'bx:
 - avoids implied latches,
 - allows the use of don't cares leading to simplified logic.
- The "FSM compiler" within the synthesis tool can re-encode your states. This process is controlled by using a synthesis attribute (passed in a comment).
 - See the Synplify guide for details.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth


79



Values x and z

- Assigning the value x to a variable tells synthesis to treat as dont-care
- Assigning z generates tristate gate
 - Z can be assigned to any variable in an assignment, but for synthesis this must occur under the control of a conditional statement
 
```
module threestate(rdy, inA, inB, sel)
input rdy, inA, inB;
output sel;
reg sel;
always @(rdy or inA or inB)
    if (rdy) sel = 1'bz
    else sel = inA & inB
endmodule
```



9/20/07


EECS 150, Fa07, Lec 08-timing-synth

80



Postsynthesis Design Validation

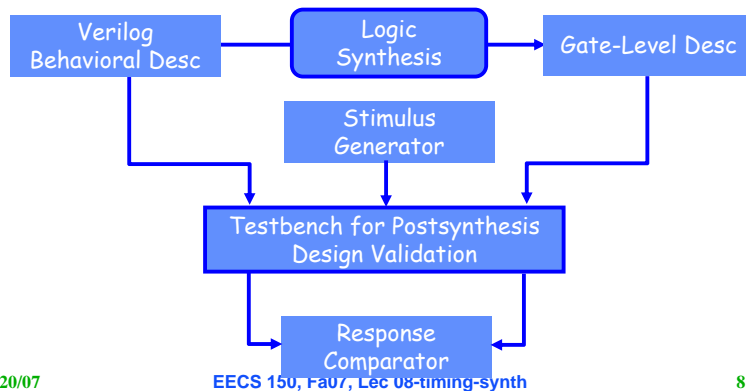- Does gate-level synthesized logic implement the same input-output function as the HDL behavioral description?




9/20/07

81



More Help

 - Online documentation for Synplify Synthesis Tool:
 - Under “refs/links” and linked to today’s lecture on calendar
 - Online examples from Synplicity.
- Bhasker (same author as Verilog reference book)
- Trial and error with the synthesis tool.
 - Synplify will display the output of synthesis in schematic form for your inspection. Try different input and see what it produces.



9/20/07

EECS 150, Fa07, Lec 08-timing-synth

82



Bottom line

- Have the hardware design clear in your mind when you write the verilog.
- Write the verilog to describe that HW
 - it is a Hardware *Description* Language not a Hardware Imagination Language.
- If you are very clear, the synthesis tools are likely to figure it out.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

83



Summary

- Timing methodology defines a set of constraints that make life simpler – as long as they are observed
- Boolean Algebra provides framework for logic simplification
- Uniting to reduce minterms
- Karnaugh maps provide visual notion of simplifications
- Algorithm for producing reduced form.
- Synthesis is part algorithms and part pattern matching
 - Work in partnership with your tool
 - Learn the idioms that it does well. Create building blocks out of them. Use those.
 - Think Hardware write code that describes it.

9/20/07

EECS 150, Fa07, Lec 08-timing-synth

84