



EECS 150 - Components and Design Techniques for Digital Systems

Lec 12 - Timing

David Culler
Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://www-inst.eecs.berkeley.edu/~cs150>

10-4-2007

Lec12 EECS150 Fa07

1



Outline

- Performance Limits of Synchronous Systems
- Delay in logic gates
- Delay in wires
- Delay in combinational networks
- Clock Skew
- Delay in flip-flops
- Glitches


10-4-2007

Lec12 EECS150 Fa07

2



 Recall: General Model of Synchronous Circuit



- All wires, except clock, may be multiple bits wide.
- Registers (reg)
 - collections of flip-flops
- clock
 - distributed to all flip-flops
 - typical rate?
- Combinational Logic Blocks (CL)
 - no internal state
 - output only a function of inputs
- Particular inputs/outputs are optional
- Optional Feedback


10-4-2007

Lec12 EECS150 Fa07

3



General Model of Synchronous Circuit

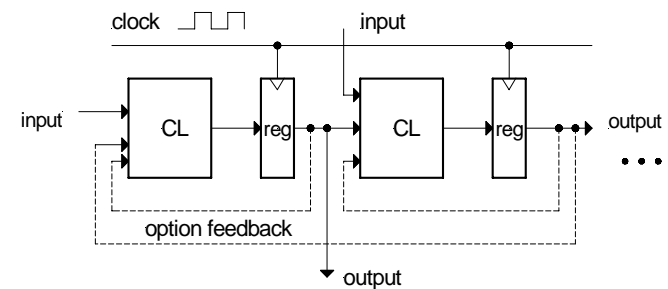

- How do we measure performance?
 - operations/sec?
 - cycles/sec?
- What limits the clock rate?
- What happens as we increase the clock rate?


10-4-2007

Lec12 EECS150 Fa07

4


Limitations on Clock Rate

1 Logic Gate Delay

 

- What are typical delay values?

2 Delays in flip-flops

 

- Both times contribute to limiting the clock period.



- What must happen in one clock cycle for correct operation?
- Assuming perfect clock distribution (all flip-flops see the clock at the same time):

– All signals must be ready and “setup” before rising edge of clock.

10-4-2007

Lec12 EECS150 Fa07


Example: Parallel-Serial Converter

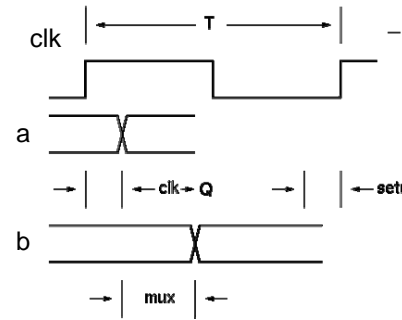 

10-4-2007

Lec12 EECS150 Fa07

General Model of Synchronous Circuit

 

- In general, for correct operation:

$$T \geq \text{time}(\text{clk} \rightarrow \text{Q}) + \text{time}(\text{CL}) + \text{time}(\text{setup})$$

$$T \geq \tau_{\text{clk} \rightarrow \text{Q}} + \tau_{\text{CL}} + \tau_{\text{setup}}$$

for all paths.

- How do we enumerate *all paths*?



- Any circuit input or register output to any register input or circuit output.
- “setup time” for circuit outputs depends on what it connects to
- “clk-Q time” for circuit inputs depends on from where it comes.

10-4-2007

Lec12 EECS150 Fa07



Recall L2: Transistor-level Logic Circuits

- Inverter (NOT gate):

  

what is the relationship between in and out?

in	out
0 volts	
3 volts	

  

10-4-2007


Lec12 EECS150 Fa07



Qualitative Analysis of Logic Delay



Improved Transistor Model:

 - We refer to transistor "strength" as the amount of current that flows for a given V_{ds} and V_{gs} .
- The strength is linearly proportional to the ratio of W/L
 - Physical property
- Turn it on harder allows more current to flow



nFET

pFET

  

What is the effective resistance?


ECS150 Fall

10-




Gate Switching Behavior



Inverter:

 

 Models inputs to other gates & wire capacitance



NAND gate:

  


When does it start? How quickly does it switch?

10-4-2007



Clarify your understanding

 

What is the 0 → 1 and 1 → 0 behavior of a NOR gate?

Why do we need pMOS and nMOS devices in a pass gate? - used for tristate

10-4-2007




Lec12 EECS150 Fa07

11



Delays in a series of gates

Cascaded gates:

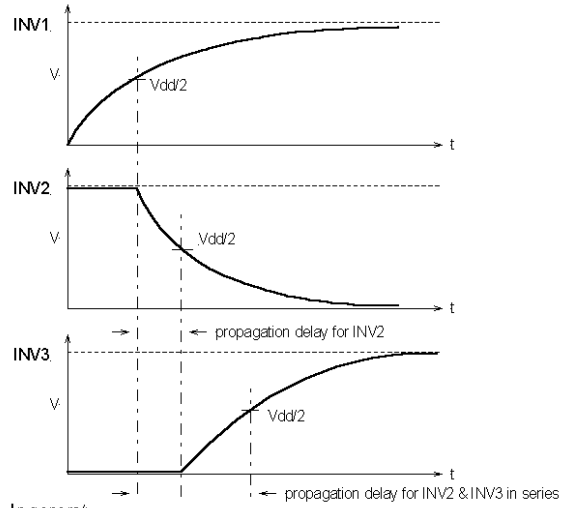  


In general: prop. delay = sum of individual prop. delays of gates in series.

10-4-2007



Gate Delay due to fan out

- Fan-out:

 


- The delay of a gate is proportional to its output capacitance. Because, gates #2 and 3 turn on/off at a later time. (It takes longer for the output of gate #1 to reach the switching threshold of gates #2 and 3 as we add more output capacitance.)



Gate Delay with a general circuit

- “Fan-in”

 
- Does it affect the delay of the individual gate?
- When does the gate begin its transition?



- What is the delay in this circuit?
- Critical Path:** the path with the maximum delay, from any input to any output.
 - In general, we include register set-up and clk-to-Q times in critical path calculation.
- Why do we care about the *critical path*?



 What is the delay through arbitrary combinational logic?




Announcements

- Reading: K&B 3.5 6.1.5-6.2.3 (were in 9/20 assignment)
- K&B 10.6 is great protocol example
 - We'll do several of those as we go
- HW 5 out today (due 10/12)
- Class survey
- Lab partners



Delay in Flip-flops

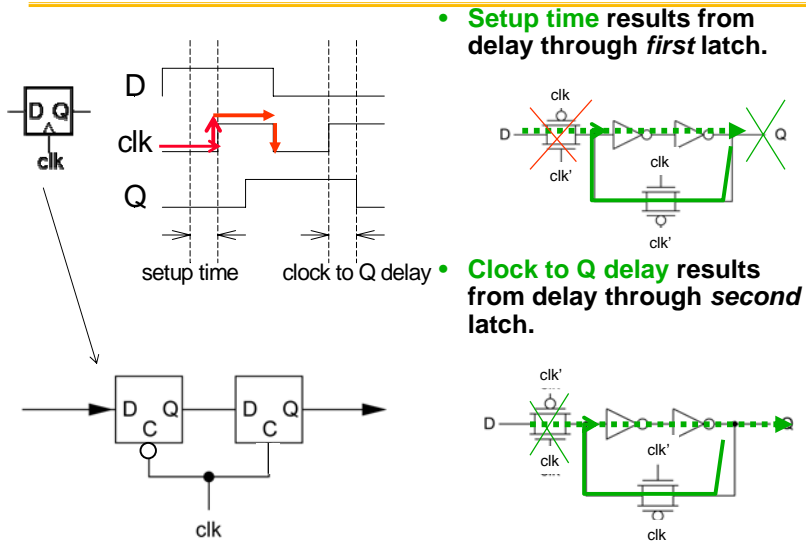

- Setup time results from delay through *first* latch.
- Clock to Q delay results from delay through *second* latch.


10-4-2007

Lec12 EECS150 Fa07

17



Wire Delay

 

- In general, wire behave as "transmission lines":
 - signal wave-front moves close to the speed of light
 - » $\sim 1ft/ns$
 - Time from source to destination is called the "transit time".
 - In ICs most wires are short, and the transit times are relatively short compared to the clock period and can be ignored.
 - Not so on PC boards.
 - ...Or long wires on fast chips
 - » Busses
 - » Global Control signals
 - » Clock
- Rule of thumb: wire must be treated as a transmission line if its length exceed $\lambda/100$.


10-4-2007

Lec12 EECS150 Fa07

18



Architectural Level Delay

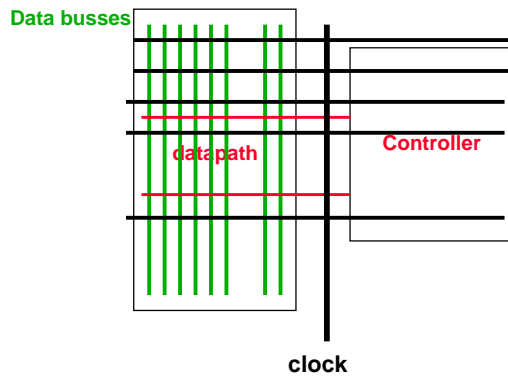

10-4-2007




Lec12 EECS150 Fa07

19



Wire Delay

- Even in those cases where the transmission line effect is negligible:
 - Wires posses distributed resistance and capacitance
 - Time constant associated with distributed RC is proportional to the *square* of the wire length
- For short wires on ICs, resistance is insignificant (relative to effective R of transistors), but C is important.
 - Typically around half of C of gate load is in the wires.
- For long wires on ICs:
 - busses, clock lines, global control signal, etc.
 - Resistance is significant, therefore distributed RC effect dominates.
 - signals are typically "rebuffered" to reduce delay:

   

10-4-2007

Lec12 EECS150 Fa07

20



Modern rule of thumb

- Transistors are cheap
 - And their local wires
- Wire is what counts
- Often pays to do extra local computation (gates) to reduce wire delay

10-4-2007


Lec12 EECS150 Fa07

21



Clock Skew

- Unequal delay in distribution of the clock signal to various parts of a circuit:
 - if not accounted for, can lead to erroneous behavior. (see next)
 - Comes about because:
 - » clock wires have delay,
 - » circuit is designed with a different number of clock buffers from the clock source to the various clock loads, or
 - » buffers have unequal delay.
 - All synchronous circuits experience some clock skew:
 - » more of an issue for high-performance designs operating with very little extra time per clock cycle.

 


10-4-2007

Lec12 EECS150 Fa07

22



Clock Skew Constraints

 

- If clock period $T = T_{CL} + T_{setup} + T_{clk \rightarrow Q}$, circuit will fail
 - Delay relative to CLK = $T_{skew} + T_{CL} + T_{setup} + T_{clk \rightarrow Q}$
- Therefore:
 1. Control clock skew
 - a) Careful clock distribution. Equalize path delay from clock source to all clock loads by controlling wires delay and buffer delay.
 - b) don't "gate" clocks.
 2. $T \geq T_{CL} + T_{setup} + T_{clk \rightarrow Q} + \text{worst case skew.}$
- Most modern large high-performance chips (microprocessors) control end to end clock skew to a few tenths of a nanosecond.


10-4-2007

Lec12 EECS150 Fa07

23



Hacking Clock Skew

 

- Note reversed buffer.
- In this case, clock skew actually provides *extra time* (adds to the effective clock period).
- This effect has been used to help run circuits as higher clock rates. Risky business!
 - What happens when reg at end of distribution tree feeds back to earlier reg?

10-4-2007

Lec12 EECS150 Fa07

24



Time to ask clarifying questions

10-4-2007

Lec12 EECS150 Fa07

25



Other effects of Delays on Combinational Logic

10-4-2007

Lec12 EECS150 Fa07

26



Time Behavior of Combinational Networks

- **Waveforms**
 - Visualization of values carried on signal wires over time
 - Useful in explaining sequences of events (changes in value)
- **Simulation tools are used to create these waveforms**
 - Input to the simulator includes gates and their connections
 - Input stimulus, that is, input signal waveforms
- **Some terms**
 - Gate delay—time for change at input to cause change at output
 - » Min delay—typical/nominal delay—max delay
 - » Careful designers design for the worst case
 - Rise time—time for output to transition from low to high voltage
 - Fall time—time for output to transition from high to low voltage
 - Pulse width—time an output stays high or low between changes

10-4-2007



Lec12 EECS150 Fa07

27



Momentary Changes in Outputs

  - Can be useful—pulse shaping circuits
- Can be a problem—incorrect circuit operation (glitches/hazards)
- **Example: pulse shaping circuit**
 - $A' \cdot A = 0$
 - delays matter in function



D remains high for three gate delays after A changes from low to high
Lec12 EECS150 Fa07

F is not always 0
pulse 3 gate-delays wide


28

10-4-2007



Dynamic Hazards

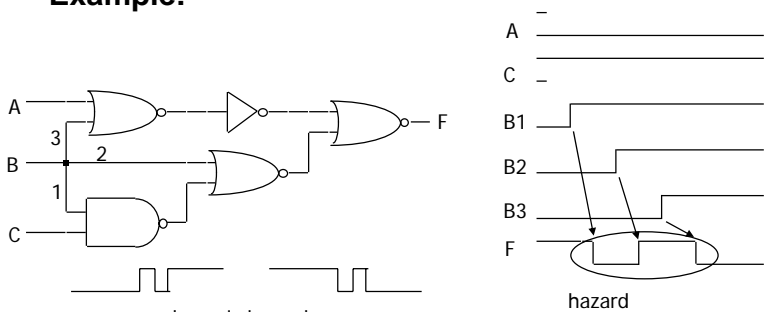- Due to the same versions of a literal taking on opposite values
 - Thru different paths with different delays and reconverging
- May cause an output that was to change value to change 3 times instead of once
- Example:



10-4-2007


dynamic hazards

Lec12 EECS150 Fa07

33



Dynamic Hazards

 

10-4-2007


Lec12 EECS150 Fa07

34



Eliminating Static Hazards

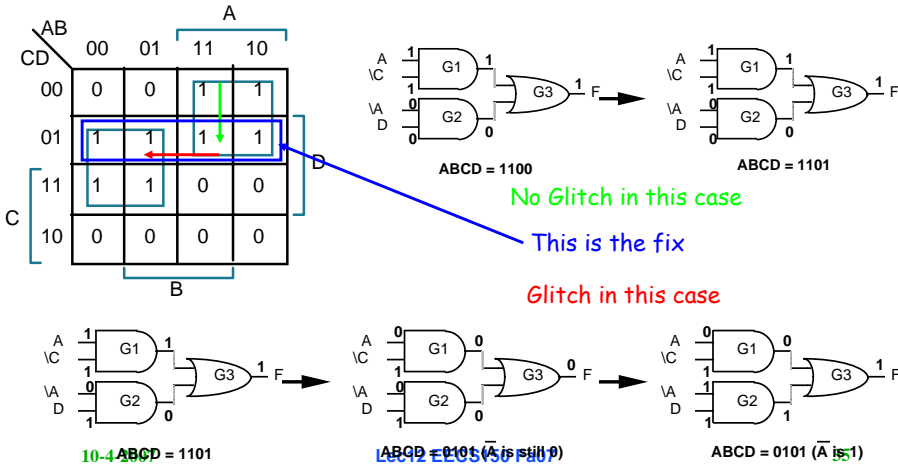- Following 2-level logic function has a hazard, e.g., when inputs change from ABCD = 0101 to 1101



10-4-2007


Lec12 EECS150 Fa07

ABCD = 0101 (A is 1)



Eliminating Dynamic Hazards

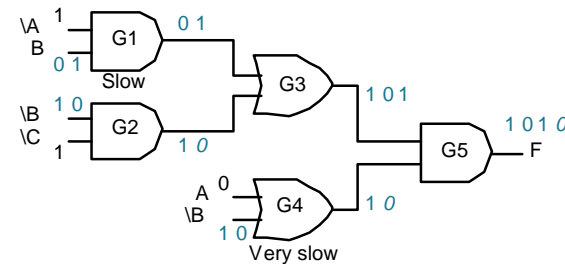- Very difficult!
- A circuit that is static hazard free can still have dynamic hazards
- Best approach:
 - Design critical circuits to be two level and eliminate all static hazards
 - OR, use good clocked synchronous design style



10-4-2007


Lec12 EECS150 Fa07

36




Protocols

 - Specified communication and coordination between distinct subsystems
- Realized by cooperating state machines
- Examples everywhere in digital design
 - Rate matching
 - Bus protocols
 - » Memory, chip-to-chip, I/O, ...
 - Arbitration for a shared resource
 - Serial protocols
 - Link protocols
 - Network protocols
- Synchronous or asynchronous
- Parallel or serial
- 2-party or multi-party



Our old friend...


Parallel to Serial Converter

 

- No "protocol" between FF's
- Every cycle they all move together
- Delays, rates, communication all designed together.




Simple Protocol Example

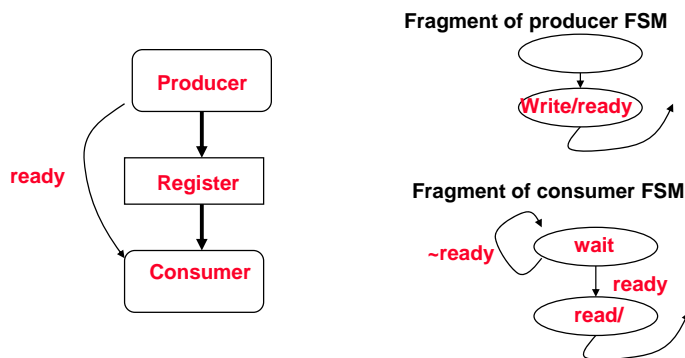

- 1-way communication protocol
- No handshake
- Assumes consumer is always ready to receive



Another Protocol Example

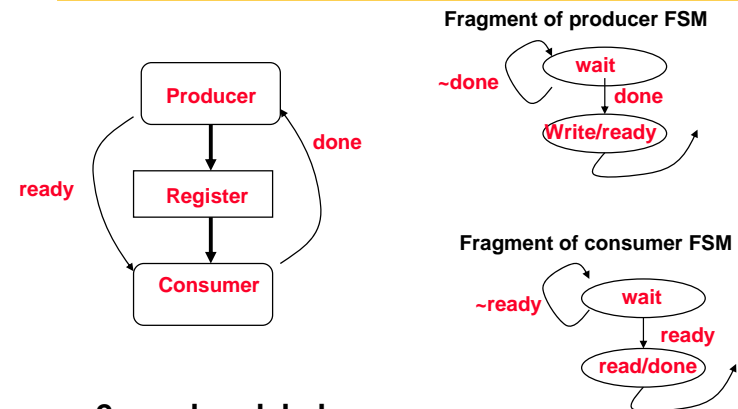

- 2-way handshake
- Assumes consumer is always ready to receive



Summary

- **All gates have delays**
 - RC delay in driving the output
- **Wires are distributed RCs**
 - Delays goes with the square of the length
- **Source circuits determines strength**
 - Serial vs parallel
- **Delays in combinational logic determine by**
 - Input delay
 - Path length
 - Delay of each gate along the path
 - Worst case over all possible input-outputs
- **Setup and CLK-Q determined by the two latches in flipflop**
- **Clock cycle : $T_{\text{cycle}} \geq T_{\text{CL}} + T_{\text{setup}} + T_{\text{clk} \rightarrow \text{Q}} + \text{worst case skew}$**

- **Delays can introduce glitches in combinational logic**
- **Subsystems glued together via protocols**
 - Delays, rates, design partitioning