



EECS 150 - Components and Design Techniques for Digital Systems

Lec 14 – Storage: DRAM, SDRAM

David Culler
Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://inst.eecs.berkeley.edu/~cs150>


10/11/2007

EECS150 Fa07 - DRAM

1



 Recall: Basic Memory Subsystem Block Diagram




RAM/ROM naming convention:

32 X 8, "32 by 8" => 32 8-bit words

1M X 1, "1 meg by 1" => 1M 1-bit words

10/11/2007

EECS150 Fa07 - DRAM

 

Question

- What is the difference between a *clock signal* and a *strobe*?

10/11/2007


EECS150 Fa07 - DRAM

3



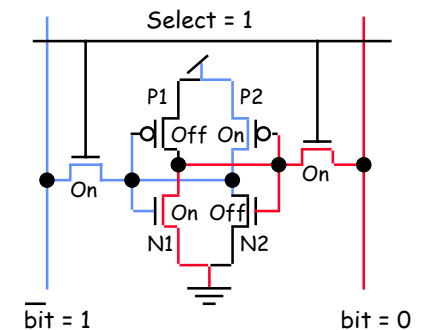Problems with SRAM

- Six transistors use up lots of area
- Consider a "Zero" is stored in the cell:
 - Transistor N1 will try to pull "bit" to 0
 - Transistor P2 will try to pull "bit bar" to 1
- If Bit lines are pre-charged high: are P1 and P2 really necessary?
 - Read starts by precharging bit and ~bit
 - Selected cell pulls one of them low
 - Sense the difference



10/11/2007

EECS150 Fa07 - DRAM


4





1-Transistor Memory Cell (DRAM)

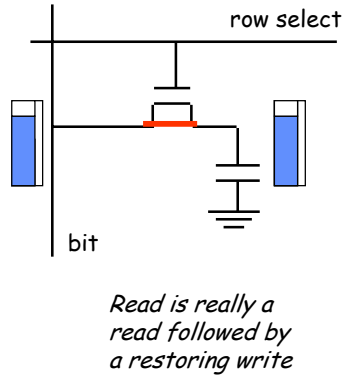- **Write:**
 - 1. Drive bit line
 - 2. Select row
- **Read:**
 - 1. Precharge bit line to $V_{dd}/2$
 - 2. Select row
 - 3. Cell and bit line share charges
 - » Minute voltage changes on the bit line
 - 4. Sense (fancy sense amp)
 - » Can detect changes of ~1 million electrons
 - 5. Write: restore the value
- **Refresh**
 - 1. Just do a dummy read to every cell. (row)




10/11/2007

EECS150 Fa07 - DRAM

5



Classical DRAM Organization (Square)

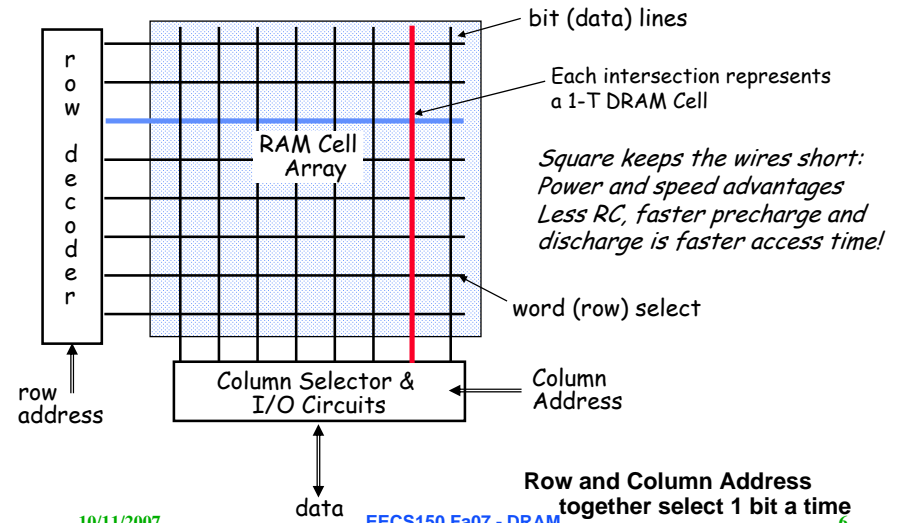


10/11/2007

EECS150 Fa07 - DRAM

6



DRAM Logical Organization (4 Mbit)

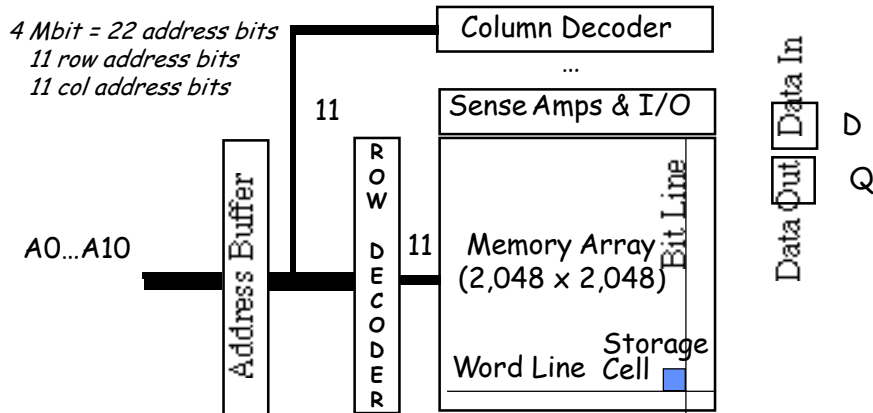

- **Square root of bits per RAS/CAS**
 - Row selects 1 row of 2048 bits from 2048 rows
 - Col selects 1 bit out of 2048 bits in such a row

10/11/2007

EECS150 Fa07 - DRAM

7




Examples



IBM 4 Mb DRAM (Dynamic Random Access Memory) chip introduced in 1989. Shown against acorn and fall foliage leaves in Burlington, Vermont where it was manufactured.



IBM 16 Mb EC/Memory Chip

 


IBM 512M SDRAM Chip

10/11/2007

EECS150 Fa07 - DRAM

Logic Diagram of a Typical DRAM

 

- Control Signals (RAS_L, CAS_L, WE_L, OE_L) are all active low
- Din and Dout are combined (D):
 - WE_L is asserted (Low), OE_L is disasserted (High)
 - » D serves as the data input pin
 - WE_L is disasserted (High), OE_L is asserted (Low)
 - » D is the data output pin
- Row and column addresses share the same pins (A)
 - RAS_L goes low: Pins A are latched in as row address
 - CAS_L goes low: Pins A are latched in as column address
 - RAS/CAS edge-sensitive

10/11/2007

EECS150 Fa07 - DRAM

9

Basic DRAM read & write



- Strobe address in two steps


10/11/2007

EECS150 Fa07 - DRAM

10

DRAM READ Timing

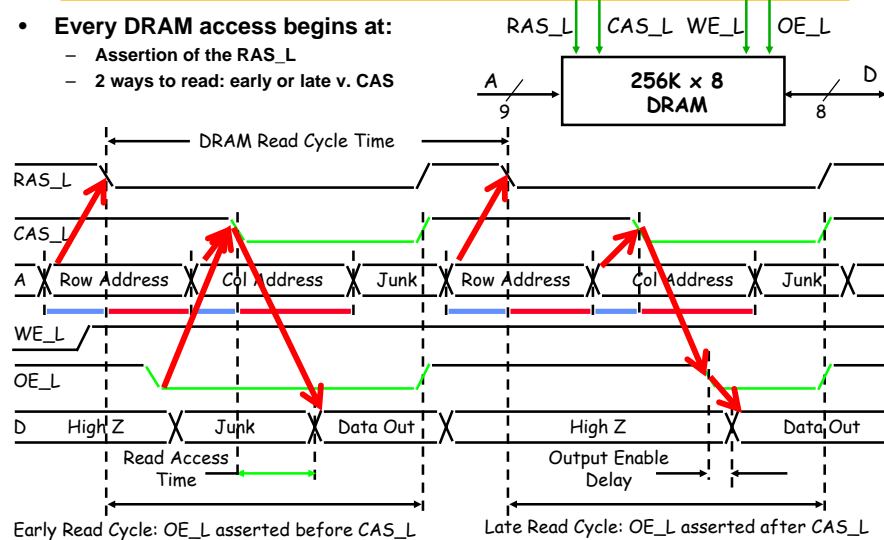- Every DRAM access begins at:
 - Assertion of the RAS_L
 - 2 ways to read: early or late v. CAS



10/11/2007

EECS150 Fa07 - DRAM

11

Early Read Sequencing

- Assert Row Address
 - Commence read cycle
 - Meet Row Addr setup time before RAS/hold time after RAS
- Assert RAS_L
- Assert OE_L
- Assert Col Address
 - Meet Col Addr setup time before CAS/hold time after CAS
- Assert CAS_L
- Valid Data Out after access time
- Disassert OE_L, CAS_L, RAS_L to end cycle


10/11/2007

EECS150 Fa07 - DRAM

12



Sketch of Early Read FSM

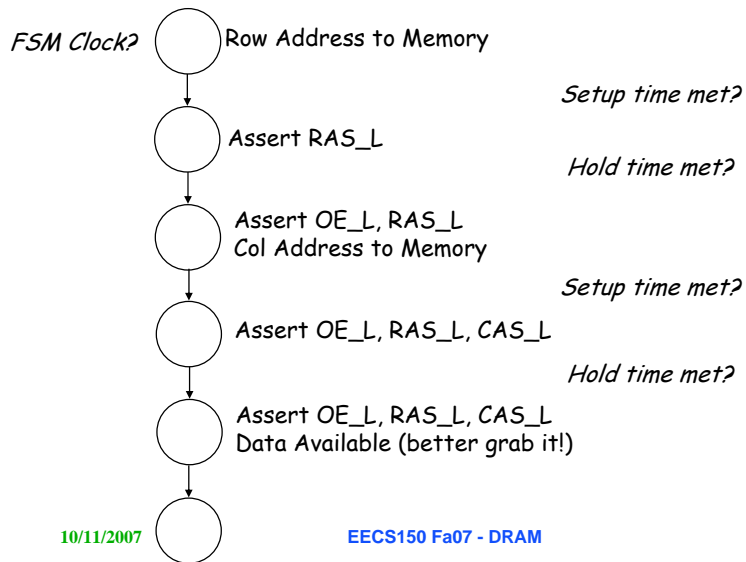

10/11/2007

EECS150 Fa07 - DRAM

13



Late Read Sequencing

- **Assert Row Address**
- **Assert RAS_L**
 - Commence read cycle
 - Meet Row Addr setup time before RAS/hold time after RAS
- **Assert Col Address**
- **Assert CAS_L**
 - Meet Col Addr setup time before CAS/hold time after CAS
- **Assert OE_L**
- **Valid Data Out after access time**
- **Disassert OE_L, CAS_L, RAS_L to end cycle**


10/11/2007

EECS150 Fa07 - DRAM

14



Sketch of Late Read FSM

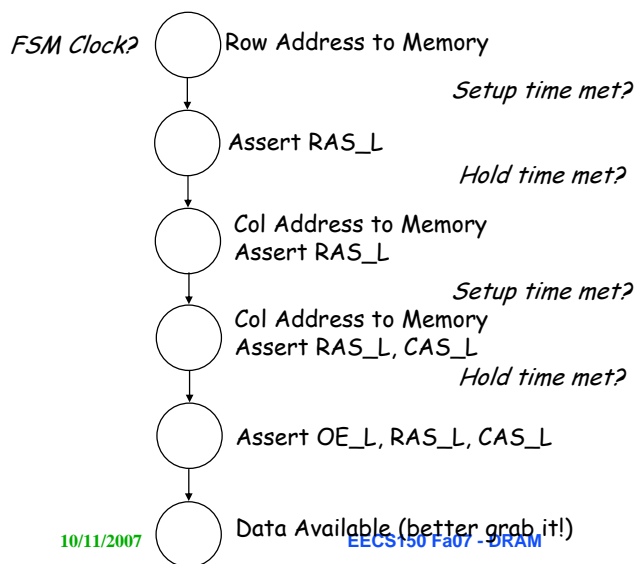

10/11/2007

EECS150 Fa07 - DRAM

15



Admin / Announcements

- Usual homework story
- Read: 10.4.2-3 and SDRAM data sheet
- We have time to understand memory protocols before using them.
- Proposal for a “low impact Mid III”
 - 1 problem a day in class over 4-5 classes.


10/11/2007

EECS150 Fa07 - DRAM

16

DRAM WRITE Timing

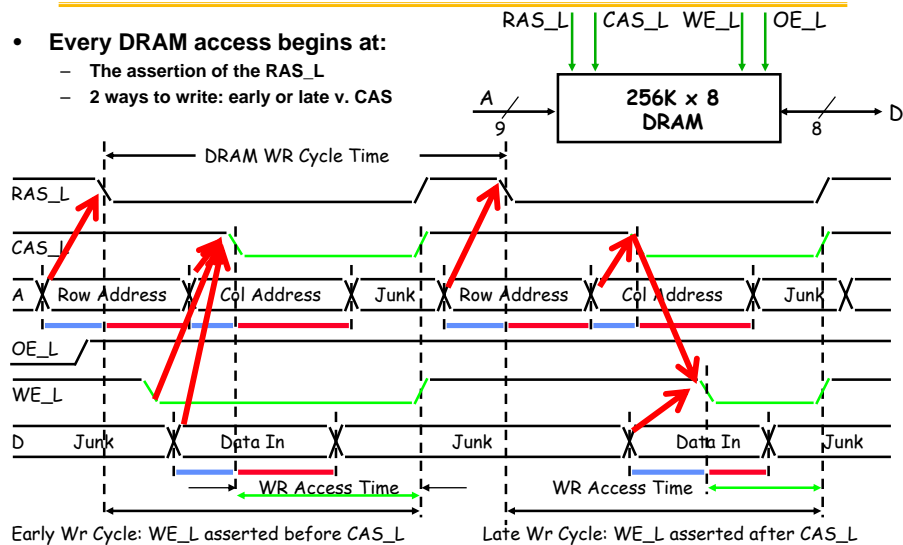- Every DRAM access begins at:
 - The assertion of the RAS_L
 - 2 ways to write: early or late v. CAS



10/11/2007

EECS150 Fa07 - DRAM

17

Key DRAM Timing Parameters

- t_{RAC} : minimum time from RAS line falling to the valid data output.
 - Quoted as the speed of a DRAM
 - A fast 4Mb DRAM $t_{RAC} = 60$ ns
- t_{RC} : minimum time from the start of one row access to the start of the next.
 - $t_{RC} = 110$ ns for a 4Mbit DRAM with a t_{RAC} of 60 ns
- t_{CAC} : minimum time from CAS line falling to valid data output.
 - 15 ns for a 4Mbit DRAM with a t_{RAC} of 60 ns
- t_{PC} : minimum time from the start of one column access to the start of the next.
 - 35 ns for a 4Mbit DRAM with a t_{RAC} of 60 ns

10/11/2007


EECS150 Fa07 - DRAM

18

Memory in Desktop Computer Systems:

- SRAM (lower density, higher speed) used in CPU register file, on- and off-chip caches.
- DRAM (higher density, lower speed) used in main memory

Processor-DRAM Gap (latency)

 

Closing the GAP:


1. Caches are growing in size.
2. Innovation targeted towards higher bandwidth for memory systems:
 - SDRAM - synchronous DRAM
 - RDRAM - Rambus DRAM
 - EDORAM - extended data out SRAM
 - Three-dimensional RAM
 - hyper-page mode DRAM video RAM
 - multibank DRAM

10/11/2007

EECS150 Fa07 - DRAM

19

DRAM with Column buffer

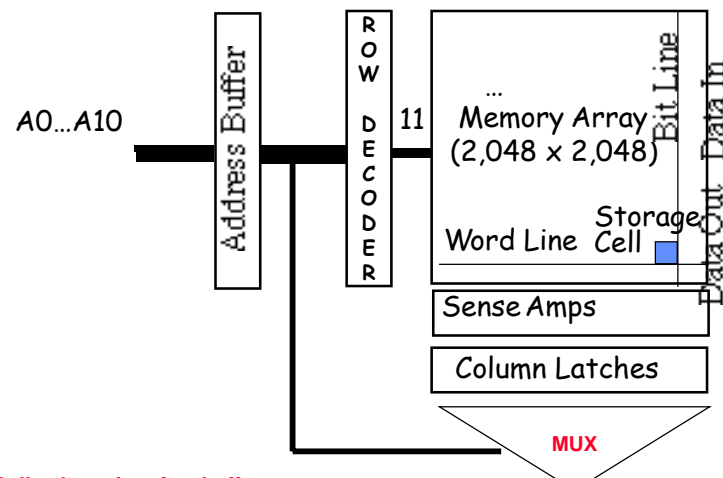

Pull column into fast buffer storage

Access sequence of bits from there

10/11/2007

EECS150 Fa07 - DRAM

20



Optimized Access to Cols in Row

- Often want to access a sequence of bits
- Page mode
 - After RAS / CAS, can access additional bits in the row by changing column address and strobing CAS
- Static Column mode
 - Change column address (without repeated CAS) to get different bit
- Nibble mode
 - Pulsing CAS gives next bit mod 4
- Video ram
 - Serial access

10/11/2007

EECS150 Fa07 - DRAM

21




More recent DRAM enhancements

- EDO - extended data out (similar to fast-page mode)
 - RAS cycle fetched rows of data from cell array blocks (long access time, around 100ns)
 - Subsequent CAS cycles quickly access data from row buffers if within an address page (page is around 256 Bytes)
- SDRAM - synchronous DRAM
 - clocked interface
 - uses dual banks internally. Start access in one bank then next, then receive data from first then second.
- DDR - Double data rate SDRAM
 - Uses both rising (positive edge) and falling (negative) edge of clock for data transfer. (typical 100MHz clock with 200 MHz transfer).
- RDRAM - Rambus DRAM
 - Entire data blocks are access and transferred out on a high-speed bus-like interface (500 MB/s, 1.6 GB/s)
 - Tricky system level design. More expensive memory chips.

10/11/2007

EECS150 Fa07 - DRAM

22

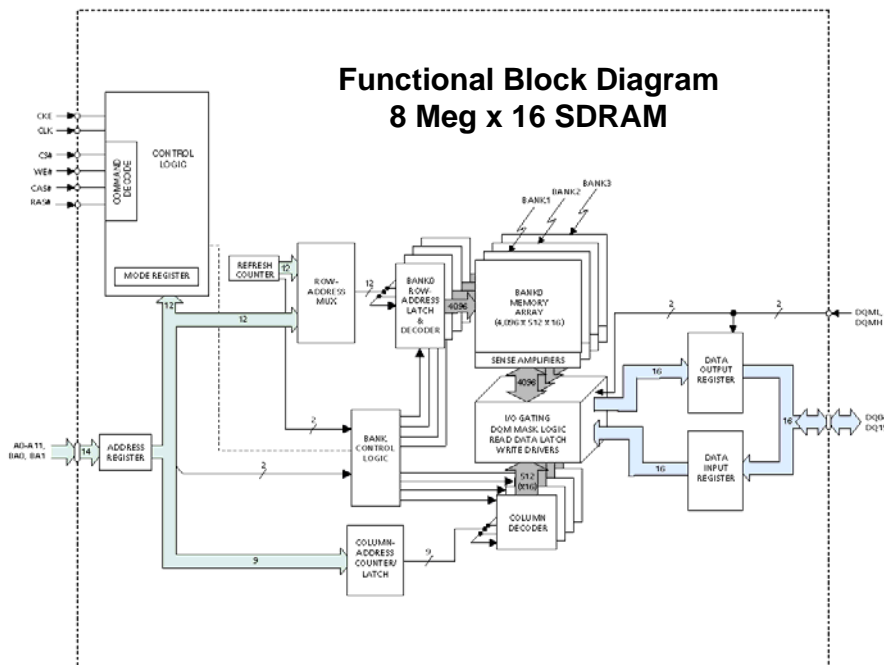

SDRAM Details

- Multiple “banks” of cell arrays are used to reduce access time:
 - Each bank is 4K rows by 512 “columns” by 16 bits (for our part)
- Read and Write operations as split into RAS (row access) followed by CAS (column access)
- These operations are controlled by sending commands
 - Commands are sent using the RAS, CAS, CS, & WE pins.
- Address pins are “time multiplexed”
 - During RAS operation, address lines select the bank and row
 - During CAS operation, address lines select the column.
- “ACTIVE” command “opens” a row for operation
 - transfers the contents of the entire to a row buffer
- Subsequent “READ” or “WRITE” commands modify the contents of the row buffer.
- For burst reads and writes during “READ” or “WRITE” the starting address of the block is supplied.
 - Burst length is programmable as 1, 2, 4, 8 or a “full page” (entire row) with a burst terminate option.
- Special commands are used for initialization (burst options etc.)
- A burst operation takes $\approx 4 + n$ cycles (for n words)


10/11/2007

EECS150 Fa07 - DRAM

24



READ burst (with auto precharge)

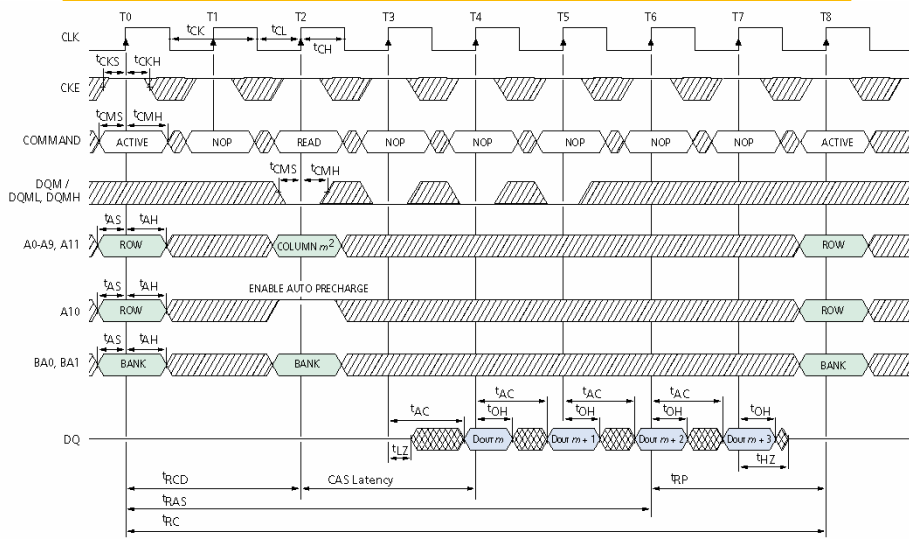


10/11/2007

EECS150 Fa07 - DRAM

25

WRITE burst (with auto precharge)

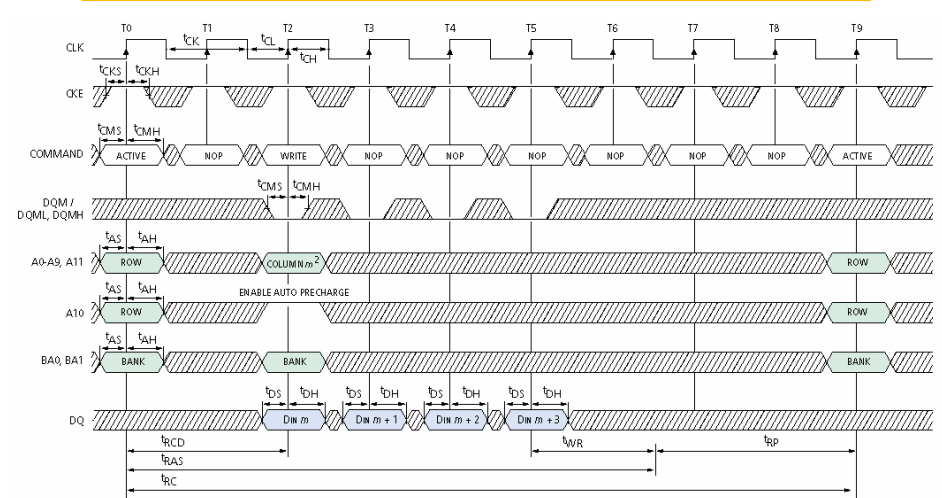

See datasheet for more details.

Verilog simulation models available.

10/11/2007


EECS150 Fa07 - DRAM

26

Volatile Memory Comparison

The primary difference between different memory types is the bit cell.


SRAM Cell

 

- Larger cell \Rightarrow lower density, higher cost/bit
- No dissipation
- Read non-destructive
- No refresh required
- Simple read \Rightarrow faster access
- Standard IC process \Rightarrow natural for integration with logic

10/11/2007

DRAM Cell

 

- Smaller cell \Rightarrow higher density, lower cost/bit
- Needs periodic refresh, and refresh after read
- Complex read \Rightarrow longer access time
- Special IC process \Rightarrow difficult to integrate with logic circuits
- Density impacts addressing


EECS150 Fa07 - DRAM

27

SDRAM Recap

• General Characteristics

 - Optimized for high density and therefore low cost/bit
- Special fabrication process – DRAM rarely merged with logic circuits.
- Needs periodic refresh (in most applications)
- Relatively slow because:
 - » High capacity leads to large cell arrays with high word- and bit-line capacitance
 - » Complex read/write cycle. Read needs “precharge” and write-back



- Multiple clock cycles per read or write access
- Multiple reads and writes are often grouped together to amortize overhead. Referred to as “bursting”.

10/11/2007

EECS150 Fa07 - DRAM

28