



EECS 150 - Components and Design Techniques for Digital Systems

Lec 15 – Addition, Subtraction, and Negative Numbers

David Culler

Electrical Engineering and Computer Sciences
University of California, Berkeley

<http://www.eecs.berkeley.edu/~culler>
<http://inst.eecs.berkeley.edu/~cs150>



Overview

- Recall basic positional notation
- Binary Addition
 - Full Adder (Boolean Logic Revisited)
- Ripple Carry
- Carry-select adder
- Carry lookahead adder
- Binary Number Representation
 - Sign & Magnitude, Ones Complement, Twos Complement


10/16/2007

EECS150-Fa07 L15 addition



Manipulating representations of numbers

- Example (from 2nd grade)

 

- Sequence of decimal digits (radix 10)
- Position represents significance (most -> least)
- Carry into next position
- 3-to-2 conversion at each step
- Results may be one digit longer, but assumed you could “make room” for it

10/16/2007

EECS150-Fa07 L15 addition



Positional Notation

- Sequence of digits: $D_{k-1} D_{k-2} \dots D_0$
represents the value

$$D_{k-1}B^{k-1} + D_{k-2}B^{k-2} + \dots + D_0 B^0$$

where $D_i \in \{0, \dots, B-1\}$

- B is the “base” or “radix” of the number system
- Example: 2004_{10} ,
- Can convert from any radix to any other
 - $1101_2 = 13_{10} = 0D_{16}$
 - $1CE8_{16} = 1 \cdot 16^3 + 12 \cdot 16^2 + 14 \cdot 16^1 + 8 \cdot 16^0 = 7400_{10}$
 - $436_8 = 4 \cdot 8^2 + 3 \cdot 8^1 + 6 \cdot 8^0 = 286_{10}$

10/16/2007

EECS150-Fa07 L15 addition


Computer Number Systems

- We all take positional notation for granted
 - $D_{k-1} D_{k-2} \dots D_0$ represents $D_{k-1}B^{k-1} + D_{k-2}B^{k-2} + \dots + D_0 B^0$ where $B \in \{0, \dots, B-1\}$
- We all understand how to compare, add, subtract these numbers
 - Add each position, write down the position bit and possibly carry to the next position
- Computers represent finite number systems
 - Generally radix 2
- How do they efficiently compare, add, sub?
 - How do we reduce it to networks of gates and FFs?
- Where does it break down?
 - Manipulation of finite representations doesn't behave like same operation on conceptual numbers

10/16/2007

EECS150-Fa07 L15 addition

Unsigned Numbers - Addition

 

Example: 3 + 2 = 5

Unsigned binary addition

Is just addition, base 2

Add the bits in each position and carry

$$\begin{array}{r}
 1 \\
 0011 \\
 + 0010 \\
 \hline
 0101
 \end{array}$$

How do we build a combinational logic circuit to perform addition?

=> Start with a truth table and go from there

10/16/2007

EECS150-Fa07 L15 addition

Binary Addition: Half Adder


A _i	B _i	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

A _i	B _i	0	1
0	0	0	1
1	1	1	0

$$\text{Sum} = \bar{A}_i B_i + A_i \bar{B}_i = A_i \oplus B_i$$

A _i	B _i	0	1
0	0	0	0
1	0	0	1

$$\text{Carry} = A_i B_i$$

 


Half-adder Schematic

But each bit position may have a carry in...

10/16/2007

EECS150-Fa07 L15 addition

Full-Adder (derivation)

 

A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = CI \text{ xor } A \text{ xor } B$$

$$CO = B CI + A CI + A B = CI (A + B) + A B$$

CI	A	B	00	01	11	10
0	0	0	0	1	0	1
1	0	0	1	0	1	0

CI	A	B	00	01	11	10
0	0	0	0	0	1	0
1	0	0	1	1	1	1




10/16/2007

EECS150-Fa07 L15 addition



Full Adder

 


Now we can connect them up to do multiple bits...

10/16/2007

EECS150-Fa07 L15 addition



Ripple Carry

 


10/16/2007

EECS150-Fa07 L15 addition




Full Adder from Half Adders (little aside)

Standard Approach: 6 Gates

 

Alternative Implementation: 5 Gates

 

$$A B + C I (A \text{ xor } B) = A B + B C I + A C I$$



10/16/2007

EECS150-Fa07 L15 addition



Delay in the Ripple Carry Adder

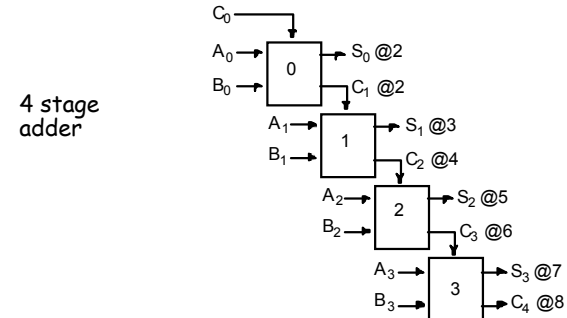 Critical delay: the propagation of carry from low to high order stages



final sum and carry


10/16/2007

EECS150-Fa07 L15 addition



Ripple Carry Timing

 Critical delay: the propagation of carry from low to high order stages



T0: Inputs to the adder are valid

T2: Stage 0 carry out (C1)

T4: Stage 1 carry out (C2)

T6: Stage 2 carry out (C3)

T8: Stage 3 carry out (C4)

10/16/2007

EECS150-Fa07 L15 addition

2 delays to compute sum
but last carry not ready until 6 delays later




Recall: Virtex-E CLB

CLB = 4 logic cells (LC) in two slices

LC: 4-input function generator, carry logic, storage element

80 x 120 CLB array on 2000E

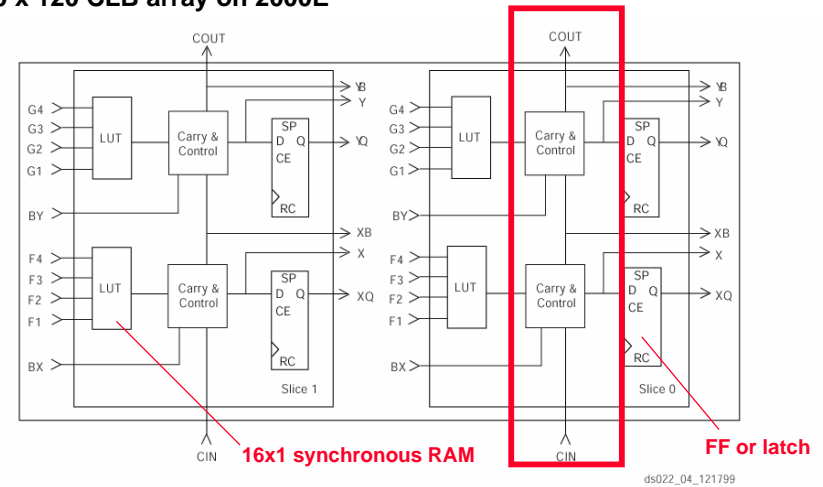


ds022_04_121799



Adders (cont.)

Ripple Adder

 

Ripple adder is inherently slow because, in general s7 must wait for c7 which must wait for c6 ...

$$T \propto n, \text{ Cost} \propto n$$

How do we make it faster, perhaps with more cost?

Classic approach: Carry Look-Ahead


Or use a MUX !!!

10/16/2007

EECS150-Fa07 L15 addition



Carry Select Adder

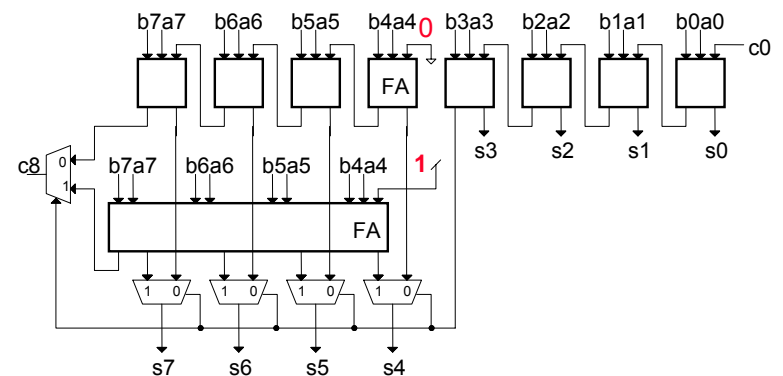

$$T = T_{\text{ripple_adder}} / 2 + T_{\text{MUX}}$$


$$\text{COST} = 1.5 * \text{COST}_{\text{ripple_adder}} + (n+1) * \text{COST}_{\text{MUX}}$$

10/16/2007

EECS150-Fa07 L15 addition



Extended Carry Select Adder

 

- What is the optimal # of blocks and # of bits/block?
 - If # blocks too large delay dominated by total mux delay
 - If # blocks too small delay dominated by adder delay per block

\sqrt{N} stages of \sqrt{N} bits


$T \propto \sqrt{N}$,
Cost $\approx 2 \cdot \text{ripple} + \text{muxes}$

10/16/2007

EECS150-Fa07 L15 addition



Carry Select Adder Performance

 

- Compare to ripple adder delay:
 - $T_{\text{total}} = 2 \sqrt{N} T_{FA} - T_{FA}$, assuming $T_{FA} = T_{\text{MUX}}$
 - For ripple adder $T_{\text{total}} = N T_{FA}$
 - “cross-over” at $N=3$, Carry select faster for any value of $N>3$.
- Is \sqrt{N} really the optimum?
 - From right to left increase size of each block to better match delays
 - Ex: 64-bit adder, use block sizes [12 11 10 9 8 7 7]
- How about recursively defined carry select?

10/16/2007

EECS150-Fa07 L15 addition



Announcements


- Reading Katz 5.6 and Appendix A
- Mid III will just stay put in final slot – no more fussing with it.
- Project demo at Lab Lecture friday
- Don't hedge on lab workload reporting
 - It matters to us and is NOT a negative in your grade
- Lab5 | CP1 | CP2 crunch
 - It should lighten
 - Don't hesitate to get guidance on the specifics of your approach from the TAs. They are there to help.
 - Lab5 solution walk-thru Friday after lab lecture

10/16/2007


EECS150-Fa07 L15 addition



What really happens with the carries

 

A	B	Cout	S	Carry action
0	0	0	Cin	kill
0	1	Cin	~Cin	Propagate
1	0	Cin	~Cin	propagate
1	1	1	Cin	generate

 

Carry Generate $G_i = A_i B_i$ *must generate carry when $A = B = 1$*

Carry Propagate $P_i = A_i \text{ xor } B_i$ *carry in will equal carry out here*


All generates and propagates in parallel at first stage. No ripple.

10/16/2007

EECS150-Fa07 L15 addition



Carry Kill / Prop / Gen example

 

10/16/2007

EECS150-Fa07 L15 addition




Carry Look Ahead Logic

Carry Generate $G_i = A_i B_i$ *must generate carry when $A = B = 1$*

Carry Propagate $P_i = A_i \oplus B_i$ *carry in will equal carry out here*

Sum and Carry can be re-expressed in terms of generate/propagate:
 
$$S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$$




$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$= A_i B_i + C_i (A_i + B_i)$$

$$= A_i B_i + C_i (A_i \oplus B_i)$$

$$= G_i + C_i P_i$$

 

10/16/2007

EECS150-Fa07 L15 addition



All Carries in Parallel

Re-express the carry logic for each of the bits:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Each of the carry equations can be implemented in a two-level logic network


Variables are the adder inputs and carry in to stage 0!

10/16/2007

EECS150-Fa07 L15 addition




CLA Implementation

 

Adder with Propagate and Generate Outputs

Increasingly complex logic

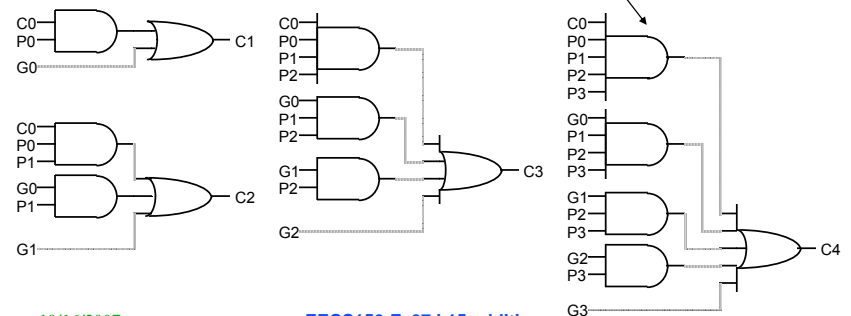


10/16/2007

EECS150-Fa07 L15 addition



How do we extend this to larger adders?

 


- **Faster carry propagation**
 - 4 bits at a time
- **But still linear**
- **Can we get to log?**
- **Compute propagate and generate for each adder BLOCK**

10/16/2007

EECS150-Fa07 L15 addition



Cascaded Carry Lookahead

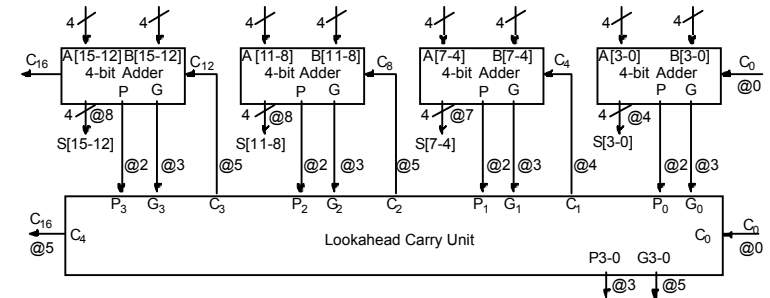

- 4 bit adders with internal carry lookahead
- second level carry lookahead unit, extends lookahead to 16 bits
- One more level to 64 bits

10/16/2007

EECS150-Fa07 L15 addition



Trade-offs in combinational logic design


- *Time vs. Space Trade-offs*
 - Doing things fast requires more logic and thus more space
 - Example: carry lookahead logic
- *Simple with lots of gates vs complex with fewer*
- *Arithmetic Logic Units*
 - Critical component of processor datapath
 - Inner-most "loop" of most computer instructions

10/16/2007

EECS150-Fa07 L15 addition



So what about subtraction?

 


- **Develop subtraction circuit using the same process**
 - Truth table for each bit slice
 - Borrow in from slice of lesser significance
 - Borrow out to slice of greater significance
 - Very much like carry chain
- **Homework exercise**

10/16/2007

EECS150-Fa07 L15 addition



Finite representation?

 

- What happens when $A + B > 2^N - 1$?
 - Overflow
 - Detect?
 - » Carry out
- What happens when $A - B < 0$?
 - Negative numbers?
 - Borrow out?

10/16/2007

EECS150-Fa07 L15 addition



Number Systems



- Desirable properties:
 - Efficient encoding (2^n bit patterns. How many numbers?)
 - Positive and negative
 - » Closure (almost) under addition and subtraction
 - Except when overflow
 - » Representation of positive numbers same in most systems
 - » Major differences are in how negative numbers are represented
 - Efficient operations
 - » Comparison: =, <, >
 - » Addition, Subtraction
 - » Detection of overflow
 - Algebraic properties?
 - » Closure under negation?
 - » $A == B$ iff $A - B == 0$
 - Three Major schemes:
 - sign and magnitude
 - ones complement
 - twos complement
 - excess notation
- Which one did you learn in 2nd grade?

10/16/2007

EECS150-Fa07 L15 addition



Sign and Magnitude

  

High order bit is sign: 0 = positive (or zero), 1 = negative
 Remaining low order bits is the magnitude: 0 (000) thru 7 (111)
 Number range for n bits = +/- $2^{n-1} - 1$
 Representations for 0?

Operations: =, <, >, +, - ???

10/16/2007

EECS150-Fa07 L15 addition



Ones Complement

Bit manipulation:

simply complement each of the bits

0111 -> 1000

Algebraically ...

N is positive number, then \bar{N} is its negative 1's complement

$$\bar{N} = (2^n - 1) - N$$

Example: 1's complement of 7

2^4	10000
-1	- 00001

	1111
-7	- 0111

	1000


-7 in 1's comp.

10/16/2007

EECS150-Fa07 L15 addition



Ones Complement on the number wheel

 


Subtraction implemented by addition & 1's complement
 Sign is easy to determine
 Closure under negation. If A can be represented, so can -A
 Still two representations of 0!
 If $A = B$ then is $A - B == 0$?
 Addition is **almost** clockwise advance, like unsigned

10/16/2007 EECS150-Fa07 L15 addition



Twos Complement number wheel

 

Easy to determine sign (0?)
 Only one representation for 0
 Addition and subtraction just as in unsigned case
 Simple comparison: $A < B$ iff $A - B < 0$
 One more negative number than positive number
 - one number has no additive inverse
 10/16/2007 EECS150-Fa07 L15 addition



Twos Complement (algebraically)

$$N^* = 2^n - N \quad 2^4 = 10000$$

Example: Twos complement of 7

$$\text{sub } 7 = \underline{0111}$$

1001 = repr. of -7

Example: Twos complement of -7

$$\text{sub } -7 = \underline{1001}$$

0111 = repr. of 7

Bit manipulation:

Twos complement: take bitwise complement and add one

0111 → 1000 + 1 → 1001 (representation of -7)

1001 → 0110 + 1 → 0111 (representation of 7)

10/16/2007 EECS150-Fa07 L15 addition



How is addition performed in each number system?

- Operands may be positive or negative

10/16/2007 EECS150-Fa07 L15 addition



Sign Magnitude Addition

Operand have same sign: unsigned addition of magnitudes

result sign bit is the same as the operands' sign	4	0100	-4	1100
	+ 3	0011	+ (-3)	1011
	7	0111	-7	1111

Operands have different signs:

subtract smaller from larger and keep sign of the larger

	4	0100	-4	1100
	- 3	1011	+ 3	0011
	1	0001	-1	1001

10/16/2007

EECS150-Fa07 L15 addition



Ones complement addition

Perform unsigned addition, then add in the end-around carry

4	0100	-4	1011
+ 3	0011	+ (-3)	1100
7	0111	-7	10111
		End around carry	└─ 1
			1000


4	0100	-4	1011
- 3	1100	+ 3	0011
1	10000	-1	1110
	End around carry	└─ 1	
	0001		

10/16/2007

EECS150-Fa07 L15 addition



When carry occurs

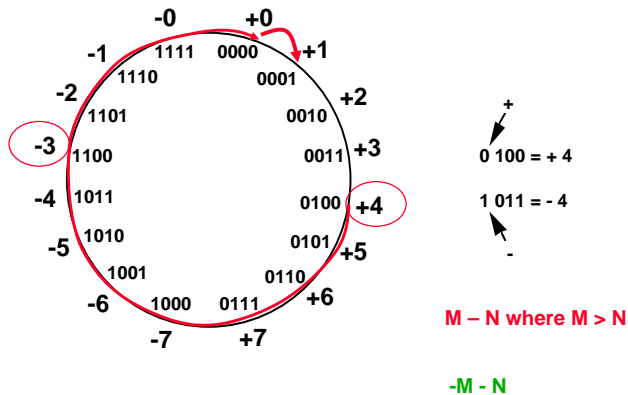

10/16/2007

EECS150-Fa07 L15 addition



Why does end-around carry work?

Recall: $\bar{N} = (2^n - 1) - N$

End-around carry work is equivalent to subtracting 2^n and adding 1

$$M - N = M + \bar{N} = M + (2^n - 1 - N) = (M - N) + 2^n - 1 \quad (\text{when } M > N)$$

$$\begin{aligned}
 -M + (-N) &= \overline{M} + \bar{N} = (2^n - M - 1) + (2^n - N - 1) \\
 &= 2^n + [2^n - 1 - (M + N)] - 1
 \end{aligned}$$

$M + N < 2^{n-1}$

after end around carry:

$$= 2^n - 1 - (M + N)$$

this is the correct form for representing $-(M + N)$ in 1's comp!

10/16/2007

EECS150-Fa07 L15 addition



Twos Complement Addition

Perform unsigned addition and
Discard the carry out.

4	0100	-4	1100
	+ 3	+ (-3)	1101
	7	-7	11001

Overflow?

4	0100	-4	1100
	- 3	+ 3	0011
	1	-1	1111


Simpler addition scheme makes twos complement the most common choice for integer number systems within digital systems

10/16/2007

EECS150-Fa07 L15 addition



Twos Complement number wheel

 

$-M + -N$ where $N + M \leq 2^n - 1$

$-M + N$ when $N > M$

10/16/2007

EECS150-Fa07 L15 addition



2s Comp: ignore the carry out

$-M + N$ when $N > M$:

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

Ignoring carry-out is just like subtracting 2^n

$-M + -N$ where $N + M \leq 2^{n-1}$

$$-M + (-N) = M^* + N^* = (2^n - M) + (2^n - N)$$

$$= 2^n - (M + N) + 2^n$$

After ignoring the carry, this is just the right twos compl. representation for $-(M + N)$!

10/16/2007

EECS150-Fa07 L15 addition




2s Complement Overflow

How can you tell an overflow occurred?

Add two positive numbers to get a negative number

 or two negative numbers to get a positive number



10/16/2007

EECS150-Fa07 L15 addition



2s comp. Overflow Detection

5	0111 0101	-7	1000 1001
3	0011	-2	1100
-8	1000	7	10111
Overflow		Overflow	
5	0000 0101	-3	1111 1101
2	0010	-5	1011
7	0111	-8	11000
No overflow		No overflow	


Overflow occurs when carry in to sign does not equal carry out

10/16/2007

EECS150-Fa07 L15 addition



2s Complement Adder/Subtractor

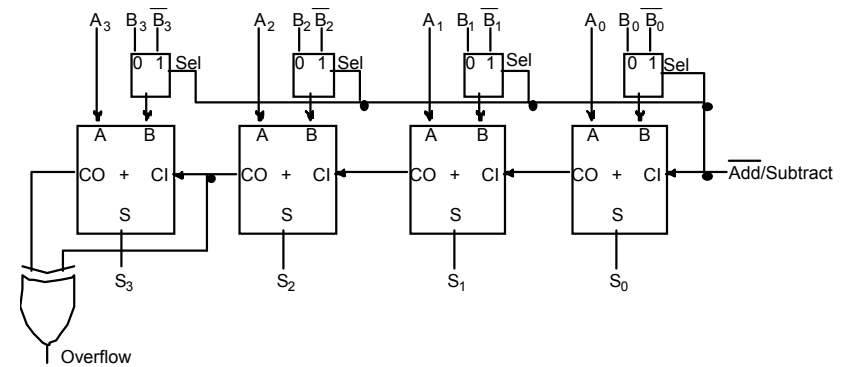

$$A - B = A + (-B) = A + \overline{B} + 1$$

10/16/2007

EECS150-Fa07 L15 addition



Summary

- **Circuit design for unsigned addition**
 - Full adder per bit slice
 - Delay limited by Carry Propagation
 - » Ripple is algorithmically slow, but wires are short
- **Carry select**
 - Simple, resource-intensive
 - Excellent layout
- **Carry look-ahead**
 - Excellent asymptotic behavior
 - Great at the board level, but wire length effects are significant on chip
- **Digital number systems**
 - How to represent negative numbers
 - Simple operations
 - Clean algorithmic properties
- **2s complement is most widely used**
 - Circuit for unsigned arithmetic
 - Subtract by complement and carry in
 - Overflow when cin xor cout of sign-bit is 1

10/16/2007

EECS150-Fa07 L15 addition