

EECS 150 - Components and Design Techniques for Digital Systems

Lec 19 – Putting it together

Case Study: A Serial Line Transmitter/Receiver

10-30-07


David E. Culler

Electrical Engineering and Computer Sciences
University of California, Berkeley


Outline

- Quick Review
- A Serial Line Transmitter/Receiver
 - Designing hardware to communicate over a single wire.
 - The data will be sent serially
 - The clocks on the two ends are completely asynchronous.
 - Communication protocol – RS232

Recall: Levels of Design Representation

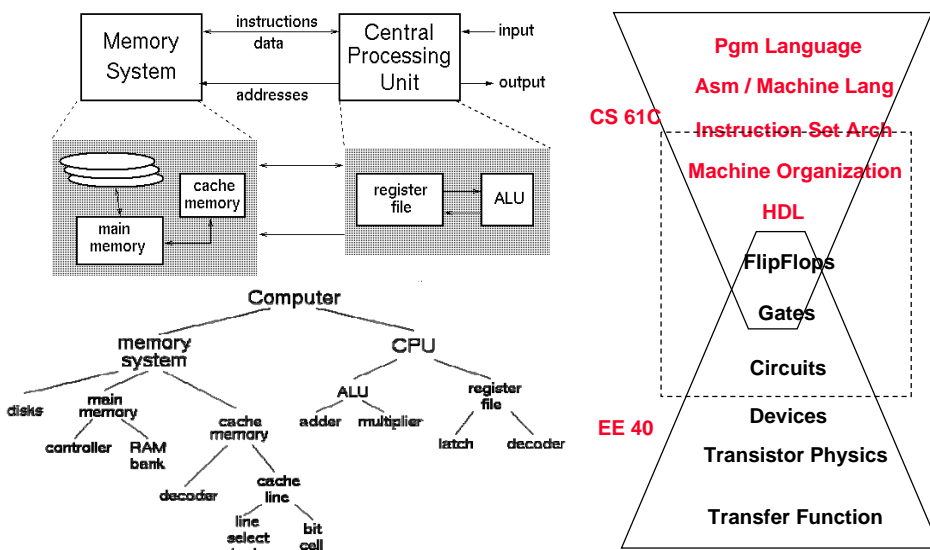

Datapath + Control

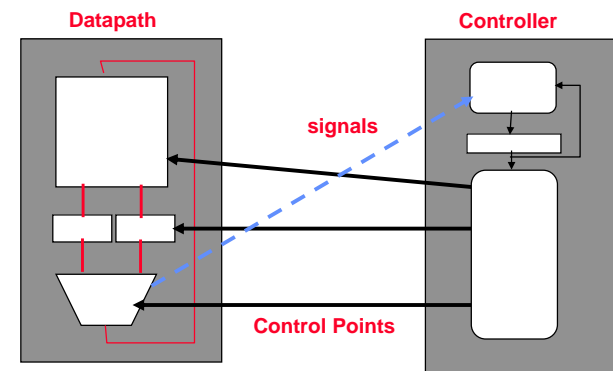

- **Datapath:** Storage, FU, interconnect sufficient to perform the desired functions
 - Inputs are Control Points
 - Outputs are signals
- **Controller:** State machine to orchestrate operation on the data path
 - Based on desired function and signals

Topics since MidTerm I

- **Project**
 - Clock domains, protocols, integration of digital subsystems
 - Controller design, interfaces, buffering, matching
- **Timing**
 - propagation delays, setup, hold, critical path, fan-out, wires
- **Static RAM**
 - 6T cell, organization (decode, cells, row, col mux, drive & sense)
 - shared data I/O, Read/Write Protocol,
- **Dynamic DRAM**
 - 1T cell, organization (decoders, row buffers, refresh)
 - Multiplexed address, RAS, CAS, protocols (page, static col, ...)
- **Number Systems**
 - Integer, Fix Point, Floating Point
 - Unsigned, 2s comp, sign mag., 1s comp, excess. Operations
- **Arithmetic Circuits**
 - Addition, Subtraction, Compare, Multiply
- **Error detection, correction, coding**
 - Parity, Hamming, SECDED, redundancy check, CRC

Motivation

- **Data Transmission in asynchronous circuits**
 - Handshaking
 - Oversampling
- **Design techniques**
 - Timing diagram
 - Top-down design
 - Bubble-and-arc
- **Communication Protocol – RS232**
 - one of the most heavily used standards ever developed for computing equipment.
 - Baud rate: 9600 ~ 56000 bps

Keypad & LCD screen

- standard parts...




Problem Specification (1)

- **Design two subsystems:**
 - Transmitter
 - » Takes input from a telephone-like keypad.
 - » Sends a byte corresponding to the key over a single wire one bit at a time.
 - Receiver
 - » Receives the serial data sent by the transmitter
 - » Displays it on a small LCD screen

 Problem Specification (2)

- RS232 protocol for formatting the data on the wire
- The wire is normally high – quiescent value
- A data begins with a *start bit* – low for one bit
- 8 data bits w/ msb first
- After the 8 bits, the wire must be high for at least one bit time before the next byte's start bit – *stop bit*




Understanding the Specification (1)

- Two devices will be completely asynchronous to each other.
 - The single wire will carry only “data”
 - The receiving side should be able to determine when a start bit is starting.
 - If sampling the wire once every bit time we may just miss the start bit between two high values.
 - We need to have a faster clock that will sample the wire faster than once every bit cycle.
- Oversampling
 - sample multiple times during each bit time to make sure that we pick out the starting falling edge of each byte's transmission.
 - *Oversampling* is a common technique in communication circuits

Understanding the Specification (2)


- LCD device is asynchronous.
 - There is no clock.
 - We have asynchronous control signals
- Robust and Modular
 - Need to make sure the data has been transmitted.
 - Data processing speeds are not the same.
- Handshaking
 - Need to make sure your data has been transferred to the destination.
 - 1. Sender: Request
 - 2. Receiver: Request Acknowledged
 - 3. Sender: OK...
 - 4. Receiver: Work done!!

 

Design Techniques

- Timing Diagram
 - Oversampling needs to pick up falling edge of input signal and interacts with counters.
 - Handshaking is between asynchronous circuits and synchronous circuits.
 - In general, timing diagram is very important in digital design.
- Top Down & Bubble-and-arc Diagram
 - Top Down design: define larger block and break it into smaller blocks.
 - Bubble-and-arc for finite state machines.


Implementation (1)

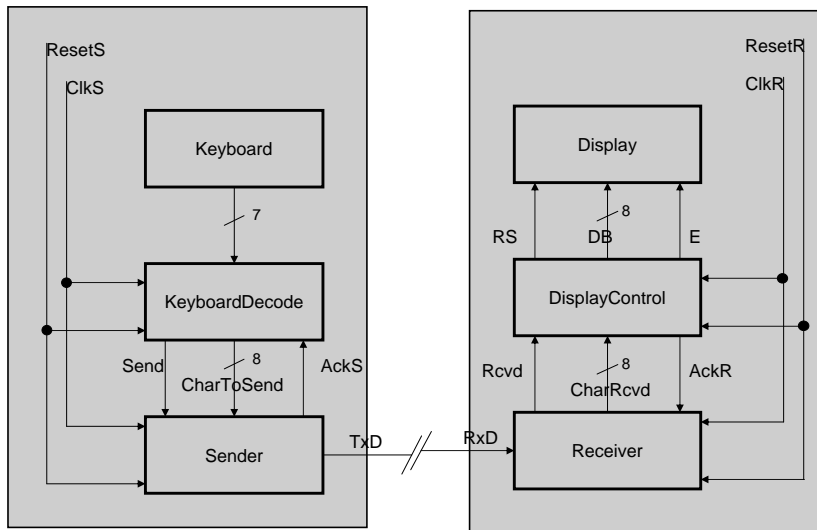


Implementation (2)

- **Sender**
 - Keyboard - input device
 - KeyboardDecode – decodes the signals from the keypad and turns them in to the appropriate character code for the button. Bridges KB and Sender domains.
 - Sender – takes the byte and serially transmits it over the single wire
- **Receiver**
 - Display – LCD output
 - DisplayControl – gives data and controls to the LCD appropriately to get the corresponding character to show up on the screen. Bridges domain.
 - Receiver – observes the signal wire coming from the sender and determines when a byte has been received.

Keyboard (1)

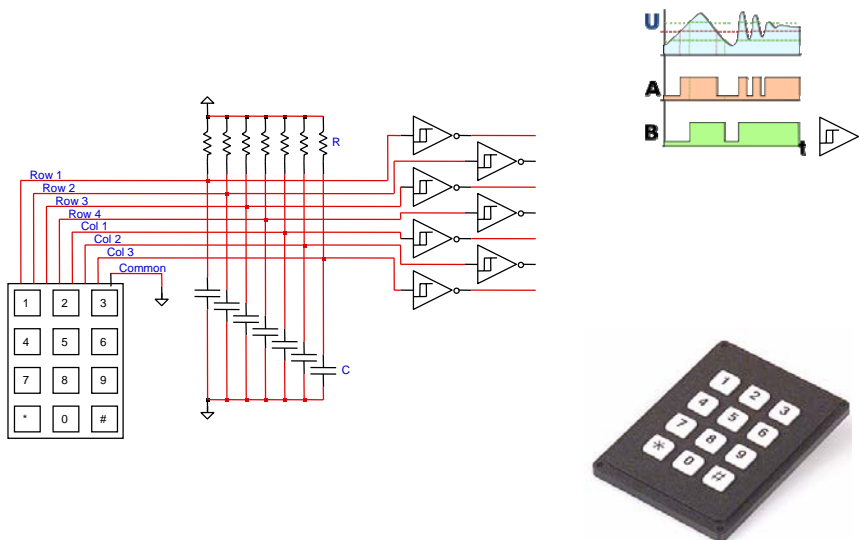


Keyboard (2)

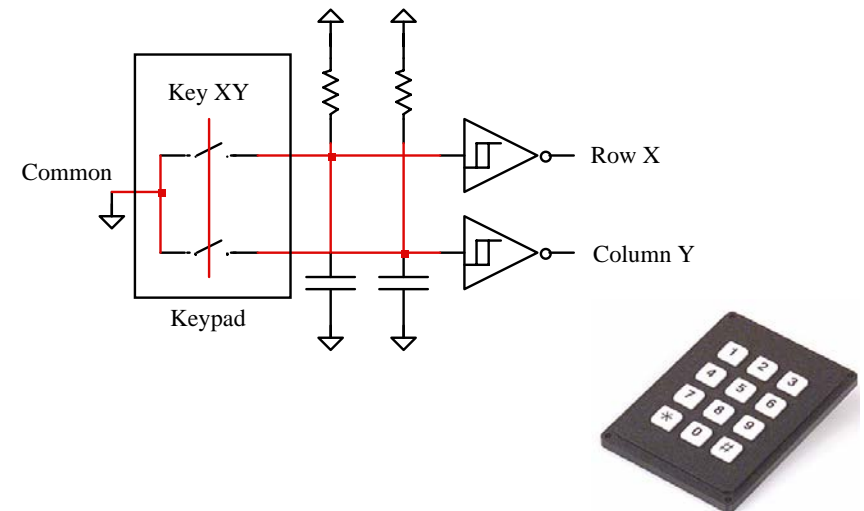


KeyboardDecode

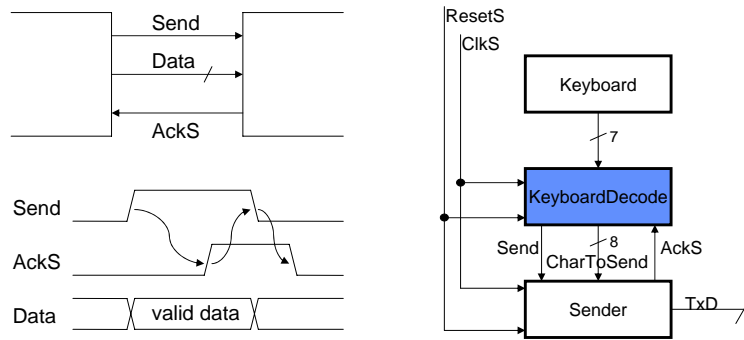- It decodes key presses into the 8-bit character code.
- Four-cycle handshake – robust and modular




KeyboardDecode – Handshaking (1)

 - Handshake between the KeyboardDecode block and the Sender block.
- **Send** is raised first.
- Raise **AckS** in response.
- This in turn will be seen by the original block that is now assured its raising of the **Send** output has been observed. It then lowers **Send**
- Lower **AckS**.





KeyboardDecode – Handshaking (2)

 - Either block can take more time to do what it needs to do by delaying when it raises or lowers its signal.
- If data is being sent along with the handshake, the data should be held constant from when **Send** is raised to when the acknowledgement, via **AckS**, is received.




KeyboardDecode – Handshaking (3)

  

- What happens if a second key is pressed?

KeyboardDecode

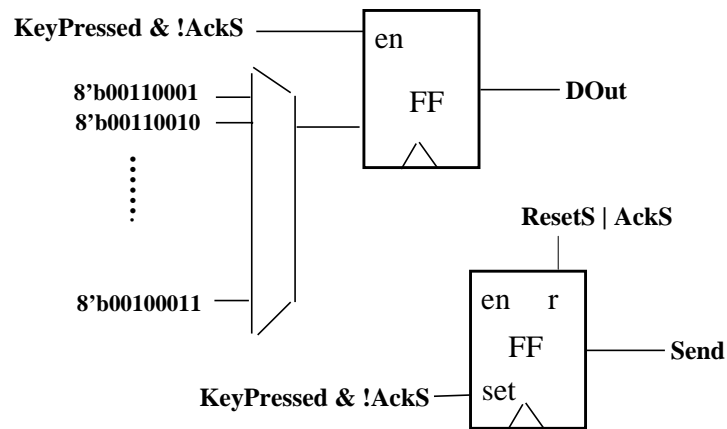

KeyboardDecode – Verilog

Module KeyboardDecode (ClkS, ResetS, R1, R2, R3, R4, C1, C2, C3, AckS, Send, DOut);

```
input ClkS, ResetS, AckS;
input R1, R2, R3, R4, C1, C2, C3;
output Send;
output [7:0] DOut;
```

```
reg [7:0] DOut;
reg send;
wire KeyPressed;
```

```
assign KeyPressed = (R1 | R2 | R3 | R4) & (C1 | C2 | C3);
```


KeyboardDecode – Verilog(Decoding)

```
always @ (posedge ClkS) begin
  if (KeyPressed & !AckS) begin
    if (R1 & C1) DOut <= 8'b00110001; //code for 1
    else if (R1 & C2) DOut <= 8'b00110010; //code for 2
    else if (R1 & C3) DOut <= 8'b00110011; //code for 3
    else if (R2 & C1) DOut <= 8'b00110100; //code for 4
    else if (R2 & C2) DOut <= 8'b00110101; //code for 5
    else if (R2 & C3) DOut <= 8'b00110110; //code for 6
    else if (R3 & C1) DOut <= 8'b00110111; //code for 7
    else if (R3 & C2) DOut <= 8'b00111000; //code for 8
    else if (R3 & C3) DOut <= 8'b00111001; //code for 9
    else if (R4 & C1) DOut <= 8'b00101010; //code for *
    else if (R4 & C2) DOut <= 8'b00110000; //code for 0
    else if (R4 & C3) DOut <= 8'b00100011; //code for #
  end
end
```

We use ASCII codes because the display uses


KeyboardDecode – Verilog(Handshaking)
 
```
always @ (posedge ClkS) begin
  if (ResetS)
    Send <= 0;
  else if (KeyPressed & !AckS)
    Send <= 1;
  else if (AckS)
    Send <= 0;
end
```





Sender

 - It serializes data into the RS232 format.
- It implements the other half of the four-cycle handshake with the KeyboardDecode module.
- It sends 10 bits over the serial line for each key pressed on the keyboard.



Sender – Block Diagram & Bubble-and-arc

 
 


Sender – Verilog (1)

```
Module Sender (ClkS, ResetS, Send, DIn, AckS, TxD);
  input ClkS, ResetS, Send;
  input [7:0] DIn;
  output AckS, TxD;
```

```
  reg AckS;
  reg [7:0] Data;
  reg [3:0] BitCount;
```

  
```
  always @ (posedge ClkS) begin
    if (ResetS) AckS <= 0;
    else if (~AckS & Send) AckS <= 1;
    else if (AckS & BitCount[3]) AckS <= 0;
  end
```



Sender – Verilog (2)

```
  always @ (posedge ClkS) begin
    if (Send & ~AckS)      Data <= DIn;
    else if (AckS && BitCount != 0) Data <= {Data[6:0], 1'b0};
  end
```
 
```
  always @ (*) begin
    if (AckS & BitCount == 0) TxD = 0;
    else if (AckS) TxD = Data[7];
    else TxD = 1;
  end
```




Sender – Verilog (3)

```

always @ (posedge ClkS) begin
  if (ResetS)          BitCount <= 0;
  else if (Send & ~AckS) BitCount <= 0;
  else                 BitCount <= BitCount + 1;
end

```

 


Announcements

- Midterm on Thursday 11/1
 - 1-page notes
- Midterm Review on Tuesday 10/30
 - 8:00-10:00 in 125 Cory
- Clarify HW due time

Receiver

 - It needs to sample the input to determine when a start bit occurs
- Then, it stores the value of the 8 bits after the start bit
- After that, it passes them on to the DisplayControl module.



Receiver – Verilog (1)

```


Module Receiver (ClockR, ResetR, RxD, AckR, DOut, Rcvd);
  input ClockR, ResetR, RxD, AckR;
  output [7:0] DOut;
  output Rcvd;

```

```

reg [7:0] DOut, Data;
reg Rcvd, Receiving;
wire [3:0] BitCount;
wire [1:0] CycleCount;

```

 

```

always @ (posedge ClockR) begin
  if (ResetR)          Receiving <= 0;
  else if (~Receiving & ~RxD) Receiving <= 1;
  else if (Receiving && BitCount == 9) Receiving <= 0;
end


```


Receiver – Verilog (2)

```

Counter Cycle ( .Clock(ClockR),
                .Reset(ResetR | (~Receiving & ~RxD)),
                .Set(1'b0),
                .Load(),
                .Enable(Receiving),
                .In(),
                .Count(CycleCount));
defparam Cycle.width = 2;

```

 


Receiver – Verilog (3)

```

Counter Bit ( .Clock(ClockR),
              .Reset(ResetR | (~Receiving & ~RxD)),
              .Set(1'b0),
              .Load(),
              .Enable(Receiving & CycleCount == 3),
              .In(),
              .Count(BitCount));
defparam Bit.width = 4;

```

 


Receiver – Verilog (4)

```

ShiftRegister SIPO ( .Pin(),
                    .SIn(RxD),
                    .POut(Data),
                    .SOut(),
                    .Load(),
                    .Enable(Receiving && CycleCount == 1),
                    .Clock(ClkR),
                    .Reset(ResetR));

```

 


Receiver – Verilog (5)

```

Register DataRegister (.Clock(ClkR),
                      .Reset(ResetR),
                      .Set(),
                      .Enable(BitCount == 9 && CycleCount == 0),
                      .In(Data),
                      .Out(DOut))


```

 

Receiver – Verilog (6)


```

 always @ (posedge ClkR) begin
  if (ResetR)                Rcvd <= 0;
  else if (BitCount == 9 && CycleCount == 0) Rcvd <= 1;
  else if (AckR)              Rcvd <= 0;
end
  
```



Display – LCD (1)

 - Enable driven interface
- At a falling edge of the Enable signal, LCD interprets the mode and the data inputs.
- Setup Time and Hold Time of LCD < ~10ns
- Our Clock is much slower than this.




Display – LCD (2)

- The RS input is used to indicate how to interpret the data bits
- 0: Command 1: Character
- Whenever we reset our circuit, we need to execute the four operations below.


Operation	RS	DB7...DB0
Clear Display	0	0000 0001
Function Set	0	0011 0011
Display On	0	0000 1100
Entry Mode Set	0	0000 0110
Write Character	1	DDDD DDDD

DisplayControl

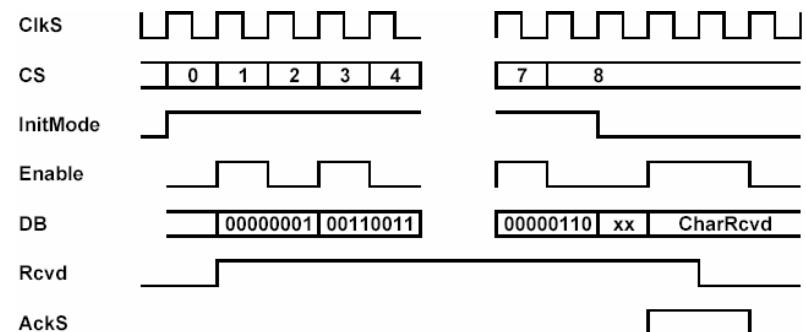- Two main tasks:
 - Initialize LCD.
 - Display the characters received by the receiver module.
- Four-cycle handshake with the Receiver module using *Rcvd* and *AckR*



DisplayControl – FSM(Counter)

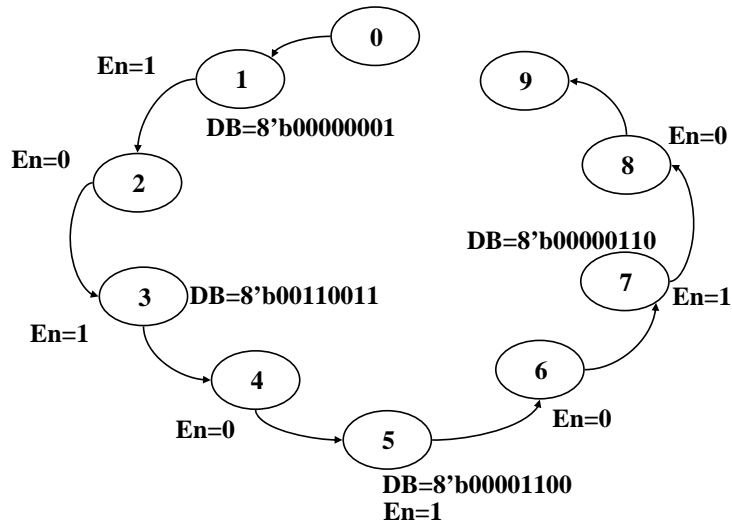

DisplayControl – Verilog (1)

```

Module DisplayControl (ClkR, ResetR, Rcvd, CharRcvd, AckR, DB,
RS, Enable);
input ClkR, ResetR, Rcvd;
input [7:0] CharRcvd;
output AckR, RS, Enable;
output [7:0] DB;
  
```

```

reg AckR;
reg initMode; //indicates if the initialize sequence is in progress
reg [7:0] DB;
reg[3:0] CS;
  
```

```

assign RS = ~initMode;
  
```


DisplayControl – Verilog (2)

```

always @ (posedge ClkR) begin // FSM/Counter
  if (ResetR) CS <= 0;
  else if (initMode) CS <= CS + 1;
end
  
```

```

 always @ (posedge ClkR) begin //FSM
  if (ResetR) initMode <= 1;
  else if (initMode == 1 && CS == 9) initMode <= 0;
end
  
```




DisplayControl – Verilog (3)

```

always @ (posedge ClkR) begin
  if (initMode & CS == 0) DB <= 8'b00000001;
  else if (initMode & CS == 2) DB <= 8'b00110011;
  else if (initMode & CS == 4) DB <= 8'b00001100;
  else if (initMode & CS == 6) DB <= 8'b00000110;
  else if (~initMode & Rcvd) DB <= CharRcvd;
end
  
```



```

 assign Enable = (initMode? CS[0] : AckR);
  
```




DisplayControl – Verilog (4)
  
```
always @ (posedge ClkR) begin
  if (ResetR) AckR <= 0;
  else if (~initMode & Rcvd & ~AckR) AckR <= 1;
  else if (~initMode & ~Rcvd) AckR <= 0;
end
```



Review: Design hierarchy

 

Summary

- **Point of this case study**
 - to show how to breakdown a larger problem into components
 - to show how to define the interfaces between components
- **There are many ways to accomplish this, the design presented here is merely one of these.**
- **Most of the design choices were made so as to make the implementation easy to understand.**