



EECS 150 - Components and Design Techniques for Digital Systems

Lec 20 – RTL Design Optimization 11/6/2007

Shauki Elassaad




**Electrical Engineering and Computer Sciences
University of California, Berkeley**

Slides adapted from Prof. Culler's 2004 lecture

<http://www-inst.eecs.berkeley.edu/~cs150>




Levels of Design Representation

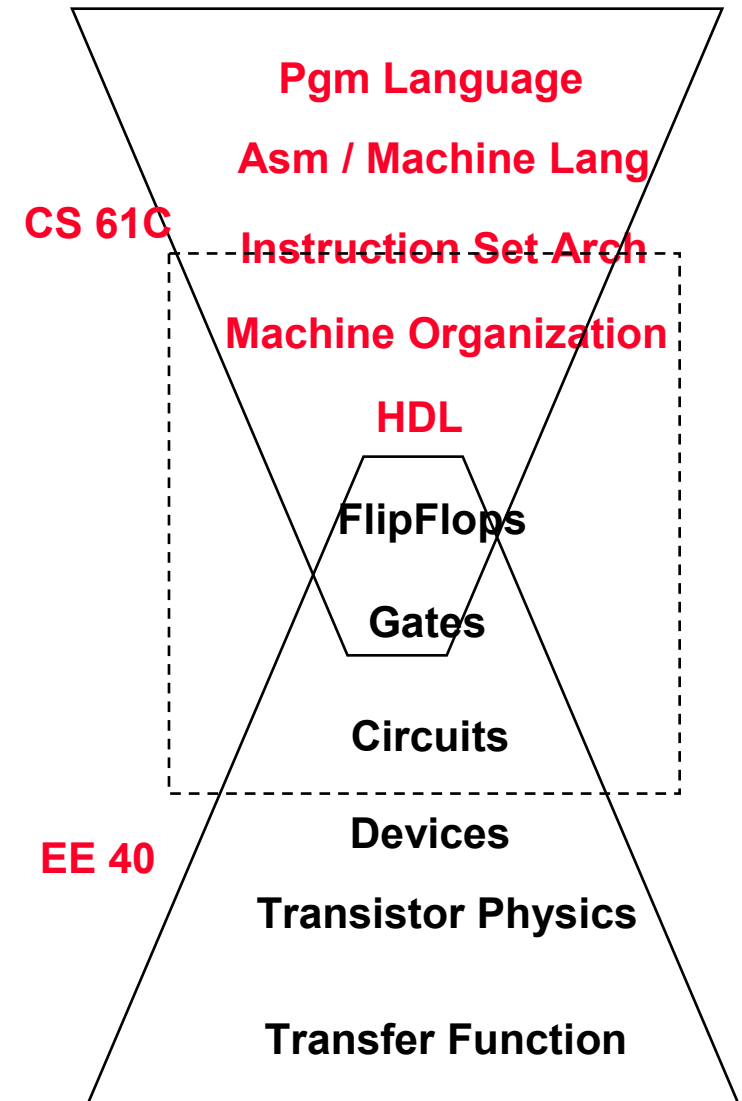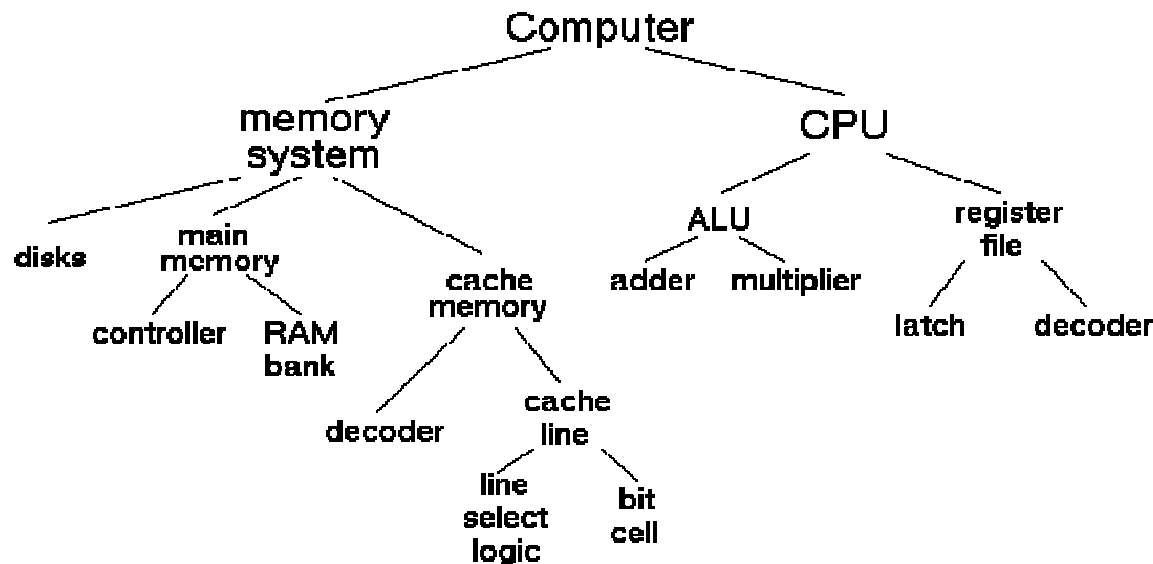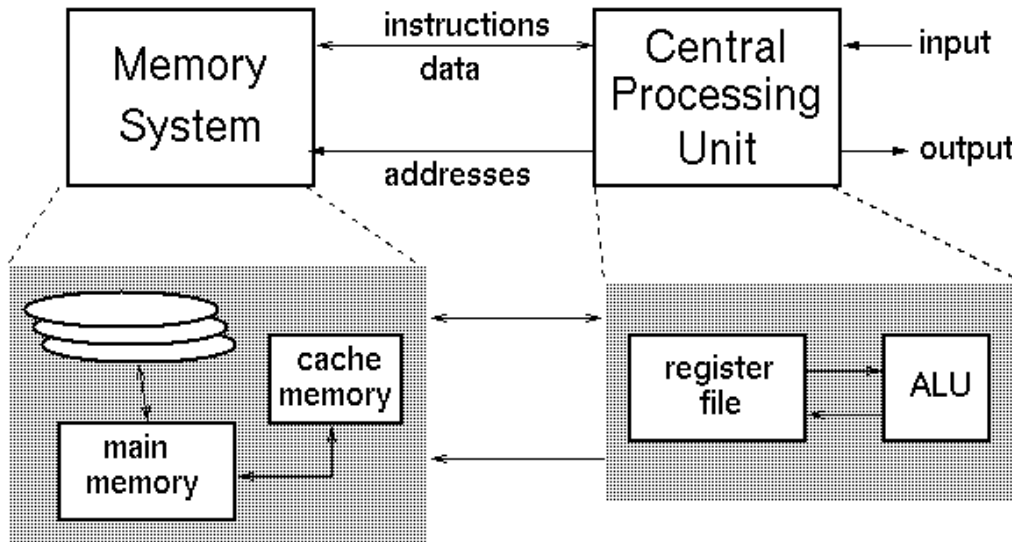




A Standard High-level Organization

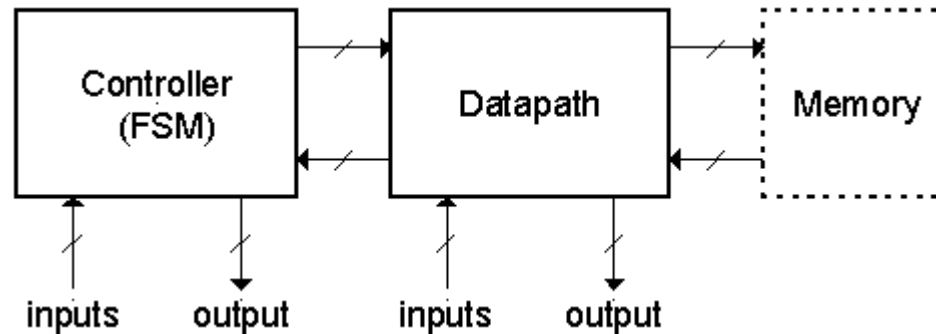


- **Controller**
 - accepts external and control input, generates control and external output and sequences the movement of data in the datapath.
- **Datapath**
 - is responsible for data manipulation. Usually includes a limited amount of storage.
- **Memory**
 - optional block used for long term storage of data structures.

 - **Standard model for CPUs, micro-controllers, many other digital sub-systems.**
- **Usually *not* nested.**
- **Often cascaded:**





Datapath vs Control

 


- **Datapath: Storage, FU, interconnect sufficient to perform the desired functions**
 - Inputs are Control Points
 - Outputs are signals
- **Controller: State machine to orchestrate operation on the data path**
 - Based on desired function and signals



Register Transfer Level Descriptions

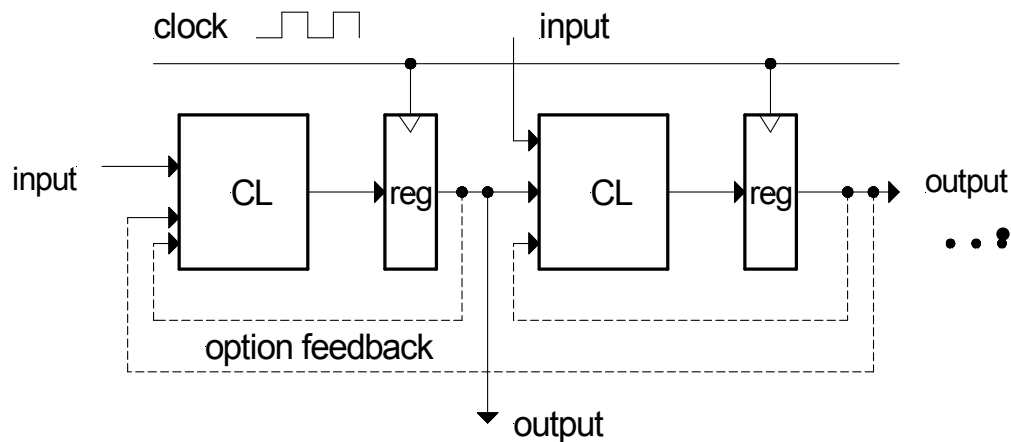- A standard high-level representation for describing systems.
- It follows from the fact that all synchronous digital system can be described as a set of state elements connected by combination logic (CL) blocks:



- RTL comprises a set of *register transfers* with optional operators as part of the transfer.

- Example:

$\text{regA} \leftarrow \text{regB}$

$\text{regC} \leftarrow \text{regA} + \text{regB}$

if (start==1) $\text{regA} \leftarrow \text{regC}$

- Personal style:

- use “;” to separate transfers that occur on separate cycles.
- Use “,” to separate transfers that occur on the same cycle.

Example (2 cycles):

$\text{regA} \leftarrow \text{regB}, \text{regB} \leftarrow 0;$

$\text{regC} \leftarrow \text{regA};$



RTL Abstraction

- **Increases productivity by allowing designers to focus on behavior rather than gate-level logic**
 - Design components can be specified w/ concise and modular code in verilog
 - Synthesis tools understand RTL design
- **Think of design in terms of Control and Datapath.**
- **Designers are still very close to hardware. They can think of and optimize architectures, timing (cycle-level), and other design trade-offs (power, speed, area..)**




RTL Design Process

- **Data-path Requirements**
 - How many registers do you need?
 - What transformations/operations are needed?
- **Interface Requirements**
 - What signals control the operations?
 - What order these signals are in?
- **State-machine design**
 - What are the outputs in each state?
 - Look for concurrency in the design.



A Register Transfer

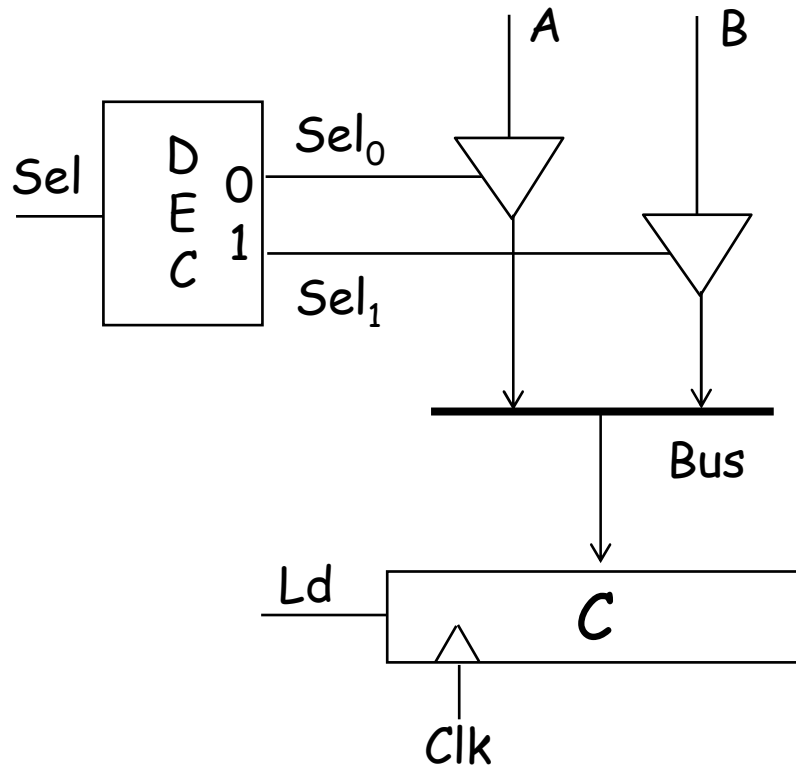


$C \leftarrow A$

$Sel \leftarrow 0; Ld \leftarrow 1$

$C \leftarrow B$

$Sel \leftarrow 1; Ld \leftarrow 1$

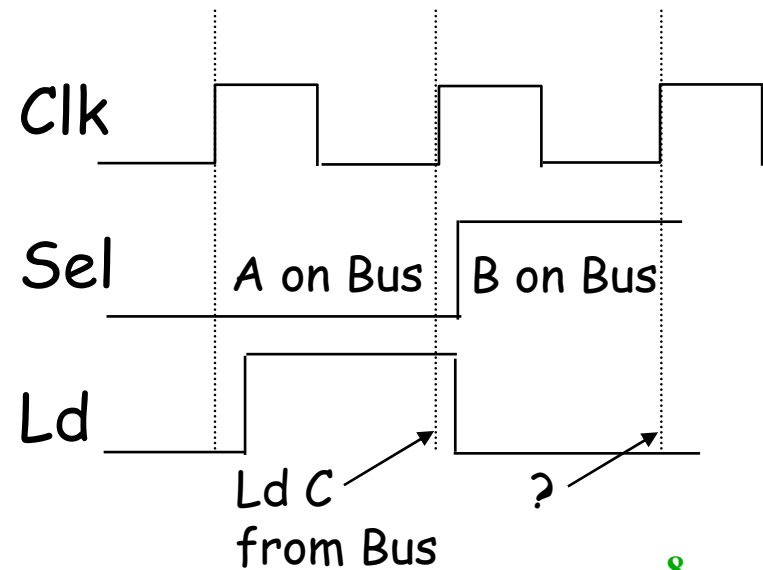




One of potentially many source regs goes on the bus to one or more destination regs

Register transfer on the clock



Register Transfers - interconnect

  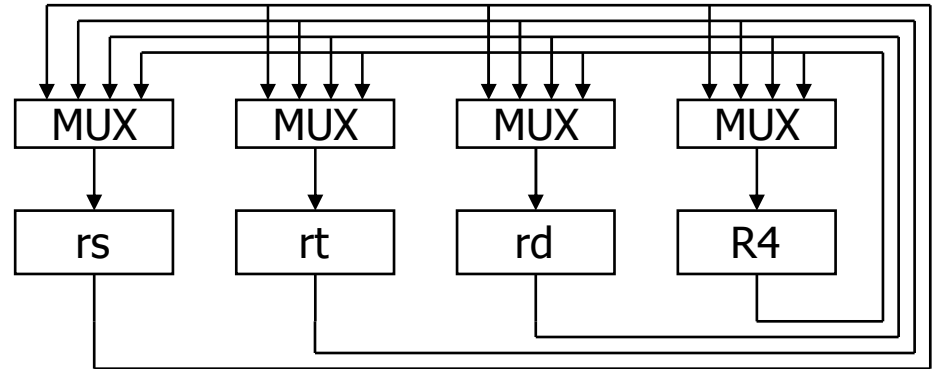
- **Point-to-point connection**
 - Dedicated wires
 - Muxes on inputs of each register
- **Common input from multiplexer**
 - Load enables for each register
 - Control signals for multiplexer
- **Common bus with output enables**
 - Output enables and load enables for each register





Register Transfer – multiple busses

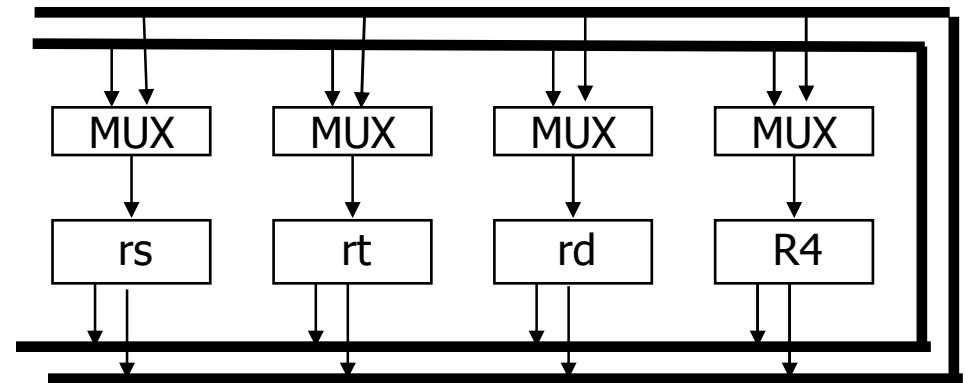
- One transfer per bus
- Each set of wires can carry one value
- **State Elements**
 - Registers
 - Register files
 - Memory
- **Combinational Elements**
 - Busses
 - ALUs
 - Memory (read)





Registers

 - **Selectively loaded – EN or LD input**
- **Output enable – OE input**
- **Multiple registers – group 4 or 8 in parallel**




OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs



Register Files

 
- **Collections of registers in one package**
 - Two-dimensional array of FFs
 - Address used as index to a particular word
 - Separate read and write addresses so can do both at same time
- **Ex: 4 by 4 register file**
 - 16 D-FFs
 - Organized as four words of four bits each
 - Write-enable (load)
 - Read-enable (output enable)





Memories

- **Larger Collections of Storage Elements**
 - Implemented not as FFs but as much more efficient latches
 - High-density memories use 1-5 switches (transistors) per bit
- **Ex: Static RAM – 1024 words each 4 bits wide**
 - Once written, memory holds forever (not true for denser dynamic RAM)
 - Address lines to select word (10 lines for 1024 words)
 - Read enable
 - » Same as output enable
 - » Often called chip select
 - » Permits connection of many chips into larger array
 - Write enable (same as load enable)
 - Bi-directional data lines
 - » output when reading, input when writing

 




ALU

- **Block Diagram**

 
- **Input: data and operation to perform**
 - » **Add, Sub, AND, OR, NOT, XOR, ...**
- **Output: result of operation and status information**





Data Path (Hierarchy)

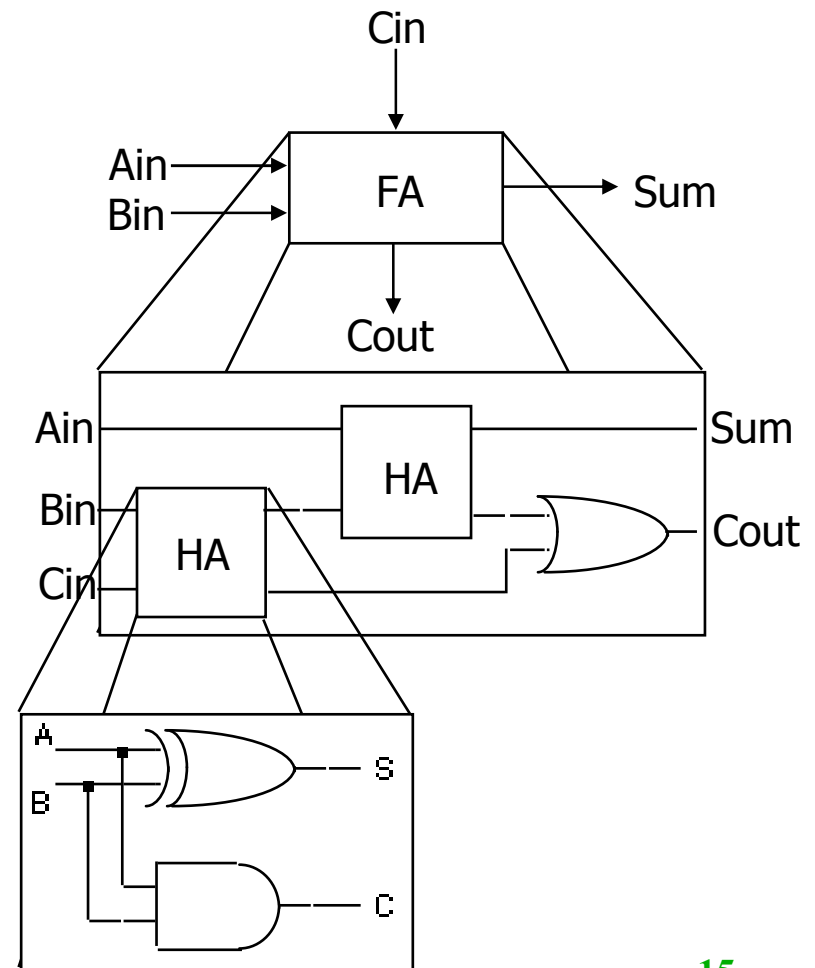
- **Arithmetic circuits constructed in hierarchical and iterative fashion**
 - each bit in datapath is functionally identical
 - 4-bit, 8-bit, 16-bit, 32-bit datapaths





 Example Data Path (ALU + Registers)


- **Accumulator**
 - Special register
 - One of the inputs to ALU
 - Output of ALU stored back in accumulator
- **One-input Operation**
 - Other operand and destination is accumulator register
 - $AC \leftarrow AC \text{ op } REG$
 - "Single address instructions"
 - » $AC \leftarrow AC \text{ op } Mem[addr]$






Data Path (Bit-slice)

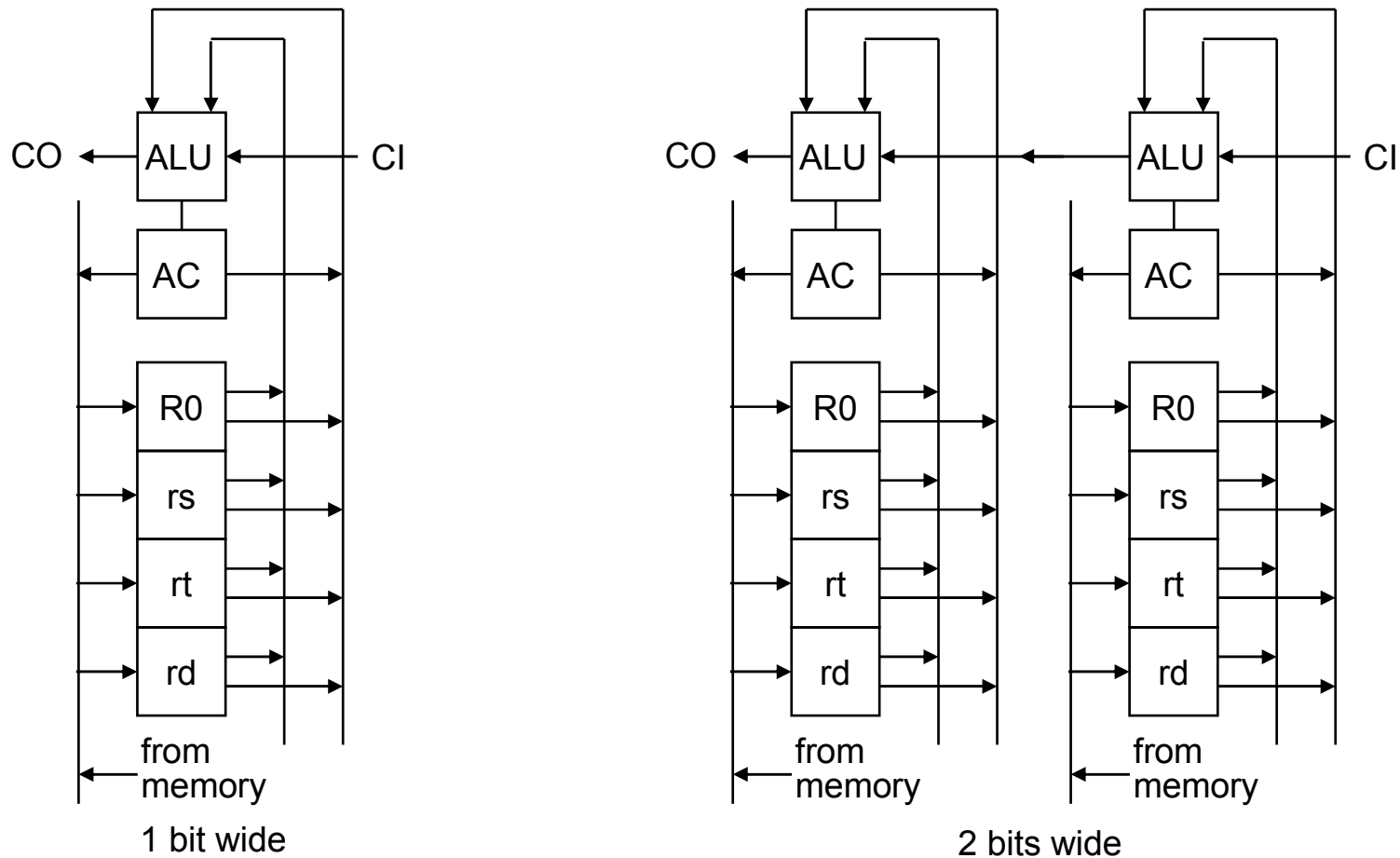- **Bit-slice concept: iterate to build n-bit wide datapaths**
- **Data bit busses run through the slice**





Example of Using RTL

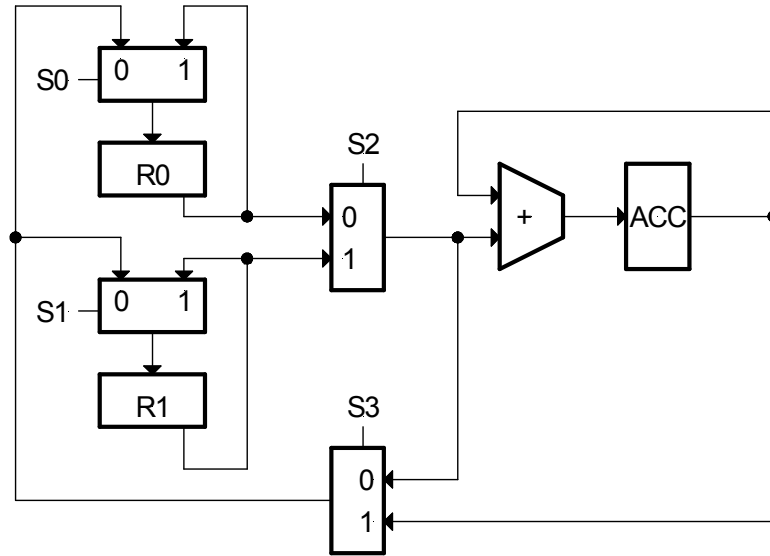

$ACC \leftarrow ACC + R0, R1 \leftarrow R0;$
 $ACC \leftarrow ACC + R1, R0 \leftarrow R1;$
 $R0 \leftarrow ACC;$

-
-
-

- **RTL description is used to sequence the operations on the datapath (dp).**
- **It becomes the high-level specification for the controller.**
- **Design of the FSM controller follows directly from the RTL sequence. FSM controls movement of data by controlling the multiplexor/tri-state control signals.**



Example of Using RTL

- RTL often used as a starting point for designing *both* the dp and the control:
- example:
 - regA \leftarrow IN;
 - regB \leftarrow IN;
 - regC \leftarrow regA + regB;
 - regB \leftarrow regC;
- From this we can deduce:
 - IN must fanout to both regA and regB
 - regA and regB must output to an adder
 - the adder must output to regC
 - regB must take its input from a mux that selects between IN and regC
- What does the datapath look like:
- The controller:



Announcements

- **Lab Etiquette**
 - Food in the lab is still a problem. If problem persists, we will be forced to close the lab when TAs are not present!
- **Discussion sessions are on for this week.**
- **No Lab Lecture this week**




Components of the data path

- **Storage**
 - Flip-flops
 - Registers
 - Register Files
 - SRAM
- **Arithmetic Units**
 - Adders, subtractors, ALUs (built out of FAs or gates)
 - Comparators
 - Counters
- **Interconnect**
 - Wires
 - Busses
 - Tri-state Buffers
 - MUX



Arithmetic Circuit Design

 - Full Adder
- Adder
- Relationship of positional notation and operations on it to arithmetic circuits
- Each component has associated costs:
 - Power
 - Speed
 - Area
 - Reliability






List Processor Example

- **RTL gives us a framework for making high-level optimizations.**
 - Fixed function unit
 - Approach extends to instruction interpreters
- **General design procedure outline:**
 1. Problem, Constraints, and Component Library Spec.
 2. “Algorithm” Selection
 3. Micro-architecture Specification
 4. Analysis of Cost, Performance, Power
 5. Optimizations, Variations
 6. Detailed Design





 1. Problem Specification

- Design a circuit that forms the sum of all the 2's complements integers stored in a linked-list structure starting at memory address 0:



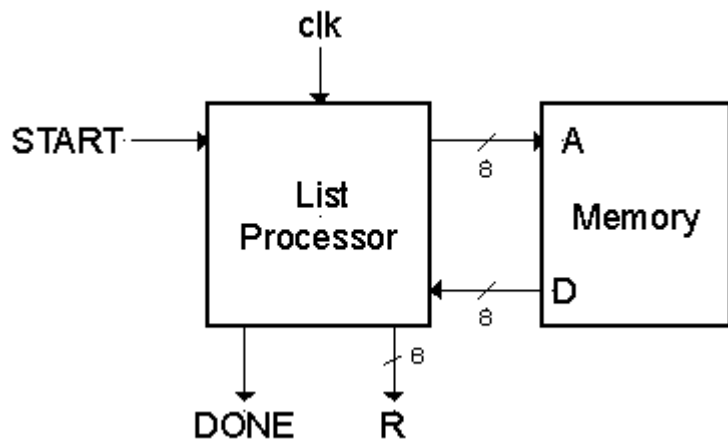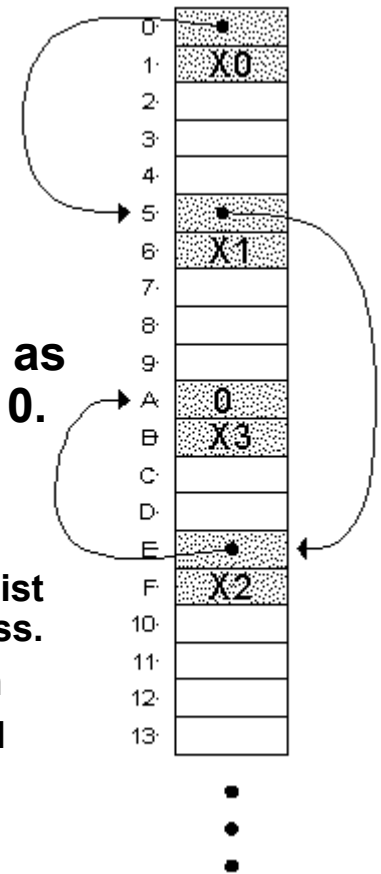- All integers and pointers are 8-bit. The link-list is stored in a memory block with an 8-bit address port and 8-bit data port, as shown below. The pointer from the last element in the list is 0. At least one node in list.



I/Os:

- START resets to head of list and starts addition process.
- DONE signals completion
- R, Bus that holds the final result



1. Other Specifications

- **Design Constraints:**
 - Usually the design specification puts a restriction on cost, performance, power or all. We will leave this unspecified for now and return to it later.

- **Component Library:**

component	delay
simple logic gates	0.5ns
n-bit register	clk-to-Q=0.5ns setup=0.5ns (data and LD)
n-bit 2-1 multiplexor	1ns
n-bit adder	(2 log(n) + 2)ns
memory	10ns read (asynchronous read)
zero compare	0.5 log(n)

(single ported memory)

Are these reasonable?



2. Algorithm Specification

- In this case the memory only allows one access per cycle, so the algorithm is limited to sequential execution. If in another case more input data is available at once, then a more parallel solution may be possible.
- ***Assume datapath state registers NEXT and SUM.***
 - NEXT holds a pointer to the node in memory.
 - SUM holds the result of adding the node values to this point.


```
If (START==1) NEXT←0, SUM←0;
repeat {
    SUM←SUM + Memory[NEXT+1];
    NEXT←Memory[NEXT];
} until (NEXT==0);
R←SUM, DONE←1;
```




3. Architecture #1

Direct implementation of RTL description:

Datapath

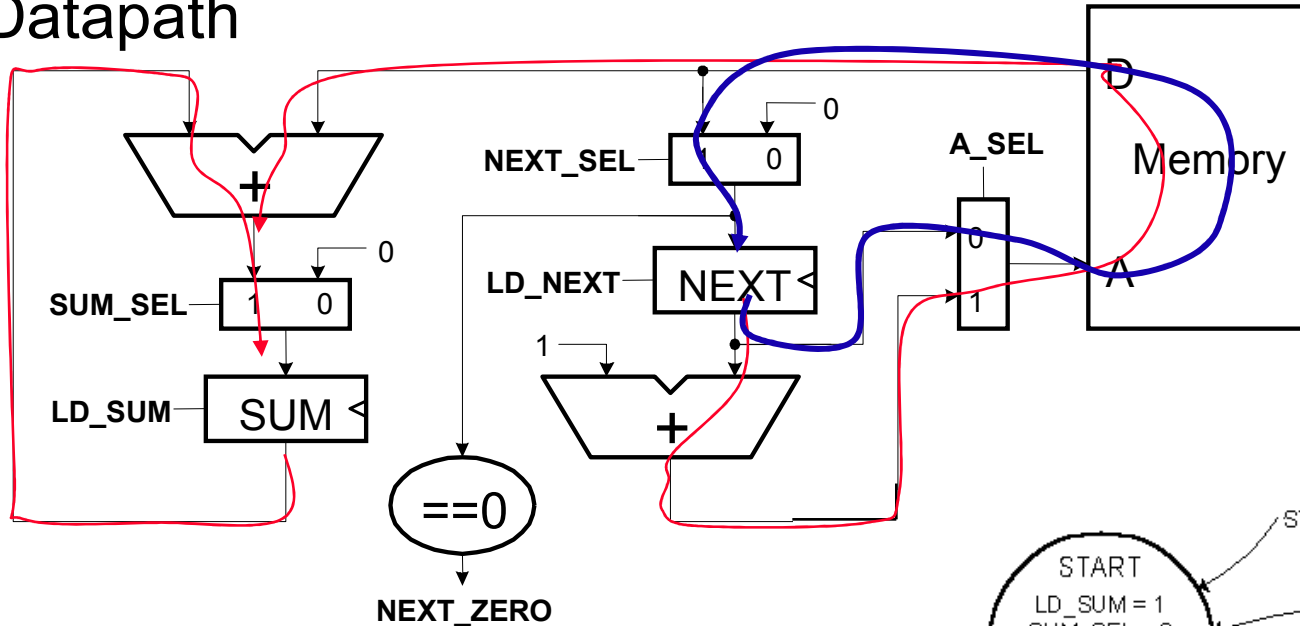

Controller

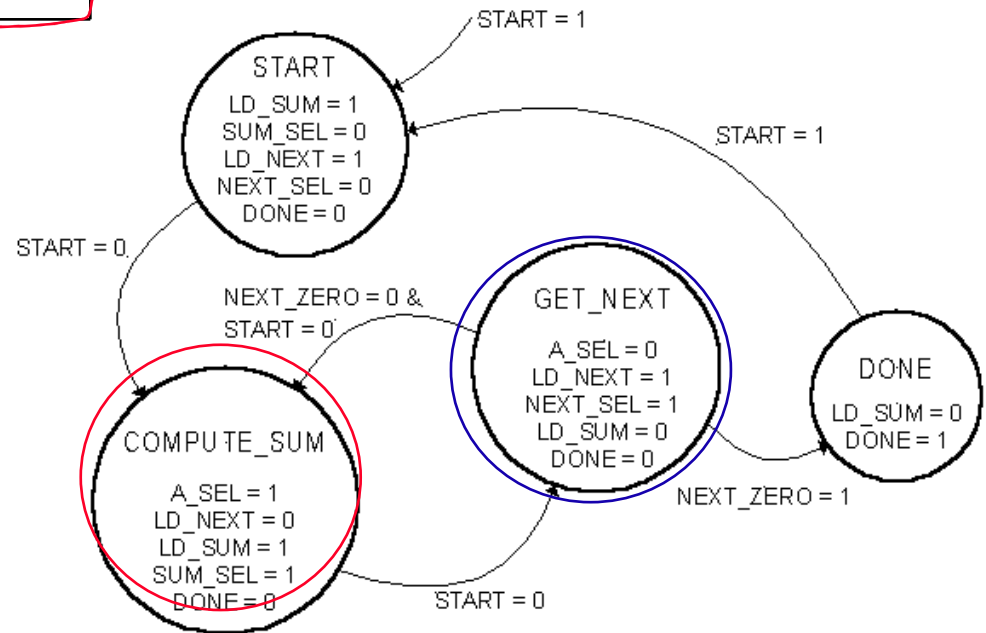

If (START==1) NEXT←0, SUM←0;
 repeat {
 SUM←SUM + Memory[NEXT+1];
 NEXT←Memory[NEXT];
 } until (NEXT==0);
 R←SUM, DONE←1;




4. Analysis of Cost, Performance, and Power

- **Skip Power for now.**
- **Cost:**
 - How do we measure it? # of transistors? # of gates? # of CLBs?
 - Depends on implementation technology. Usually we are interested in comparing the *relative* cost of two competing implementations. (Save this for later)
- **Performance:**
 - 2 clock cycles per number added.
 - What is the minimum clock period?
 - The controller might be on the critical path. Therefore we need to know the implementation, and controller input and output delay.




Possible Controller Implementation

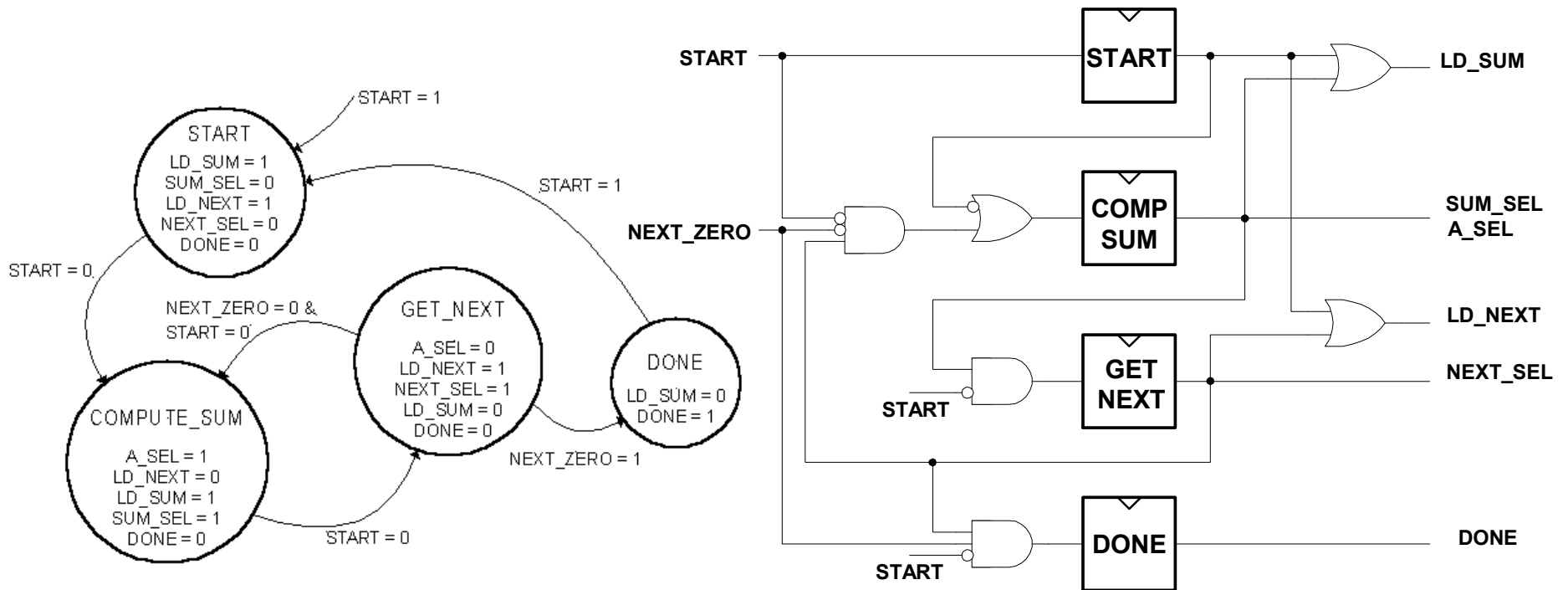

- Based on this, what is the controller input and output delay?



Critical Path...

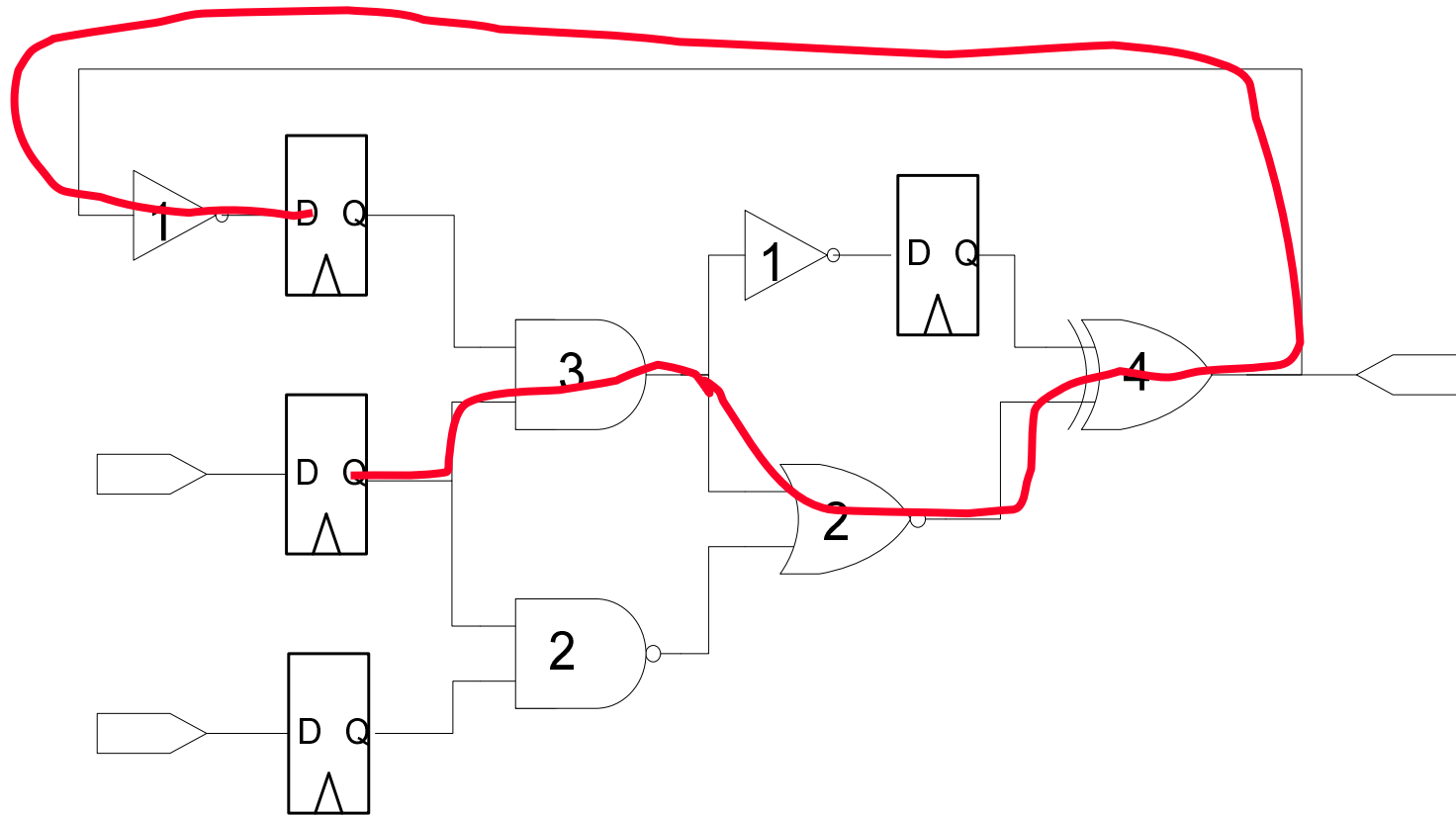


- Longest path from any reg out to any reg input




4. Analysis of Performance

COMPUTE_SUM state

 


GET_NEXT state

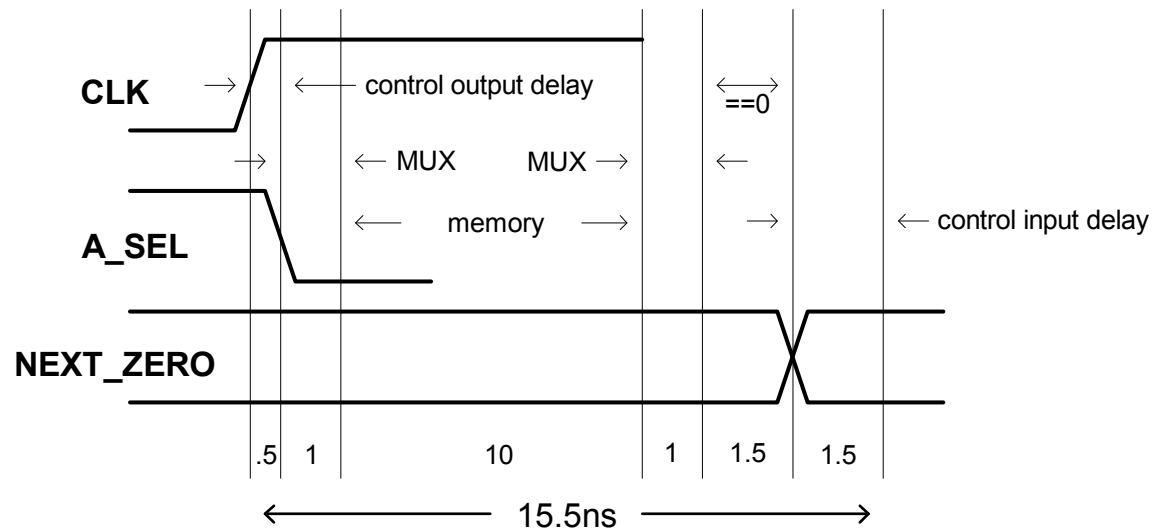



Critical paths

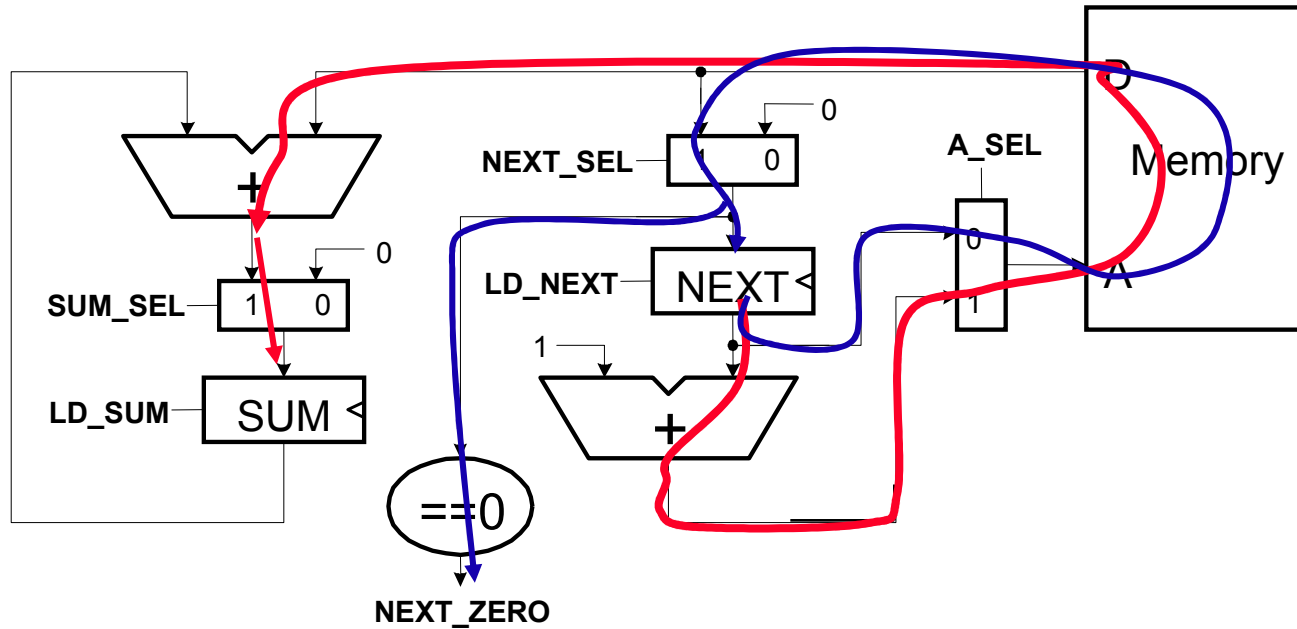

- Identify bottlenecks in design
- Share/schedule resources to improve performance



4. Analysis of Performance

- **Detailed timing:**
 - clock period (T) = max (clock period for each state)
 - T > 31ns, F < 32 MHz
- **Observation:**
 - COMPUTE_SUM state does most of the work. Most of the components are inactive in GET_NEXT state.
 - GET_NEXT does: Memory access + ...
 - COMPUTE_SUM does: 8-bit add, memory access, 15-bit add + ...
- **Conclusion:**
 - Move one of the adds to GET_NEXT.



5. Optimization


- *Add new register named NUMA, for address of number to add.*
- Update RTL to reflect our change (note still 2 cycles per iteration):

```
If (START==1) NEXT←0, SUM←0, NUMA←1;
repeat {
    SUM←SUM + Memory[NUMA];
    NUMA←Memory[NEXT] + 1,
    NEXT←Memory[NEXT] ;
} until (NEXT==0);
R←SUM, DONE←1;
```



5. Optimization

- Architecture #2:

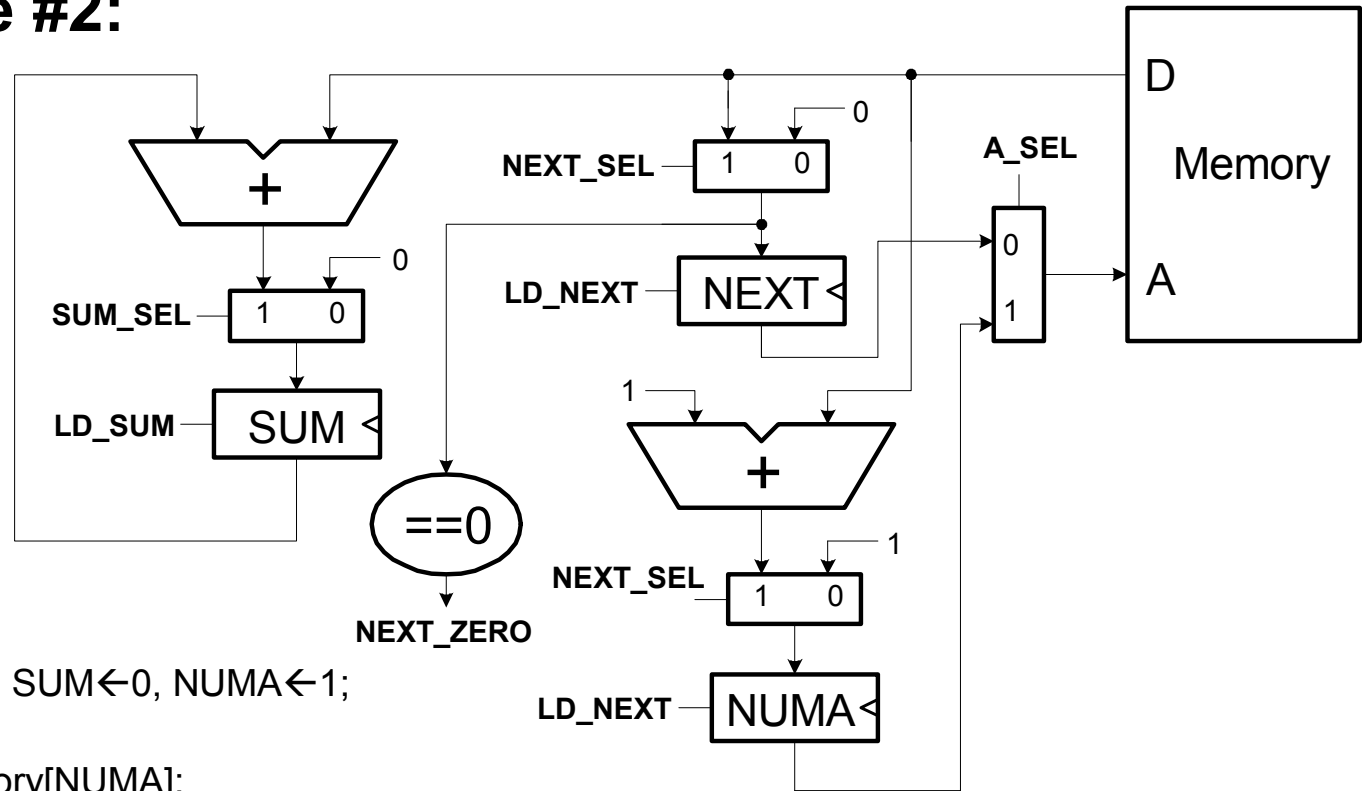

```

If (START==1) NEXT←0, SUM←0, NUMA←1;
repeat {
  SUM←SUM + Memory[NUMA];
  NUMA←Memory[NEXT] + 1, NEXT←Memory[NEXT] ;
} until (NEXT==0);
R←SUM, DONE←1;


```

- Incremental cost: addition of another register and mux.



5. Optimization, Architecture #2

COMPUTE_SUM state

 


- New timing:
Clock Period (T) = max (clock period for each state)

$$T > 23\text{ns}, F < 43\text{Mhz}$$

- Is this worth the extra cost?
- Can we lower the cost?


GET_NEXT state

 

- Notice that the circuit now only performs one add on every cycle. Why not share the adder for both cycles?



5. Optimization, Architecture #3

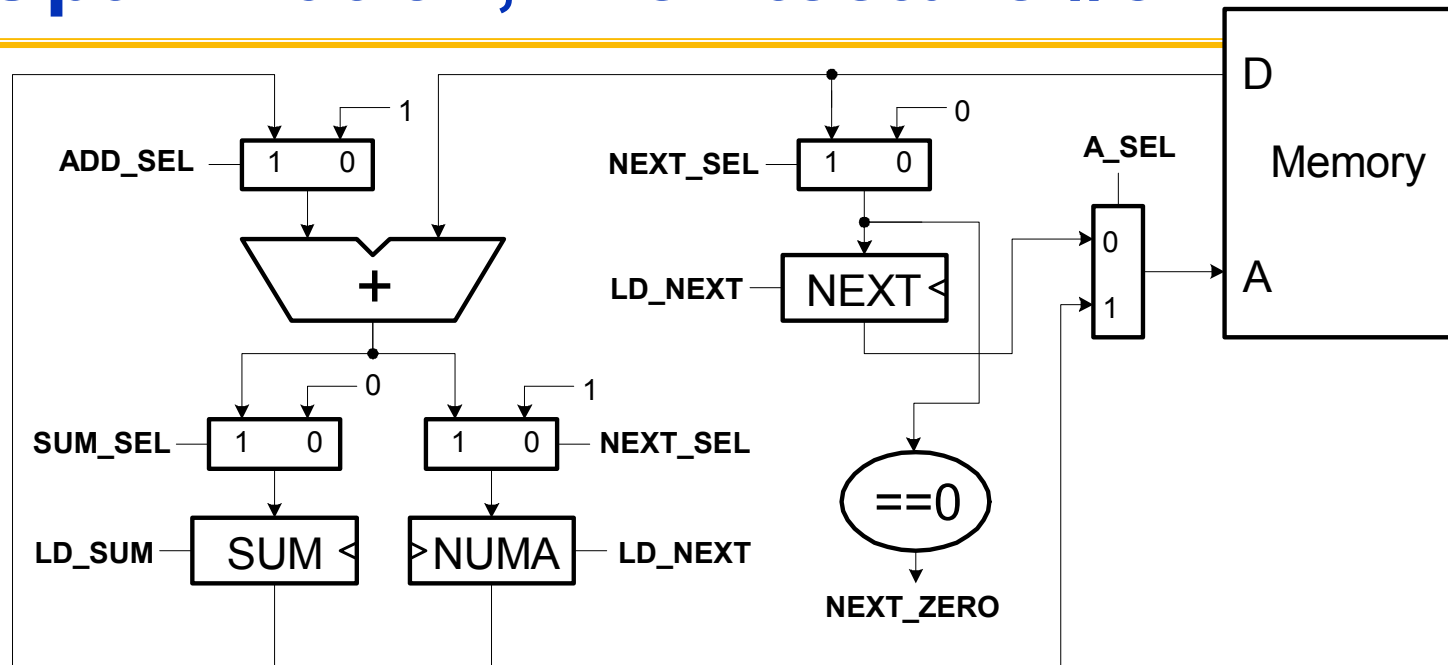

- **Incremental cost:**
 - Addition of another mux and control. Removal of an 8-bit adder.
- **Performance:**
 - mux adds 1ns to cycle time. 24ns, 41.67MHz.
- **Is the cost savings worth the performance degradation?**



Design Complexity & Productivity Gap

- Design gap is accelerating with advances in processing technology.
- RTL Designers must identify downstream problems — timing, signal integrity, reliability, and others — prior to synthesis and be able to implement design fixes where they will have a more significant impact on chip performance.
- The key to a successful design is ***design closure***. The various performance specifications comprising timing, power, and reliability, along with chip cost, are all closely coupled.



Design Gap

- **Keeping up with Moore's Law requires the implementation of disruptive design technology every few years.**
- **A common theme of advancing design technology is the continuing move to higher design abstraction levels.**