

EECS150 - Digital Design

Lecture 15 –SIFT2 + FSM

Oct. 15, 2013

Prof. Ronald Fearing

Electrical Engineering and Computer
Sciences

University of California, Berkeley

(slides courtesy of Prof. John Wawrzynek)

<http://www-inst.eecs.berkeley.edu/~cs150>

Fall 2013

EECS150 - Lec15-sift2

Page

1

Recap and Outline


- Ready/Valid Handshaking
- async FIFO
- SIFT Algorithm, part 1

Outline for Today

- SIFT Algorithm, conclusion
- FSM implementation
- FSM Moore vs Mealy
- FSM State Assignment

2

Feature Tracking Project

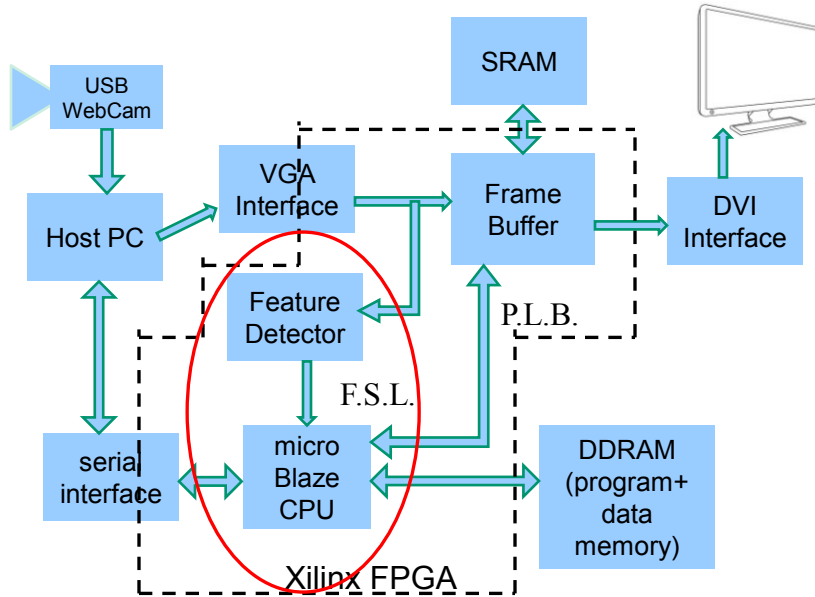

EECS150 - Lec12-video

3

review from lec14

The SIFT (Scale Invariant Feature Transform) Detector and Descriptor

- developed by David Lowe
- University of British Columbia
- US patent

Lowe, David G. (2004). Distinctive image features from scale-invariant key points. *International Journal of Computer Vision* 60(2): 91-110.

courses.cs.washington.edu/courses/cse576/11sp/.../SIFT_white2011.ppt

http://demo.ipol.im/demo/82/wait?key=ECE94E2AEE6F0D1CCD5265DB4E69D224&show=antmy_detect&action=cust_sift_matching


Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

4

review from lec14

Idea of SIFT

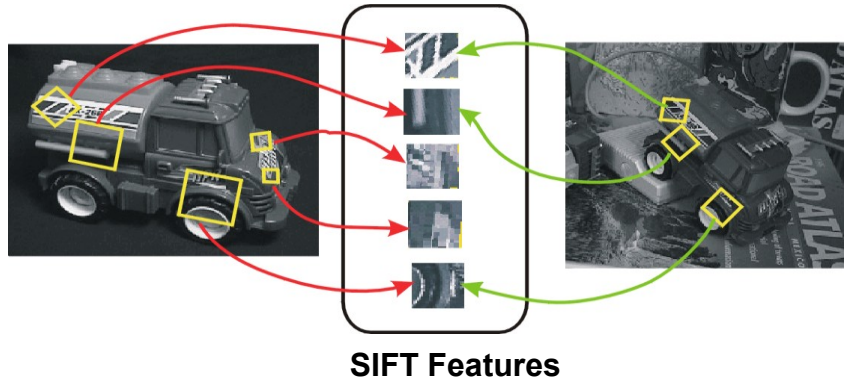- Image content is transformed into local feature coordinates that are invariant to translation, rotation, scale, and other imaging parameters




Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

5

review from lec14

Lowe's Pyramid Scheme

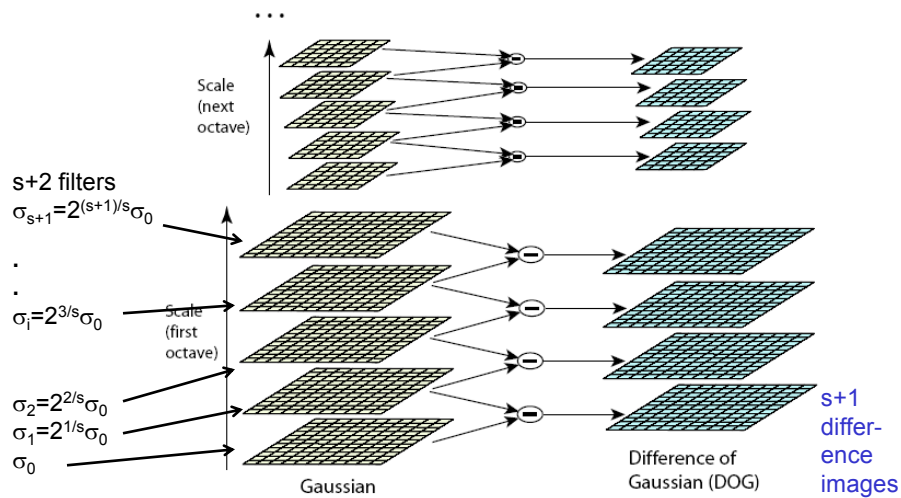

$s+3$ images including original Lowe, Fig.1

The parameter s determines the number of images per octave.


Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

6

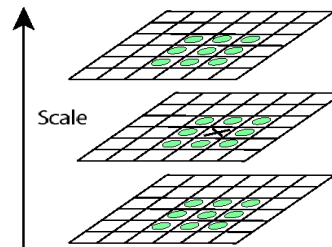2. Key point localization

- Detect maxima and minima of difference-of-Gaussian in scale space
- Each point is compared to its 8 neighbors in the current image and 9 neighbors each in the scales above and below
- total comparisons?

s+2 difference images.
top and bottom ignored.
s planes searched.



For each max or min found,
output is the **location** and
the **scale**.

- Lowe, Fig.2

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

9

Keypoint Detection

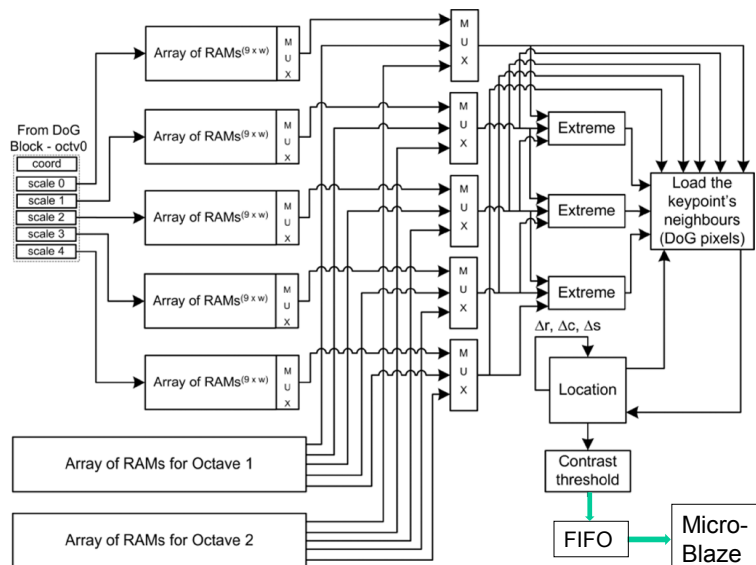


Fig. 8 : "A Parallel Hardware Architecture for Scale and Rotation Invariant Feature Detection," Bonato, et al., IEEE Trans. on Circuits and Systems for Video Tech., vol. 18, no. 12, Dec. 2008.

10

Overall Procedure at a High Level

1. Scale-space extrema detection

Search over multiple scales and image locations.

HW



2. Keypoint localization

Fit a model to determine location and scale.

Select keypoints based on a measure of stability.

SW



3. Orientation assignment

Compute best orientation(s) for each keypoint region.


4. Keypoint description

Use local image gradients at selected scale and rotation to describe each keypoint region.

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

11

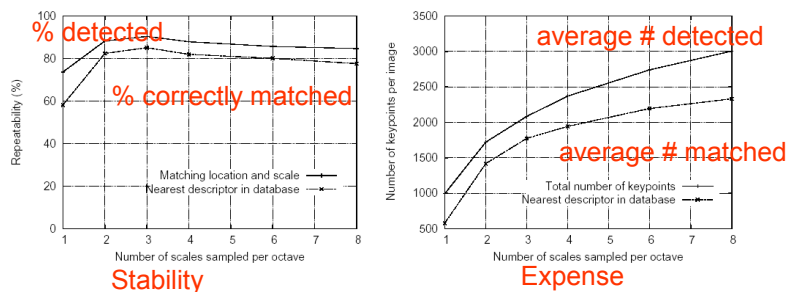Scale-space extrema detection: experimental results over 32 images that were synthetically transformed and noise added.



- Sampling in scale for efficiency
 - How many scales should be used per octave? $S=?$

- More scales evaluated, more keypoints found
- $S < 3$, stable keypoints increased too
- $S > 3$, stable keypoints decreased
- $S = 3$, maximum stable keypoints found

Lowe, Fig.3

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

12

Keypoint localization

- Once a keypoint candidate is found, perform a detailed fit to nearby data to determine
 - location, scale, and ratio of principal curvatures
- In initial work keypoints were found at location and scale of a central sample point.
- In newer work, they fit a 3D quadratic function to improve interpolation accuracy.
- The Hessian matrix was used to eliminate edge responses.


Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

13

Corners as distinctive interest points

$$M = X \begin{bmatrix} \lambda_1 & 0 \\ 0 & \lambda_2 \end{bmatrix} X^T$$

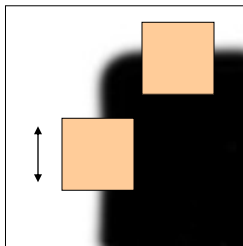
The *eigenvalues* of M reveal the amount of intensity change in the two principal orthogonal gradient directions in the window.



“edge”:

$$\begin{aligned} \lambda_1 &\gg \lambda_2 \\ \lambda_2 &\gg \lambda_1 \end{aligned}$$


One way to score the cornerness:

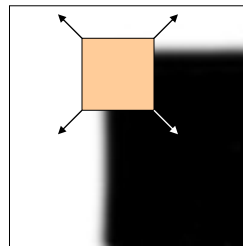

“corner”:

$$\begin{aligned} \lambda_1 \text{ and } \lambda_2 &\text{ are large,} \\ \lambda_1 &\sim \lambda_2; \end{aligned}$$
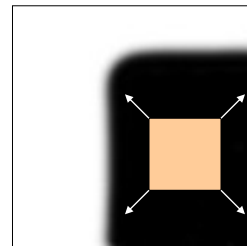
$$f = \frac{\lambda_1 \lambda_2}{\lambda_1 + \lambda_2}$$




“flat” region

$$\lambda_1 \text{ and } \lambda_2 \text{ are small;}$$

see Lowe '04 paper for details

slide credit:
CS 143, Brown Univ
James Hays, 2011

3. Orientation assignment

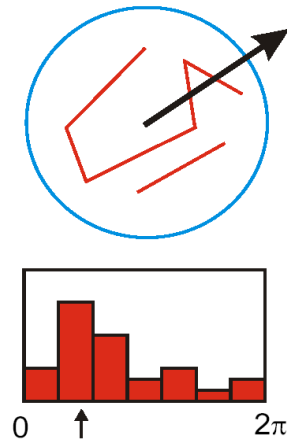


- Create histogram of local gradient directions at selected scale
- Assign canonical orientation at peak of smoothed histogram
- Each key specifies stable 2D coordinates (x, y, scale, orientation)

If 2 major orientations, use both.

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

15

Keypoint localization with orientation

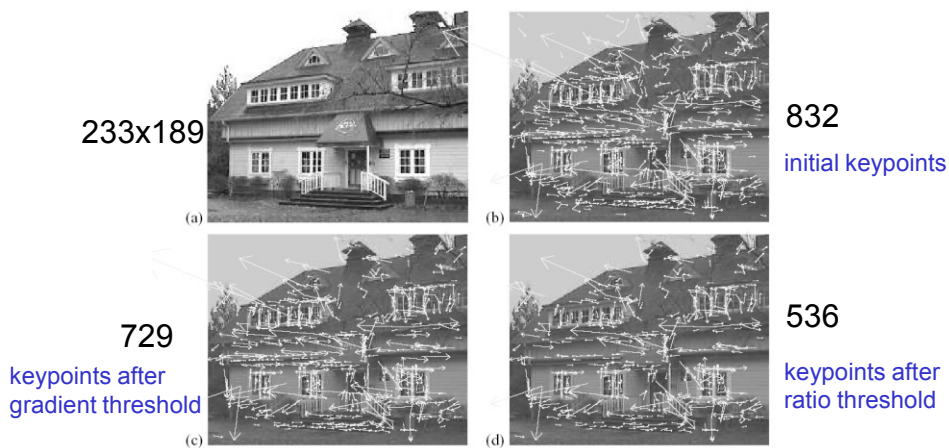

Lowe, Fig.5

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

16

4. Keypoint Descriptors

- At this point, each keypoint has
 - location
 - scale
 - orientation
- Next is to compute a descriptor for the local image region about each keypoint that is
 - highly distinctive
 - as invariant as possible to variations such as changes in viewpoint and illumination
- Normalization
 - Rotate the window to standard orientation
 - Scale the window size based on the scale at which the point was found.

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

17

Lowe's Keypoint Descriptor (shown with 2 X 2 descriptors over 8 X 8)

gradient magnitude and
orientation at each point
weighted by a Gaussian


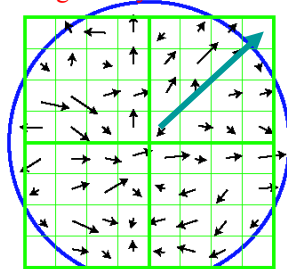


Image gradients

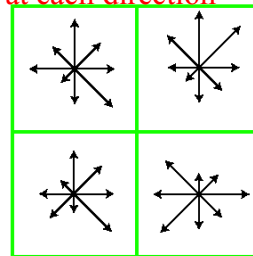orientation histograms:
sum of gradient magnitude
at each direction



Keypoint descriptor

In experiments, 4x4 arrays of 8 bin histogram is used,
a total of 128 features for one keypoint


WB

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

18

Biological Motivation

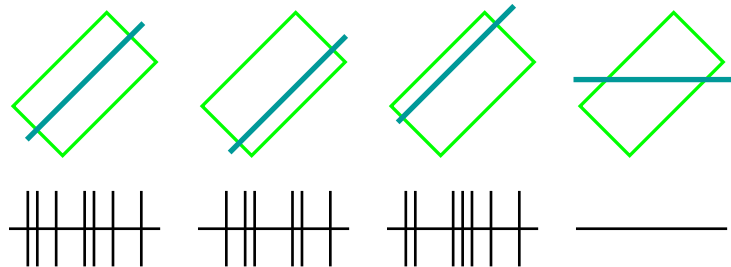- Mimic complex cells in primary visual cortex
- Hubel & Wiesel found that cells are sensitive to *orientation* of edges, but insensitive to their *position*
- This justifies spatial pooling of edge responses



[“Eye, Brain and Vision” – Hubel and Wiesel 1988]

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

19

Lowe's Keypoint Descriptor

- use the **normalized** region about the keypoint
- compute gradient magnitude and orientation at each point in the region
- **weight them by a Gaussian** window overlaid on the circle
- create an **orientation histogram** over the 4 X 4 subregions of the window
- 4 X 4 descriptors over 16 X 16 sample array were used in practice. 4 X 4 times 8 directions gives a vector of **128 values**.

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

20

Automatic mosaicing



<http://www.cs.ubc.ca/~mbrown/autostitch/autostitch.html>


Uses for SIFT

- Feature points are used also for:
 - Image alignment (homography, fundamental matrix)
 - 3D reconstruction (e.g. Photo Tourism)
 - Motion tracking
 - Object recognition
 - Indexing and database retrieval
 - Robot navigation
 - ... many others

[Photo Tourism: Snavely et al. SIGGRAPH 2006]

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington

FSM Implementation

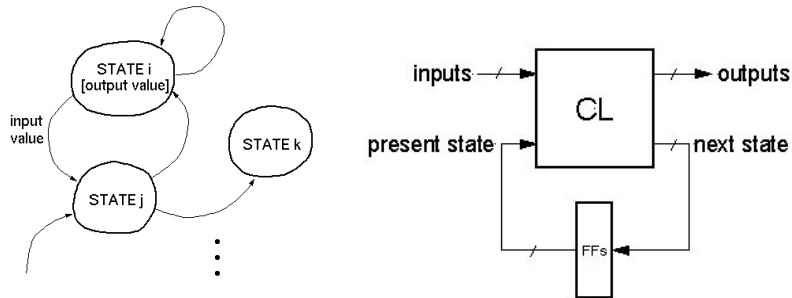

- Flip-flops form *state register*
- number of states $\leq 2^{\text{number of flip-flops}}$
- CL (combinational logic) calculates next state and output
- **Remember: The FSM follows exactly one edge per cycle.**

FSM Formal Design Process


Review of Design Steps:

1. Specify **circuit function** (English)
 - 1.1 choose Moore or Mealy
2. Draw **state transition diagram**
3. Write down **symbolic state transition table** (*case stmt*)
4. **Assign states**
5. Derive logic equations [output decoder, next state decoder]
6. Derive **circuit diagram**
 - Register to hold state
 - Combinational Logic for Next State and Outputs

Verilog



State Encoding

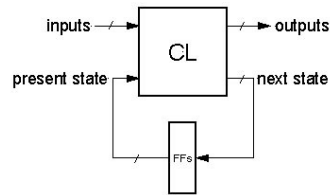

- In general:
 $\# \text{ of possible FSM state} = 2^{\# \text{ of Flip-flops}}$
 Example:
 state1 = 01, state2 = 11, state3 = 10, state4 = 00
- However, often more than $\log_2(\# \text{ of states})$ FFs are used, to simplify logic at the cost of more FFs.
- Extreme example is one-hot state encoding.

Fall 2013

EECS150 - Lec15-SIFT+FSM


Page

25

State Encoding

- **One-hot encoding of states.**
- One FF per state.

Ex: 3 States

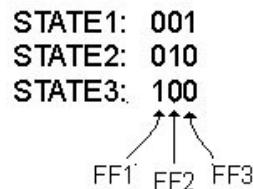

- Why one-hot encoding?
 - Simple design procedure.
 - Circuit matches state transition diagram (example next page).
 - Often can lead to simpler and faster "next state" and output logic.
- Why not do this?
 - Can be costly in terms of Flip-flops for FSMs with large number of states.
 - FPGA costs? Hint NSD...
- FPGAs are "Flip-flop rich", therefore one-hot state machine encoding is often a good approach.


WB

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page 26

One-hot encoded combination lock

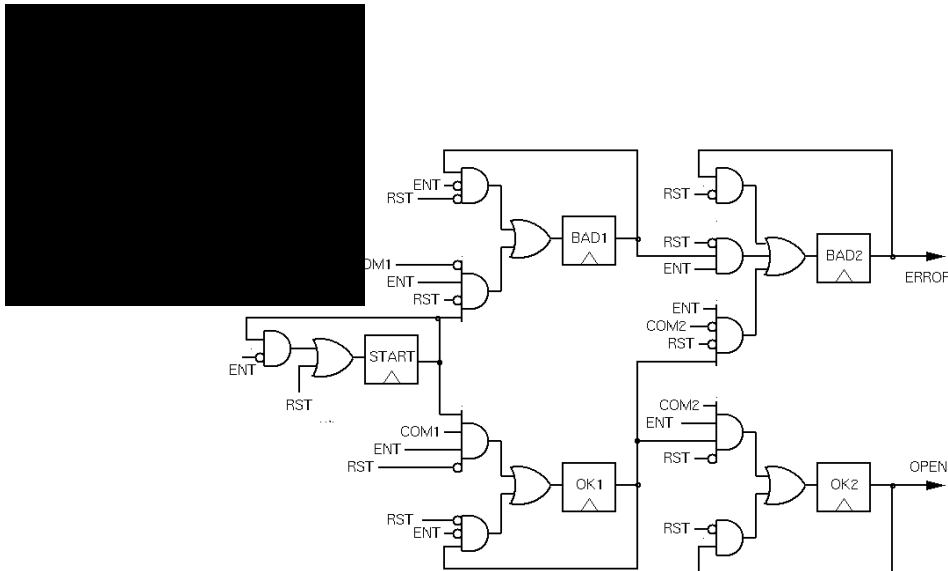


Fall 2013


27

FSM Implementation Notes

- General FSM form:

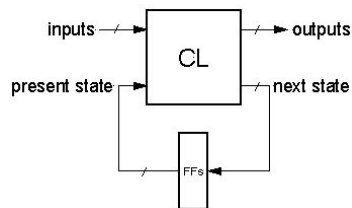

- All examples so far generate output based only on the present state:
- Commonly named **Moore Machine**
(If output functions include both present state and input then called a *Mealy Machine*)

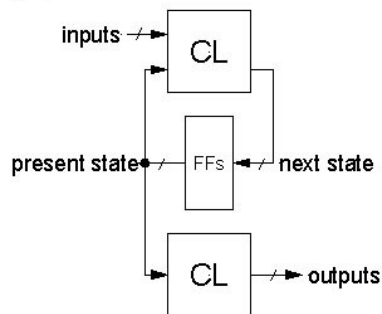

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page


28

Finite State Machines

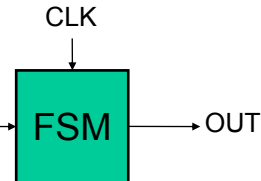- Example: Edge Detector**


Bits are received one at a time (one per cycle),
such as: 000111010 $\xrightarrow{\text{time}}$

Design a circuit that asserts^N its output for one cycle when the input bit stream changes from 0 to 1.



Try two different solutions.

State Transition Diagram Solution A

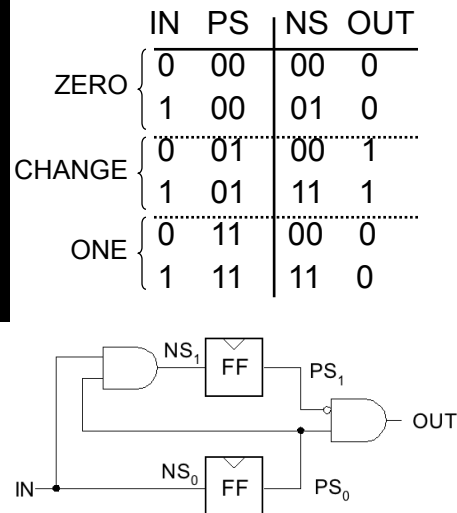

Solution B


Output depends not only on PS but also on input, IN



ZERO=0,
ONE=1

IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0

NS = IN, OUT = IN PS'

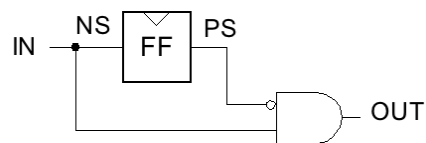

Notation:

Input condition/output


What's the *intuition* about this solution?

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page 31

Edge detector timing diagrams

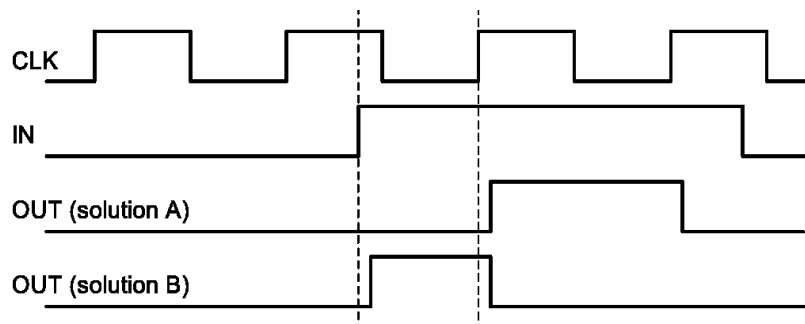

- Solution A: output follows the clock
- Solution B: output changes with input rising edge and is asynchronous wrt the clock.

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page


32

FSM Comparison

Solution A

Moore Machine

- output function only of PS
- maybe more states (why?)
- synchronous outputs
 - no glitches
 - one cycle "delay"
 - full cycle of stable output

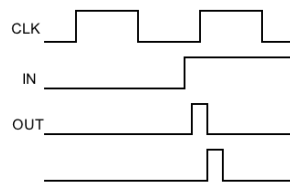


Fall 2013

EECS150 - Lec15-SIFT+FSM

Solution B

Mealy Machine

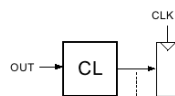- output function of both PS & input
- maybe fewer states
- asynchronous outputs
 - if input glitches, so does output
 - output immediately available
 - output may not be stable long enough to be useful (below):





If output of Mealy FSM goes through combinational logic before being registered, the CL might delay the signal and it could be missed by the clock edge.

Page



33

FSM Recap

Moore Machine

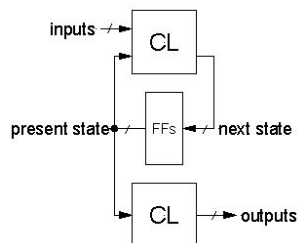 

Mealy Machine

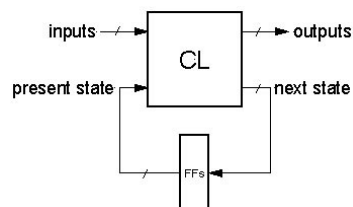 

Both machine types allow one-hot implementations.

Fall 2013


EECS150 - Lec15-SIFT+FSM

Page

34

Final Notes on Moore versus Mealy

1. A given state machine could have both Moore and Mealy style outputs. Nothing wrong with this, but you need to be aware of the timing differences between the two types.
2. The output timing behavior of the Moore machine can be achieved in a Mealy machine by “registering” the Mealy output values:

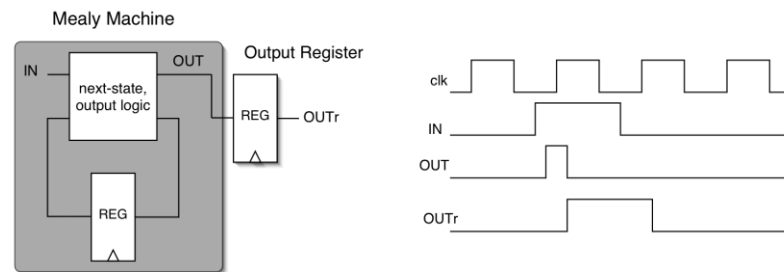

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page 35

35

General FSM Design Process with Verilog Implementation

Design Steps:

1. Specify **circuit function** (English)
 2. Draw **state transition diagram**
 3. Write down **symbolic state transition table**
 4. Assign encodings (bit patterns) to symbolic states
 5. Code as Verilog behavioral description
- ✓ Use parameters to represent encoded states.
 - ✓ Use separate always blocks for register assignment and CL logic block.
 - ✓ Use case for CL block. Within each case section assign all outputs and next state value based on inputs. *Note: For Moore style machine make outputs dependent only on state not dependent on inputs.*


Fall 2013

EECS150 - Lec15-SIFT+FSM

Page 36

FSMs in Verilog

Mealy Machine

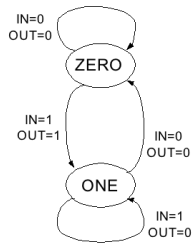


```

always @(posedge clk)
  if (rst) ps <= ZERO;
  else ps <= ns;
  ^ (ps in)
  (ps)
  RO: if (in) begin
    out = 1'b1;
    ns = ONE;
  end
  else begin
    out = 1'b0;
    ns = ZERO;
  end
  end
  E: if (in) begin
    out = 1'b0;
    ns = ONE;
  end
  else begin
    out = 1'b0;
    ns = ZERO;
  end
  end
  default: begin
    out = 1'bx;
    ns = default;
  end
  end

```

Moore Machine

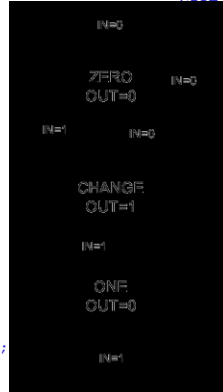

```

always @(posedge clk)
  if (rst) ps <= ZERO;
  else ps <= ns;
  always @(ps in)
    case (ps)
      0: begin
        out = 1'b0;
        if (in) ns = CHANGE;
        else ns = ZERO;
      end
      1: begin
        out = 1'b1;
        if (in) ns = ONE;
        else ns = ZERO;
      end
      2: begin
        out = 1'b0;
        if (in) ns = ONE;
        else ns = ZERO;
      end
      default: begin
        out = 1'bx;
        ns = default;
      end
    end

```

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page

37

Conclusions

- SIFT details
- State assignment
- Moore Machine
- Mealy Machine

38

Eliminating the Edge Response

see Lowe '04 paper for details if interested

- Reject flats:
 - $|D(\hat{x})| < 0.03$
- Reject edges:

$$\mathbf{H} = \begin{bmatrix} D_{xx} & D_{xy} \\ D_{xy} & D_{yy} \end{bmatrix}$$

Let α be the eigenvalue with larger magnitude and β the smaller.

$$\text{Tr}(\mathbf{H}) = D_{xx} + D_{yy} = \alpha + \beta,$$

$$\text{Det}(\mathbf{H}) = D_{xx}D_{yy} - (D_{xy})^2 = \alpha\beta.$$

Let $r = \alpha/\beta$.
So $\alpha = r\beta$

$$\frac{\text{Tr}(\mathbf{H})^2}{\text{Det}(\mathbf{H})} = \frac{(\alpha + \beta)^2}{\alpha\beta} = \frac{(r\beta + \beta)^2}{r\beta^2} = \frac{(r + 1)^2}{r},$$

$$- r < 10$$


$(r+1)^2/r$ is at a min when the 2 eigenvalues are equal.

Slides courtesy of Prof. Linda Shapiro, Dept. of CSE, U. Washington 39

Parity Checker Example


A string of bits has "even parity" if the number of 1's in the string is even.

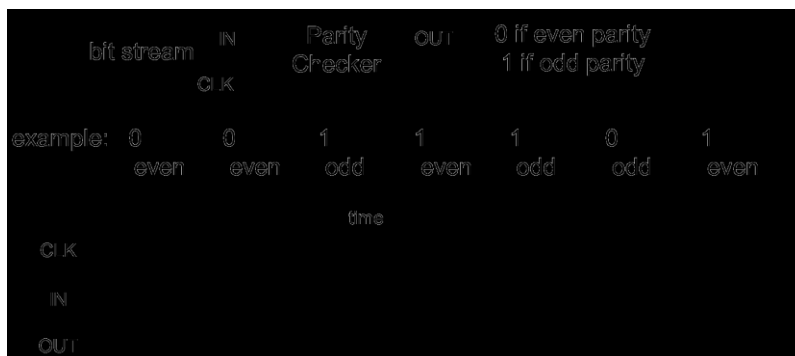- Design a circuit that accepts a bit-serial stream of bits and outputs a 0 if the parity thus far is even and outputs a 1 if odd:




Next we take this example through the "formal design process". But first, can you guess a circuit that performs this function?

Formal Design Process

 

“State Transition Diagram”

- circuit is in one of two “states”.
- transition on each cycle with each new input, over exactly one arc (edge).
- Output depends on which state the circuit is in.

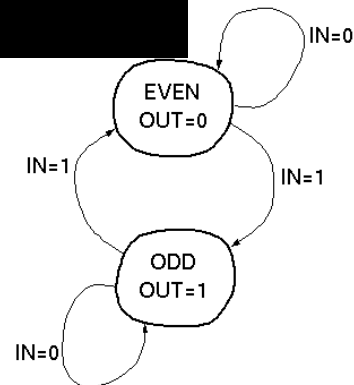

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page

41

Formal Design Process


State Transition Table:

present state	OUT	IN	next state
EVEN	0	0	EVEN
EVEN	0	1	ODD
ODD	1	0	ODD
ODD	1	1	EVEN

Invent a code to represent states:

Let 0 = EVEN state, 1 = ODD state

present state (ps)	OUT	IN	next state (ns)
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	0

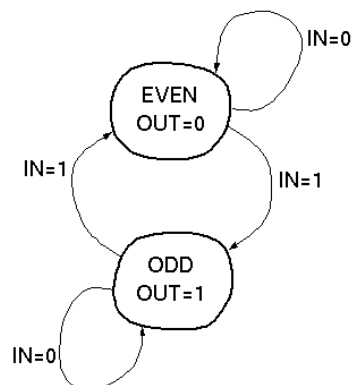

Derive logic equations from table (how?):

$OUT = PS$

$NS = PS \text{ xor } IN$

Fall 2013

EECS150 - Lec15-SIFT+FSM

Page

42

Formal Design Process

Logic equations from table:

$OUT = PS$

$NS = PS \text{ xor } IN$

- Circuit Diagram:

- XOR gate for NS calculation
- DFF to hold present state
- no logic needed for output in this example.

