

# EECS150 - Digital Design


## Lecture 7 - High-Level Design (Part 1)

Feb 12, 2013  
John Wawrzynek


### Introduction

- High-level Design Specifies:
  - How data is moved around and operated on.
  - The architecture (sometimes called *micro-architecture*):
    - The organization of state elements and combinational logic blocks
    - Functional specification of combinational logic blocks
- Optimization
  - Deals with the task of modifying an architecture and data movement procedure to meet some particular design requirement:
    - **performance, cost, power, or some combination.**
- Most designers spend most of their time on high-level organization and optimization
  - modern CAD tools help fill in the low-level details and optimization
    - gate-level minimization, state-assignment, etc.
  - A great deal of the leverage on effecting performance, cost, and power comes at the high-level.


# One Standard High-level Template

 

- Controller
  - accepts external and control input, generates control and external output and sequences the movement of data in the datapath. (puppeteer)
- Standard model for CPUs, micro-controllers, many other digital sub-systems.
- Usually *not* nested.
- Sometimes cascaded:
- Datapath
  - is responsible for data manipulation. Usually includes a limited amount of storage. (puppet)
- Memory
  - optional block used for long term storage of data structures.

 

# Register Transfer Language

 


- At the high-level we view these systems as a collection of state elements and CL blocks.
- “RTL” is a commonly used acronym for “Register Transfer Level” description.
- It follows from the fact that all synchronous digital system can be described as a set of state elements connected by combinational logic blocks.
- Though not strictly correct, some also use “RTL” to mean the Verilog or VHDL code that describes such systems.

# Register Transfer “Language” Descriptions

- We introduce a *language* for describing the behavior of systems at the register transfer level.
- Can view the operation of digital synchronous systems as a set of data transfers between registers with combinational logic operations happening during the transfer.
- We will avoid using “RTL” to mean “register transfer language.”
- RT Language comprises a set of *register transfers* with optional operators as part of the transfer.
- Example:
  - $\text{regA} \leftarrow \text{regB}$
  - $\text{regC} \leftarrow \text{regA} + \text{regB}$
  - if ( $\text{start} == 1$ )  $\text{regA} \leftarrow \text{regC}$
- My personal style:
  - use “;” to separate transfers that occur on separate cycles.
  - Use “,” to separate transfers that occur on the same cycle.
- Example (2 cycles):
  - $\text{regA} \leftarrow \text{regB}, \text{regB} \leftarrow 0;$
  - $\text{regC} \leftarrow \text{regA};$

## Example of Using RT Language

 

$\text{ACC} \leftarrow \text{ACC} + \text{R0}, \text{R1} \leftarrow \text{R0};$   
 $\text{ACC} \leftarrow \text{ACC} + \text{R1}, \text{R0} \leftarrow \text{R1};$   
 $\text{R0} \leftarrow \text{ACC};$

•  
•  
•

- In this case: RT Language description is used to sequence the operations on the datapath (dp).
- It becomes the high-level specification for the controller.
- Design of the FSM controller follows directly from the RT Language sequence. FSM controls movement of data by controlling the multiplexor control signals.

## Example of Using RT Language


- Sometimes RT Language is used as a starting point for designing *both* the datapath and the control:
- example:
  - regA ← IN;
  - regB ← IN;
  - regC ← regA + regB;
  - regB ← regC;
- From this we can deduce:
  - IN must fanout to both regA and regB
  - regA and regB must output to an adder
  - the adder must output to regC
  - regB must take its input from a mux that selects between IN and regC
- What does the datapath look like:
- The controller:

## List Processor Example


- RT Language gives us a framework for making high-level optimizations.
- General design procedure outline:
  1. Problem, Constraints, and Component Library Spec.
  2. "Algorithm" Selection
  3. Micro-architecture Specification
  4. Analysis of Cost, Performance, Power
  5. Optimizations, Variations
  6. Detailed Design
 
# 1. Problem Specification

- Design a circuit that forms the sum of all the 2's complement integers stored in a linked-list structure starting at memory address 0:




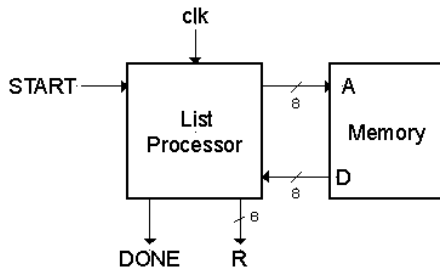- All integers and pointers are 8-bit. The link-list is stored in a memory block with an 8-bit address port and 8-bit data port, as shown below. The pointer from the last element in the list is 0. At least one node in list.



I/Os:

 - START resets to head of list and starts addition process.
- DONE signals completion
- R holds the final result



Note: We don't assume nodes are aligned on 2 Byte boundaries.

# 1. Other Specifications

- Design Constraints:
  - Usually the design specification puts a restriction on cost, performance, power or all. We will leave this unspecified for now and return to it later.
- Component Library:


component	delay
simple logic gates	0.5ns
n-bit register	clk-to-Q=0.5ns setup=0.5ns
n-bit 2-1 multiplexor	1ns
n-bit adder	$(2 \log(n) + 2)ns$
memory	10ns read (asynchronous read)
zero compare	$0.5 \log(n)$

(single ported memory)

Are these reasonable?

## Review of Register with “Clock Enable”

- Register with Clock Enable:

 

- Allows register to be either be loaded on selected clock posedge or to retain its previous value.
- Assume both data and CE require setup time = 0.5ns.
- Assume no reset input.

## 2. Algorithm Specification


- In this case the memory only allows one access per cycle, so the algorithm is limited to sequential execution. If in another case more input data is available at once, then a more parallel solution may be possible.
- *Assume datapath state registers NEXT and SUM.*
  - NEXT holds a pointer to the node in memory.
  - SUM holds the result of adding the node values to this point.

```
If (START==1) NEXT←0, SUM←0, DONE←0;
repeat {
    SUM←SUM + Memory[NEXT+1];
    NEXT←Memory[NEXT];
} until (NEXT==0);
R←SUM, DONE←1;
```

This RT Language “code” becomes the basis for DP and controller.
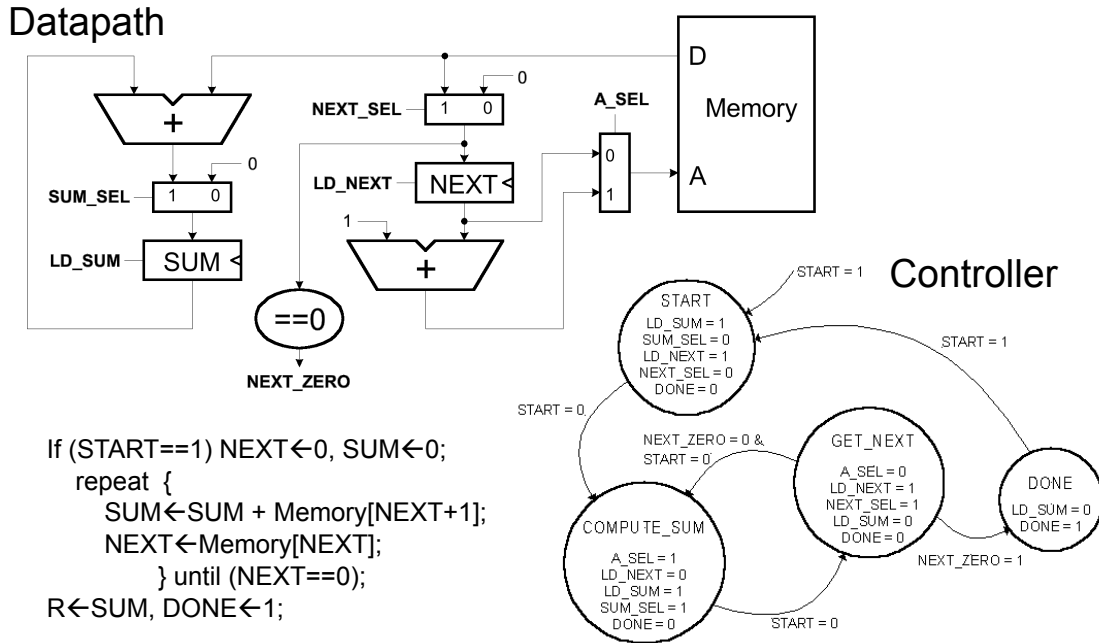
# 3. Architecture #1


Direct implementation of RTL description:



# 4. Analysis of Cost, Performance, and Power

- Skip Power for now.
- Cost:
  - How do we measure it? # of transistors? # of gates? # of CLBs?
  - Depends on implementation technology. Often we are just interested in comparing the *relative* cost of two competing implementations. (Save this for later)
- Performance:
  - 2 clock cycles per number added.
  - What is the minimum clock period?
  - The controller might be on the critical path. Therefore we need to know the implementation, and controller input and output delay.


# Possible Controller Implementation

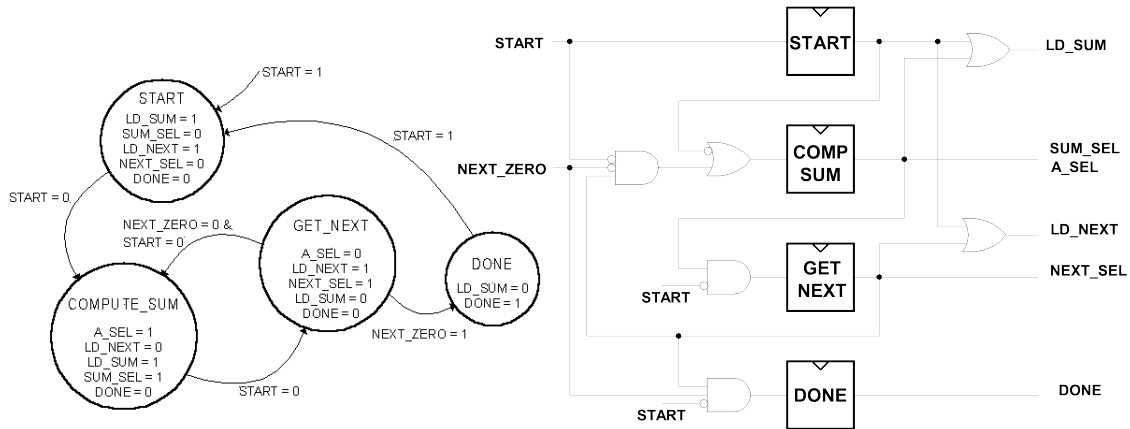


- Based on this, what is the controller input and output delay?

## 4. Analysis of Performance

COMPUTE\_SUM state

 

GET\_NEXT state

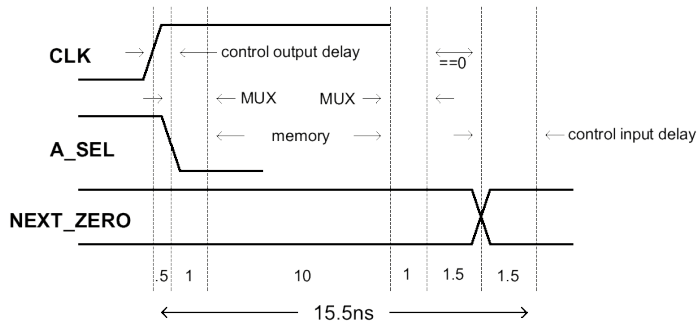

Other paths exist for each cycle in the loop. These are the worst case.



## 4. Analysis of Performance

- Detailed timing:  
clock period (T) = max (clock period for each state)  
T > 31ns, F < 32 MHz
- Observation:  
COMPUTE\_SUM state does most of the work. Most of the components are inactive in GET\_NEXT state.  
GET\_NEXT does: Memory access + ...  
COMPUTE\_SUM does: 8-bit add, memory access, 15-bit add + ...
- Conclusion:  
**Move one of the adds to GET\_NEXT.**


## 5. Optimization

- *Add new register named NUMA, for address of number to add.*
- Update code to reflect our change (note still 2 cycles per iteration):

```
If (START==1) NEXT←0, SUM←0, NUMA←1;
repeat {
    SUM←SUM + Memory[NUMA];
    NUMA←Memory[NEXT] + 1,
    NEXT←Memory[NEXT];
} until (NEXT==0);
R←SUM, DONE←1;
```

# 5. Optimization

- Architecture #2:

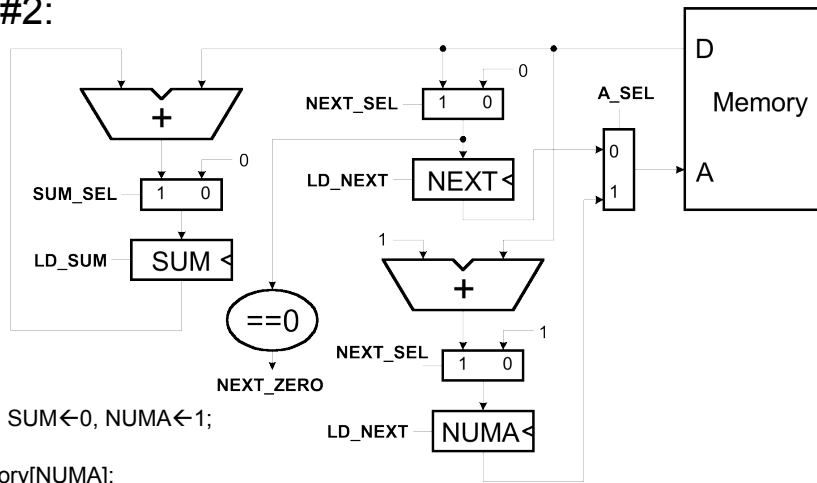


```

If (START==1) NEXT<0, SUM<0, NUMA<1;
repeat {
    SUM<SUM + Memory[NUMA];
    NUMA<Memory[NEXT] + 1, NEXT<Memory[NEXT];
} until (NEXT==0);
R<SUM, DONE<1;
    
```

- Incremental cost: addition of another register and mux.

## 5. Optimization, Architecture #2

COMPUTE\_SUM state

 


- New timing: Clock Period (T) = max (clock period for each state)

$$T > 23\text{ns}, F < 43\text{Mhz}$$


- Is this worth the extra cost?
- Can we lower the cost?

GET\_NEXT state

 

- Notice that the circuit now only performs one add on every cycle. Why not share the adder for both cycles?

## 5. Optimization, Architecture #3

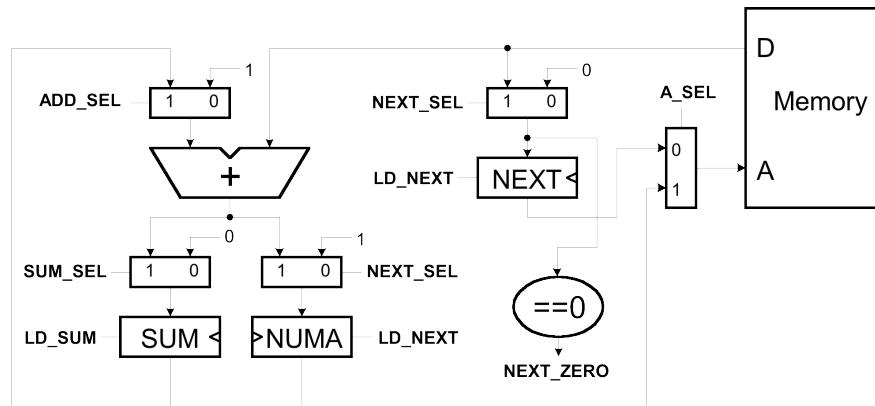

- Incremental cost:
  - Addition of another mux and control (**ADD\_SEL**). Removal of an 8-bit adder.
- Performance:
  - No change.
- Change is definitely worth it.

## Resource Utilization Charts

- One way to visualize these (and other possible) optimizations is through the use of a *resource utilization charts*.
- These are used in high-level design to help schedule operations on shared resources.
- Resources are listed on the y-axis. Time (in cycles) on the x-axis.
- Example:

<b>memory</b>	fetch A1		fetch A2				
<b>bus</b>		fetch A1		fetch A2			
<b>register-file</b>		read B1		read B2			
<b>ALU</b>			A1+B1		A2+B2		
<i>cycle</i>	1	2	3	4	5	6	7

- Our list processor has two shared resources: memory and adder

## List Example Resource Scheduling

- Unoptimized solution: 1.  $SUM \leftarrow SUM + Memory[NEXT+1]$ ; 2.  $NEXT \leftarrow Memory[NEXT]$ ;

<b>memory</b>	fetch x	fetch next	fetch x
<b>adder1</b>	next+1		next+1
<b>adder2</b>	sum		sum
	1	2	1 2

- Optimized solution: 1.  $SUM \leftarrow SUM + Memory[NUMA]$ ;  
2.  $NEXT \leftarrow Memory[NEXT]$ ,  $NUMA \leftarrow Memory[NEXT]+1$ ;

<b>memory</b>	fetch x	fetch next	fetch x	fetch next
<b>adder</b>	sum	numa	sum	numa

- How about the other combination: [add x register](#)

<b>memory</b>	fetch x	fetch next	fetch x	fetch next
<b>adder</b>	numa	sum	numa	sum

1.  $X \leftarrow Memory[NUMA]$ ,  $NUMA \leftarrow NEXT+1$ ;
2.  $NEXT \leftarrow Memory[NEXT]$ ,  $SUM \leftarrow SUM+X$ ;

- Does this work? If so, a very short clock period. Each cycle could have *independent* fetch and add.  $T = \max(T_{mem}, T_{add})$  instead of  $T_{mem} + T_{add}$ .

## List Example Resource Scheduling

- Schedule one loop iteration followed by the next:

Memory	next <sub>1</sub>		x <sub>1</sub>		next <sub>2</sub>		x <sub>2</sub>	
adder		numa <sub>1</sub>		sum <sub>1</sub>		numa <sub>2</sub>		sum <sub>2</sub>

- How can we overlap iterations? next<sub>2</sub> depends on next<sub>1</sub>.

– “slide” second iteration into first (4 cycles per result):

Memory	next <sub>1</sub>		x <sub>1</sub>	next <sub>2</sub>		x <sub>2</sub>		
adder		numa <sub>1</sub>		sum <sub>1</sub>	numa <sub>2</sub>		sum <sub>2</sub>	

– or further:

Memory	next <sub>1</sub>	next <sub>2</sub>	x <sub>1</sub>	x <sub>2</sub>	next <sub>3</sub>	next <sub>4</sub>	x <sub>3</sub>	x <sub>4</sub>	
adder		numa <sub>1</sub>	numa <sub>2</sub>	sum <sub>1</sub>	sum <sub>2</sub>	numa <sub>3</sub>	numa <sub>4</sub>	sum <sub>3</sub>	sum <sub>4</sub>

The repeating pattern is 4 cycles. Not exactly the pattern what we were looking for. But does it work correctly?

# List Example Resource Scheduling

- In this case, first spread out, then pack.

Memory	next <sub>1</sub>			x <sub>1</sub>		
adder		numa <sub>1</sub>			sum <sub>1</sub>	


Memory	next <sub>1</sub>		next <sub>2</sub>	x <sub>1</sub>	next <sub>3</sub>	x <sub>2</sub>	next <sub>4</sub>	x <sub>3</sub>	
adder		numa <sub>1</sub>		numa <sub>2</sub>	sum <sub>1</sub>	numa <sub>3</sub>	sum <sub>2</sub>	numa <sub>4</sub>	sum <sub>3</sub>

- $X \leftarrow \text{Memory}[\text{NUMA}], \text{ NUMA} \leftarrow \text{NEXT} + 1;$
- $\text{NEXT} \leftarrow \text{Memory}[\text{NEXT}], \text{ SUM} \leftarrow \text{SUM} + X;$

- Three different loop iterations active at once.
- Short cycle time (no dependencies within a cycle)
- full utilization (only 2 cycles per result)
- Initialization:  $x=0, \text{ numa}=1, \text{ sum}=0, \text{ next}=\text{memory}[0]$
- Extra control states (out of the loop)
  - one to initialize next, clear sum, set numa
  - one to finish off. 2 cycles after  $\text{next}==0$ .

## 5. Optimization, Architecture #4

- Datapath:

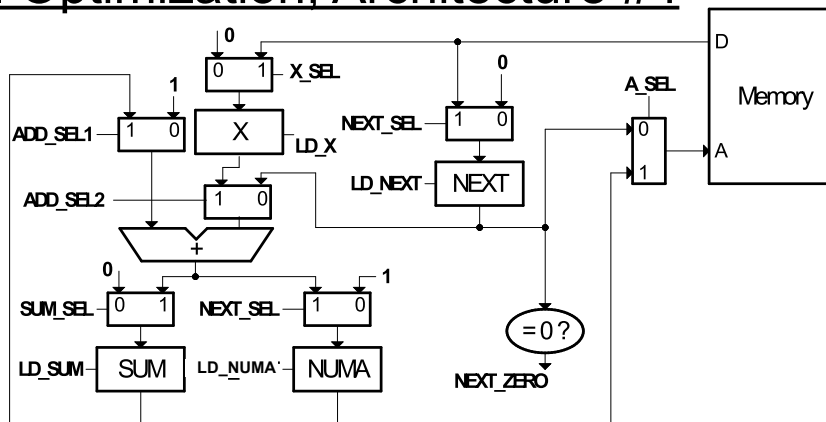

- Incremental cost:
  - Addition of another register & mux, adder mux, and control.
- Performance: find max time of the four actions
  - $X \leftarrow \text{Memory}[\text{NUMA}], \text{ NUMA} \leftarrow \text{NEXT} + 1;$   $0.5 + 1 + 10 + 1 + 0.5 = 13\text{ns}$   
 same for all  $\Rightarrow T > 13\text{ns}, F < 77\text{MHz}$
  - $\text{NEXT} \leftarrow \text{Memory}[\text{NEXT}], \text{ SUM} \leftarrow \text{SUM} + X;$

## Other Optimizations

- Node alignment restriction:
  - If the application of the list processor allows us to restrict the placement of nodes in memory so that they are aligned on even multiples of 2 bytes.
    - NUMA addition can be eliminated.
    - Controller supplies “0” for low-bit of memory address for NEXT, and “1” for X.
  - Furthermore, if we could use a memory with a 16-bit wide output, then could fetch entire node in one cycle:

$\{NEXT, X\} \leftarrow \text{Memory}[NEXT], \text{SUM} \leftarrow \text{SUM} + X;$

$\Rightarrow$  execution time cut in half (half as many cycles)

## List Processor Conclusions

- Through careful optimization:
  - clock frequency increased from 32MHz to 77MHz
  - little cost increase.
- “Scheduling” was used to overlap and to maximize use of resources.
- Questions:
  - Consider the design process we went through:
    - Could a computer program go from RTL description to circuits automatically?
    - Could a computer program derive the optimizations that we did?
    - It is the goal of “High-Level Synthesis” to do similar transformations and automatic mappings. “C-to-gates” compilers are an example.