

# **EECS150 - Digital Design**

## **Lecture 15 - CMOS Implementation Technologies**


Mar 12, 2013  
John Wawrzynek

## **Overview of Physical Implementations**

*The stuff out of which we make systems.*

- Integrated Circuits (ICs)
  - Combinational logic circuits, memory elements, analog interfaces.
- Printed Circuits (PC) boards
  - substrate for ICs and interconnection, distribution of CLK, Vdd, and GND signals, heat dissipation.
- Power Supplies
  - Converts line AC voltage to regulated DC low voltage levels.
- Chassis (rack, card case, ...)
  - holds boards, power supply, fans, provides physical interface to user or other systems.
- Connectors and Cables.

# Printed Circuit Boards

 


- fiberglass or ceramic
- 1-25 conductive layers
- ~1-20in on a side
- IC packages are soldered down.

## Multichip Modules (MCMs)


- Multiple chips directly connected to a substrate. (silicon, ceramic, plastic, fiberglass) without chip packages.

# Integrated Circuits

 

- Primarily Crystalline Silicon
- 1mm - 25mm on a side
- 100 - 1000M transistors
- (25 - 250M "logic gates")
- 3 - 10 conductive layers
- 2012 - feature size  $\sim 28\text{nm} = 0.028 \times 10^{-6} \text{m}$
- "CMOS" most common - complementary metal oxide semiconductor


## Chip in Package

 

- Package provides:
  - spreading of chip-level signal paths to board-level
  - heat dissipation.
- Ceramic or plastic with gold wires.
 
# Integrated Circuits

- Moore's Law has fueled innovation for the last 3 decades.



- “Number of transistors on a die doubles every 18 months.”
- What are the consequences of Moore's law?


## Chip-level Function Implementation Alternatives

- Full-custom:** All circuits/transistor layouts optimized for application.
  - Standard-cell:** Arrays of small function blocks (gates, FFs) automatically placed and routed.
  - Gate-array:** Partially prefabricated wafers customized with metal layers.
  - FPGA:** Prefabricated chips customized with switches and wires.
  - Microprocessor:** Instruction set interpreter customized through software.
  - Domain Specific Processor:** (DSP, NP, GPU).
- } **ASIC**

What are the important metrics of comparison?
 
# Why FPGAs?

A tradeoff exists between NRE\* cost and manufacturing costs:




The ASIC approach is only viable for products with very high volume (where NRE could be amortized), and which were not time to market (TTM) sensitive.

Cross-over point has moved to the right (favoring FPGA) implementation as ASIC NREs have increased.

## \*Non-recurring Engineering Costs
 
# CMOS Devices


- MOSFET (Metal Oxide Semiconductor Field Effect Transistor).




The gate acts like a capacitor. A high voltage on the gate attracts charge into the channel. If a voltage exists between the source and drain a current will flow. In its simplest approximation, the device acts like a switch.

# Transistor-level Logic Circuits

Inverter (NOT gate):

 

NAND gate:

 

Note:

- out = 0 iff a AND b = 1 therefore out = (ab)'

- pFET network and nFET networks are **duals** of one another.


How about AND gate?

# Transistor-level Logic Circuits

Simple rule for wiring up MOSFETs:

nFET is used only to pass logic zero.  
pFET is used only to pass logic one.


For example, consider the NAND gate:

 

Note: This rule is sometimes violated by expert designers under special conditions.

# Transistor-level Logic Circuits

NOR gate:

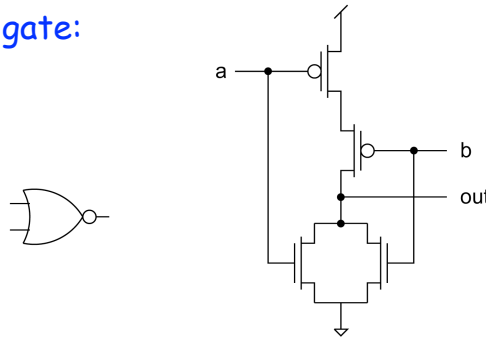


Note:

- $out = 0$  iff  $a$  OR  $b = 1$  therefore  $out = (a+b)'$
- Again pFET network and nFET networks are **duals** of one another.


Other more complex functions are possible. Ex:  $out = (a+bc)'$

## CMOS Logic Gates in General

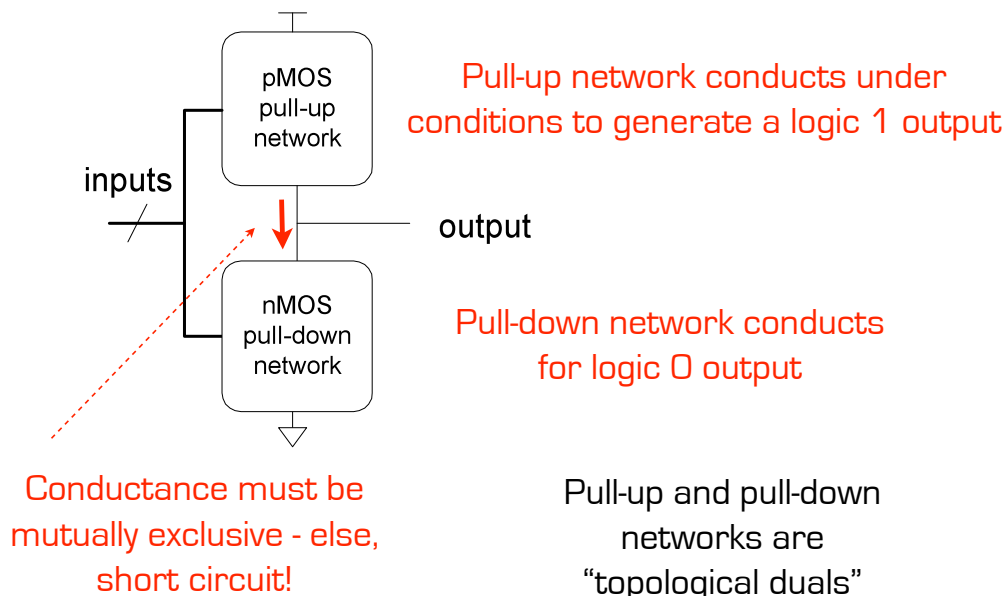
 
# Transmission Gate


- Transmission gates are the way to build "switches" in CMOS.
- In general, both transistor types are needed:
  - nFET to pass zeros.
  - pFET to pass ones.
- The transmission gate is bi-directional (unlike logic gates).





- Does not directly connect to Vdd and GND, but can be combined with logic gates or buffers to simplify many logic structures.

# Transmission-gate Multiplexor

2-to-multiplexor:  
 $C = sa + s'b$

 


Switches simplify  
 the implementation:

  

Compare the cost to logic  
 gate implementation.

# 4-to-1 Transmission-gate Mux

 


- The series connection of pass-transistors in each branch effectively forms the AND of  $s_1$  and  $s_0$  (or their complement).
- Compare cost to logic gate implementation

Lec15-CMOS

Page 15

 
# Alternative 4-to-1 Multiplexor

- This version has less delay from in to out.
- In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).







# Tri-state Buffers

 


## Variations:

 


Inverting buffer

 

Inverted enable

 


 transmission gate useful in implementation



 
# Tri-state Buffers

Tri-state buffers enable "bidirectional" connections.




 Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".




# Tri-state Based Multiplexor


Multiplexor

 

If  $s=1$  then  $c=a$  else


 


 Transistor Circuit for inverting multiplexor:




# Latches and Flip-flops

Positive level-sensitive latch:

  

 Positive Edge-triggered **flip-flop** built from two level-sensitive latches:



Latch Implementation:

