


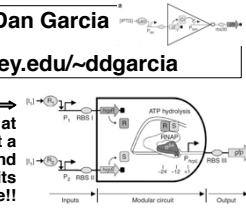
inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**  
**Lecture 24**  
**State Circuits : Circuits that Remember**



**Lecturer SOE Dan Garcia**  
[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

2011-10-21

Hi to Murali Krishna Yeleswarapu listening from Bangalore, India!



**Bio NAND gate** ⇒ Researchers at Imperial College in London have built a biological NAND gate using E. Coli, and showed you could build bigger circuits too. You can't ask for more relevance!!

[www.nature.com/ncomms/journal/v2/n10/full/ncomms1516.html](http://www.nature.com/ncomms/journal/v2/n10/full/ncomms1516.html)

CS61C L24 State Elements : Circuits that Remember (1) Garcia, Fall 2011 © UCB

### Review

- ISA is very important abstraction layer
  - Contract between HW and SW
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types of circuits:
  - Stateless Combinational Logic (&,!,~)
  - State circuits (e.g., registers)

CS61C L24 State Elements : Circuits that Remember (2) Garcia, Fall 2011 © UCB


### Uses for State Elements

1. As a place to store values for some indeterminate amount of time:
  - Register files (like \$1-\$31 on the MIPS)
  - Memory (caches, and main memory)
2. Help control the flow of information between combinational logic blocks.
  - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.

CS61C L24 State Elements : Circuits that Remember (3) Garcia, Fall 2011 © UCB
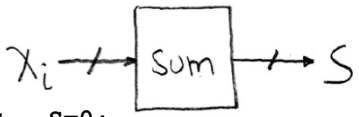
### Accumulator Example

Why do we need to control the flow of information?




Want:  $s=0;$   
 for ( $i=0; i<n; i++$ )  
 $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S.

CS61C L24 State Elements : Circuits that Remember (4) Garcia, Fall 2011 © UCB


### First try...Does this work?

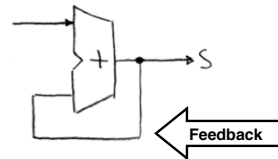


Nope!  
 Reason #1... What is there to control the next iteration of the 'for' loop?  
 Reason #2... How do we say: 's=0'?

CS61C L24 State Elements : Circuits that Remember (5) Garcia, Fall 2011 © UCB

### Second try...How about this?

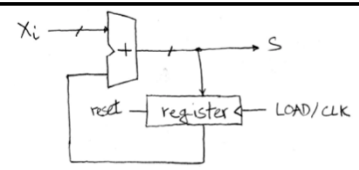

Rough timing...

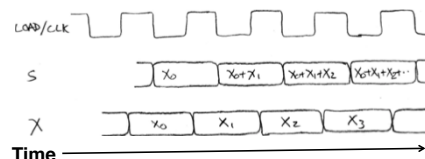

Register is used to hold up the transfer of data to adder.

CS61C L24 State Elements : Circuits that Remember (6) Garcia, Fall 2011 © UCB

### Register Details...What's inside?

- n instances of a "Flip-Flop"
- Flip-flop name because the output flips and flops between 0,1
- D is "data", Q is "output"
- Also called "d-type Flip-Flop"

*Cal* CS61C L24 State Elements : Circuits that Remember (7) Garcia, Fall 2011 © UCB

### What's the timing of a Flip-flop? (1/2)

- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."
- Example waveforms:

*Cal* CS61C L24 State Elements : Circuits that Remember (8) Garcia, Fall 2011 © UCB

### What's the timing of a Flip-flop? (2/2)

- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."
- Example waveforms (more detail):

*Cal* CS61C L24 State Elements : Circuits that Remember (9) Garcia, Fall 2011 © UCB

### Accumulator Revisited (proper timing 1/2)

- Reset input to register is used to force it to all zeros (takes priority over D input).
- $S_{i-1}$  holds the result of the  $i^{th}-1$  iteration.
- Analyze circuit timing starting at the output of the register.

*Cal* CS61C L24 State Elements : Circuits that Remember (10) Garcia, Fall 2011 © UCB

### Accumulator Revisited (proper timing 2/2)

- reset signal shown.
- Also, in practice X might not arrive to the adder at the same time as  $S_{i-1}$
- $S_i$  temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.

*Cal* CS61C L24 State Elements : Circuits that Remember (11) Garcia, Fall 2011 © UCB

### Maximum Clock Frequency

Hint...  
Frequency = 1/Period

- What is the maximum frequency of this circuit?

Max Delay = Setup Time + CLK-to-Q Delay + CL Delay

*Cal* CS61C L24 State Elements : Circuits that Remember (12) Garcia, Fall 2011 © UCB

### Pipelining to improve performance (1/2)

Extra Register are often added to help speed up the clock rate.

**Timing...**

Note: delay of 1 clock cycle from input to output.  
Clock period limited by propagation delay of adder/shifter.

CS61C L24 State Elements - Circuits that Remember (13) Garcia, Fall 2011 © UCB

### Pipelining to improve performance (2/2)

- Insertion of register allows higher clock frequency.
- More outputs per second.

**Timing...**

CS61C L24 State Elements - Circuits that Remember (14) Garcia, Fall 2011 © UCB

### Recap of Timing Terms

- Clock (CLK) - steady square wave that synchronizes system
- Setup Time - when the input must be stable before the rising edge of the CLK
- Hold Time - when the input must be stable after the rising edge of the CLK
- "CLK-to-Q" Delay - how long it takes the output to change, measured from the rising edge of the CLK
- Flip-flop - one bit of state that samples every rising edge of the CLK (positive edge-triggered)
- Register - several bits of state that samples on rising edge of CLK or on LOAD (positive edge-triggered)

CS61C L24 State Elements - Circuits that Remember (15) Garcia, Fall 2011 © UCB

### Administrivia

- **Project 2 Part Two, Due Sunday 2011-10-23 @23:59:59**
- **Homework 4 out next will be directly connected to this material!**
- **Please do the reading (in the PDFs) for this material to really understand it!**

CS61C L24 State Elements - Circuits that Remember (16) Garcia, Fall 2011 © UCB

### Finite State Machines (FSM) Introduction

- You have seen FSMs in other classes.
- Same basic idea.
- The function can be represented with a "state transition diagram".
- With combinational logic and registers, any FSM can be implemented in hardware.

CS61C L24 State Elements - Circuits that Remember (17) Garcia, Fall 2011 © UCB

### Finite State Machine Example: 3 ones...

FSM to detect the occurrence of 3 consecutive 1's in the input.

**Draw the FSM...**

Assume state transitions are controlled by the clock: on each clock cycle the machine checks the inputs and moves to a new state and produces a new output...

CS61C L24 State Elements - Circuits that Remember (18) Garcia, Fall 2011 © UCB

### Hardware Implementation of FSM

... Therefore a register is needed to hold the a representation of which state the machine is in. Use a unique bit pattern for each state.

Combinational logic circuit is used to implement a function maps from *present state and input to next state and output.*

Cal CS61C L24 State Elements : Circuits that Remember (19) Garcia, Fall 2011 © UCB

### Hardware for FSM: Combinational Logic

Next lecture we will discuss the detailed implementation, but for now can look at its functional specification, truth table form.

#### Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

Cal CS61C L24 State Elements : Circuits that Remember (20) Garcia, Fall 2011 © UCB

### General Model for Synchronous Systems

- Collection of CL blocks separated by registers.
- Registers may be back-to-back and CL blocks may be back-to-back.
- Feedback is optional.
- Clock signal(s) connects only to clock input of registers.

Cal CS61C L24 State Elements : Circuits that Remember (21) Garcia, Fall 2011 © UCB

### Peer Instruction

- 1) HW feedback akin to SW recursion
- 2) The minimum period of a usable synchronous circuit is at least the CLK-to-Q delay
- 3) You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

123  
a: FFF  
a: FFT  
b: FTF  
b: FTT  
c: TFF  
c: TTF  
d: TTF  
e: TTT

Cal CS61C L24 State Elements : Circuits that Remember (25) Garcia, Fall 2011 © UCB

### Design Hierarchy

Cal CS61C L24 State Elements : Circuits that Remember (24) Garcia, Fall 2011 © UCB

### “And In conclusion...”

- State elements are used to:
  - Build memories
  - Control the flow of information between other state elements and combinational logic
- D-flip-flops used to build registers
- Clocks tell us when D-flip-flops change
  - Setup and Hold times important
- We pipeline long-delay CL for faster clock
- Finite State Machines extremely useful
  - You'll see them again 150, 152, 164, 172, ...

Cal CS61C L24 State Elements : Circuits that Remember (25) Garcia, Fall 2011 © UCB