

inst.eecs.berkeley.edu/~cs61c

UC Berkeley CS61C : Machine Structures

Lecture 23 – Representations of Combinational Logic Circuits



2011-10-24

Lecturer SOE Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Android Brain on Robots! ⇒

“Half the weight of some robots is due to on-board computers and the batteries needed to power them. This lightweight robot uses an Android phone as the brain, with the phone’s gyroscope and camera as sensors, with cloud help!”




www.technologyreview.com/business/38953/page1/

Review

- **State elements are used to:**
 - **Build memories**
 - **Control the flow of information between other state elements and combinational logic**
- **D-flip-flops used to build registers**
- **Clocks tell us when D-flip-flops change**
 - **Setup and Hold times important**
- **We pipeline long-delay CL for faster clock**
- **Finite State Machines extremely useful**
 - **Represent states and transitions**



Truth Tables

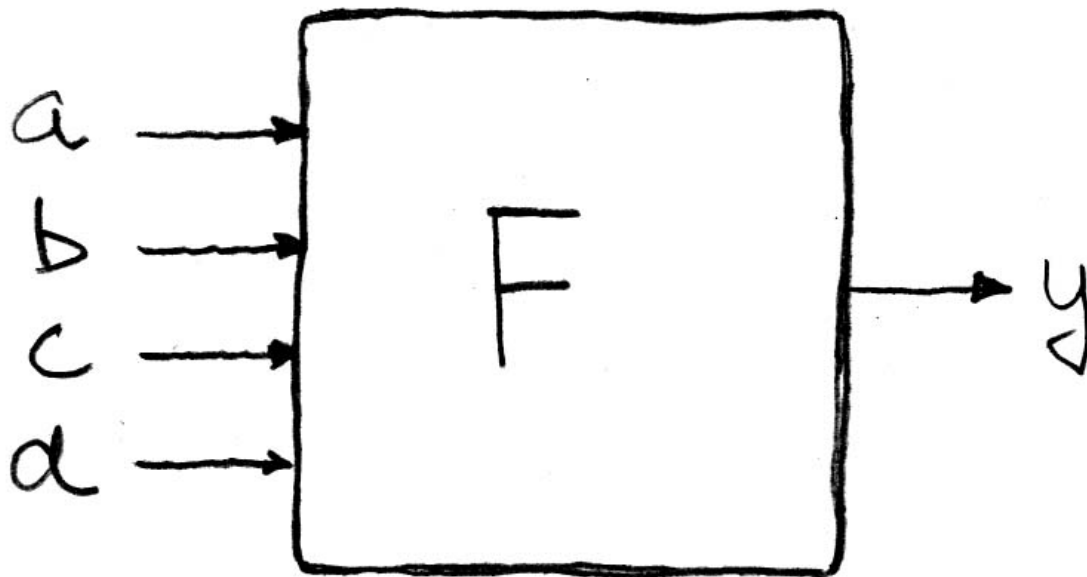


a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

TT Example #1: 1 iff one (not both) a,b=1

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



TT Example #2: 2-bit adder

 

A	B	C
a_1a_0	b_1b_0	$c_2c_1c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How
Many
Rows?



TT Example #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

**How
Many
Rows?**


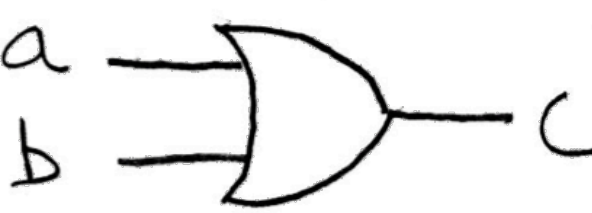
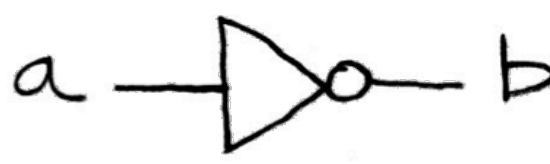


TT Example #4: 3-input majority circuit

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1




Logic Gates (1/2)

AND		<table border="1"><thead><tr><th>ab</th><th>c</th></tr></thead><tbody><tr><td>00</td><td>0</td></tr><tr><td>01</td><td>0</td></tr><tr><td>10</td><td>0</td></tr><tr><td>11</td><td>1</td></tr></tbody></table>	ab	c	00	0	01	0	10	0	11	1
ab	c											
00	0											
01	0											
10	0											
11	1											
OR		<table border="1"><thead><tr><th>ab</th><th>c</th></tr></thead><tbody><tr><td>00</td><td>0</td></tr><tr><td>01</td><td>1</td></tr><tr><td>10</td><td>1</td></tr><tr><td>11</td><td>1</td></tr></tbody></table>	ab	c	00	0	01	1	10	1	11	1
ab	c											
00	0											
01	1											
10	1											
11	1											
NOT		<table border="1"><thead><tr><th>a</th><th>b</th></tr></thead><tbody><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></tbody></table>	a	b	0	1	1	0				
a	b											
0	1											
1	0											

And vs. Or review – Dan's mnemonic

AND Gate

Symbol

 

Definition

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Logic Gates (2/2)


XOR



NAND



NOR

 

ab	c
00	0
01	1
10	1
11	0

ab	c
00	1
01	1
10	1
11	0

ab	c
00	1
01	0
10	0
11	0



2-input gates extend to n-inputs


- N-input XOR is the only one which isn't so obvious
- It's simple: XOR is a 1 iff the # of 1s at its input is odd \Rightarrow

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




Truth Table \Rightarrow Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


Truth Table \Rightarrow Gates (e.g., FSM circ.)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 

or equivalently...

 

Administrivia

- **The next project will have a performance component, and we will celebrate the winners!**
- **How many hours on project 2?**
 - a) **0-10**
 - b) **10-20**
 - c) **30-40**
 - d) **50-60**
 - e) **60-70**




Boolean Algebra

- **George Boole, 19th Century mathematician**

- **Developed a mathematical system (algebra) involving logic**

- later known as “Boolean Algebra”

 


- **Primitive functions: AND, OR and NOT**

- **The power of BA is there's a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA**



+ means OR, \cdot means AND, \bar{x} means NOT

 Boolean Algebra (e.g., for majority fun.)




$$y = a \cdot b + a \cdot c + b \cdot c$$


$$y = ab + ac + bc$$

Boolean Algebra (e.g., for FSM)

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 


or equivalently...

 

$$y = PS_1 \cdot \overline{PS_0} \cdot INPUT$$

BA: Circuit & Algebraic Simplification

 


original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

 

simplified circuit

**BA also great for
circuit verification
Circ X = Circ Y?
use BA to prove!**



Laws of Boolean Algebra

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\bar{x}y + x = x + y$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$(\bar{x} + y)x = xy$$

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

complementarity

laws of 0's and 1's

identities

 idempotent law

commutativity

associativity

distribution

uniting theorem

uniting theorem v.2

DeMorgan's Law



Boolean Algebraic Simplification Example

$$\begin{aligned}y &= ab + a + c \\ &= a(b + 1) + c && \text{distribution, identity} \\ &= a(1) + c && \text{law of 1's} \\ &= a + c && \text{identity}\end{aligned}$$



Canonical forms (1/2)


	<i>abc</i>	<i>y</i>		Sum-of-products (ORs of ANDs)
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1		
$\bar{a} \cdot \bar{b} \cdot c$	001	1		
	010	0		
	011	0		
$a \cdot \bar{b} \cdot \bar{c}$	100	1		
	101	0		
$a \cdot b \cdot \bar{c}$	110	1		
	111	0		



Canonical forms (2/2)

$$\begin{aligned}y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\ &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) \\ &= \bar{a}\bar{b}(1) + a\bar{c}(1) \\ &= \bar{a}\bar{b} + a\bar{c}\end{aligned}$$

distribution
complementarity
identity

 

Peer Instruction

- 1) $(a+b) \cdot (\bar{a}+b) = b$
- 2) N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND
- 3) You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	123
a:	FFF
a:	FFT
b:	FTF
b:	FTT
c:	TFF
d:	TFT
e:	TF
e:	TTT

Peer Instruction Answer

1) $(a+b) \cdot (\bar{a}+b) = a\bar{a}+ab+b\bar{a}+bb = 0+b(a+\bar{a})+b = b+b = b$ **TRUE**

2) (next slide)

3) You can use NOR(s) with clever wiring to simulate AND, OR, & NOT.

$$\text{NOR}(a,a) = \overline{a+a} = \overline{aa} = \bar{a}$$

Using this NOT, can we make a NOR an OR? An And?

TRUE

1) $(a+b) \cdot (\bar{a}+b) = b$

2) N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND

3) You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	123
a:	FFF
a:	FFT
b:	FTF
b:	FTT
c:	TFF
d:	TFT
e:	TF
e:	TTT

Peer Instruction Answer (B)

- 2) N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND... **FALSE**

Let's confirm!

CORRECT 3-input				
XYZ	AND	OR	XOR	NAND
000	0	0	0	1
001	0	1	1	1
010	0	1	1	1
011	0	1	0	1
100	0	1	1	1
101	0	1	0	1
110	0	1	0	1
111	1	1	1	0

CORRECT 2-input				
YZ	AND	OR	XOR	NAND
00	0	0	0	1
01	0	1	1	1
10	0	1	1	1
11	1	1	0	0



“And In conclusion...”

- Pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
 - You’ll see them again in 150, 152 & 164
- Use this table and techniques we learned to transform from 1 to another

