

www.eetimes.com/electronics-news/4230235/Thailand-floods-take-toll-on-PC-makers

## EE Times 61C In the News

### Thailand Floods Take Toll on PC Makers

Sylvie Barak 10/31/2011

The Thai floods have already claimed the lives of hundreds of people, with tens of thousands more having had to flee their homes in Bangkok. On a financial scale too the floods have wreaked havoc...



Around 25 percent of the world's hard drive manufacturing plants are situated in and around Bangkok...

Western Digital corp., the world's largest producer of hard disc drives has had to close all its factories in Thailand down completely, as has Toshiba corp. and a number of other smaller HDD makers, leaving the industry with just two months' worth of remaining inventory.

"We expect PC sales to be lower than expected. As a result, we expect weakness in DRAM prices," a Samsung executive said

11/1/11 Fall 2011 - Lecture #29 1

## CS 61C: Great Ideas in Computer Architecture (Machine Structures)

### Lecture 29: Single-Cycle CPU Datapath Control Part 2

Instructors:  
Mike Franklin  
Dan Garcia

<http://inst.eecs.Berkeley.edu/~cs61c/fa11>

11/1/11 Fall 2011 - Lecture #29 2

### Review: Processor Design 5 steps

- Step 1: Analyze instruction set to determine datapath requirements
  - Meaning of each instruction is given by register transfers
  - Datapath must include storage element for ISA registers
  - Datapath must support each register transfer
- Step 2: Select set of datapath components & establish clock methodology
- Step 3: Assemble datapath components that meet the requirements
- Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer
- Step 5: Assemble the control logic


11/1/11 Fall 2011 - Lecture #29 3

### Processor Design: 5 steps

- Step 1: Analyze instruction set to determine datapath requirements
  - Meaning of each instruction is given by register transfers
  - Datapath must include storage element for ISA registers
  - Datapath must support each register transfer
- Step 2: Select set of datapath components & establish clock methodology
- Step 3: Assemble datapath components that meet the requirements
- Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer
- Step 5: Assemble the control logic

11/2/11 Fall 2011 - Lecture #29 4
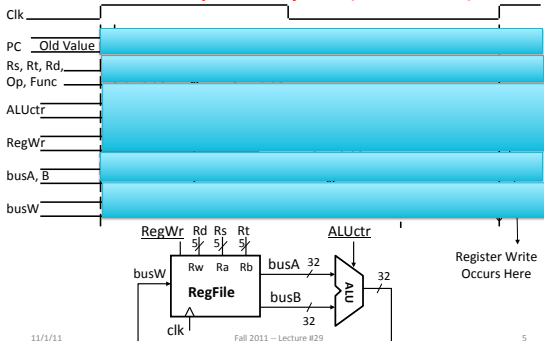
### Register-Register Timing: One Complete Cycle (Add/Sub)




Register Write Occurs Here

11/1/11 Fall 2011 - Lecture #29 5
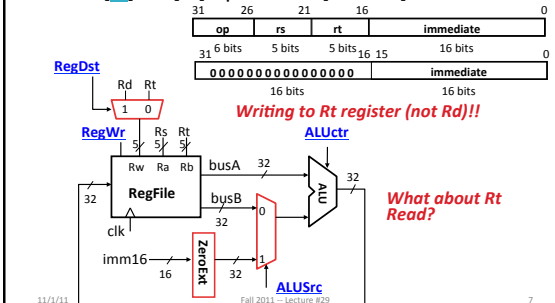
### 3c: Logical Op (or) with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



Writing to Rt register (not Rd)!!

What about Rt Read?

11/1/11 Fall 2011 - Lecture #29 7

### 3d: Load Operations

- $R[rt] = Mem[R[rs] + SignExt[imm16]]$
- Example: `lw rt, rs, imm16`

11/1/11

### 3e: Store Operations

- $Mem[R[rs] + SignExt[imm16]] = R[rt]$
- Ex.: `sw rt, rs, imm16`

### 3e: Store Operations

- $Mem[R[rs] + SignExt[imm16]] = R[rt]$
- Ex.: `sw rt, rs, imm16`

### 3f: The Branch Instruction

`beq rs, rt, imm16`

- mem[PC] Fetch the instruction from memory
- Equal =  $R[rs] == R[rt]$  Calculate branch condition
- if (Equal) Calculate the next instruction's address
  - $PC = PC + 4 + (SignExt(imm16) \times 4)$
- else
  - $PC = PC + 4$

### Datapath for Branch Operations

`beq rs, rt, imm16`

Datapath generates condition (Equal)

Already have mux, adder, need special sign extender for PC, need equal compare (sub?)

### Instruction Fetch Unit including Branch







- if (Zero == 1) then  $PC = PC + 4 + SignExt[imm16] * 4$ ; else  $PC = PC + 4$

- How to encode nPC\_sel?
  - Direct MUX select?
  - Branch inst. / not branch inst.
- Let's pick 2nd option

Q: What logic gate?

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

11/2/11 Fall 2010 - Lecture #27 14

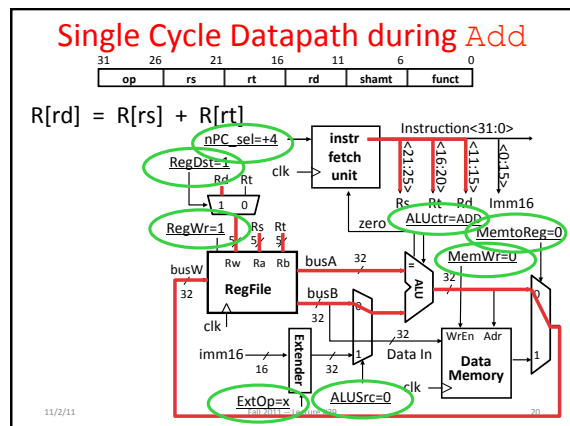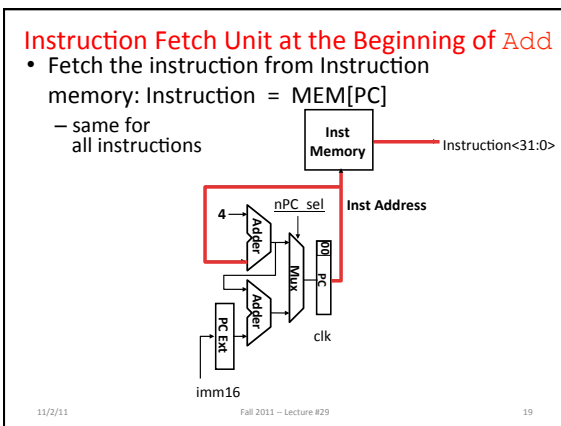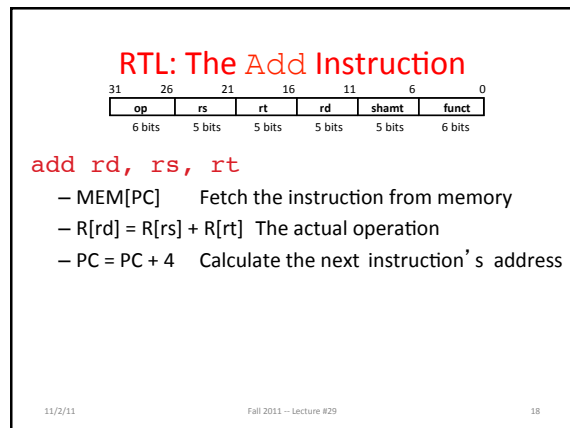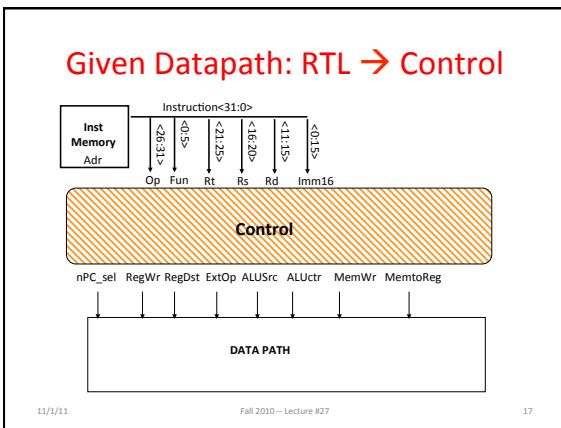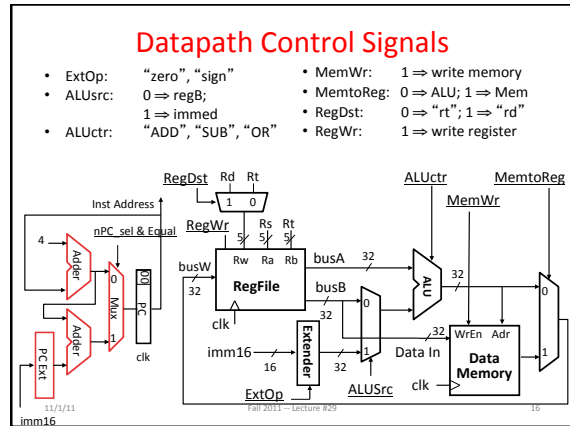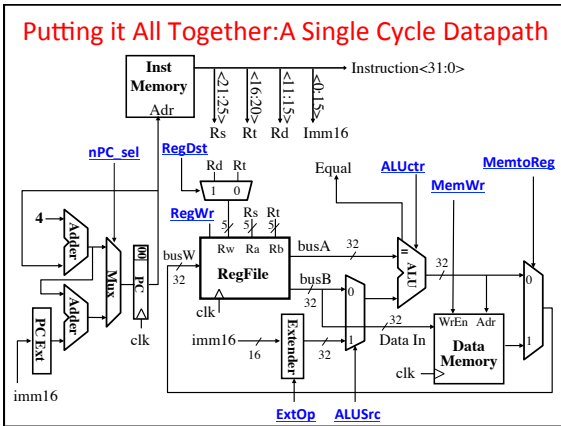

### Instruction Fetch Unit at End of Add

- PC = PC + 4
  - Same for all instructions except: Branch and Jump

11/2/11 Fall 2011 - Lecture #29 21

### P&H Figure 4.17

11/2/11 Fall 2011 - Lecture #29 22

### Summary of the Control Signals (1/2)

inst Register Transfer

```

add R[rd] ← R[rs] + R[rt]; PC ← PC + 4
    ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"

sub R[rd] ← R[rs] - R[rt]; PC ← PC + 4
    ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"

ori R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
    ALUSrc=Im, Extop="z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"

lw R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
    ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
    nPC_sel = "+4"

sw MEM[ R[rs] + sign_ext(Imm16) ] ← R[rs]; PC ← PC + 4
    ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00
    else PC ← PC + 4
    nPC_sel = "br", ALUctr = "SUB"
    
```

11/1/11 Fall 2010 - Lecture #27 23

### Summary of the Control Signals (2/2)

See Appendix A

func	10 0000	10 0010	We Don't Care :-)				
op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	x	0	1	1	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

R-type: op rs rt rd shamt funct add, sub  
 I-type: op rs rt immediate ori, lw, sw, beq  
 J-type: op target address jump

11/1/11 Fall 2010 - Lecture #27 24

### Boolean Expressions for Controller

```

RegDst = add + sub
ALUSrc = ori + lw + sw
MemtoReg = lw
RegWrite = add + sub + ori + lw
MemWrite = sw
nPCsel = beq
Jump = jump
ExtOp = lw + sw
ALUctr[0] = sub + beq (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1] = or
    
```

Where:

```

rtype = ~op5 * ~op4 * ~op3 * ~op2 * ~op1 * ~op0
ori = ~op5 * ~op4 * op3 * op2 * ~op1 * op0
lw = ~op5 * ~op4 * ~op3 * ~op2 * op1 * op0
sw = op5 * ~op4 * op3 * ~op2 * op1 * op0
beq = ~op5 * ~op4 * ~op3 * op2 * ~op1 * ~op0
jump = ~op5 * ~op4 * ~op3 * ~op2 * op1 * ~op0
    
```

How do we implement this in gates?

```

add = rtype * func3 * ~func4 * ~func3 * ~func2 * ~func1 * ~func0
sub = rtype * func3 * ~func4 * ~func3 * ~func2 * func1 * ~func0
    
```

11/1/11 Fall 2010 - Lecture #27 25

### Controller Implementation

11/1/11 Fall 2010 - Lecture #27 26

### Peer Instruction


- 1) We should use the main ALU to compute  $PC=PC+4$  in order to save some gates
- 2) The ALU is inactive for memory reads (loads) or writes (stores).

- a) 12
- b) FF
- c) FT
- d) TT
- e) Help!

### Summary: Single-cycle Processor

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
  - Formulate Logic Equations
  - Design Circuits




### Bonus Slides

- How to implement Jump

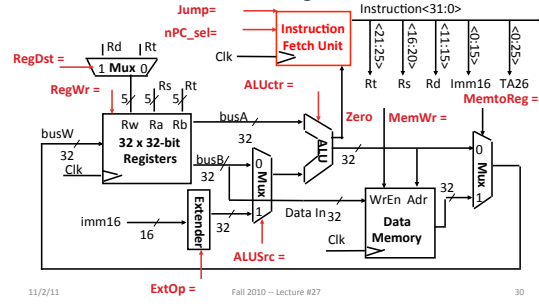
### Single Cycle Datapath during Jump

- New PC = { PC[31..28], target address, 00 }


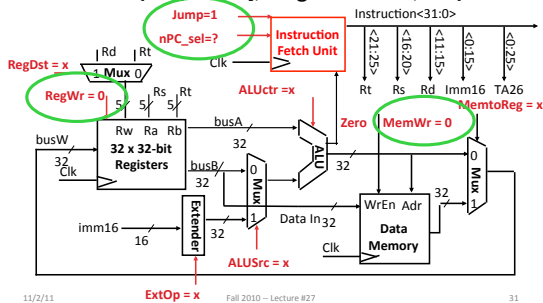
### Single Cycle Datapath during Jump

- New PC = { PC[31..28], target address, 00 }



### Instruction Fetch Unit at the End of Jump

- New PC = { PC[31..28], target address, 00 }

