 


Problem 1: Energy-Storage Elements and 1st-Order Circuits [16 points in total]

- a) Consider the capacitive voltage-divider circuit below. Find V_{out} . How will V_{out} change if a small load capacitance $C_{load} < 2 \mu\text{F}$ is connected between terminals a and b ? [4 pts]



$$V_{out} = \frac{8 \mu\text{F}}{8 \mu\text{F} + 2 \mu\text{F}} (10 \text{ V}) = 8 \text{ V}$$


↑
capacitance between terminals a and b

$$V_{out} = \underline{8 \text{ Volts}}$$

V_{out} will [increase, decrease, not change] (circle one) when C_{load} is connected, because

the capacitance between terminals a and b will increase.

- b) Consider the following RC circuit:

 

Provide a physical reason why it takes longer for v_c to reach its final value if R is increased.

(Why is the characteristic time constant τ proportional to R ?) [2 pts]


$$i = \frac{V_0 - v_c}{R} = C \frac{dv_c}{dt}$$

v_c will take longer to reach its final value if R is increased because


the current flowing through R (to charge C) will decrease, hence it will take longer to deliver the charge $Q = CV_0$.

Problem 1 (continued)

 
c) Assume that the circuit below is operating in steady state with the switch open for $t < 0$. Find and accurately sketch $v(t)$ for all t . [10 pts]




$t < 0$:

 

$t > 0$:

 


$t = \infty$:

 

$$\tau = \frac{L}{R} = \frac{3\text{H}}{2\text{k}\Omega + 1\text{k}\Omega} = 1\text{ms}$$

$$v = 0 + [-10 - 0]e^{-t/1\text{ms}} = -10e^{-1000t}$$

For $t < 0$: $v(t) = 5\text{V}$. For $t > 0$: $v(t) = -10e^{-1000t}$

 

Problem 2: Semiconductor Materials and Devices [17 points in total]

a) Consider a Si sample maintained at $T = 300\text{K}$, uniformly doped with Arsenic atoms to a concentration $3 \times 10^{16} \text{ cm}^{-3}$. The electron mobility = $1000 \text{ cm}^2/\text{V}\cdot\text{s}$; hole mobility = $400 \text{ cm}^2/\text{V}\cdot\text{s}$.

i) Estimate the resistivity of this sample. (Use $q = 1.6 \times 10^{-19} \text{ C}$ in your calculation.) [4 pts]

As is a Column V element \rightarrow donor in Si

$$N_D = 3 \times 10^{16} \text{ cm}^{-3}, N_A = 0 \Rightarrow n = 3 \times 10^{16} \text{ cm}^{-3}, p = \frac{n_i^2}{n} \approx 3000 \text{ cm}^{-3}$$

$$\rho = [q\mu_n n + q\mu_p p]^{-1} \approx [q\mu_n n]^{-1} \text{ since } n \gg p$$

$$= [1.6 \times 10^{-19} \times 1000 \times 3 \times 10^{16}]^{-1} = [4.8]^{-1} \approx 0.2 \Omega\text{-cm}$$

resistivity $\approx 0.2 \Omega\text{-cm}$

ii) How will the resistivity of this sample change if it were to be doped additionally with $3 \times 10^{16} \text{ cm}^{-3}$ Phosphorus atoms? [3 pts] carrier mobilities would be degraded

P is also a Column V element \rightarrow donor in Si

since $N_D + N_A \uparrow$


$$N_D = 6 \times 10^{16} \text{ cm}^{-3}, N_A = 0 \Rightarrow n = 6 \times 10^{16} \text{ cm}^{-3}$$

The resistivity will [increase, decrease, not change] (circle one)

by a factor that is [greater than, less than, equal to] (circle one) 2 when phosphorus is added because

the number of conduction electrons will double, but μ_n will decrease

 b) Explain (using 1 or 2 sentences) why a pn junction has capacitance. [2 pts]




A pn junction has capacitance because

charge is stored in the depletion region of a pn junction.

The width of the depletion region, and hence the charge stored, varies with the bias voltage. $C_j \equiv \left| \frac{dQ}{dV_D} \right|$

Problem 2 (continued)

 c) Assume the diodes in the circuit below can be modeled as perfect rectifiers.



i) For what values of V_{in} is $D1$ on? Explain your reasoning. [3 pts]

$D1$ is on for $V_{in} > 1\text{ Volt}$ because
 forward current can flow in $D1$ as long as $V_{in} > V_{out}$.
 $D2$ fixes V_{out} at 1V , unless V_{in} causes V_{out} to be $> 1\text{ Volt}$.

ii) For what values of V_{in} is $D2$ on? Explain your reasoning. [2 pts]


$D2$ is on for $V_{in} < 2\text{ Volts}$ because
 if V_{in} exceeds 2V , V_{out} will exceed 1 Volt and $D2$ will be
 reverse biased. (If $D2$ is on for $V_{in} > 2\text{V}$, reverse current would have to
 flow in $D2$ - which cannot be.)

iii) Accurately plot V_{out} vs. V_{in} on the axes provided. [3 pts]

For $V_{in} < 2\text{V}$, $D2$ is on and
 so V_{out} is fixed at 1V .


For $V_{in} > 2\text{V}$, $D2$ is off and

$$\text{so } V_{out} = \frac{1\text{ k}\Omega}{1\text{ k}\Omega + 1\text{ k}\Omega} V_{in} = \frac{1}{2} V_{in}$$

 

Problem 3: MOSFET and Common-Source Amplifier [17 points in total]

 a) The following is the i_D - v_{DS} characteristic of an n-channel MOSFET:



Indicate how this characteristic would change (by drawing the modified i_D - v_{DS} characteristic with appropriate changes in I_{DSAT} and V_{DSAT}):

i) when V_T is lowered – use a labeled solid line on the plot above [2 pts]

$$I_{DSAT} = k' \frac{W}{2L} (V_{GS} - V_T)^2 \text{ increases}$$

$$V_{DSAT} = V_{GS} - V_T \text{ increases}$$

$$\text{slope at small } v_{DS} = k' \frac{W}{L} (V_{GS} - V_T - \frac{v_{DS}}{2}) \text{ increases}$$

ii) when channel-length modulation is significant – use a labeled dashed line on the plot above [2 pts]

$$\text{no change in } V_{DSAT}, \text{ slope at small } v_{DS}$$

$$\text{slope in saturation region} > 0$$

iii) when the current is limited by velocity saturation, rather than pinch-off – use a labeled dotted line on the plot above [2 pts]



$$V_{DSAT} = \frac{L}{\mu} v_{sat} < V_{GS} - V_T \text{ (decreases)}$$

$$I_{DSAT} \text{ decreases}$$

$$\text{slope at small } v_{DS} \text{ unchanged}$$

Problem 3 (continued)

 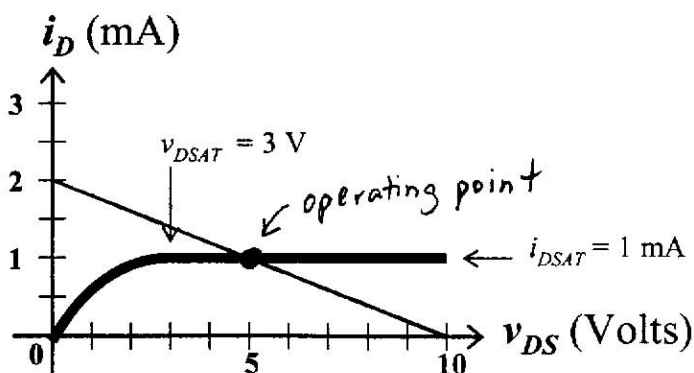b) Below to the left is the i_D vs. v_{DS} characteristic for a long n-channel MOSFET with $V_T = 1$ V.



What is V_{GS} ? [2 pts]

$$V_{DSAT} = V_{GS} - V_T$$

$$3 = V_{GS} - 1 \Rightarrow V_{GS} = 4 \text{ V}$$

$V_{GS} = 4 \text{ Volts}$

c) Suppose the MOSFET in part (b) is used in the amplifier circuit shown above to the right.

i) Draw the load line on the MOSFET i_D - v_{DS} plot (above to the left). [3 pts]


ii) In what region is the MOSFET operating? [2 pts]

The MOSFET is operating in the [linear, saturation, cutoff] (circle one) region because

$V_{DS} > V_{DSAT} \text{ and } i_D > 0$

iii) What is the incremental change in the output voltage (i.e. v_{out}) for a -1 mV change in the input voltage (i.e. $v_{gs} = -1$ mV)? [4 pts]

small-signal equivalent circuit:

 

$$i_{DSAT} = k' \frac{W}{2L} (V_{GS} - V_T)^2 = 1 \text{ mA}$$

$$\Rightarrow k' \frac{W}{2L} (3)^2 = 1 \text{ mA}$$

$$k' \frac{W}{L} = \frac{2}{9} \text{ mA/V}^2$$

$$g_m = \frac{\partial i_D}{\partial v_{GS}} = \frac{\partial}{\partial v_{GS}} \left[k' \frac{W}{2L} (V_{GS} - V_T)^2 \right]$$

$$= k' \frac{W}{L} (V_{GS} - V_T)$$

$$= \frac{2}{9} \frac{\text{mA}}{\text{V}^2} \times 3 \text{ V} = \frac{2}{3} \text{ mS}$$

$$v_{out} = -g_m v_{gs} (5 \text{ k}\Omega)$$

$$= -\frac{2}{3} \times 10^{-3} (-10^{-3}) (5 \times 10^3)$$

$v_{out} = 3.3 \text{ mV}$