

**Homework Assignment #1**

Due at 11 AM in 240 Cory on Friday, 9/5/03


\* Be sure to put your name and section number on your paper

**Problem 1: Digital representation of a voltage signal**

Some audio systems are advertised to use 18-bit analog-to-digital conversion. If the maximum possible value of the microphone output voltage is  $250 \mu\text{V}$  and this voltage can be either + or - with respect to ground, what is the voltage resolution of the system? Assume that one bit is used to encode whether the voltage is positive or negative.

**Problem 2: Current and voltage**

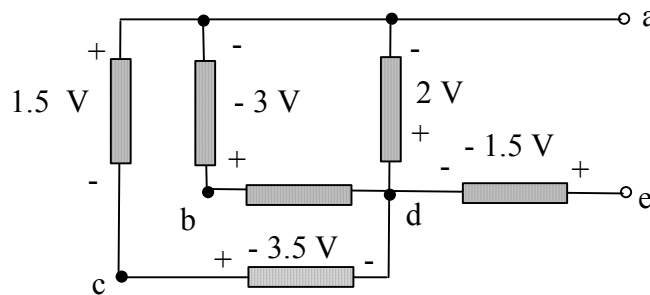
- a) Suppose a  $32 \mu\text{A}$  current flows (in the +x direction) in a semiconductor sample of cross-sectional area  $10 \mu\text{m}^2$ .
- (i) What is the average number of electrons per second that flow past a fixed reference cross section that is perpendicular to the direction of flow?
  - (ii) What is the current density at a fixed reference cross section that is perpendicular to the direction of flow?
- b) Consider the following electric circuit:



- (i) What is  $v_{ae}$  in Volts?
- (ii) What is  $v_{bd}$  in Volts?

**Problem 3: Power**

(Problem 1.28 in the textbook)

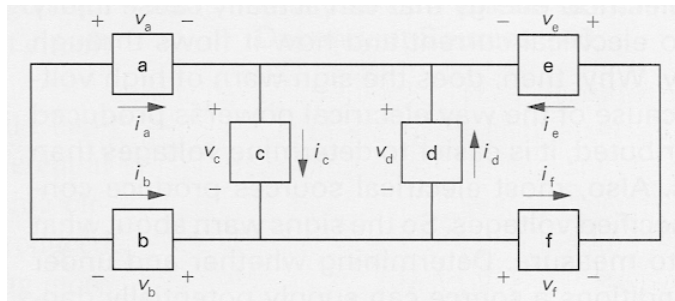


- a) In the circuit shown, identify which elements have the voltage and current reference polarities defined using the passive sign convention.
- b) The numerical values of the currents and voltages for each element are given below. How much total power is absorbed, and how much is delivered in this circuit?

ELEMENT	VOLTAGE (V)	CURRENT (A)
a	-8	7
b	-2	-7
c	10	15
d	10	5
e	-6	3
f	-4	3

**Problem 4: Voltage and current sources**

(Problem 2.7 in the textbook)

If the interconnection shown below is valid, find the total power developed in the circuit. If the interconnection is not valid, explain why.

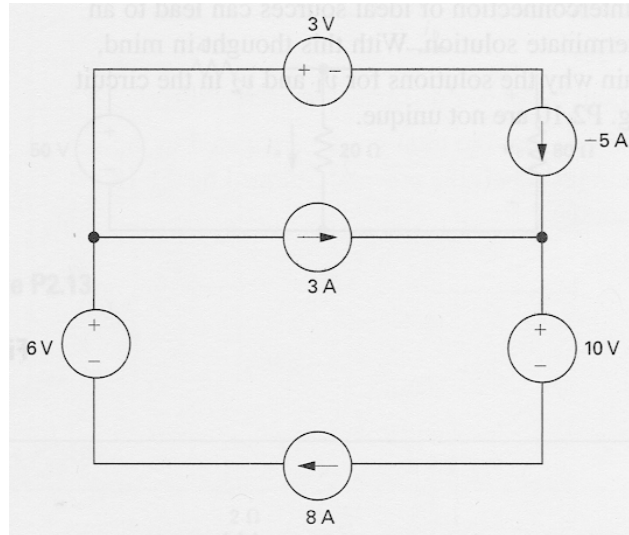

**Problem 5: Resistor circuit**

(Problem 2.14 in the textbook)

The currents  $i_1$  and  $i_2$  in the circuit shown below are 20 A and 15 A, respectively.

- a) Find the power supplied by each voltage source.
- b) Show that the total power supplied (by the sources) equals the total power dissipated in the resistors.

