

# EE40 Homework #1 Solutions

1

- 1) 18 bit A/D. signal range from  $-250\mu\text{V}$  to  $250\mu\text{V}$   
1 bit for  $\pm$ , 17 remaining bits divide up the 0 to  $250\mu\text{V}$  range  
voltage resolution =  $\left(\frac{250\mu\text{V}}{2^{17}-1}\right) = \frac{250 \cdot 10^{-6}\text{V}}{131071} = 1.9 \cdot 10^{-9}\text{V}$

$$\boxed{1.9\text{ nV resolution}}$$

- 2) a)  $I = 32\mu\text{A}$   $A = 10\mu\text{m}^2$   $I = \frac{dQ}{dt} \rightarrow \text{charge/time}$

i) avg. #  $e^-/\text{sec} = \frac{(\text{amount of charge/time})}{(\text{amount of charge}/e^-)}$

$$= I \text{ C/s} / (1.6 \cdot 10^{-19} \text{ C}/e^-)$$

$$= 32\mu / (-1.6 \cdot 10^{-19})$$

$$\boxed{= 2 \cdot 10^{14} e^-/\text{sec}}$$


ii) current density = current/area


$$= I/A = (32\mu\text{A}) / (10\mu\text{m}^2) =$$

$$= 32 \cdot 10^{-6} \text{ A} / (10 \cdot (10^{-4})^2 \text{ cm}^2)$$

$$\boxed{= 320 \text{ A/cm}^2}$$


2) b)

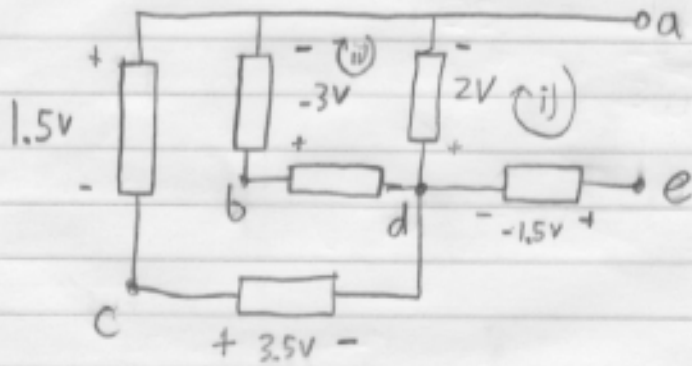

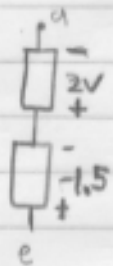i)  $V_{ae} =$    $V_{ae} = V_a - V_e = (-2V) + (1.5V) = -0.5V$

$V_{ae} = -0.5V$

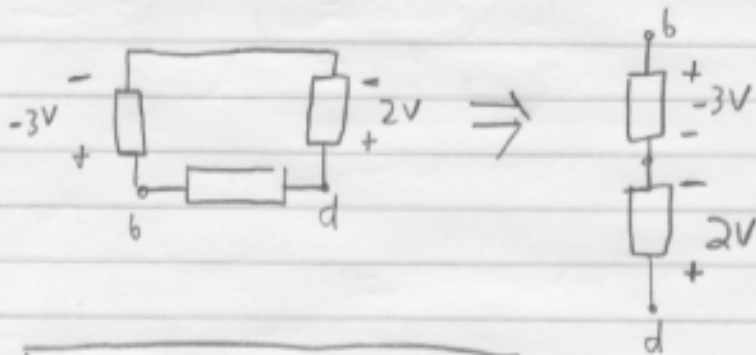
ii)  $V_{bd}$  - look at the center of the circuit



$V_{bd} = (-3V) - (2V) = -5V$

$V_{bd} = -5V$

3) Remember the passive sign convention

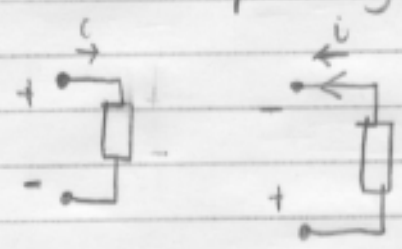

$p > 0$  - power is delivered to the box  
 $p < 0$  - power is extracted from the box


a) elements a, c, e, f are following the passive sign convention  
 b, d do not

b)	element	passive sign convention	V	I	$V \cdot i$
	a	yes	-8	7	$(-8)(7)$
	b		-2	-7	$(-2)(-7)$
	c	yes	10	15	$(10)(15)$
	d		10	5	$(10)(5)$
	e	yes	-6	3	$(-6)(3)$
	f	yes	-4	3	$(-4)(3)$

element	power
a	-56
b	-14
c	150
d	-50
e	-18
f	-12


Total Power Delivered - 150 Watts  
 Total Power Absorbed - 150 Watts

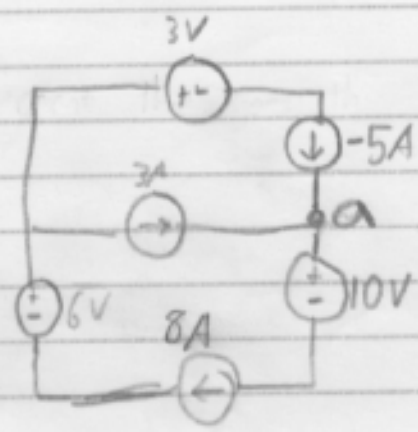4) This connection is invalid.  
 Look at point a. 8 amps are leaving the point, and  $(3 + (-5))$  amps are going into point a. Therefore, there is a contradiction because a wire cannot absorb charge.



KCL at point a.  
 $0 \neq 3 - 5 - 8$

5)  $i_1 = 20A$   $i_2 = 15A$

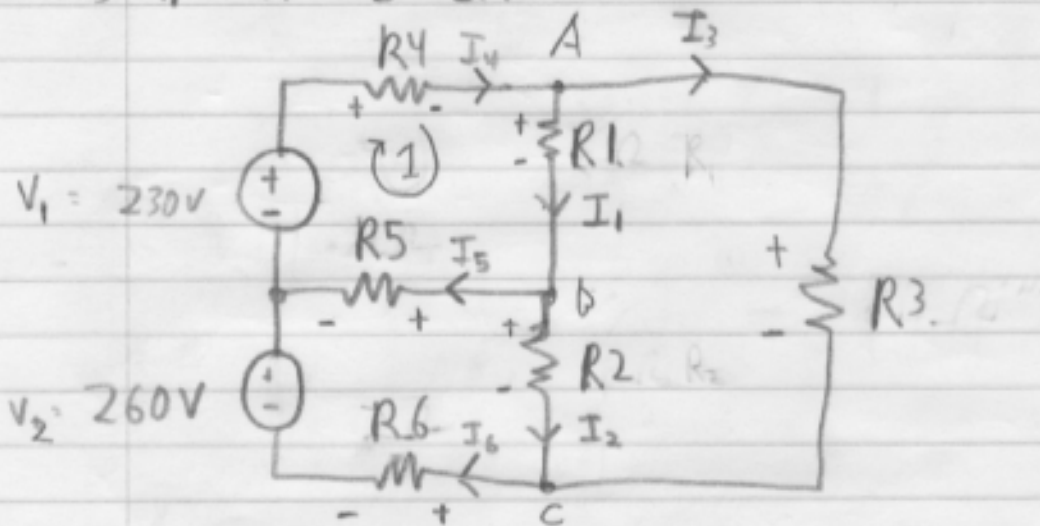

$V=RI$   $P=IV=I^2R$

$I_1 = 20A$   $I_2 = 15A$  KCL  $\Rightarrow 0 = I_1 - I_2 - I_5 \Rightarrow I_5 = 5A$   
@ B

KVL Loop 1  $0 = -230V + I_4 R_4 + I_1 R_1 + I_5 R_5 \Rightarrow I_4 = 25A$

KCL at point A.  $0 = I_4 - I_3 - I_1 \Rightarrow I_3 = 5A$

KCL at point C  $0 = I_3 + I_2 - I_6 \Rightarrow I_6 = 20A$

KCL

KCL

Power supplied by  $V_1 = P_{V1} = V_1 \cdot I_4 = (230)(25) = 5750 W$

"  $V_2 = P_{V2} = V_2 \cdot I_6 = (260)(20) = 5200 W$

" absorbed "  $R_1 = I_1^2 R_1 = 3200 W$

" " "  $R_2 = I_2^2 R_2 = 3600 W$

$R_3 = I_3^2 R_3 = 200 = 2000 W$

$R_4 = I_4^2 R_4 = 1250 = 12500 W$

$R_5 = I_5^2 R_5 = 100 = 1000 W$

$R_6 = I_6^2 R_6 = 800 = 8000 W$

Total Power absorbed = 10950 W

" Power supplied = 10950 W

Note: Power absorbed should always equal power supplied