

EECS 40 Homework #2 Solutions Fall 2003


Problem 1

c) Start off with what we know:

Bulb rated for power = 20W and works with voltage supply = 12 V DC

Model our circuit as shown in the figure below:

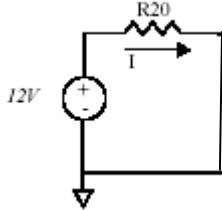
- Voltage supply is modeled as an ideal independent voltage source supplying 12V
- Light bulb is modeled as a resistor



Then $P = VI$ or $P = V^2/R_{20}$ so solving for R_{20} , we get $R_{20} = V^2/P$ which implies:
 $R_{20} = 144/20 [(J/C)^2/J/s] = 7.2 [(J/C)/(C/s)] = 7.2\Omega$

Similarly, for a light bulb rated for 50W operation, $R_{50} = 144/50 [V/A] = 2.9\Omega$

b)

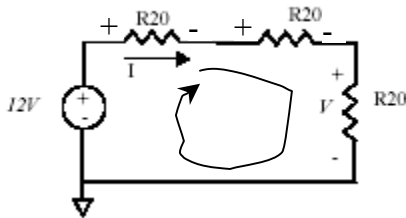

Note that we have three resistors in series so $R_{eq} = 3 \cdot R_{20} = 3 \times 7.2\Omega = 21.6\Omega$.

Using KVL for the loop shown we get: $I \cdot R_{eq} - 12 [V] = 0$ which implies that:

$$I = 12/21.6 [A] = 0.56 A$$

Then $V = IR_{20} = 0.56 \times 7.2 [A \cdot \Omega] = 4 V$ and the power dissipated in each bulb is given by:

$$P = VI = 4 \times 0.56 [V \cdot A] = 2.2 W$$


c) As in part b) we use KVL for the loop but replace the last resistance with a 50W-rated bulb as shown in the figure of the problem. We get the following equation:

$7.2I + 7.2I + 2.9I [\Omega \cdot A] - 12 [V] = 0$ which implies $I = 0.7A$, and

$V = I \cdot R_{50} = 0.7 \times 2.9 = 2 V$. The power dissipated in the 50W-bulb is:

$$P = V \cdot I = 2V \cdot 0.7A = 1.4 W$$

Problem 2

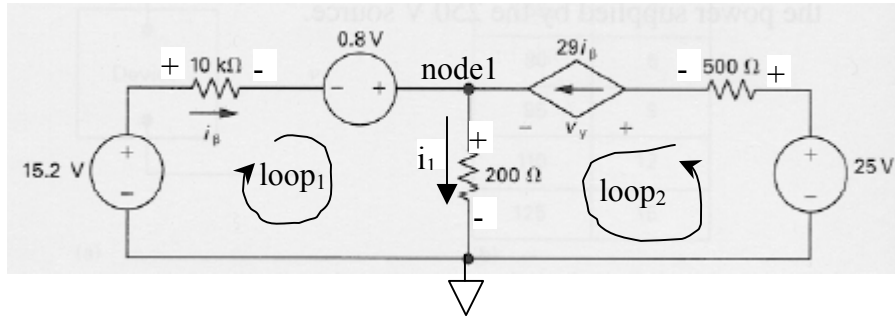

- a) To find the voltage v_y we first need to find the current i_1 and then perform KVL in loop 2. To find i_1 , we perform KCL at node 1 and then use KVL in loop 1.

KCL at node 1: $i_\beta + 29i_\beta = i_1$ which implies $i_1 = 30i_\beta$

KVL at loop 1: $i_\beta \times 10[\text{k}\Omega] - 0.8[\text{V}] + 30i_\beta \times 200[\Omega] - 15.2[\text{V}] = 0$ which gives
 $16\,000 [\Omega] \times i_\beta = 16 [\text{V}]$ which implies $i_\beta = 1\text{mA}$

KVL at loop 2: $30[\text{mA}] \times 200[\Omega] - 25[\text{V}] + 29[\text{mA}] \times 500[\Omega] + v_y = 0$ which gives
 $6 - 25 + 14.5 + v_y = 0$ which implies $v_y = 4.5 \text{ V}$

b)

Element	Power generated	Power absorbed
10 kΩ resistor		$P = I^2R: 1 [\text{mA}^2] \times 10 \text{ k}\Omega = 0.01 \text{ W}$
200 Ω resistor		$P = I^2R: 30^2 [\text{mA}^2] \times 200 \Omega = 0.18 \text{ W}$
500 Ω resistor		$P = I^2R: 29^2 [\text{mA}^2] \times 500 \Omega = 0.42 \text{ W}$
Dep. current source		$P = IV: 29[\text{mA}] \times 4.5 \text{ V} = 0.13 \text{ W}$
15.2 V source	$P = IV: 1\text{mA} \times 15.2 \text{ V} = 0.015 \text{ W}$	
0.8 V source	$P = IV: 1\text{mA} \times 0.8 \text{ V} = 0.0008 \text{ W}$	
25 V source	$P = IV: 29\text{mA} \times 25 \text{ V} = 0.72 \text{ W}$	
TOTAL	0.74 W	0.74 W


Problem 3

- c) We know for any two resistances in parallel we have $R_1 \cdot R_2 / (R_1 + R_2)$ (see equation 3.15 of textbook); if $R_1 = R_2 = R$ then the expression reduces to $R^2 / 2R$ which is equivalent to $R/2$.

- c) For n resistors of value R in parallel, we obtain the following:


$1/R_{eq} = 1/R + 1/R + 1/R + \dots + 1/R$ which implies that $1/R_{eq} = n/R$ or $R_{eq} = R/n$.

- c) We need an equivalent resistance of $5.5\text{k}\Omega$ using only $2\text{k}\Omega$ resistors. To get $0.5 \text{ k}\Omega$ we can put 4 $2\text{k}\Omega$ resistances in parallel: $R_{eq} = 2/4 = 0.5 \text{ k}\Omega$. Now we need to construct $5 \text{ k}\Omega$ circuit that we can put in series with the $0.5 \text{ k}\Omega$ circuit. This can be obtained by putting 2 $2\text{k}\Omega$ resistors in series to get $4 \text{ k}\Omega$ and 2 $2\text{k}\Omega$ in parallel which can be put in series with the rest of the network. Our network is shown below; all the resistors shown are $2\text{k}\Omega$.

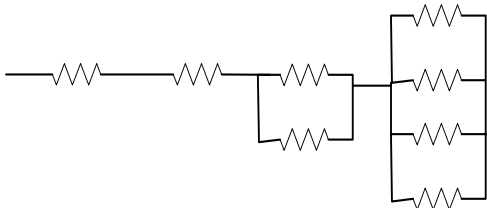

Problem 4

a)

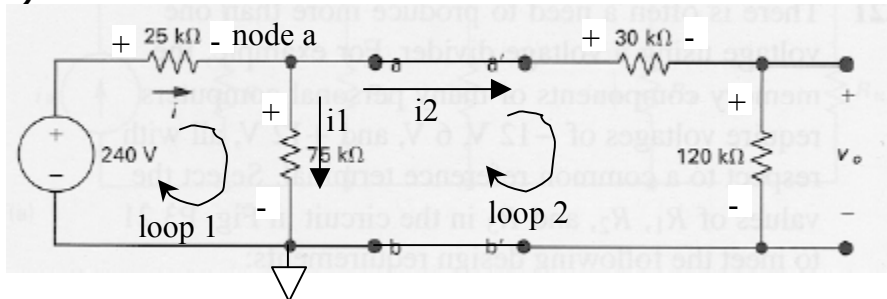


KVL at loop 2: $30\,000 \times i_2 + 120\,000 \times i_2 - 75\,000 \times i_1 = 0$ implies that $i_1 = 2 \times i_2$

Then KCL at node a: $i = i_1 + i_2$ implies that $i = 3 \times i_2$

KVL at loop 1: $25\,000 \times i + 75\,000 \times i_1 - 240 = 0$ and substituting for i_1 and i in terms of i_2 , we obtain $225 \times i_2 = 240$ which implies $i_2 = 1.07 \text{ mA}$.

Then $v_o = i_2 \times 120\,000 = 1.07 \text{ mA} \times 120\,000 = 128 \text{ V}$.

b)

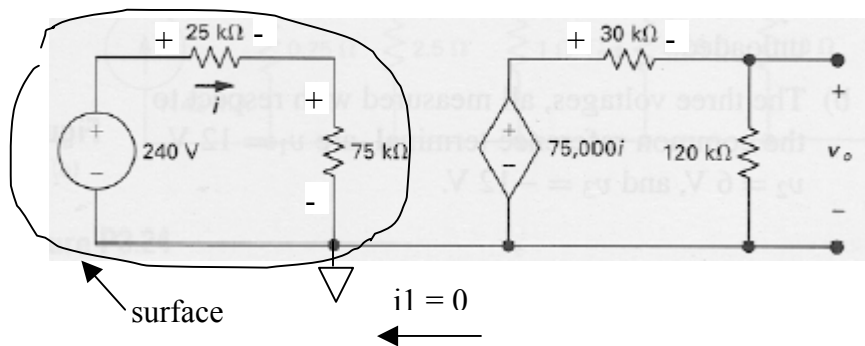


Using the voltage divider formula, the voltage across the $75\text{k}\Omega$ resistor is given by: $(75/100) \times 240 \text{ V} = 180 \text{ V}$. This implies that: $i = 180/75\,000 = 2.4 \text{ mA}$.

Then the dependent voltage source is $75\,000 \times 2.4 = 180 \text{ V}$. Using the voltage divider formula again for the second part of the circuit, v_o is given by $(120/150) \times (75\,000 \times i) = 144 \text{ V}$.


c) It has no effect since the current $i_1 = 0$.

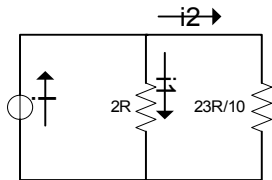Problem 5

First reduce the circuit given to the one below using series and parallel resistance rules. $2R \parallel 2R$ is simply R . Then R in series with R is $2R$. $3R \parallel 3R$ is $3R/2$. $R \parallel 4R$ is $4R/5$. Then $3R/2$ in series with $4R/5$ is $23R/10$. Then we obtain the i_2 in terms of i using the current divider rule: $i_2 = i \times 2R / (2R + 23R/10) = 20i/43$.



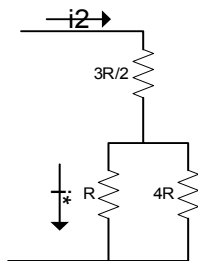Then we use the current divider rule again for the portion of the circuit on the right shown below



So we get $i^* = i_2 \times 4R/5R = (20i/43) \times (4/5) = 16i/43$