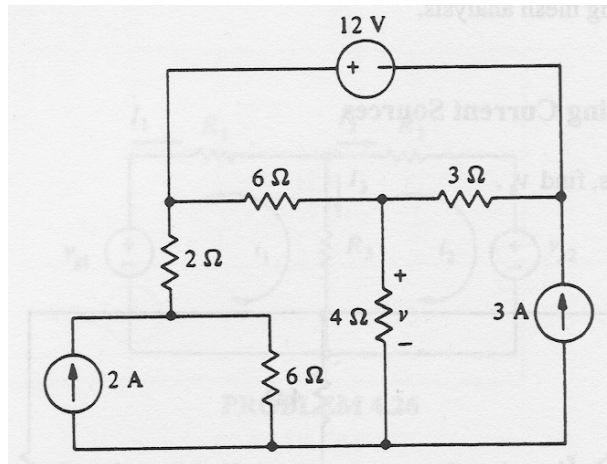


Homework Assignment #3

Due at 11 AM in 240 Cory on Friday, 9/19/03

* Be sure to put your name and **Discussion Section number** on your paper

Problem 1: Circuit Analysis Methods




Find the current in the 3 Ω resistor

- a) using the node-voltage method.
- b) using the mesh-current method.


Problem 2: Nodal Analysis of a circuit with dependent sources

Find the power absorbed by the 8 Ω resistor in the circuit below, using nodal analysis.

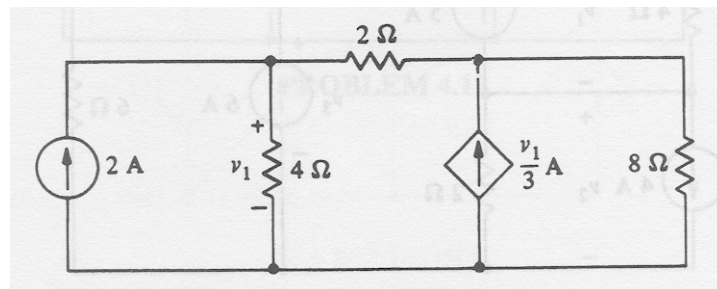


Problem 3: Source Transformation

Use a series of source transformations to find i_o in the following circuit:

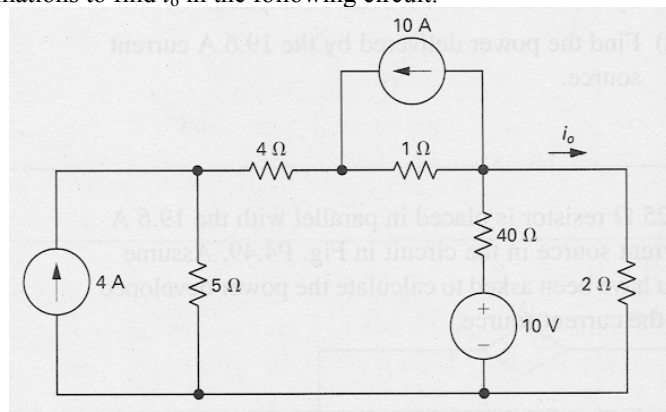

Problem 4: Thévenin Equivalent Circuit


Given the following circuit:

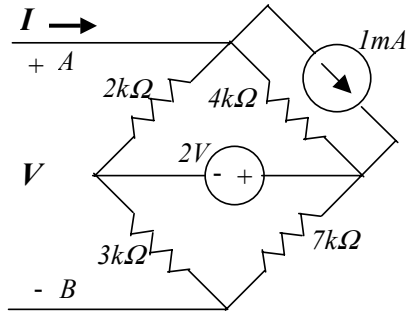

- Find the Thévenin equivalent with respect to the terminals A,B:
- Plot the I - V characteristic for this circuit.
- What is the power delivered by the circuit if a $5\text{ k}\Omega$ resistor is connected between A and B?

Problem 5: Superposition

Consider the following circuit:

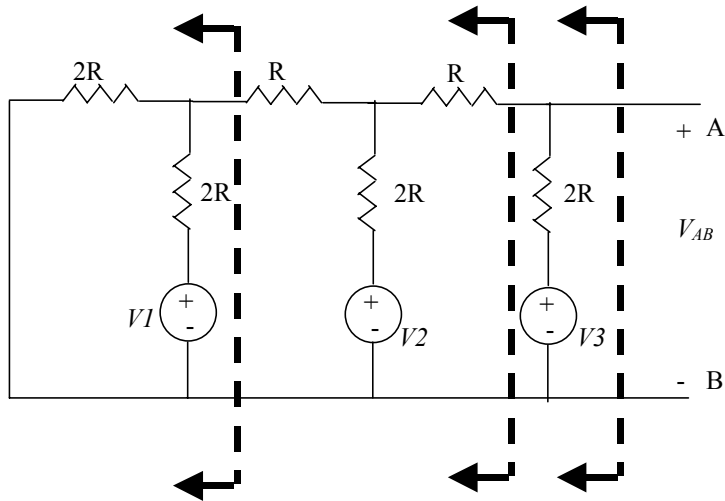

- Find V_{AB} using superposition.
- Find V_{AB} by applying Thévenin's theorem successively to the circuit to the left of the dotted lines.