

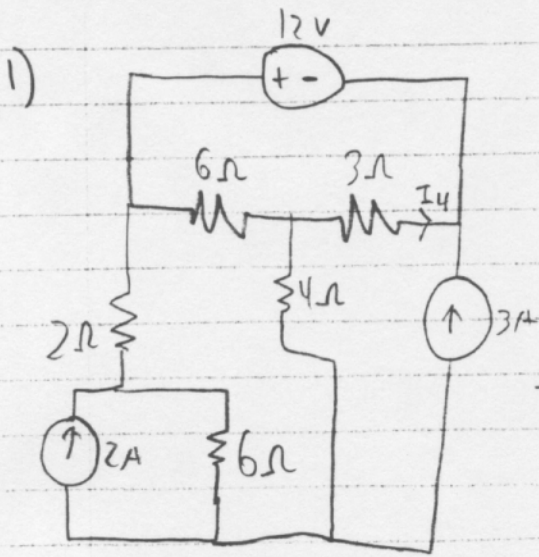


Homework #3: Solutions

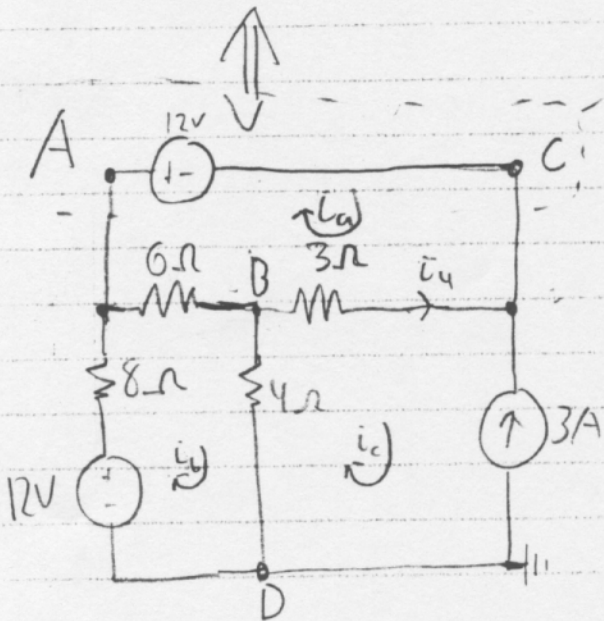

USING SOURCE TRANSFORMATION

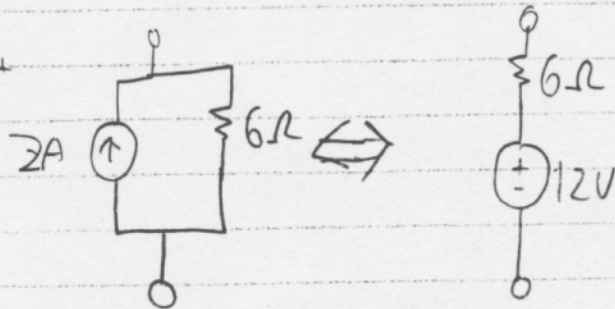

SUPERNODE

a) NODE-ANALYSIS

$$(1) \left(\frac{V_A - 12}{8} \right) + \left(\frac{V_A - V_B}{6} \right) + \left(\frac{V_C - V_B}{3} \right) - 3 = 0 \quad (A)$$

$$(2) \left(\frac{V_B - V_A}{6} \right) + \left(\frac{V_B - V_C}{3} \right) + \left(\frac{V_B}{4} \right) = 0 \quad (B)$$

$$(3) V_A - V_C = 12$$

$$\therefore V_A = 20 \quad V_B = V_C = 8V$$

$$\therefore i_4 = \frac{V_B - V_C}{3} = \boxed{0A}$$

b) MESH ANALYSIS

Loop ACBA: $12V + 3(i_a - i_c) + 6(i_a - i_b) = 0$

Loop ABDA: $-12 + 8i_b + 6(i_b - i_a) + 4(i_b - i_c) = 0$


$i_c = -3A$

$i_a = -3A$

$i_b = -1A$

$i_c = -3A$

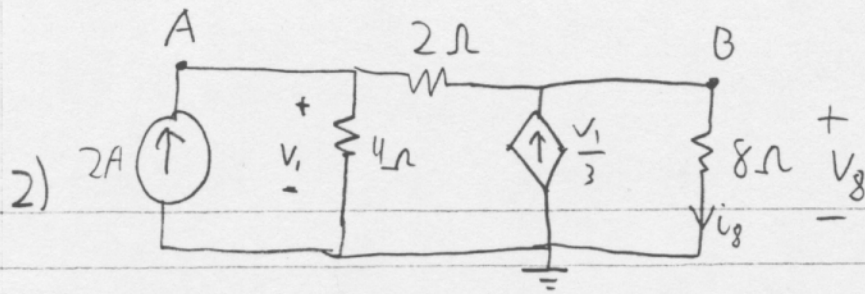$\Rightarrow \boxed{i_4 = i_c - i_a = 0A}$




NODE ANALYSIS at A & B :


Node A: $2 - \frac{V_1}{4} - \frac{V_1 - V_8}{2} = 0$ $\Rightarrow V_8 = 32V$

Node B: $\frac{V_1}{3} - \frac{V_8 - V_1}{2} - \frac{V_8}{8} = 0$ $V_1 = 24V$

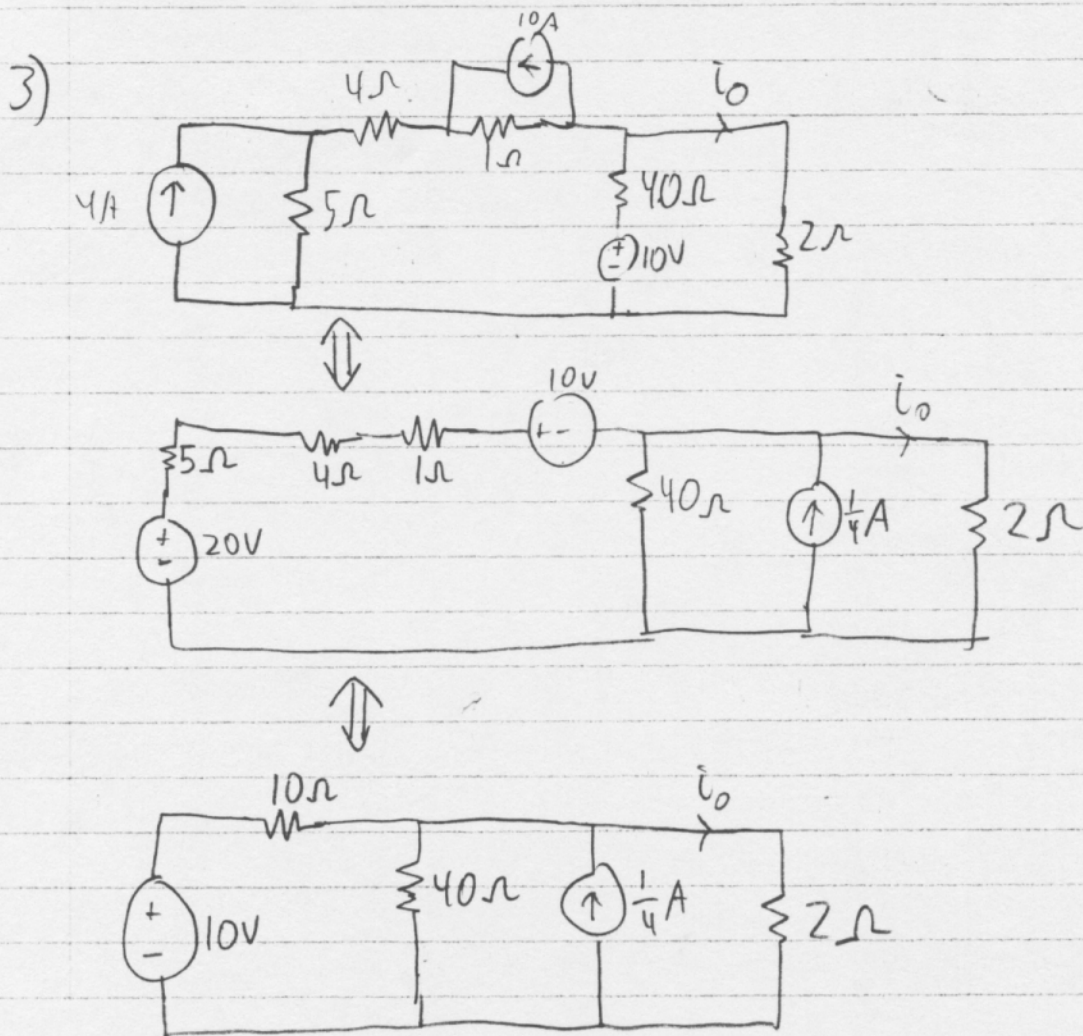$P = I \cdot V = \frac{V^2}{R} = \frac{32^2}{8\Omega} = 128 \text{ Watts}$
 The 8Ω resistor is absorbing 128 Watts




EQUIVALENTLY,

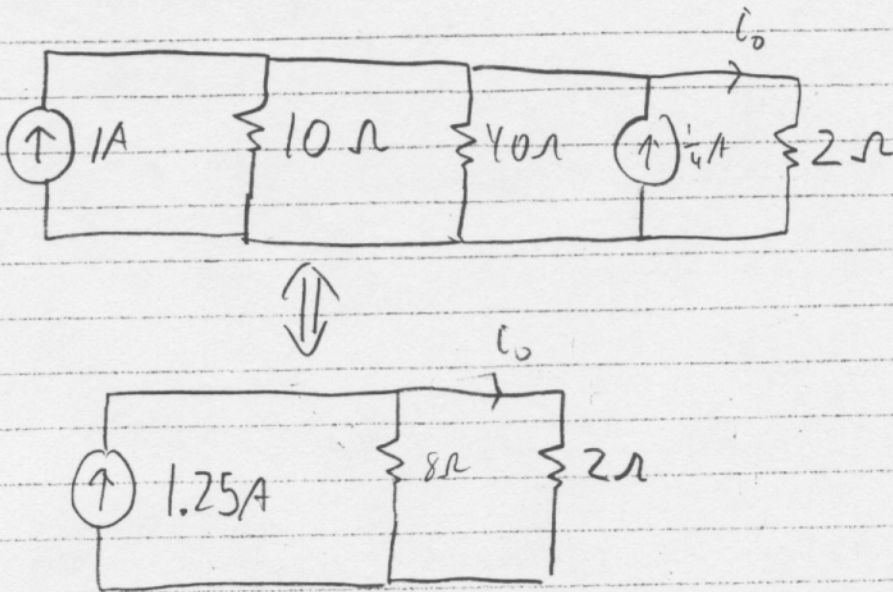

CURRENT DIVIDER
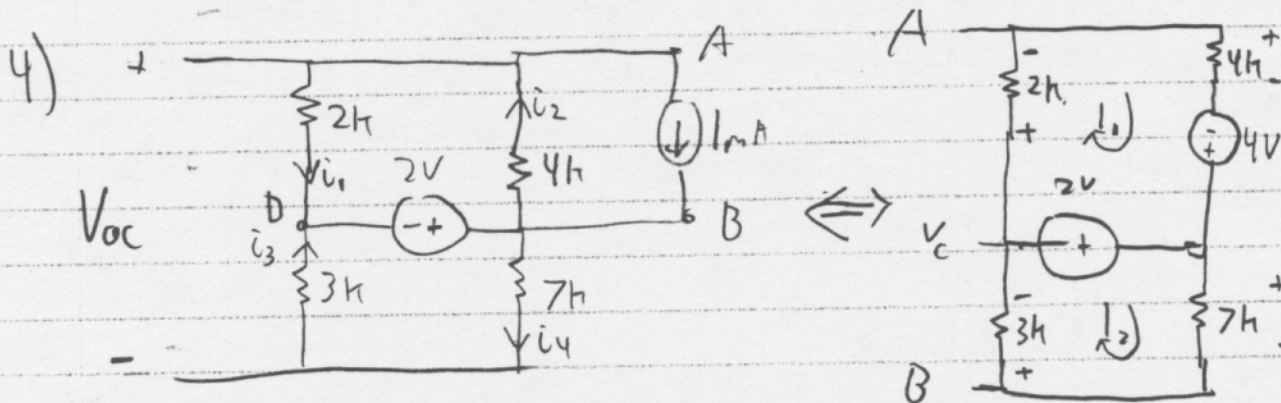
$$i_o = \left(\frac{5}{4}\right) \left(\frac{8}{8+2}\right) = 5 \left(\frac{2}{10}\right) = \boxed{1A}$$



Mesh Analysis

$$0 = -4V + 2V + 2k i_1 + 4k i_1 \Rightarrow i_1 = \frac{2}{6} \text{ mA}$$

$$0 = -2 + 7k i_2 + 3k i_2 \Rightarrow i_2 = \frac{2}{10} \text{ mA}$$


$$V_b - V_c = (3k)(i_2) = .6 \text{ V}$$

$$V_c - V_a = (2k)(i_1) = .66 \text{ V}$$

$$V_{AB} = V_{OC} = V_{TH}$$


$$-(V_c - V_a) - (V_b - V_c) = V_a - V_b = -1.266 \text{ V}$$

R_{TH} - turn off all sources

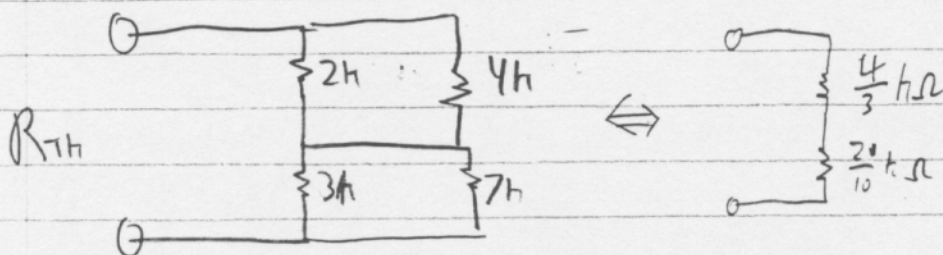

$$R_{TH} = \left(\frac{10^3}{30}\right) k\Omega = 3.43 k\Omega$$


THEVENIN EQUIVALENT

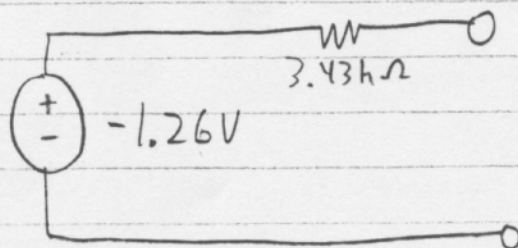


b) I-V $V = V_{TH} + iR = -1.26 + 3430i$

4) part b)

5

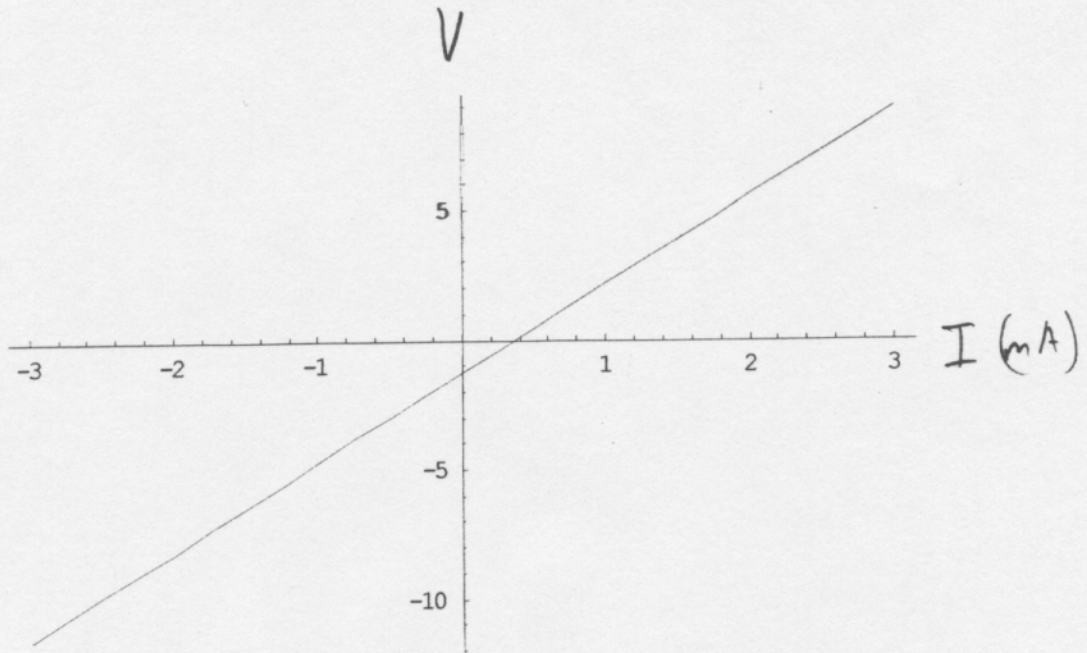

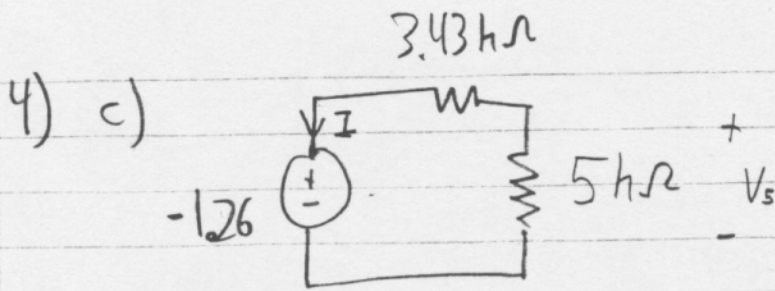




$$I = \frac{-V}{R} = \frac{+1.26}{(3.43 + 5)k} = +.1502 \text{ mA}$$

PASSIVE
SIGN
CONVENTION

$$P = IV = (-1.26)(.1502) \text{ mW} = -.189 \text{ mW}$$

(Power is being delivered)

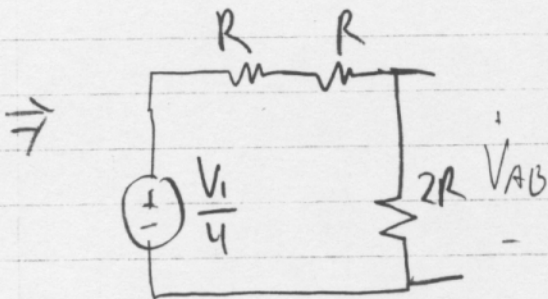
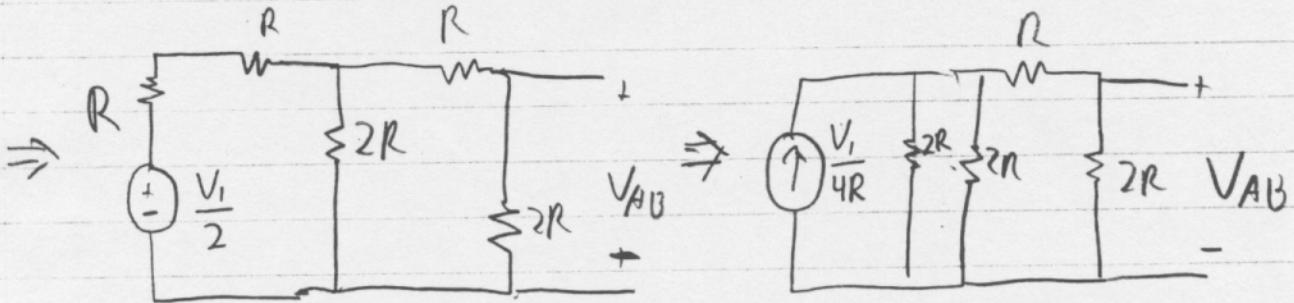
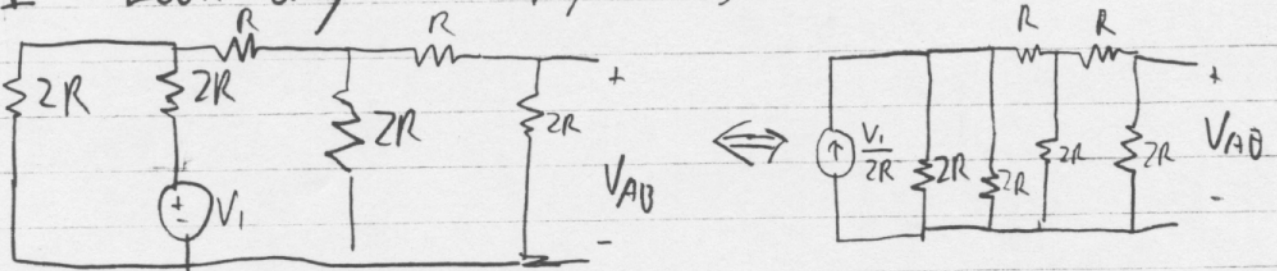
5) 1st - Look only at V_1 ; $V_2 = V_3 = 0$



VOLTAGE DIVIDER



$$V_{AB}^{(1)} = \left(\frac{V_1}{4}\right) \left(\frac{2R}{2R + 2R}\right) = \frac{V_1}{8}$$

2nd $V_1 = V_3 = 0$

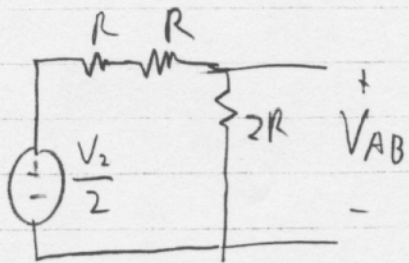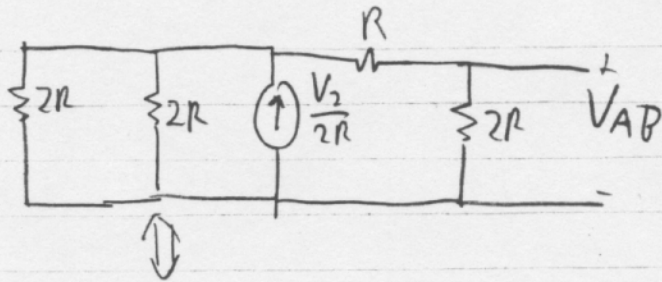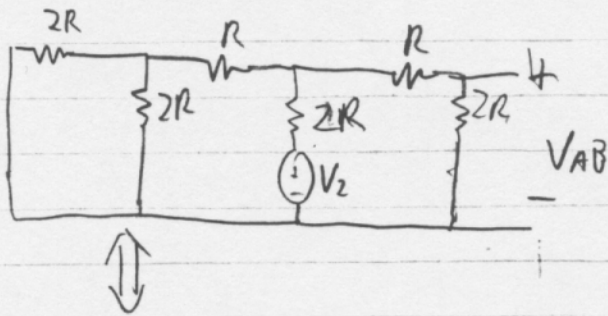

$$V_{AB}^{(2)} = \left(\frac{V_2}{2}\right) \left(\frac{2R}{2R+2R}\right) = \frac{V_2}{4}$$

3rd $V_1 = V_2 = 0$

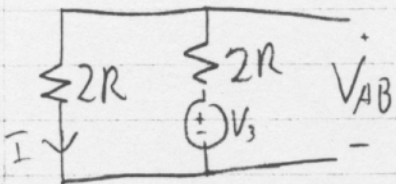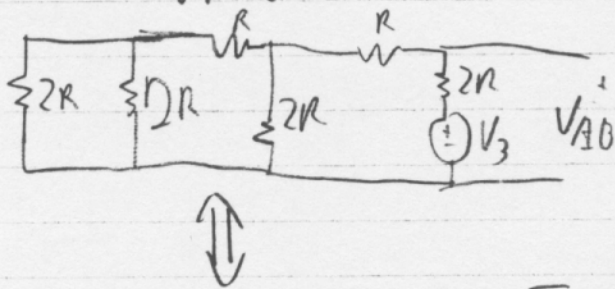


$$I = \frac{V_3}{4R}$$

$$V_{AB}^{(3)} = (2R)(I) = \frac{V_3}{2}$$


$$\therefore V_{AB} = V_{AB}^{(1)} + V_{AB}^{(2)} + V_{AB}^{(3)} = \boxed{\frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2}}$$

b) 1st look at the far left part

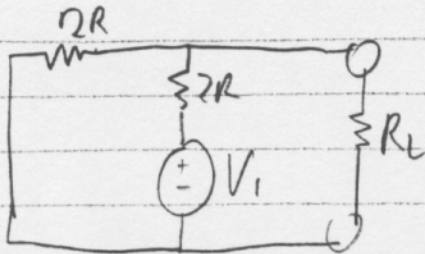


$$R_{TH} = R \quad (\text{set } V_1 = 0)$$

$$V_{TH} = V_{OC} = \frac{V_1}{2}$$

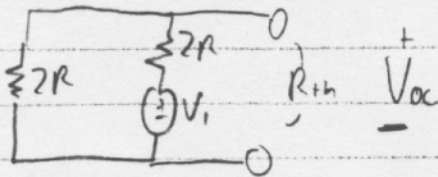

2nd look at next part

$$\text{set } V_2 = V_{TH}^{(1)} = 0$$

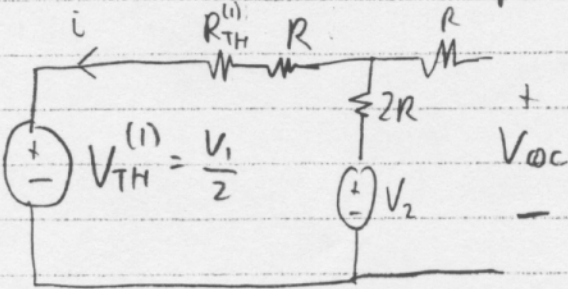


$$R_{TH}^{(2)} = (2R \parallel 2R) + R = 2R$$

$$i = \frac{V_2 - \frac{V_1}{2}}{4R}$$

$$V_{OC} = V_{TH}^{(2)} = \left(\frac{V_1}{2}\right) + i \cdot 2R = \frac{V_1}{4} + \frac{V_2}{2}$$

3rd

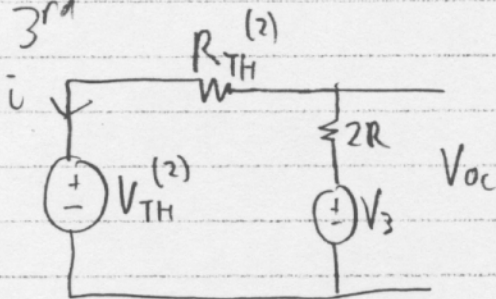

$$i = \frac{V_3 - V_{TH}^{(2)}}{4R}$$

$$V_{AB} = V_{OC} = V_{TH}^{(2)} + R_{TH}^{(2)} i = \left(\frac{V_1}{2}\right) + (2R) \left(\frac{V_3 - V_{TH}^{(2)}}{4R}\right) = \frac{V_{TH}^{(2)}}{2} + \frac{V_3}{2}$$

$$= \frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2}$$