


Homework Assignment #4

Due at 11 AM in 240 Cory on Friday, 9/26/03

* Be sure to put your name and **Discussion Section number** on your paper; **otherwise 5 pts will be deducted from your score!**

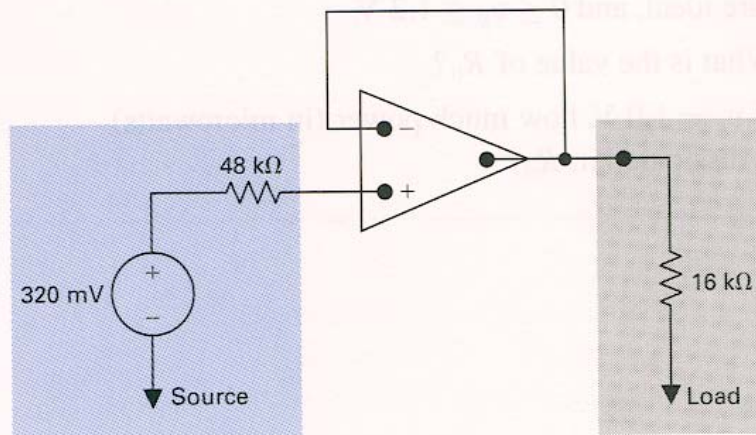Problem 1: Voltage Follower


Assume that the ideal op amp in the circuit below is operating in its linear region.



- Calculate the power delivered to the $16\text{ k}\Omega$ load resistor
- Repeat (a) with the op amp removed from the circuit, that is, with the $16\text{ k}\Omega$ resistor connected directly in series with the voltage source and the $48\text{ k}\Omega$ resistor.
- What is the ratio of the power found in (a) to that found in (b)?
- Does the insertion of the op amp between the source and the load serve a useful purpose? Explain.

Problem 2: Ideal Op Amp Circuit Analysis


Given the following circuit:

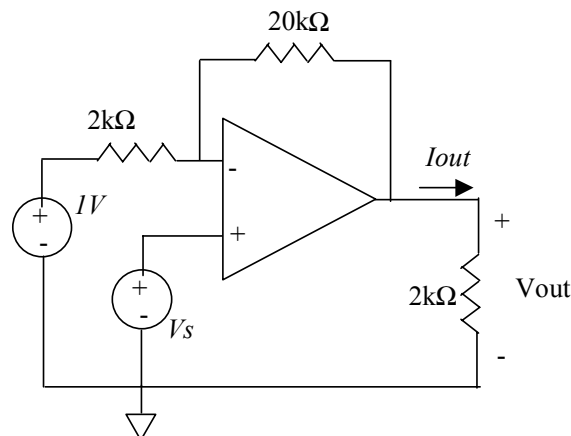

- Find V_{out} as a function of V_s , assuming that the op amp is ideal and operating in its linear region.
- Due to supply voltage limitations, $0V \leq V_{out} \leq 10V$. Plot V_{out} vs. V_s .


Problem 3: Non-Inverting Summing Amplifier Circuit Design

Assume the op amp in the circuit below is ideal and operating in the linear region. Design the circuit so that $v_o = 4v_a + 2v_b + v_c$. (Specify the numerical values of R_b , R_c , and R_f .)

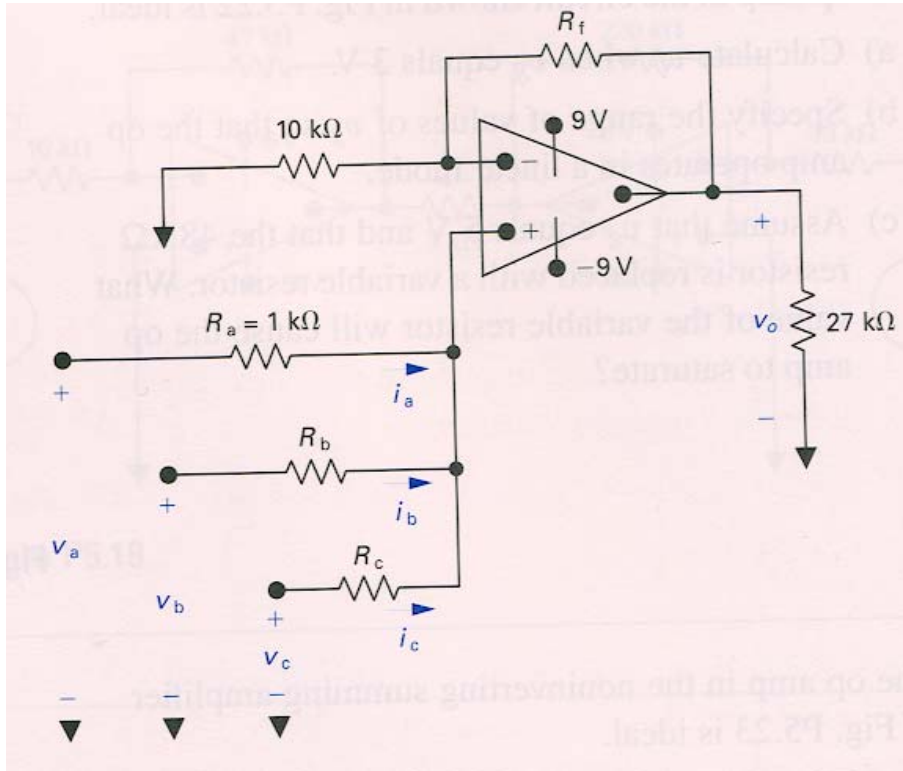

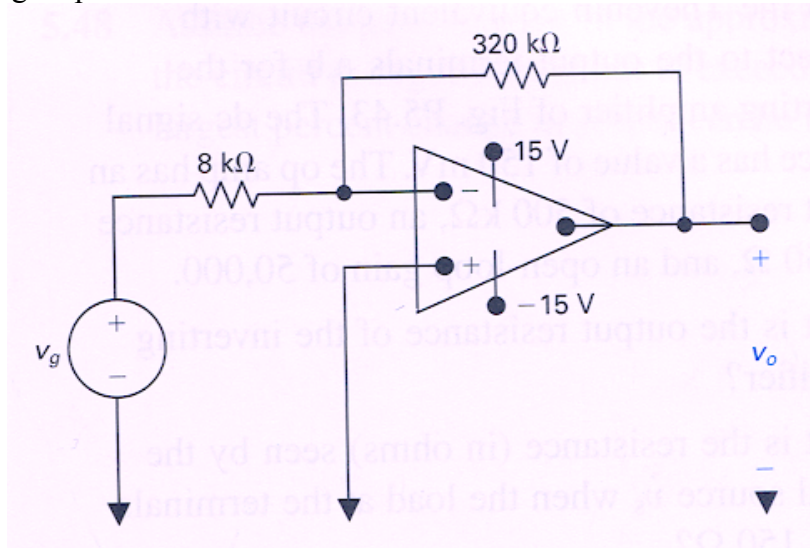Problem 4: Realistic Op Amp

Consider the inverting amplifier circuit below.



The op amp has input resistance $R_i = 400 \text{ k}\Omega$, output resistance $R_o = 2 \text{ k}\Omega$, open-loop gain $A = 500,000$. Assume that the op amp is operating in its linear region. **Also suppose that the amplifier is loaded with a 1 kΩ resistor.**

- a) Calculate the voltage gain (v_o/v_g) of the amplifier.
- b) Repeat (a) assuming the op amp is ideal.