


EE40

HW#5 Soln.

1) a)  $C = 10 \mu\text{F}$   $V = 20\text{V}$

$$Q = VC = .2 \text{ mC}$$


$$E = \frac{1}{2} CV^2 = 2 \text{ mJ}$$

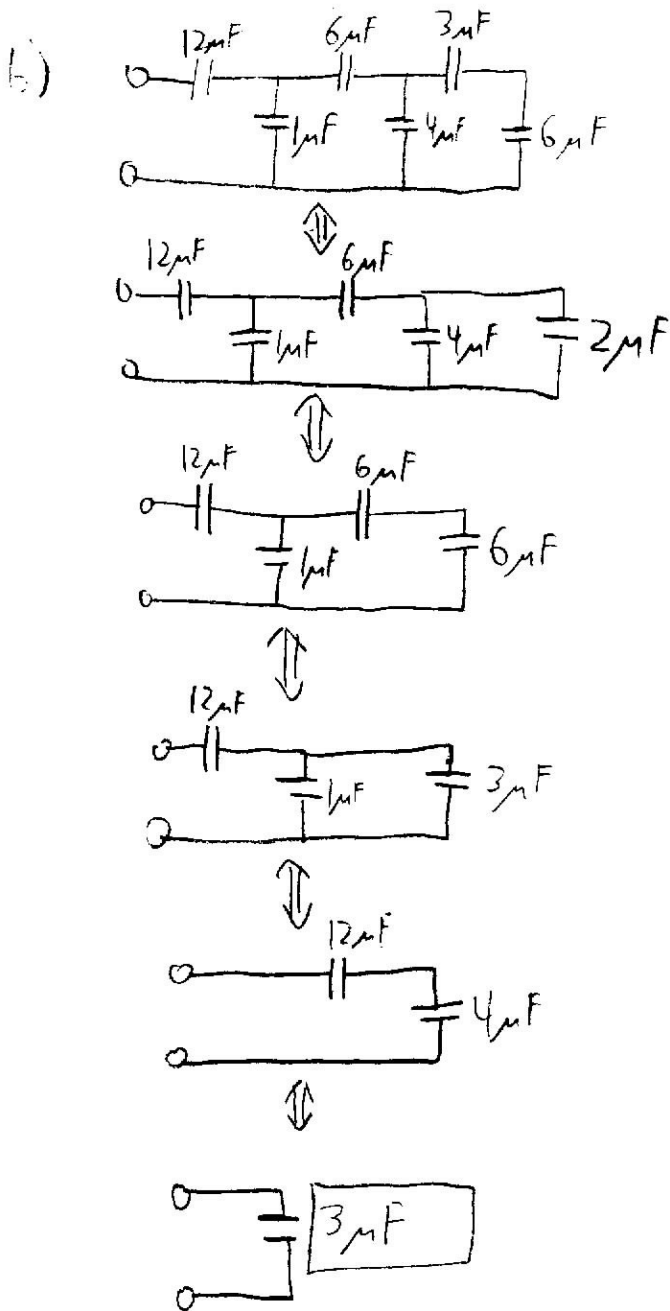


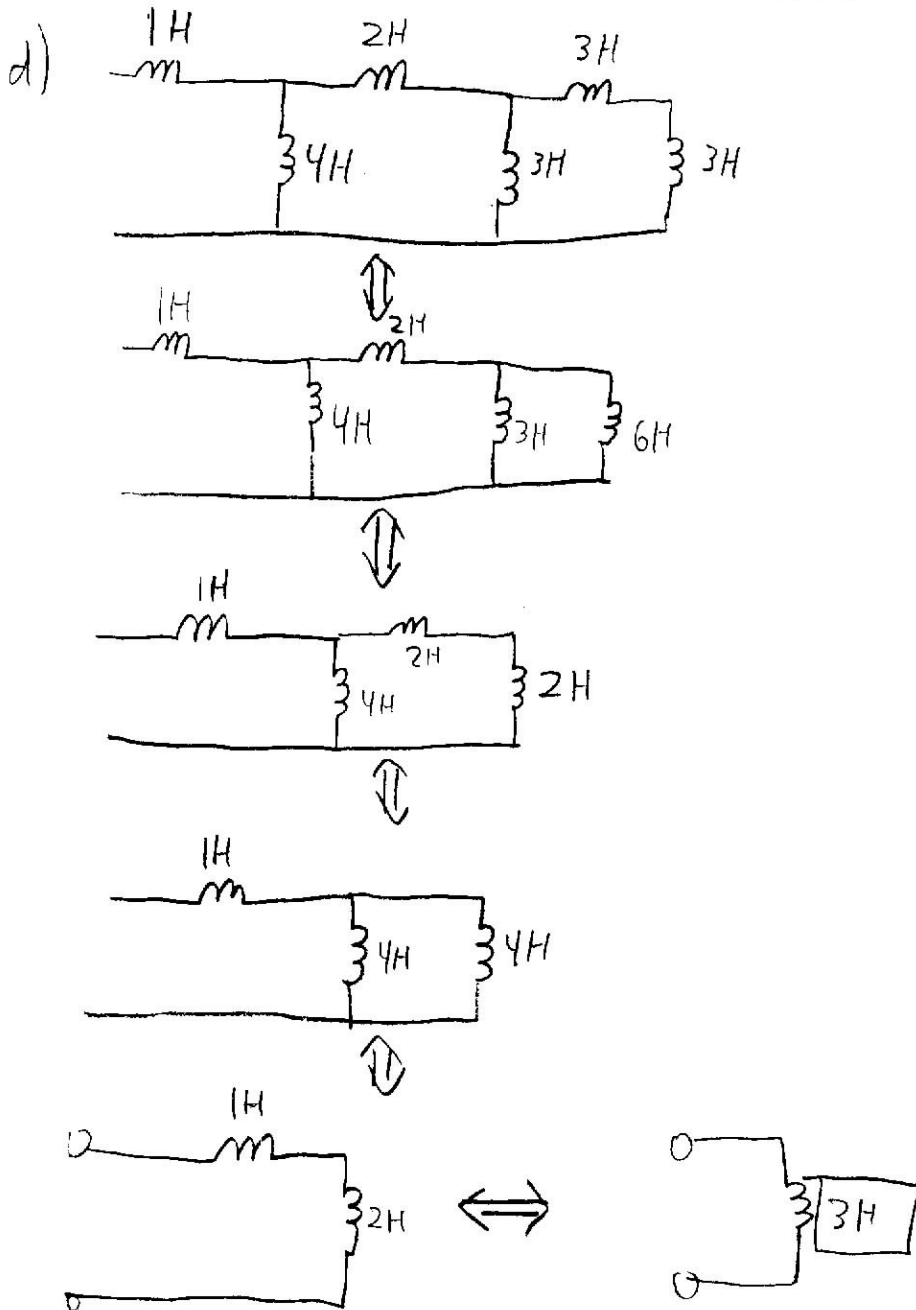c)  $L = 5\text{mH}$     $i = 200\text{mA}$

$$\lambda = Li = (5\text{mH})(200\text{mA}) = \boxed{1\text{mWb}}$$

$$E = \frac{1}{2}Li^2 = \left(\frac{1}{2}\right)(5 \cdot 10^{-3}\text{H})(.2\text{A})^2 = \boxed{.1\text{mJ}}$$



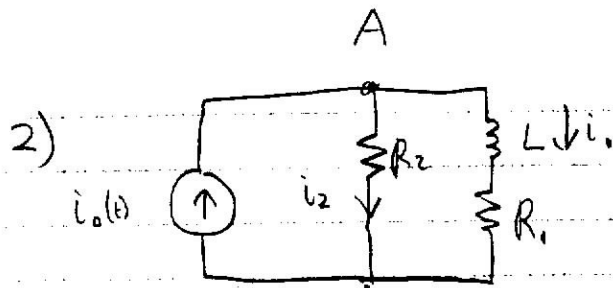

at steady-state  
the inductor becomes  
a short

$$i_o(t < 0) = -1 \text{ mA} \quad i_o(t > 0) = 2 \text{ mA}$$

$$R_1 = 2 \text{ k}\Omega \quad R_2 = 3 \text{ k}\Omega \quad L = 20 \text{ mH}$$

$$a) \quad i_1(0^-) = \left( \frac{R_2}{R_1 + R_2} \right) i_o(0^-) = \left( \frac{3}{2+3} \right) (-1 \text{ mA}) = -0.6 \text{ mA}$$

$$i_1(0^+) = i_1(0^-)$$

$$i_f = \left( \frac{R_2}{R_1 + R_2} \right) i_o(\infty) = \left( \frac{3}{5} \right) (2 \text{ mA}) = 1.2 \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{20 \text{ mH}}{(R_1 + R_2)} = 4 \mu\text{sec} \quad t_0 = 0$$

$$i_1(t) = i_f + [i_1(0^-) - i_f] \exp\left\{-\frac{(t-t_0)}{\tau}\right\} \quad t > 0$$

$$i_2(t) = i_o(t) - i_1(t) = .8 + 1.8 \exp\left\{-\frac{t}{4}\right\} \text{ mA} \quad t > 0$$

$$V_A = R_2 i_2(t) \quad t > 0$$

$$V_A(t) = 2.4 + 5.4 \exp\left(-\frac{t}{4 \mu\text{sec}}\right) \text{ V} \quad t > 0$$


b) at  $t = 5\tau$  the transient is  $\approx .6\%$  of its initial value

$$V_A(5\tau) = 2.4 + 5.4 \exp\left(-\frac{5\tau}{\tau}\right) = 2.43 \text{ V}$$

$$5\tau = 20 \mu\text{sec}$$

$$c) \quad V_A(t < 0) = (R_2)(i_o(t < 0) - i_1(t < 0)) = 3 \text{ k}\Omega \cdot (-.4 \text{ mA}) = -1.2 \text{ V}$$

3)

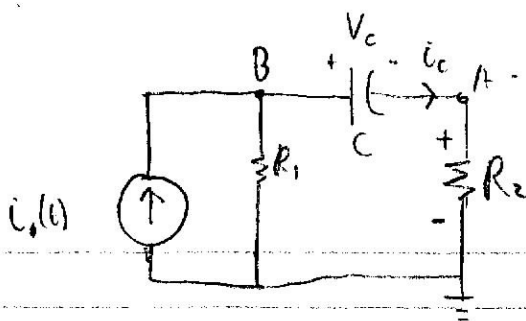

$$i_s(t < 0) = 4 \text{ mA}$$

$$i_s(t > 0) = 0 \text{ mA}$$

$$R_1 = 500 \Omega$$

$$R_2 = 1500 \Omega$$

$$C = 1 \mu\text{F}$$

at steady state the cap. becomes an open

$$V_c(t < 0) = V_B - V_A = (4 \text{ mA})(500) - 0 = 2 \text{ V}$$

$$V_c(0^-) = V_c(0^+) = 2 \text{ V}$$

$$V_c(\infty) = V_B - V_A = (0 \text{ mA})(500) - 0 = 0 \text{ V}$$

$$\tau = (R_1 + R_2)C = 2 \text{ msec} \quad t_0 = 0$$


$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] \exp(-t/\tau) \quad t > 0$$



$$V_c(t) = \begin{cases} 2 \text{ V} & t < 0 \\ 2 \exp(-t/2 \text{ msec}) \text{ V} & t \geq 0 \end{cases}$$

$$V_A = i_c R_2 = R_2 C \frac{dV_c}{dt} = \begin{cases} 0 & t < 0 \\ -1.5 \cdot \exp\left(\frac{-t}{2 \text{ msec}}\right) & t \geq 0 \end{cases}$$

b) the transient dies down  $\sim 5\tau = 10 \text{ milliseconds}$

c) 10's of Volts

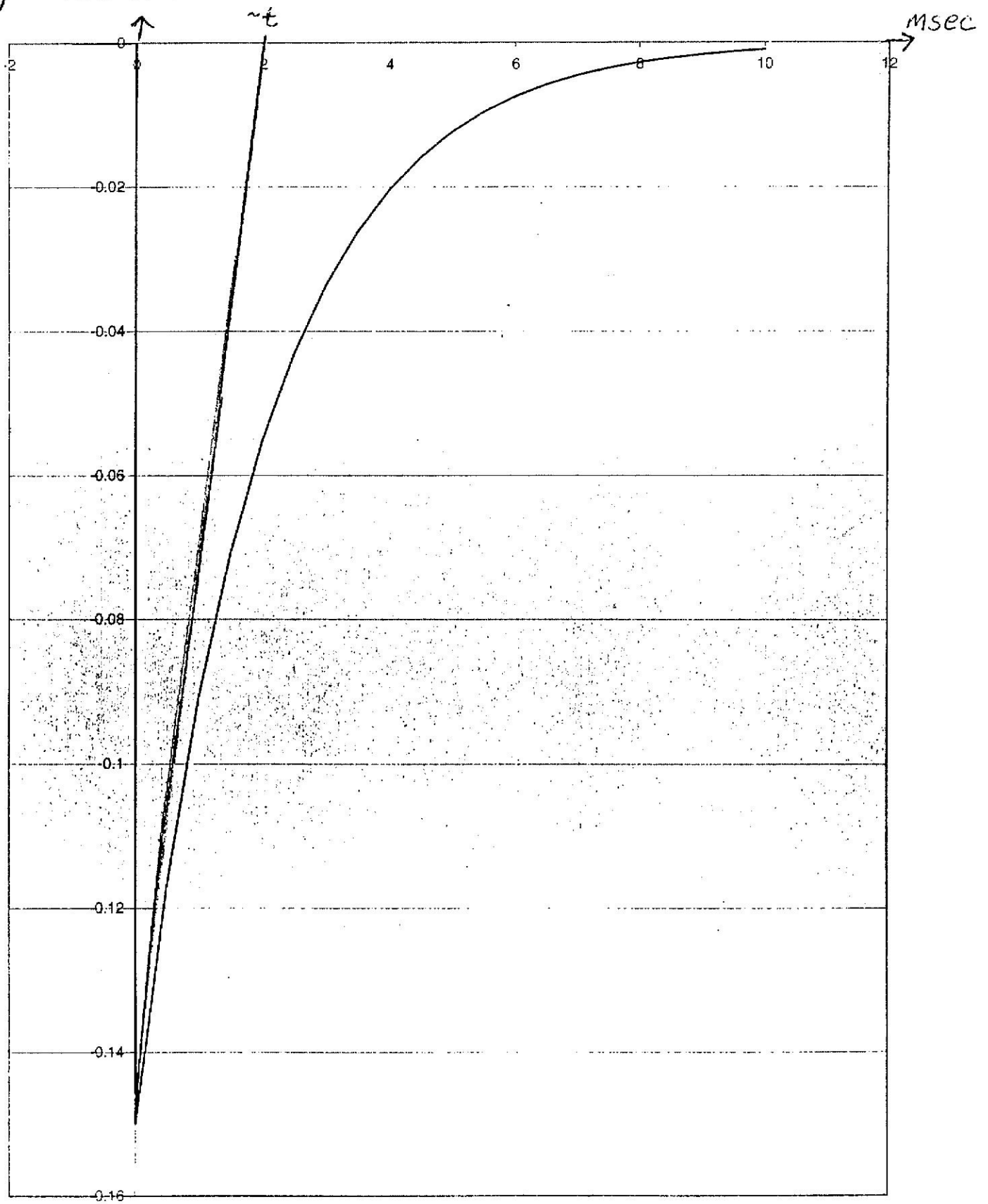

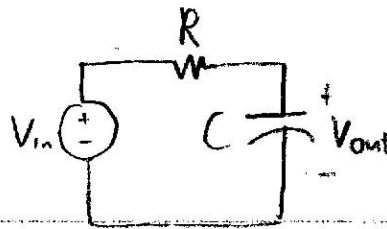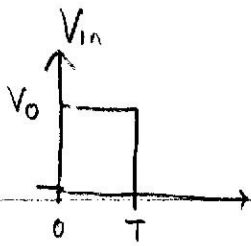

4)

- a) analyze, assuming that  $V_{in}(t > 0) = V_0$   
 $V_{out}(0) = xV_0 = V_{out}(0^+)$   
 $V_{out}(\infty) = V_0$  (the cap becomes an open)  
 $\tau = RC \quad t_0 = 0$

$$V_{out}(t) = V_{out}(\infty) + [V_{out}(0^+) - V_{out}(\infty)] \exp(-(t-t_0)/\tau) \quad T \nless t > 0$$

$$V_{out}(t) = V_0 + [xV_0 - V_0] \exp(-t/RC) \quad 0 < t < T$$

- b)  $t_0 = T \quad \tau = RC$  analyze assuming  $V_{in}(t > T) = 0$   
 $V_{out}(T) = V_{out}(T^+) = V_0 [1 + [x-1] \exp(-T/RC)]$

$$V_{out}(\infty) = 0$$

$$V_{out}(t) = V_{out}(T^+) \exp(-(t-T)/RC) \quad t > T$$

- c) let  $V_{out}(2T) = xV_0 \quad \therefore$  the output will be periodic

Let  $V_{out}(T^+)$  be as defined above



$$V_{out}^{(1)}(t) = \begin{cases} V_0 [1 + (x-1) \exp(-t/RC)] & 0 < t < T \\ V_{out}(T^+) \exp(-(t-T)/RC) & T < t < 2T \end{cases}$$

$k \in \mathbb{N}$

$$\max^{(1)}(V_{out}(t)) = V_{out}(T^+)$$

$$\min^{(1)}(V_{out}(t)) = xV_0$$

$$V_0 > V_{out}(T^+) > xV_0 > 0$$

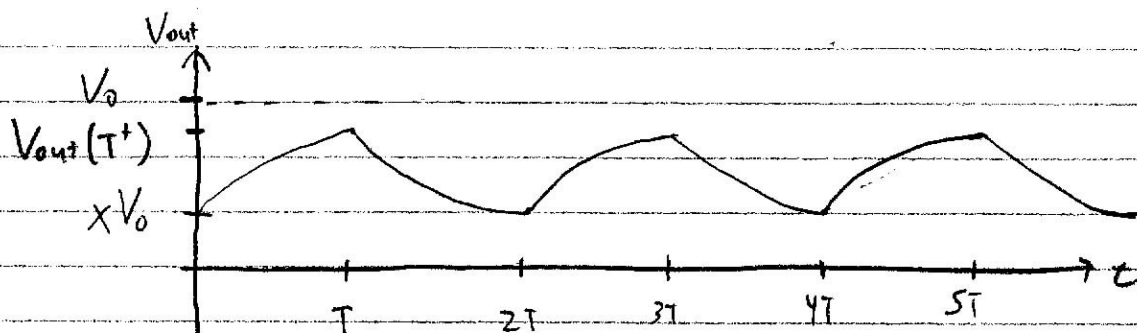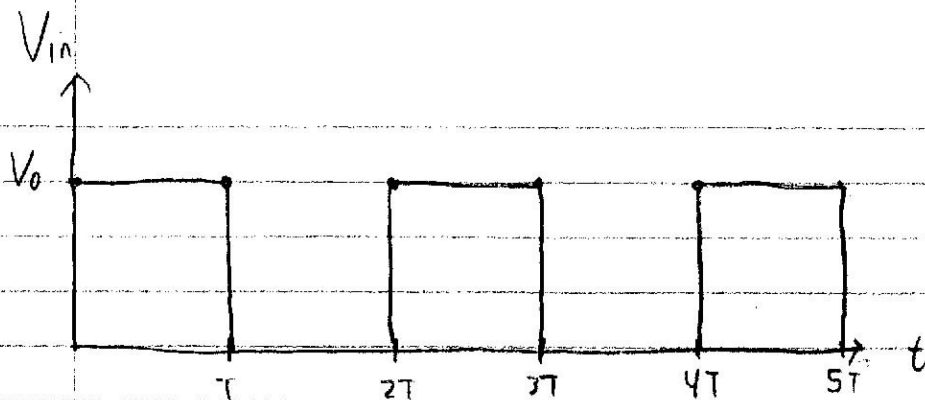

- Solving for  $x$ :

we know  $V_{out}(2T) = V_{out}(0) = xV_0$

$$V_{out}(0) = V_{out}(2T)$$

$$V_0 [1 + (x-1)e^{-T/RC}] = V_0 [1 - (x-1)\exp(-T/RC)] \exp\left(\frac{-(2T-T)}{RC}\right)$$

let  $\alpha = \exp(-T/RC)$

$$x - x\alpha = \alpha + \alpha^2(x-1)$$

$$x = \left( \frac{\alpha - \alpha^2}{1 - \alpha^2} \right) = \left( \frac{1 - \alpha}{\alpha^{-1} - \alpha} \right) = \left( \frac{1 - \exp(-T/RC)}{\exp(T/RC) - \exp(-T/RC)} \right)$$