


Homework Assignment #9

Due at 11:00 AM in 240 Cory on Friday, 11/14/03

* Be sure to put your **Discussion Section number** on your paper; **otherwise 5 pts will deducted from your score!**

Problem 1: Inverter Circuits and Noise Margins

- a) Describe qualitatively how an NMOS inverter circuit (below left) works. Explain how relatively large noise margins NM_H and NM_L can be achieved. (Refer to Slide 6 of Lecture 26 for the definitions of NM_H and NM_L).
- b) Describe qualitatively how a CMOS inverter (below right) works. What are its advantages (with respect to noise margins, power consumption, and size) as compared with the NMOS inverter?

 

Problem 2: CMOS Logic Gates


(Read: pp. 199-202 of Section 6.2.1, Rabaey *et al.*)

A static CMOS logic gate is a combination of two networks: a *pull-up network* of PMOS transistors, and a *pull-down network* of NMOS transistors. The pull-up network provides a connection between the output and the power-supply V_{DD} anytime the output of the logic gate is meant to be **1** (based on the inputs). The pull-down network provides a connection between the output and GND anytime the output of the logic gate is meant to be **0** (based on the inputs). Remember that NMOS devices are turned on with a high (logic **1**) input voltage, whereas PMOS devices are turned on with a low (logic **0**) input voltage, and that transistors connected in series correspond to an AND function, whereas transistors connected in parallel correspond to an OR function. (Refer to Slides 5 & 6 of Lecture 27.)


Design a complex CMOS logic gate to implement the function $F = \overline{(A + B \cdot C)}$

Problem 3: Combinational Logic Circuits

 - a) Write the truth table for the following Boolean expression: $F = \overline{(A + B \cdot C)}$. Draw a logic circuit to realize this expression using AND, OR, and NOT gates.
- b) Consider the following logic circuit:



- i) Write the Boolean expression for F.
- ii) Suppose the values of the four input variables A B C D as a function of time are as shown in the timing diagram below. Draw F as a function of time.

 

Problem 4: Logic Circuit Synthesis

Consider the adder circuit whose truth table is given in Slide 8 of Lecture 29.

- a) Write a “sum-of-products” expression for the sum bit S_0 .
- b) Simplify this logical expression (using either the method used to simplify the expression for S_1 in class on 11/7, or a Karnaugh map).
- c) Draw the logic circuit for S_0 using only NAND gates.