

EE40 Homework #10

Due Nov 19 (Thursday), 12:00 noon in Cory 240

Reading Assignments

Chapter 12 of Hambley

Supplement Reading on MOS Circuits

http://www.inst.eecs.berkeley.edu/~ee40/fa09/handouts/EE40_MOS_Circuit.pdf

Problem 1: Region of Operation (Hambley P12.8)

Determine the region of operation for each of the enhancement transistors and the currents shown in figure 1 below. The transistors have $|V_{t0}|=1V$, $K=0.1mA/V^2$

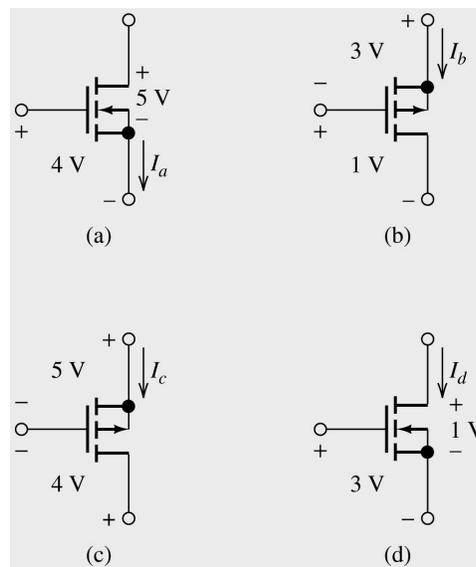


Fig.1 Transistor schematics for Problem 1

Problem 2 Find transistor current (Hambley P12.14)

Given that the enhancement transistor shown in figure 2 below has $V_{t0}=1V$, $K=0.5mA/V^2$ find the value of the resistance R.

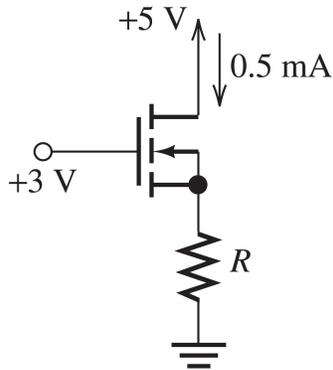


Fig.2 Transistor schematic for problem 2

Problem 3 Load Line Analysis (Hambley P12.20)

Consider the amplifier shown in figure 3

- Find $V_{gs}(5)$ assuming the coupling capacitor is a short circuit at the signal frequency, but an open at DC. (Hint: Apply the superposition principle for AC and DC sources)
- If the FET has $V_{t0}=1V$, $K=0.5mA/V^2$ sketch its drain characteristics to scale for $V_{gs}=\{1,2,3,4\}$ V
- Draw the load line for the amplifier on the characteristics
- find the values of V_{dsq} , V_{dsmin} V_{dsmax}

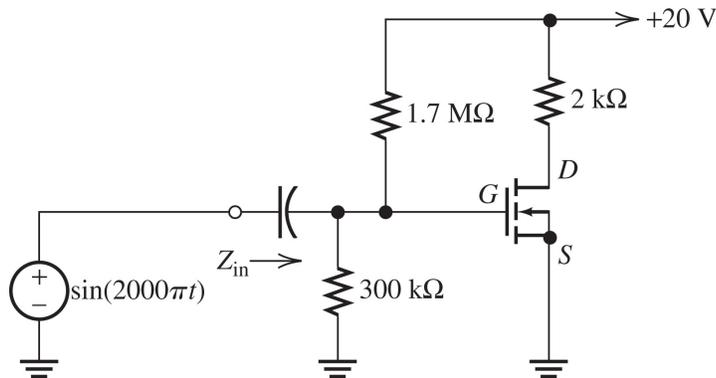


Fig. 3: Amplifier for problem 3

Problem 4 Bias Circuit (Hambley P12.31)

- Find the value of I_{dq} for the circuit in Figure 4. Assume $V_{t0}=4V$, $K=1mA/V^2$
- Repeat for Assume $V_{t0}=2V$, $K=2mA/V^2$

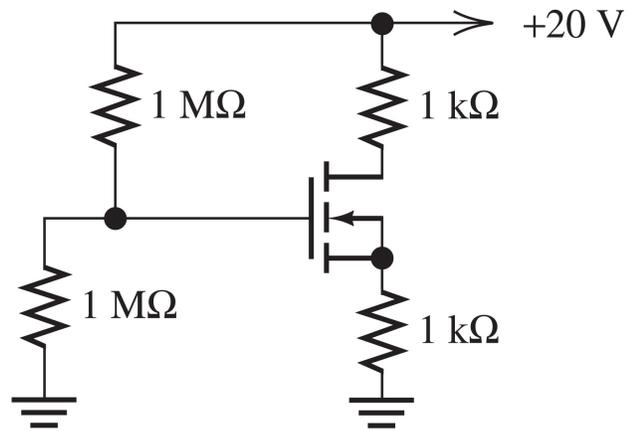


Fig. 4 Schematic for Problem 4

Problem 5 W/L Ratio (Hambley P12.35)

Both transistors shown in figure 5 have $k_p = 100 \mu\text{A}/\text{V}^2$ and $V_{t0} = 0.5\text{V}$. Determine the value of R needed so that $i_{D1} = 0.2\text{mA}$. For what range of V_x is the second transistor operating in the saturation region? What is the value of i_{D2} . Provided that V_x is large enough that the second transistor operates in saturation, to what ideal circuit element is the transistor equivalent?

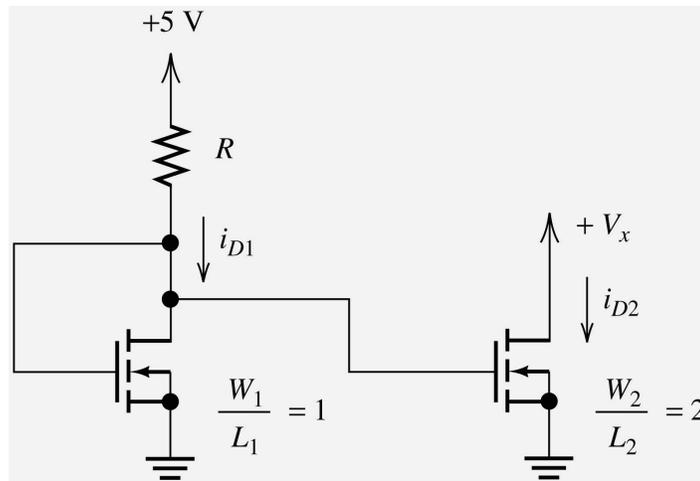


Fig.5 Schematic for problem 5

Problem 6 Small Signal Model Parameters (Hambley 12.42)

A certain NMOS transistor has the characteristic shown in figure 6. Graphically determine the value of g_m and R_{ds} at the operating point defined by $V_{dsQ} = 6\text{V}$ and $V_{gsQ} = 2.5\text{V}$.

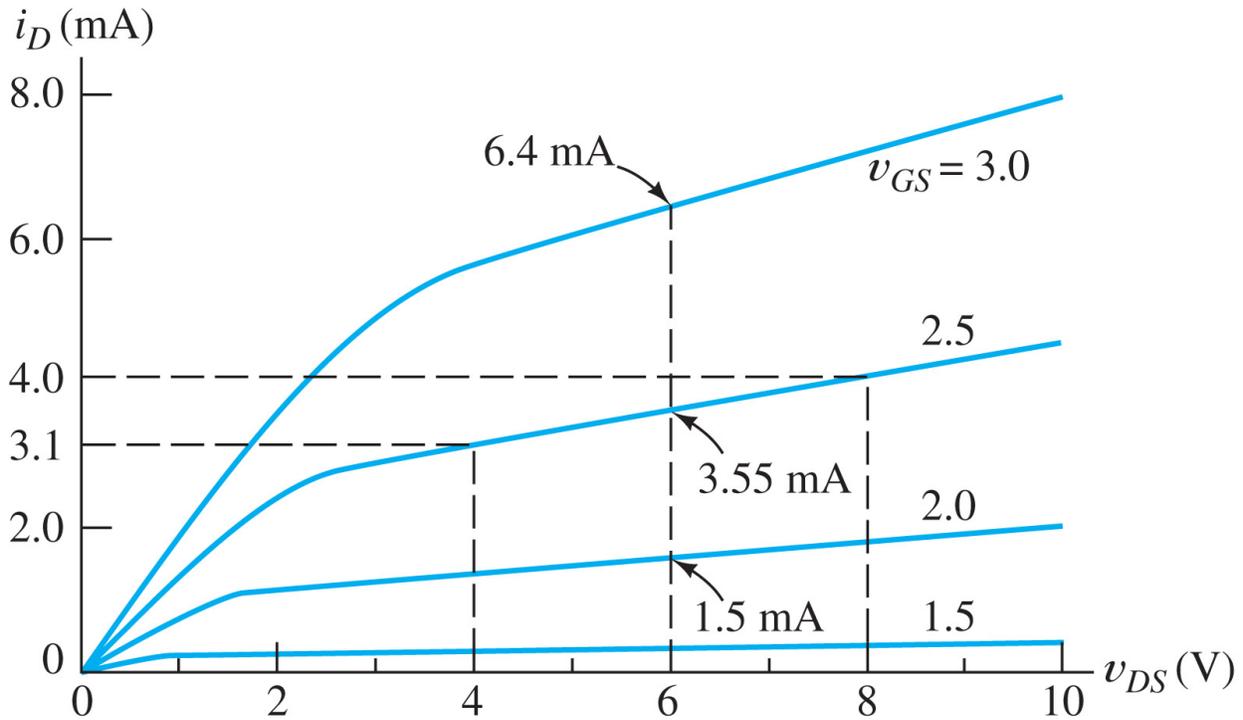


Fig.6 MOS Characteristic for problem 6

Problem 7 Common Source Amplifier (count as two problems for score) (Hambley P12.52)

Consider the amplifier in Fig. 7

- Draw the small signal equivalent circuit assuming the capacitors C_1 and C_2 are short circuits for the signal
- Assume that R_d is infinite and derive expressions for the voltage gain, and input and output resistance.
- Find I_{DQ} if $R=100K$ Ohm, $R_f=100K$ Ohm, $R_d=3K$ Ohm and $R_L=10K$ Ohm, $V_{DD}=20V$ $V_{t0}=5V$, $K=1mA/V_2$ Determine the value of g_m at the Q point.
- Evaluate the expressions found in part b by using the values given in part c.
- Find $v_o(t)$ if $v(t)=0.2 \sin(2000 \pi t)$
- Is this amplifier inverting or non-inverting

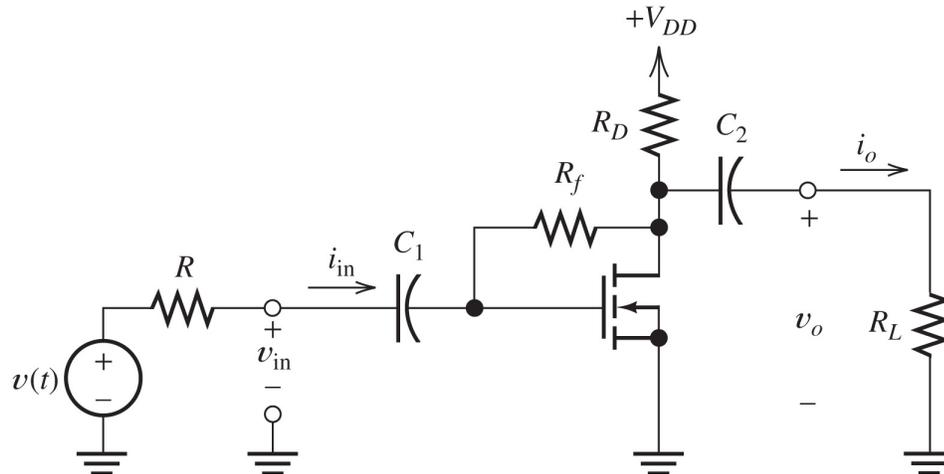


Fig.7 Amplifier for Problem 7

Problem 8 Source Follower (Hambley P 12.55)

Consider the common-source amplifier and the source follower. Which amplifier would be used if a voltage gain magnitude larger than unity was needed? Which one would be used to obtain a low output resistance?

Problem 9 CMOS Logic Gates (Hambley P12.60)

- Draw the circuit of a 3-input CMOS nand-gates
- Draw its equivalent circuit (open and closed switches) if all three inputs are high (logic "1")
- Repeat if all three inputs are low.