

Reading List

Chapter 14.4, 14.7, 14.8, 14.9 of Hambley textbook


14.9 of Hambley textbook

Chapter 3 of Hambley textbook

P1. (Hambley 14.23) Output Impedance of Op-Amp Circuits

Analyze each of the ideal op-amp circuits shown in the figure below to find expressions for i_o . What is the value of the output impedance for each of these circuits? Why?

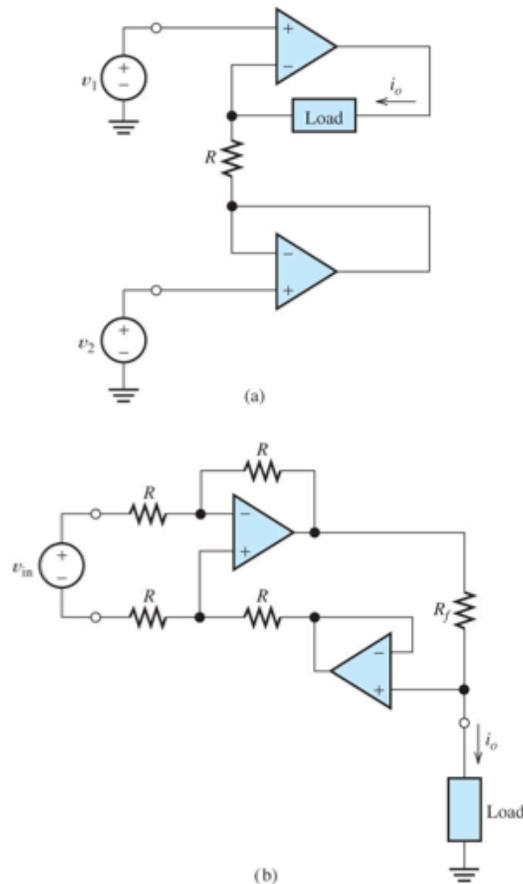(Note: the bottom end of the input voltage source is not grounded in part b of the figure. Thus, we say this source is floating)



Copyright © 2008 Pearson Prentice Hall, Inc.

Fig.1 Circuit schematics for problem 1.

P2.(Hambley 14.30) Gain Tolerance

Suppose that we design an inverting amplifier using 5% tolerance resistors and an ideal op-amp. The nominal amplifier gain is -2. What are the minimum and maximum gain possible, assuming the resistors are within the stated tolerance? What is the percentage tolerance of the gain? (Gain tolerance % = $100 \cdot (\text{GainMax} - \text{GainMin}) / (\text{GainNominal})$)

P3.(Hambley P14.34) Two Op-Amp Circuits in Tandem

The circuit shown in the figure below employs negative feedback. Use the summing point constraint for both amps to derive expressions for the voltage gains $A_1=V_{o1}/V_{in}$; $A_2=V_{o2}/V_{in}$

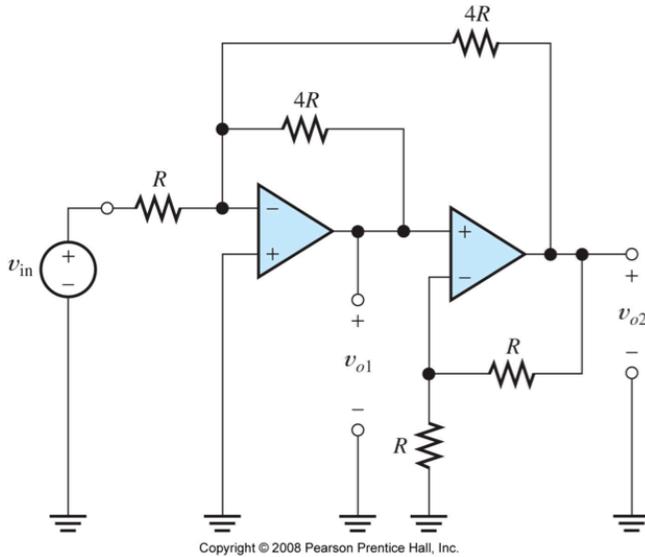


Fig.2 Circuit Schematic for Problem 3

P4.(Hambley 14.48) Analysis with full Op-Amp Model

The objective of this problem is to investigate the effects of finite gain, finite input impedance, and non-zero output impedance of the op-amp on the inverting amplifier. The circuit, including the op-amp model, is shown in the figure below.

A. Derive an expression for the circuit voltage gain v_o/v_s . Evaluate for $A_{OL}=10^5$, $R_{in} = 1M$ Ohm, $R_o = 25$ Ohm, $R_1=1K$ Ohm, $R_2=10K$ Ohm. Compare this results to the gain with an ideal op-amp.

B. Derive an expression for the circuit input impedance $Z_{in} = v_s/i_s$. Evaluate for $A_{OL}=10^5$, $R_{in} = 1M$ Ohm, $R_o = 25$ Ohm, $R_1=1K$ Ohm, $R_2=10K$ Ohm. Compare this results to the input impedance with an ideal op-amp.

C. Derive an expression for the circuit output impedance $Z_o = v_o/i_o$. Evaluate for $A_{OL}=10^5$, $R_{in} = 1M$ Ohm, $R_o = 25$ Ohm, $R_1=1K$ Ohm, $R_2=10K$ Ohm. Compare this results to the output impedance with an ideal op-amp.


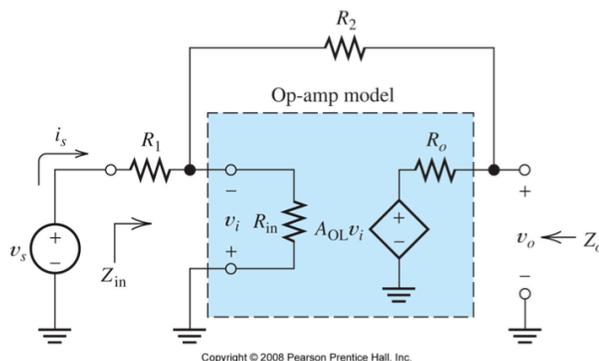
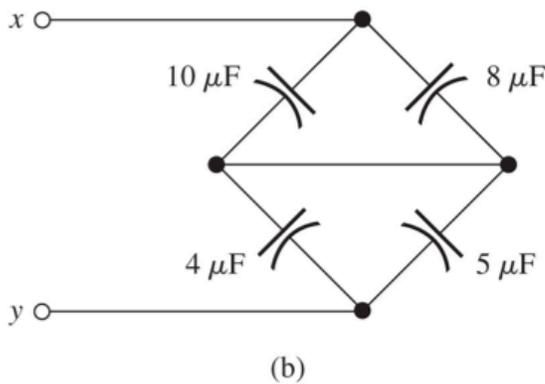


Fig.3 Circuit Schematic for Problem 4

P5 (Hambley 3.25) Capacitors in Series and in Parallel

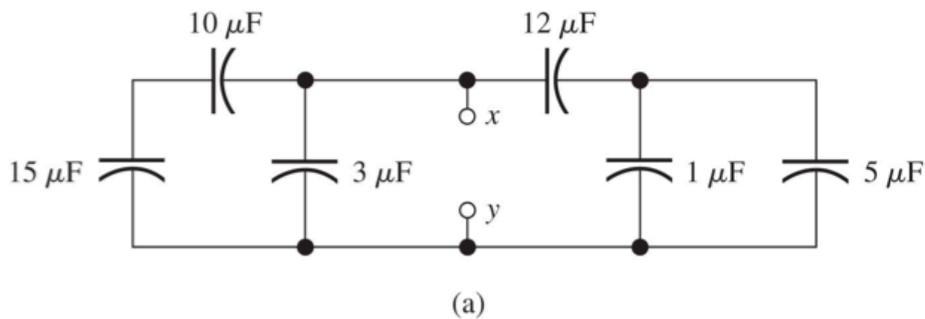Find the equivalent capacitance between terminals X and Y for each of the circuits shown in the figure



Copyright © 2008 Pearson Prentice Hall, Inc.

Fig.4 Circuit Schematic for Problem 5

P6.(Hambley 3.28) Capacitors Charging Behavior

Two initially uncharged capacitors $C_1=15\mu\text{F}$ and $C_2=10\mu\text{F}$ are connected in series. Then, a 10V source is connected to the series combination, as shown in the figure below. Find the voltages v_1 and v_2 after the source is applied. (Hint: the charges stored on the two capacitors must be equal because the current is the same in both capacitors)

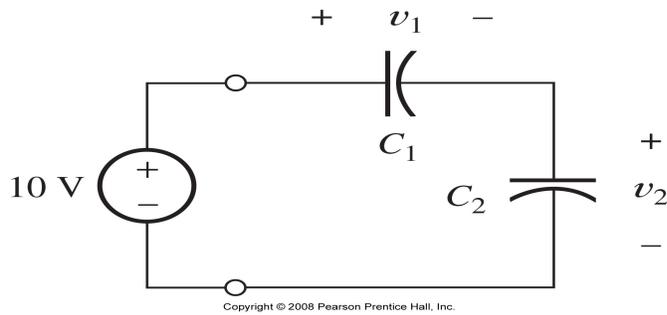


Fig.5 Circuit Schematic for Problem 6

P7 (Hambley 3.48) Inductor Behavior

The voltage across a 2H inductance is shown in the figure below. The initial current in the inductance is $i(0)=0$. Sketch the current, power, and stored energy to scale versus time.


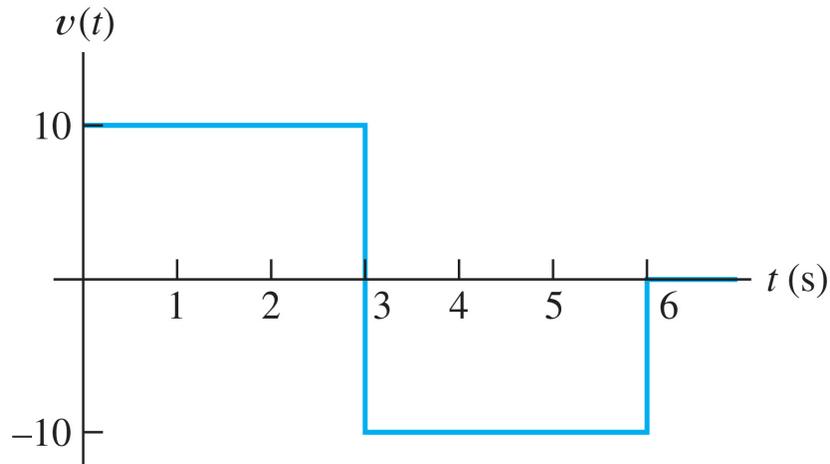
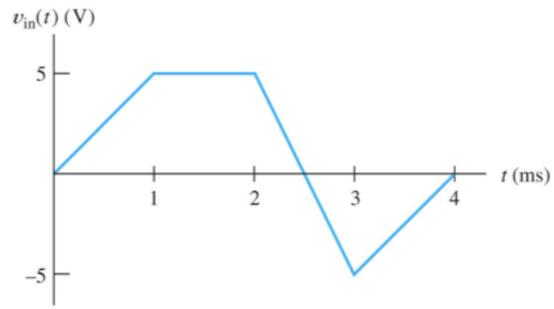


Fig.6 Voltage waveform for Problem 7

P8. (Hambley 14.75) Differentiator

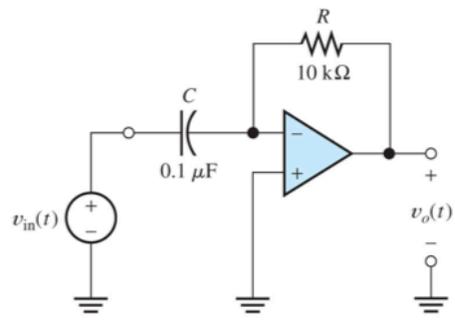Sketch the output voltage of the ideal op-amp circuit shown in the figure below to scale versus time.



Copyright © 2008 Pearson Prentice Hall, Inc.

Fig.7 Circuit Schematic for Problem 8