

Name

Solutions

EE 42

Midterm 2

April 13, 2004

PLEASE WRITE YOUR NAME ON EACH ATTACHED PAGE

PLEASE SHOW YOUR WORK TO RECEIVE PARTIAL CREDIT

Problem 1: 15 Points Possible _____

Problem 2: 15 Points Possible _____

Problem 3: 15 Points Possible _____

Problem 4: 15 Points Possible _____

Problem 5: 15 Points Possible _____


Problem 6: 15 Points Possible _____

Problem 7: 10 Points Possible _____

TOTAL: 100 Points Possible _____

Name Solutions.

Problem 1: 15 Points Possible

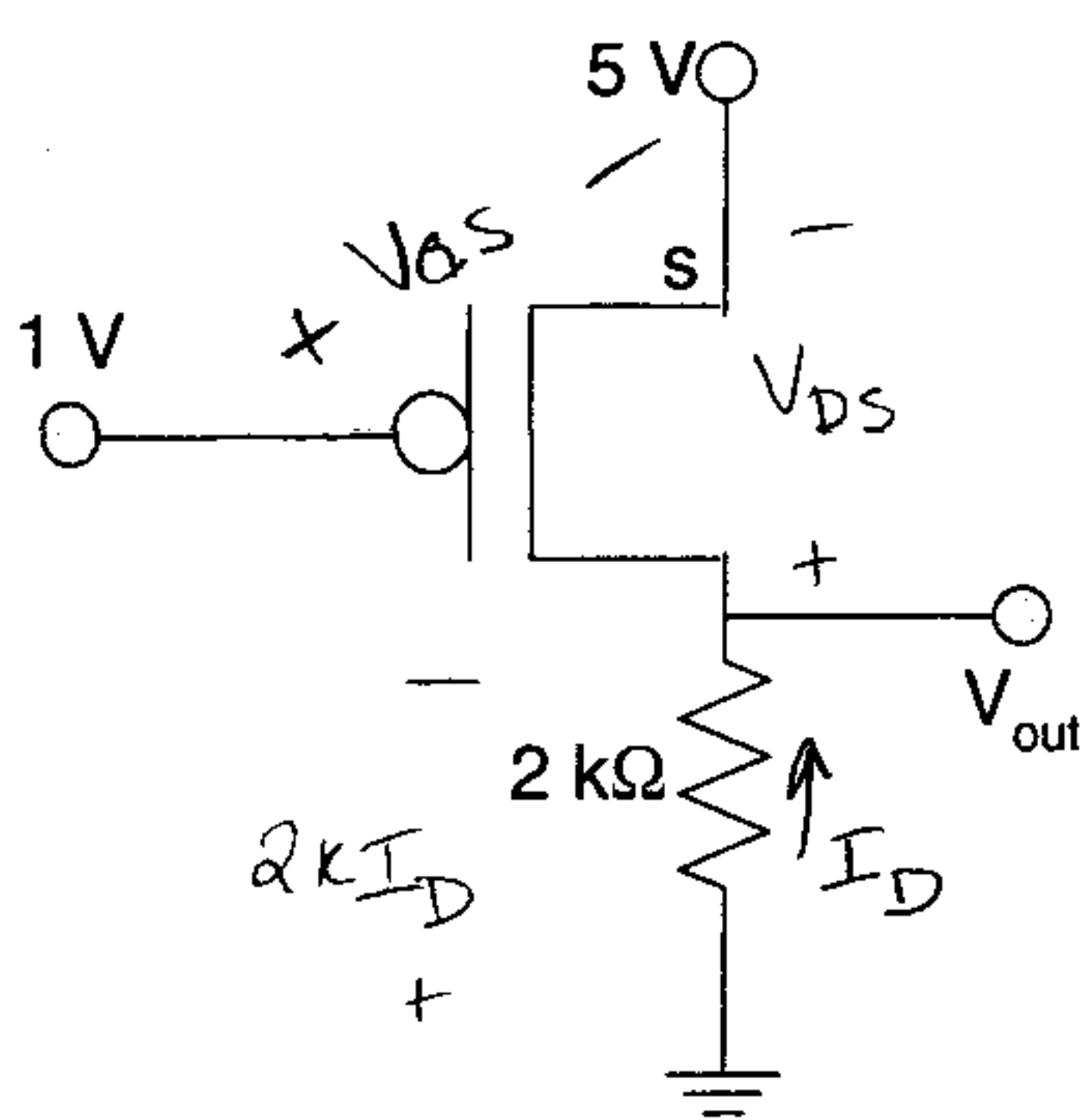

$$W/L \mu_p C_{ox} = 1 \text{ mA/V}^2$$

$$\lambda_p = 0 \text{ V}^{-1}$$

$$V_{TH(p)} = -1 \text{ V}$$

Find V_{out} .

$$V_{GS} = -4 \text{ V} \quad \text{Not cutoff.}$$

Guess saturation. $I_D = -\frac{1}{2} \cdot 1 \text{ mA/V}^2 \cdot (-4 \text{ V} - (-1 \text{ V}))^2 = -4.5 \text{ mA}$

$$2 \text{ k}\Omega I_D + V_{DS} + 5 \text{ V} = 0 \quad V_{DS} = 4 \text{ V} \neq V_{GS} - V_{TH(p)}$$

Must be triode mode. (also, V_{DS} can't be positive for PMOS) $= -3 \text{ V}$

$$I_D = -1 \text{ mA/V}^2 \left(-4 \text{ V} - (-1 \text{ V}) - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\frac{I_D}{-1} = -\frac{5 + V_{DS}}{2 \text{ k}\Omega} \quad \text{from above}$$

Simultaneously solve: $V_{DS} = \{-6.19, -0.81\}$

$$I_D = -\frac{5 + -0.81}{2 \text{ k}\Omega}$$

$$V_{out} = -2 \text{ k}\Omega I_D = \underline{4.19 \text{ V}}$$


↑
impossible for triode

Name Solutions


Problem 2: 15 Points Possible

| Inputs | | | | Output |
|--------|---|---|---|--------|
| A | B | C | D | F |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

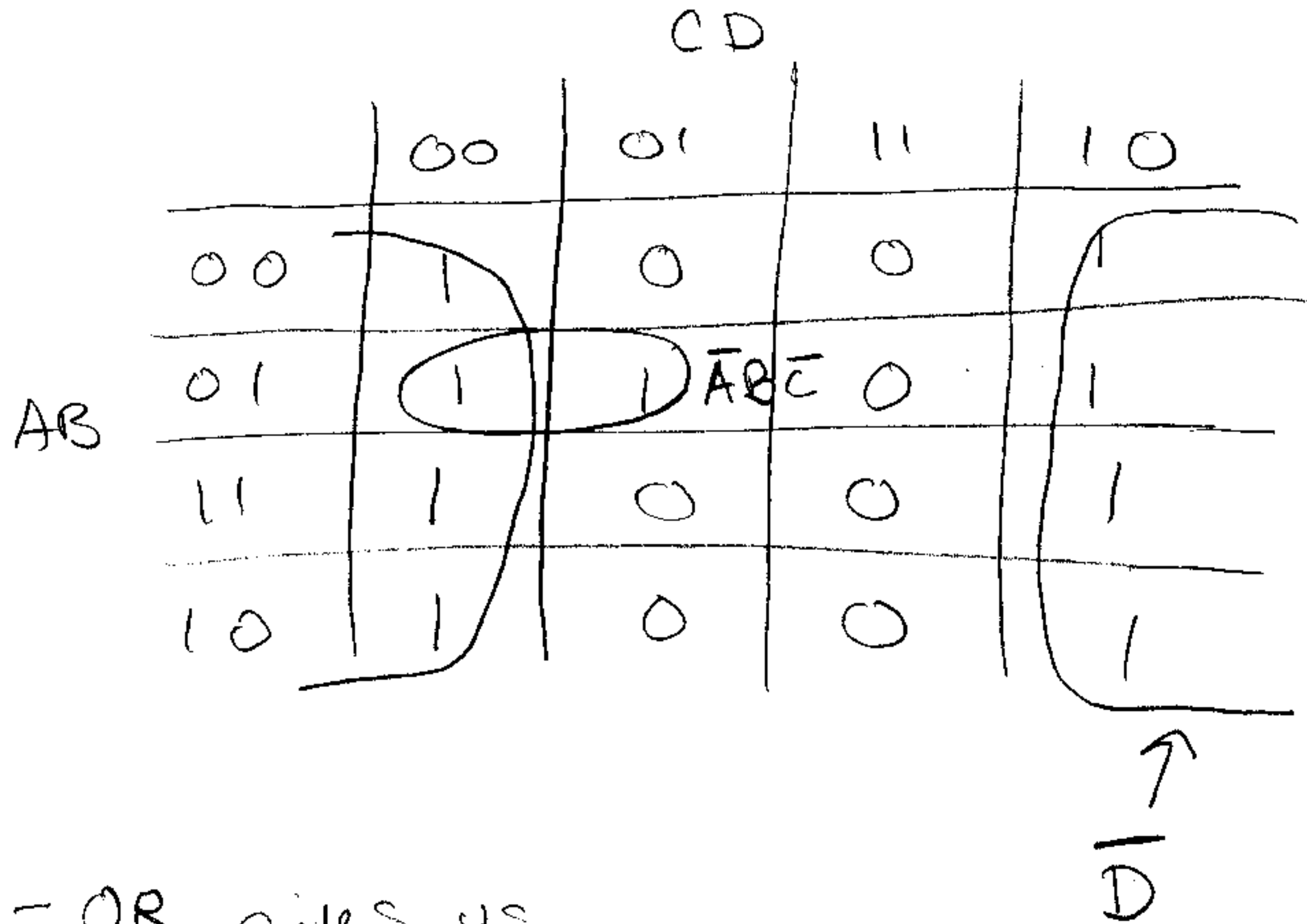
- a) Write the simplest sum-of-products expression for F in terms of A, B, C, D.
 b) Draw the logic circuit for this function using only NAND gates.



Regular AND-OR gives us

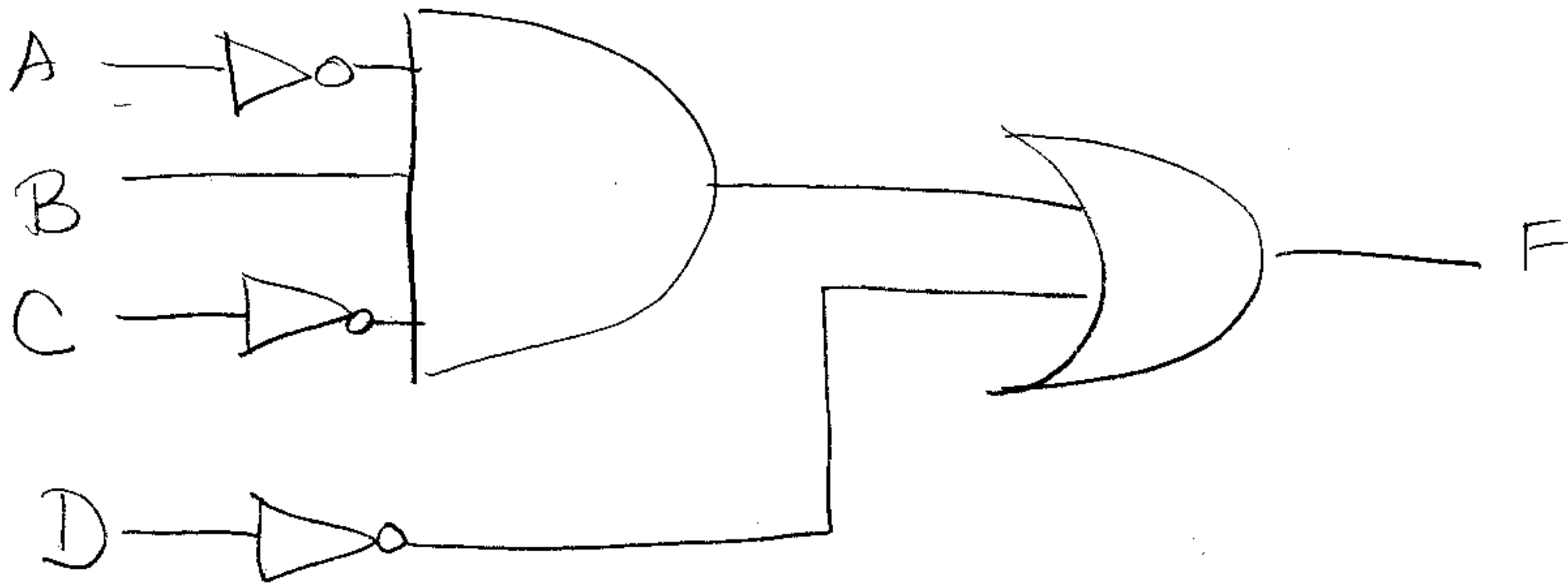


So NAND-NAND is

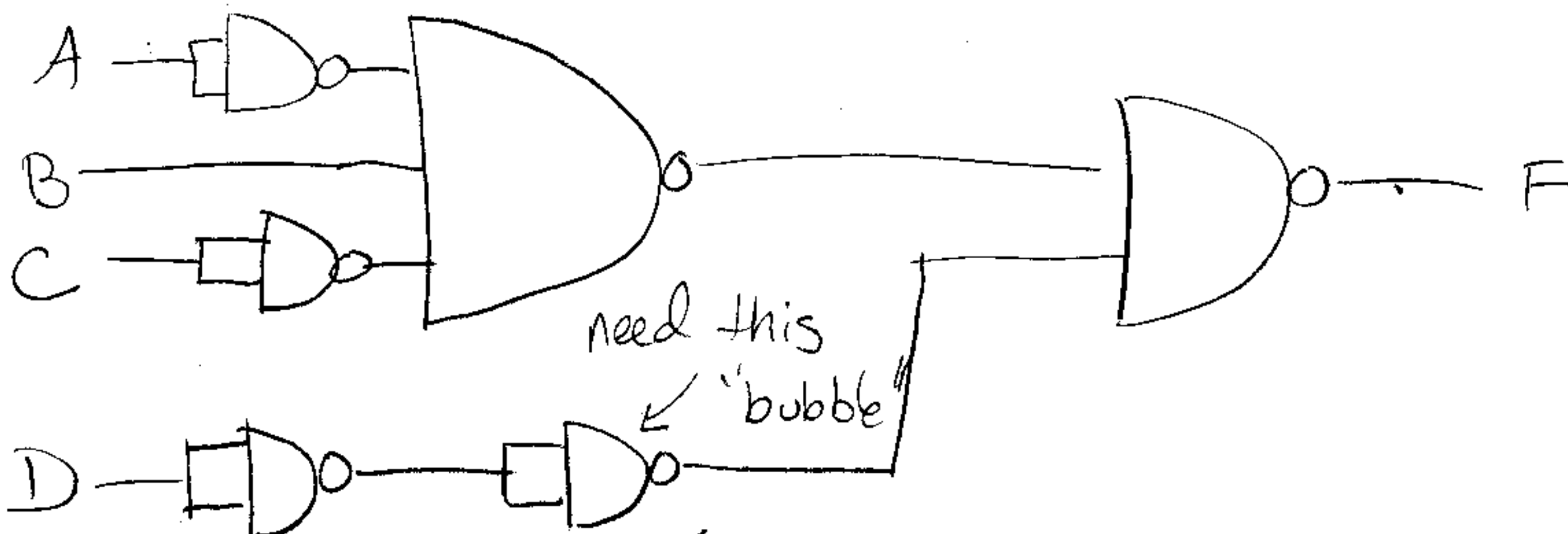

these cancel, acceptable with both removed.





Name Solutions

Problem 3: 15 Points Possible

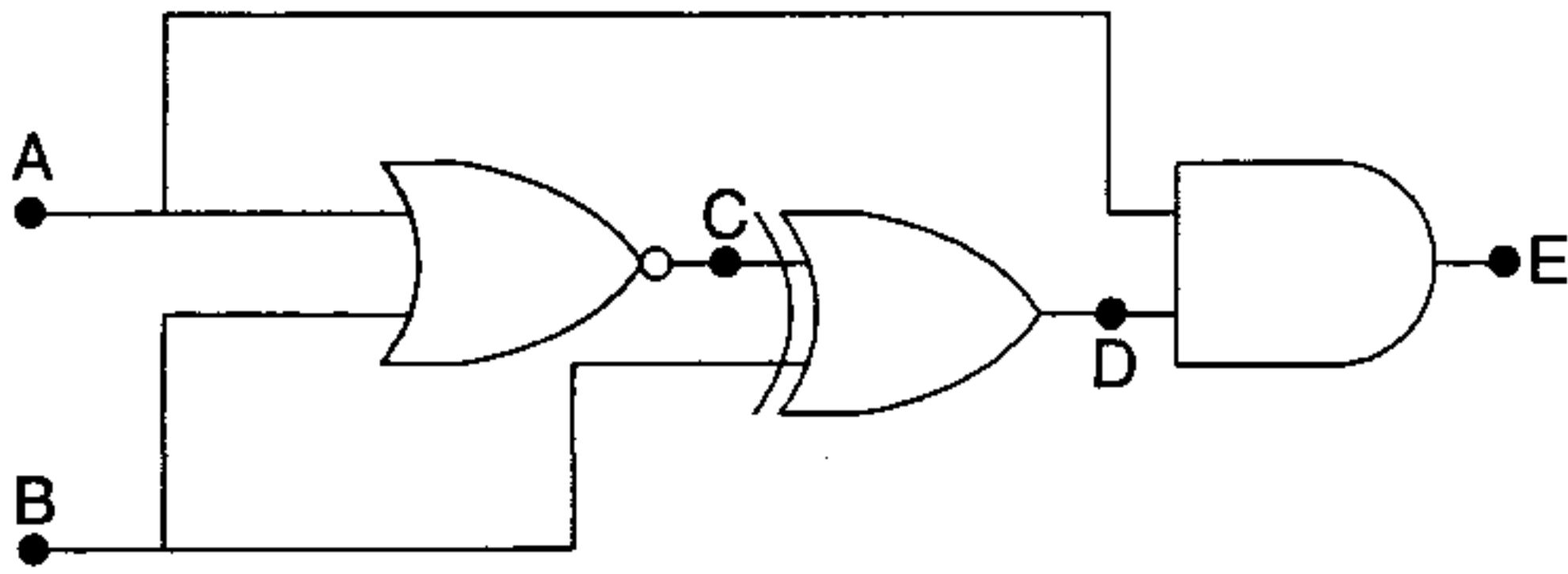


Assume that each gate shown has a propagation delay of t_p .

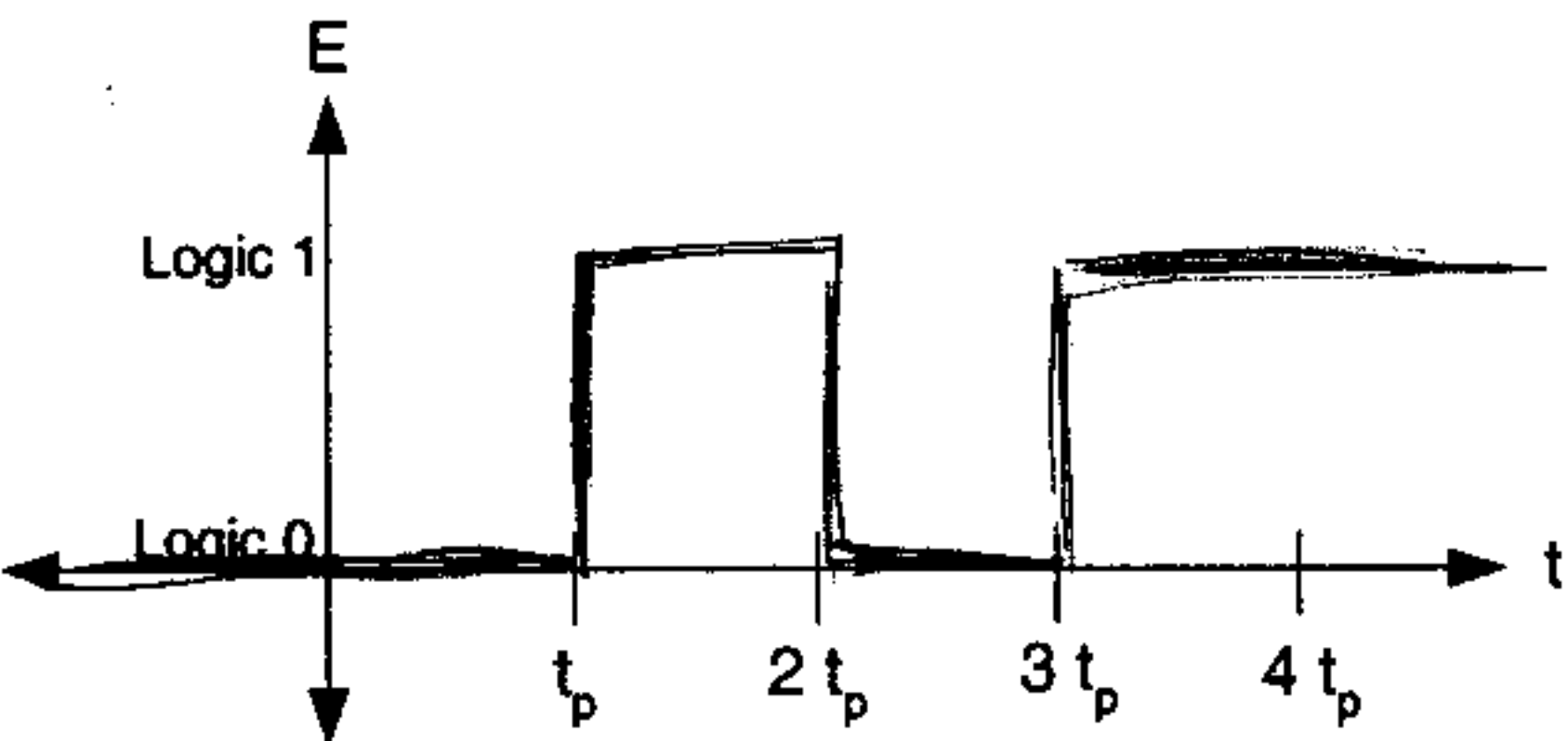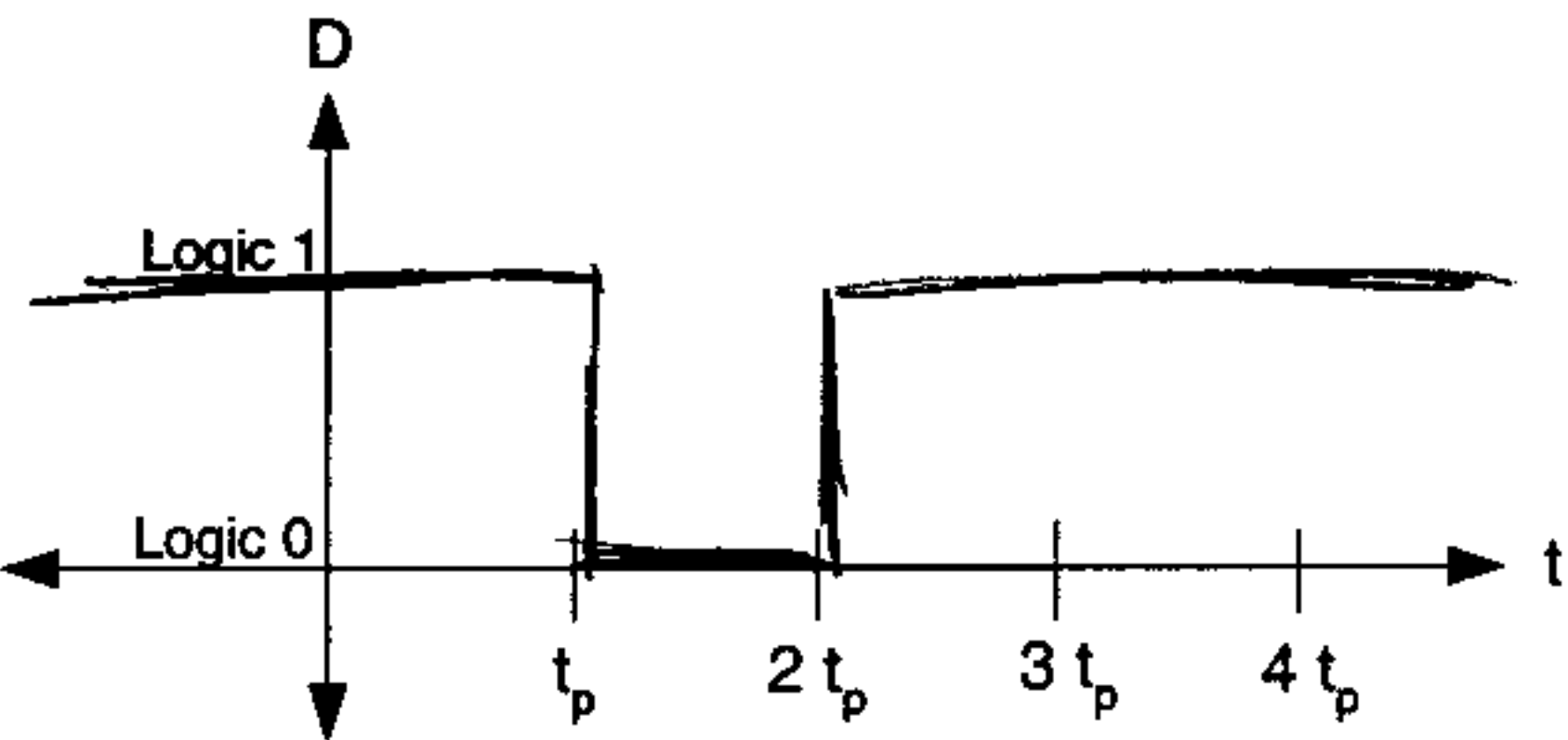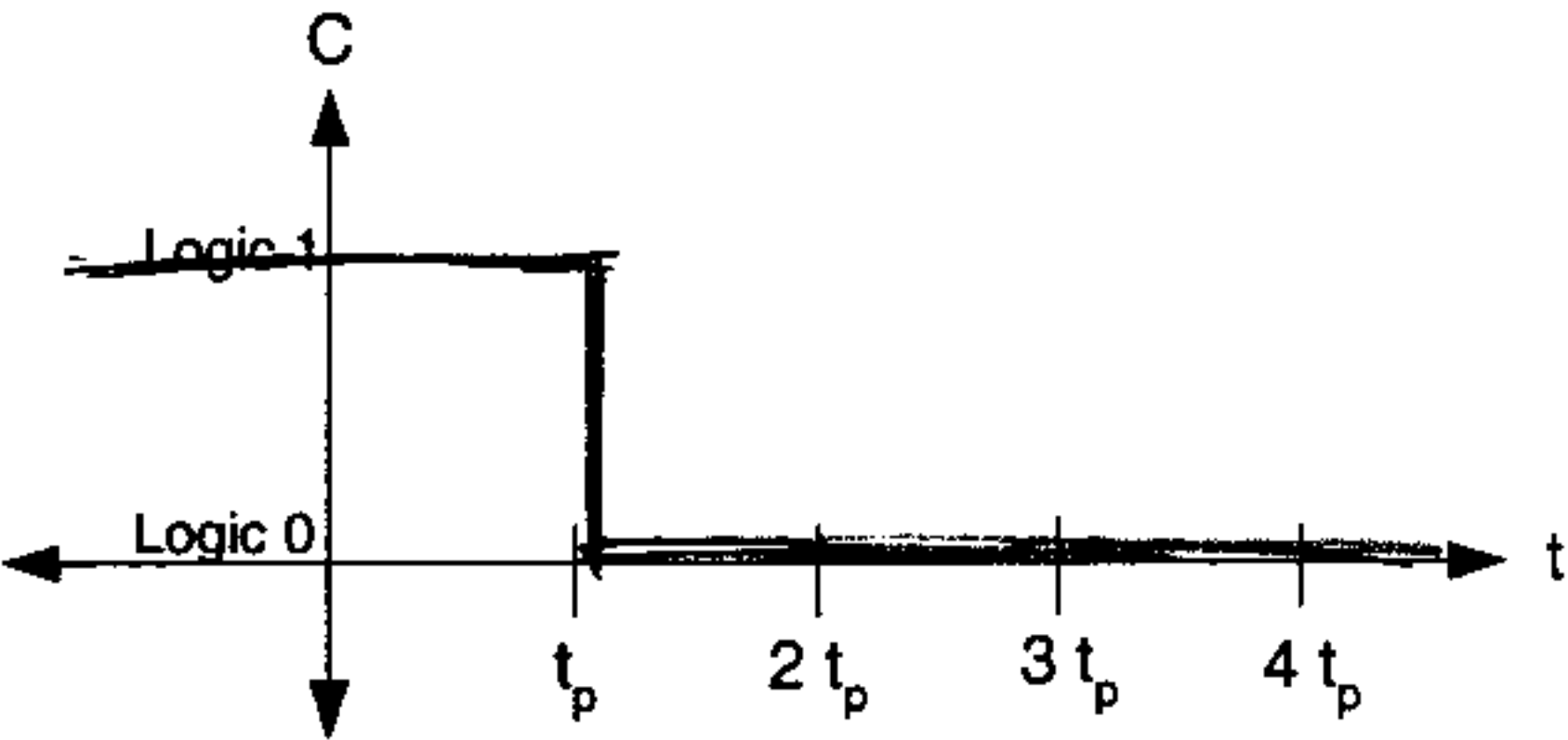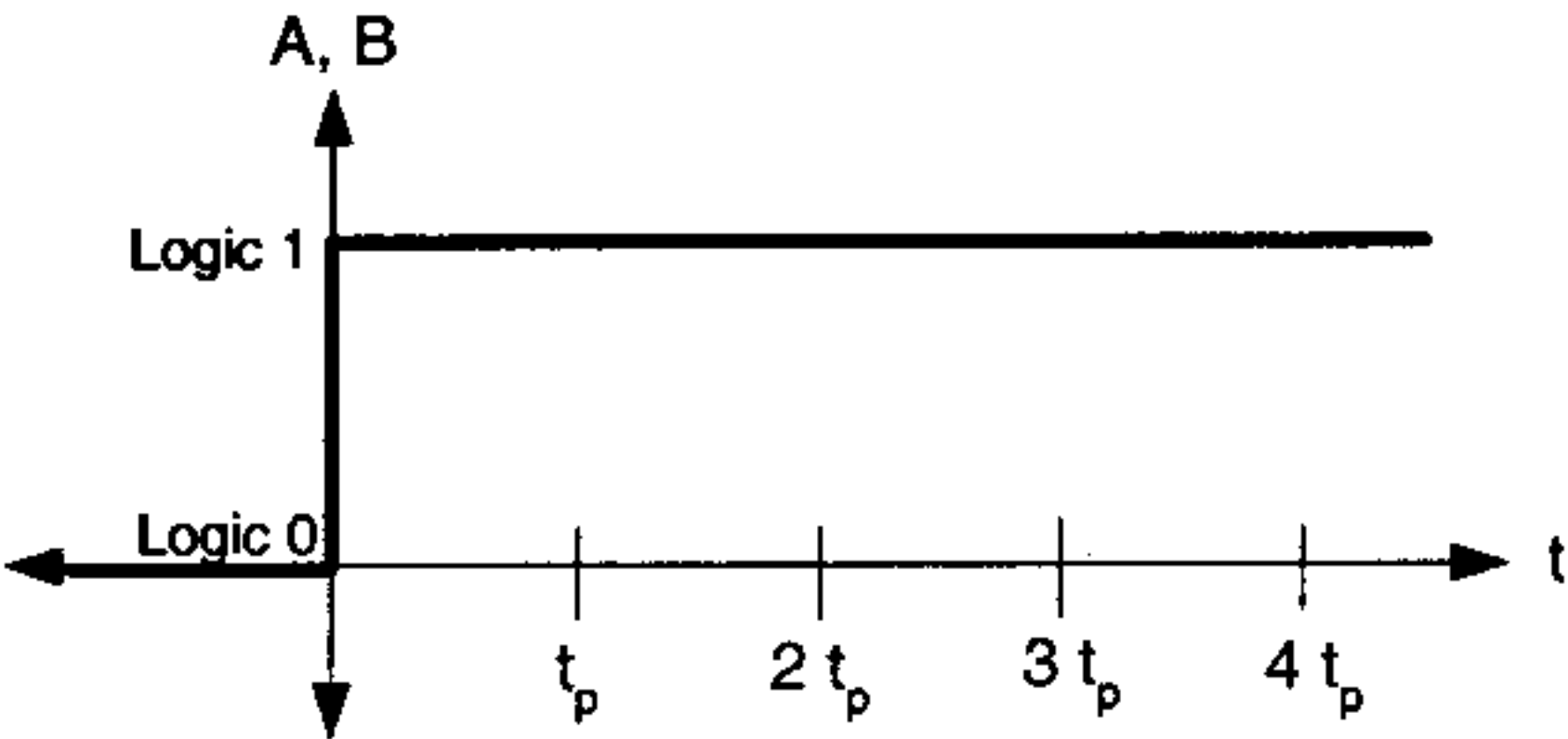With signals A and B as shown below, sketch signals C, D, and E on the axes provided.



Name _____


Problem 4: 15 Points Possible

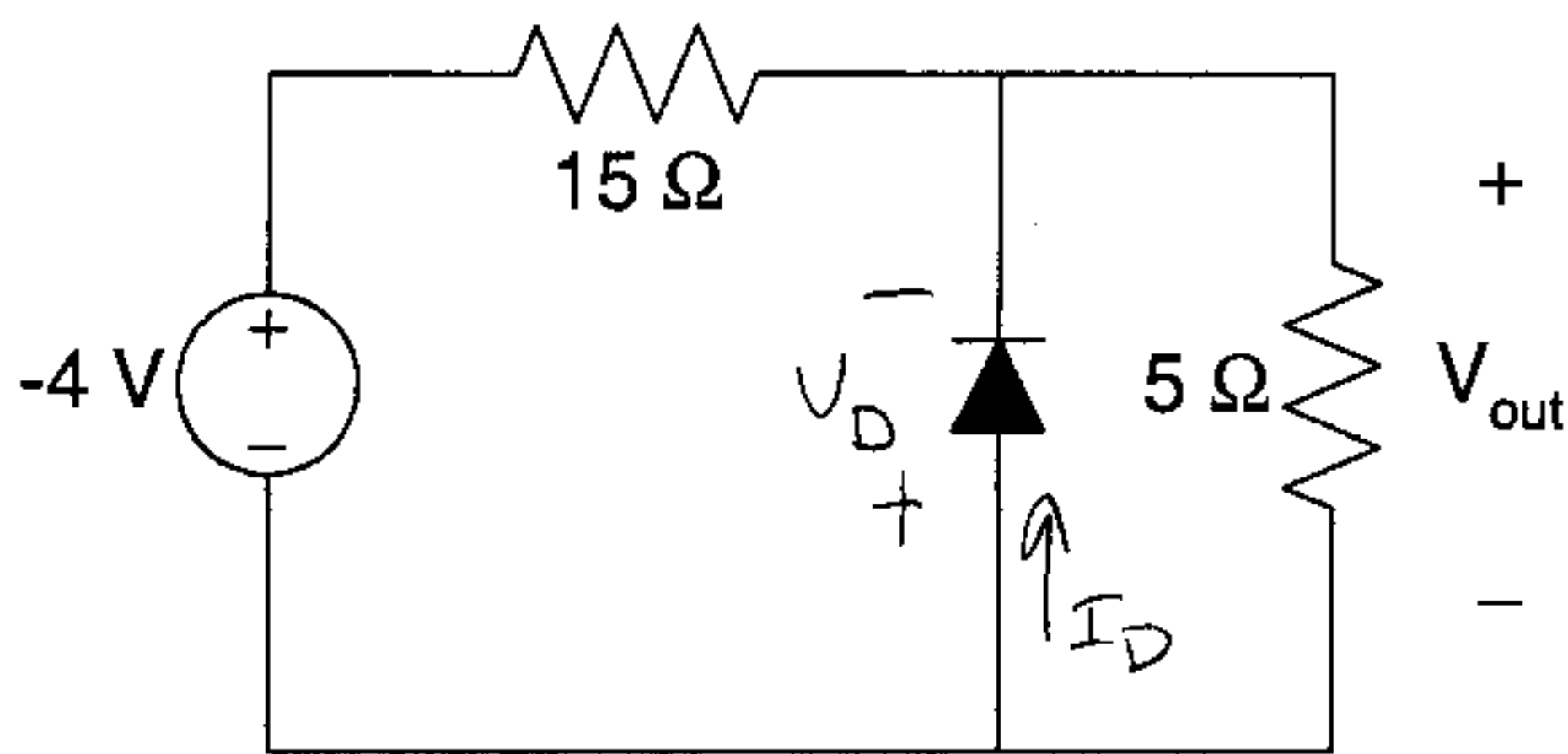

Use the large-signal model for the diode, with $V_F = 2\text{ V}$.

Find V_{out} .

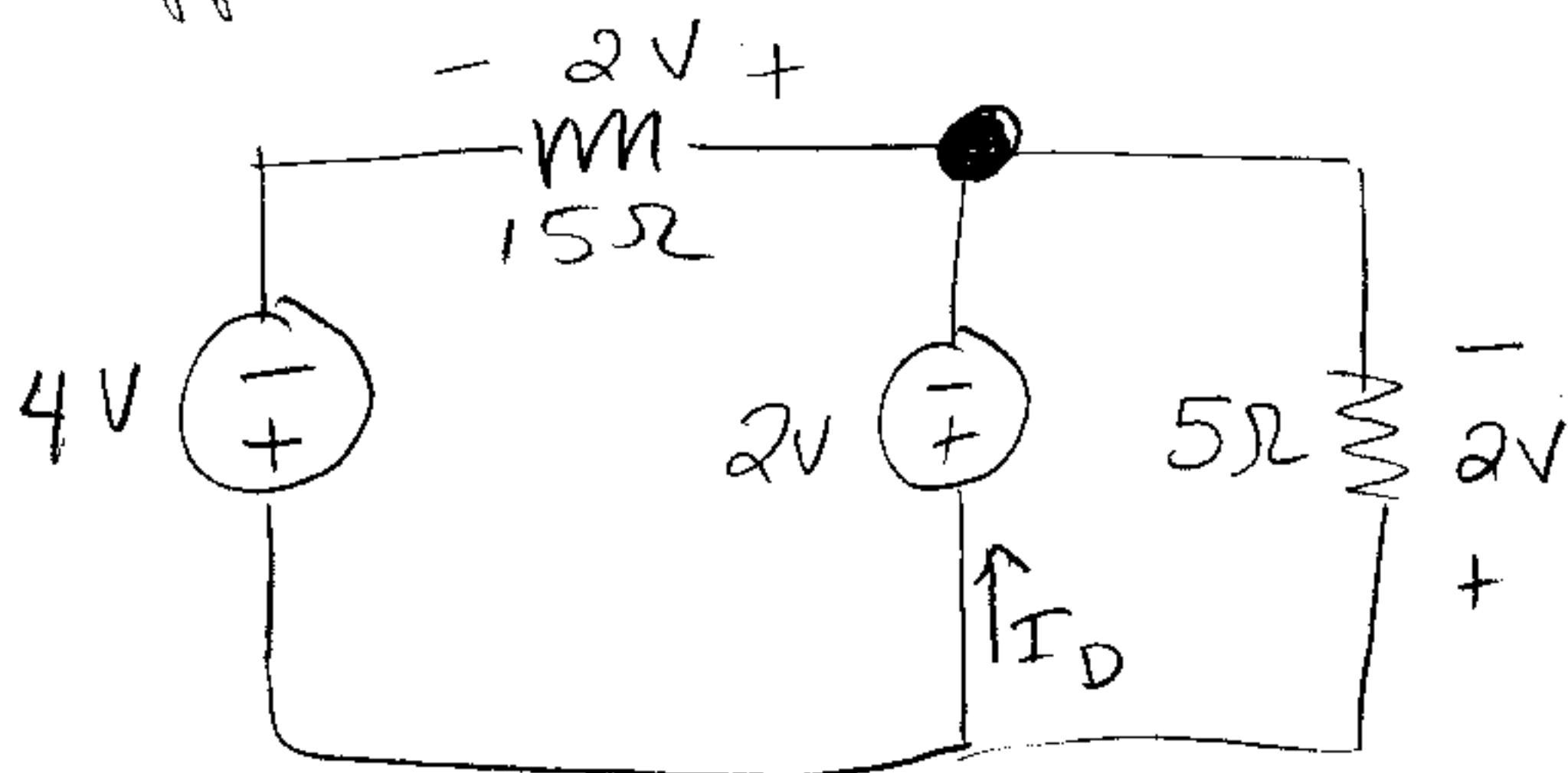Suppose diode is forward biased. Verify $I_D \geq 0$.




By KVL, $15\text{ k}\Omega$ has 2 V as shown.

KCL at dot:

$$I_D + \frac{2\text{ V}}{5\Omega} = \frac{2\text{ V}}{15\Omega}$$

$$I_D = -\frac{4}{15}\text{ A} \quad \text{Not forward biased!}$$

Must be reverse biased.

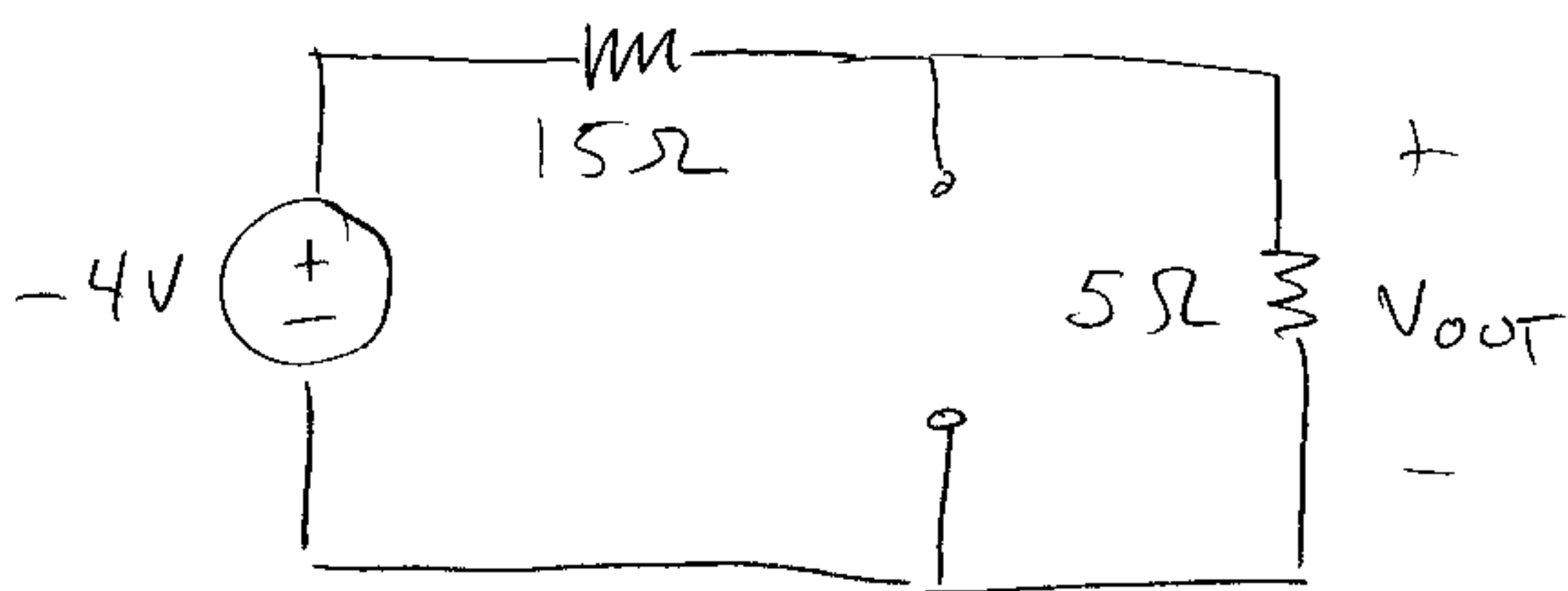


Resistors now in series,

By voltage division,

$$V_{out} = -4\text{ V} \cdot \frac{5\Omega}{5\Omega + 15\Omega} = \boxed{-1\text{ V}}$$

Name _____

Problem 5: 15 Points Possible

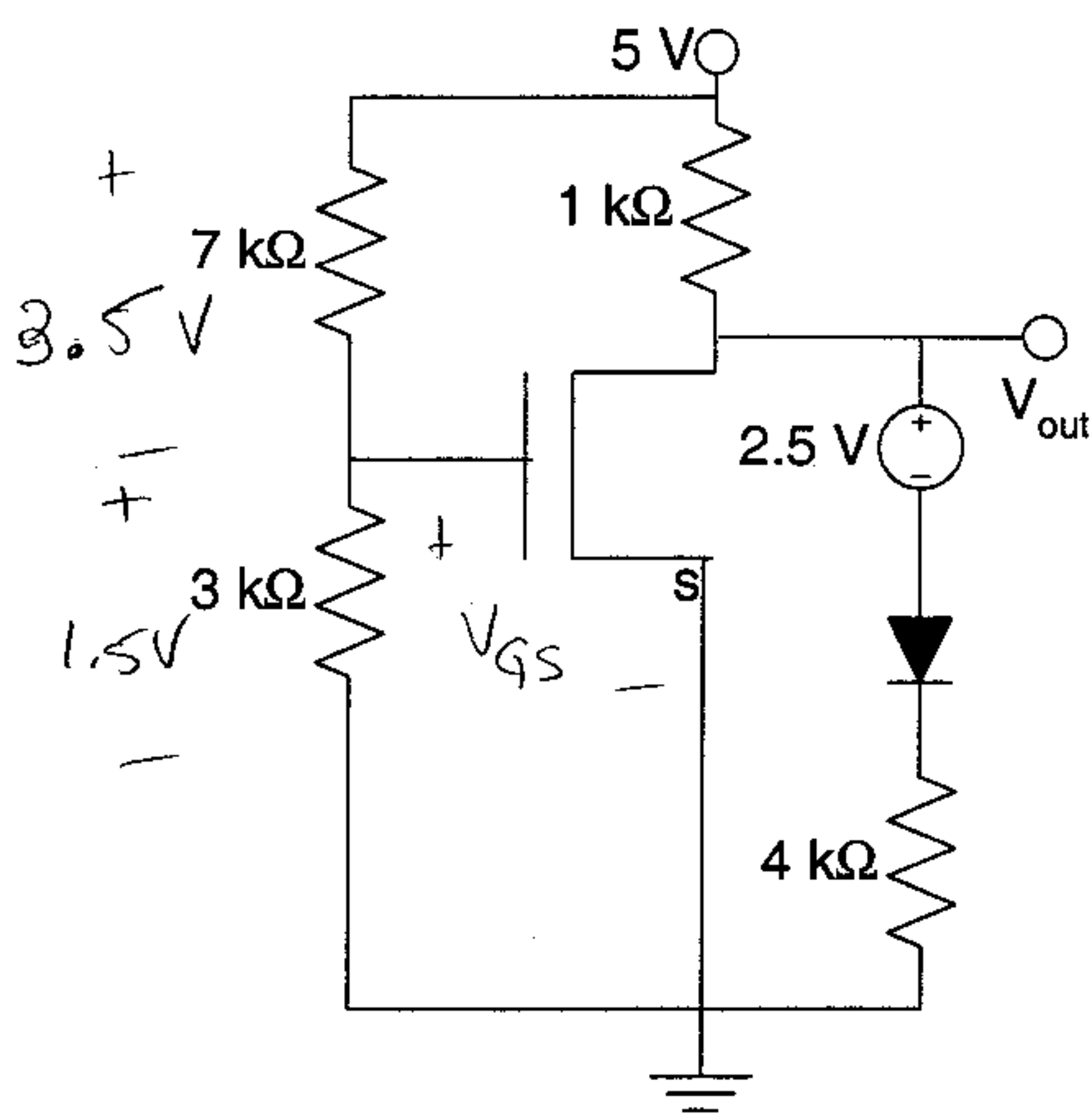

$W/L \mu_n C_{ox} = 1 \text{ mA/V}^2$

$\lambda_n = 0 \text{ V}^{-1}$

$V_{TH(n)} = 1 \text{ V}$

Use the large-signal model for the diode with $V_F = 2 \text{ V}$.


Find V_{out} .

By voltage division, $3\text{k}\Omega$ resistor has 1.5 V

$V_{GS} = 1.5 \text{ V}$ Not cutoff. Guess saturation.

$$I_D = \frac{1}{2} \cdot 1 \text{ mA/V}^2 (1.5 \text{ V} - 1 \text{ V})^2 = \frac{1}{8} \text{ mA}$$

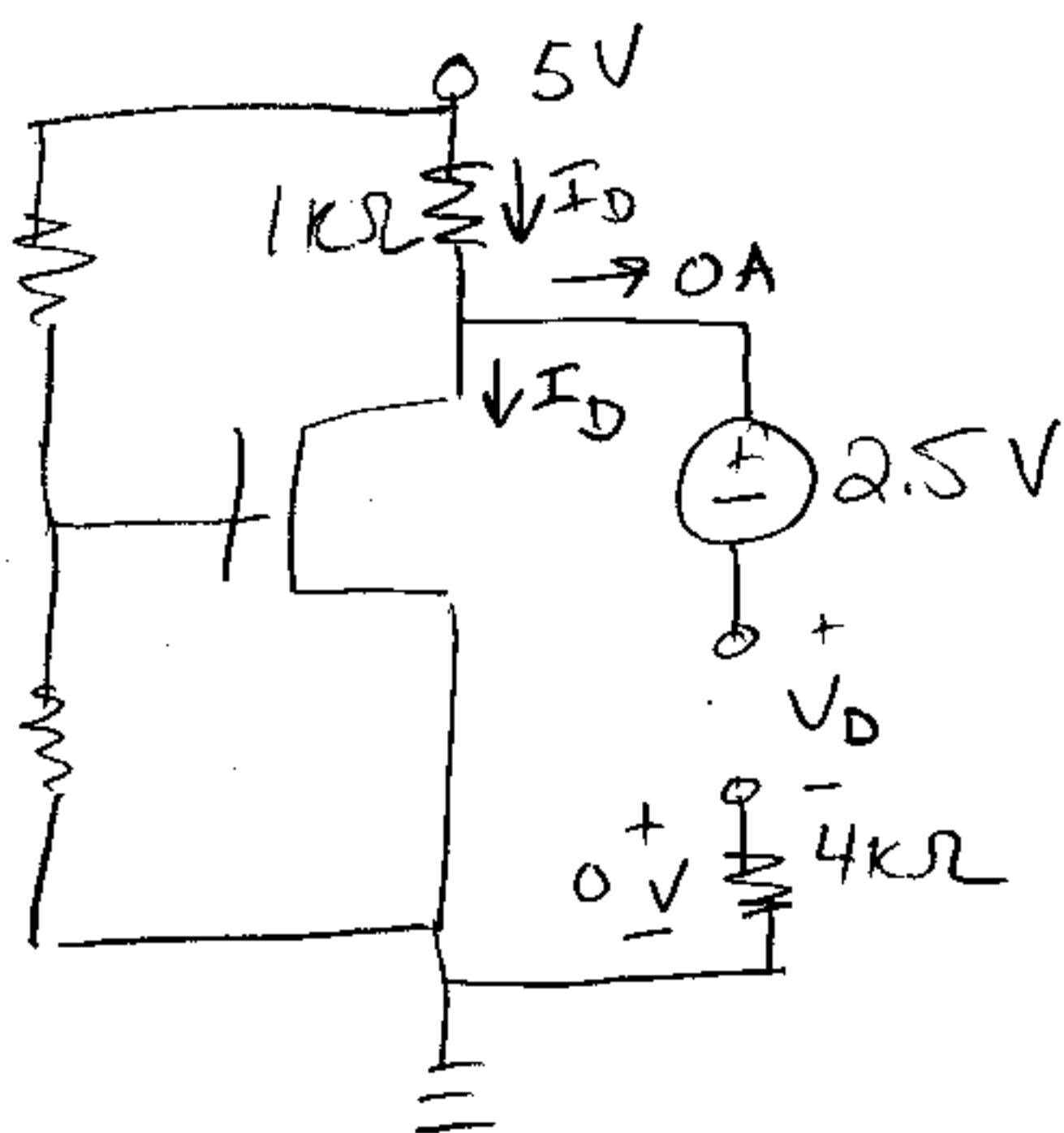Now find V_{DS} to verify saturation. Guess reverse bias for diode out of laziness. Must verify $V_D \leq 2 \text{ V}$.



Since 0 A thru open circuit,

$1\text{k}\Omega$ resistor carries I_D .


Also, $4\text{k}\Omega$ resistor has 0 V .

KVL:

$$-0 \text{ V} - V_D - 2.5 \text{ V} - 1\text{k}\Omega I_D + 5 \text{ V} = 0$$

$$V_D = 2.375 \text{ V} \quad \text{not reverse biased!}$$

Must be forward biased.

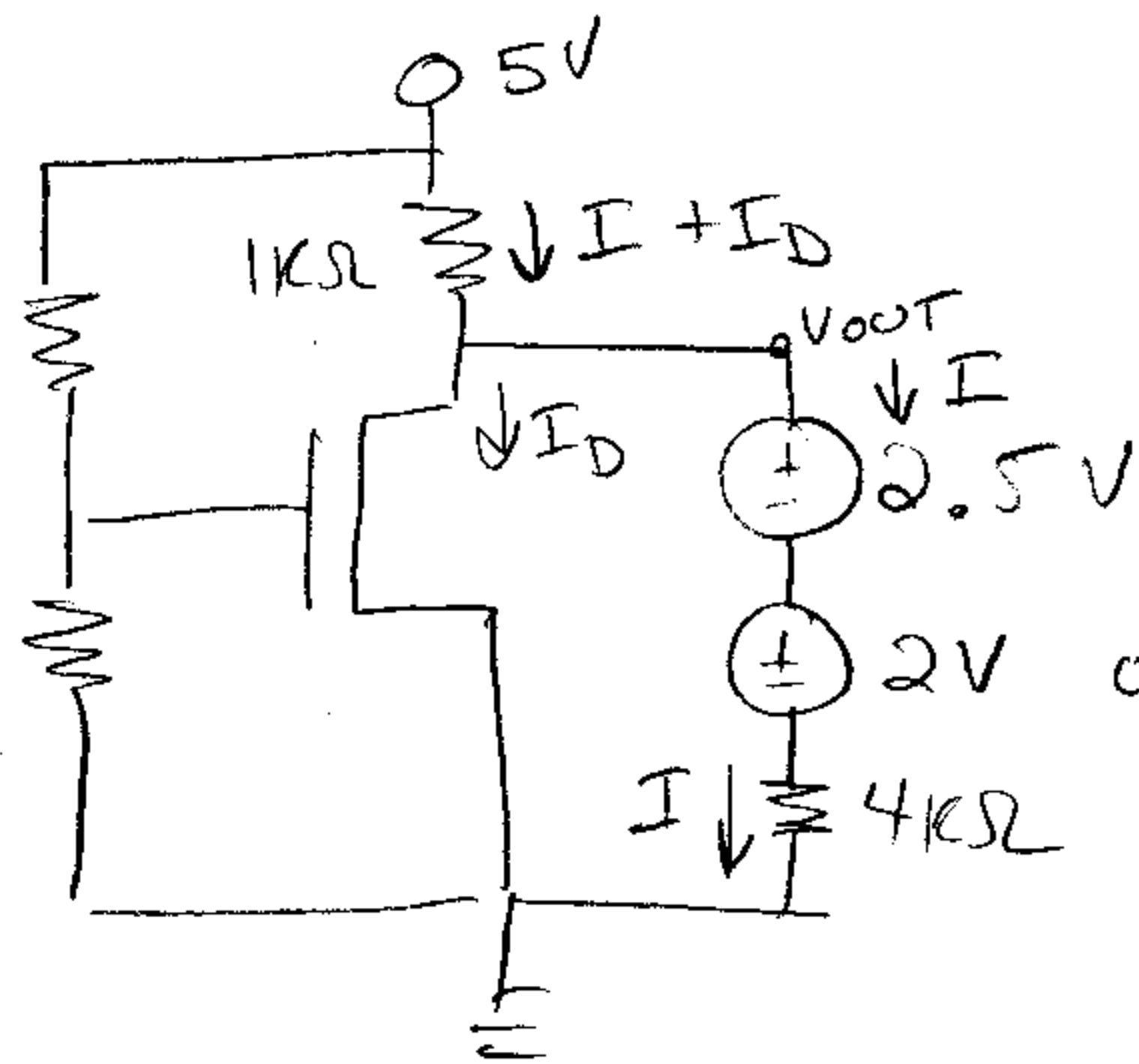

Now diode branch can conduct current. Call it I .

By KVL,

$$0 = -4k\Omega I - 2V - 2.5V - 1k\Omega(I + I_D) + 5V$$

$I_D = 1/8 \text{ mA}$ from saturation assumption

$$I = \frac{5V - 2V - 2.5V - 1/8 V}{5k\Omega}$$

$$= \frac{3}{40} \text{ mA}$$


Still need to verify $V_{DS} > \underbrace{V_{GS} - V_{TH}}_{1.5V - 1V = 0.5V}$ for saturation.

$$V_{DS} = 2.5V + 2V + 4k\Omega I_D = 4.8V \quad \text{OK for saturation!}$$

$$V_{out} = V_{DS} = 4.8V$$

Name _____

Problem 6: 15 Points Possible

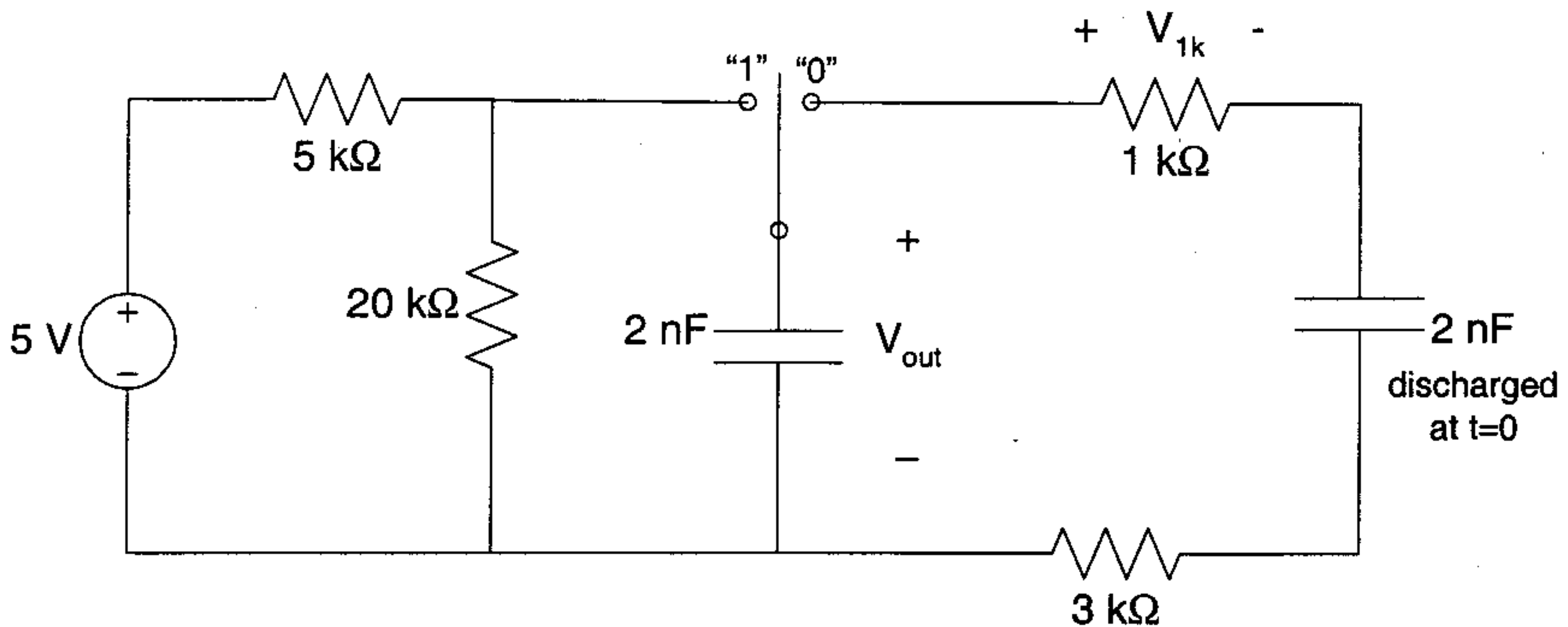


Suppose the circuit has been in position "1" for a long time.

At $t = 0$, it switches to position "0".

At $t = 4 \mu\text{s}$, it switches back to position "1".

- Find $V_{\text{out}}(t)$ for all $t \geq 0$.
- Find $V_{1k}(t)$ for all $t \geq 0$.
- Find the total energy absorbed by the $1 \text{ k}\Omega$ resistor over the time period $t \geq 0$ (ending at ∞).

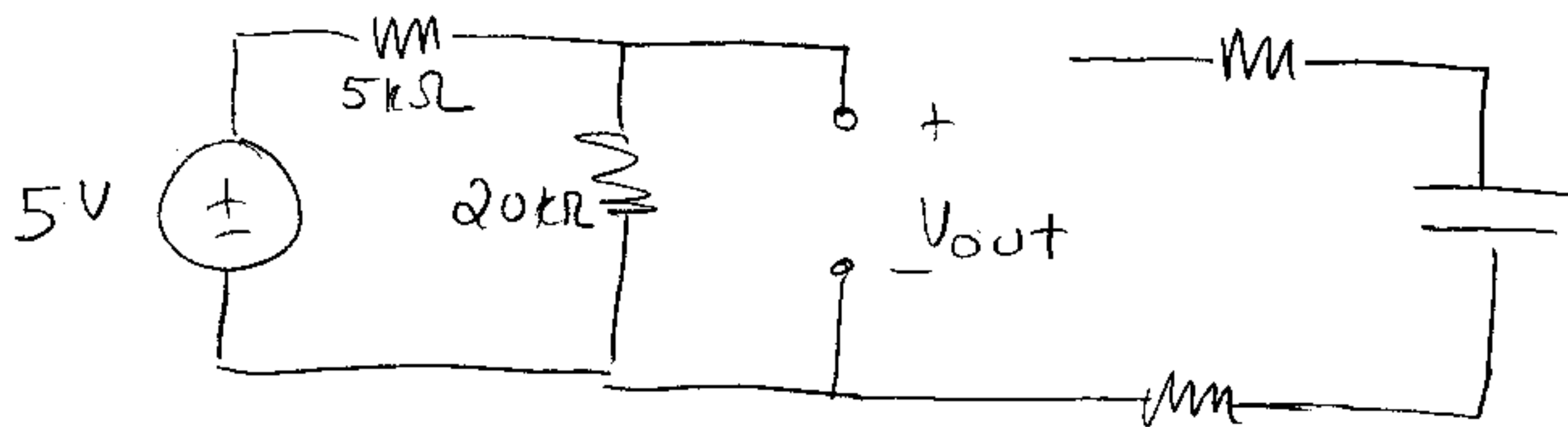a) Use $t = 0^-$ circuit to find $V_{\text{out}}(0)$.




After a long time, capacitor acts like open circuit.

By voltage division,

($5\text{k} + 20\text{k}$ act in series)

$$V_{\text{out}} = \text{Voltage over } 20\text{k} \\ = 5\text{V} \cdot \frac{20\text{k}\Omega}{20\text{k}\Omega + 5\text{k}\Omega} = 4\text{V}$$

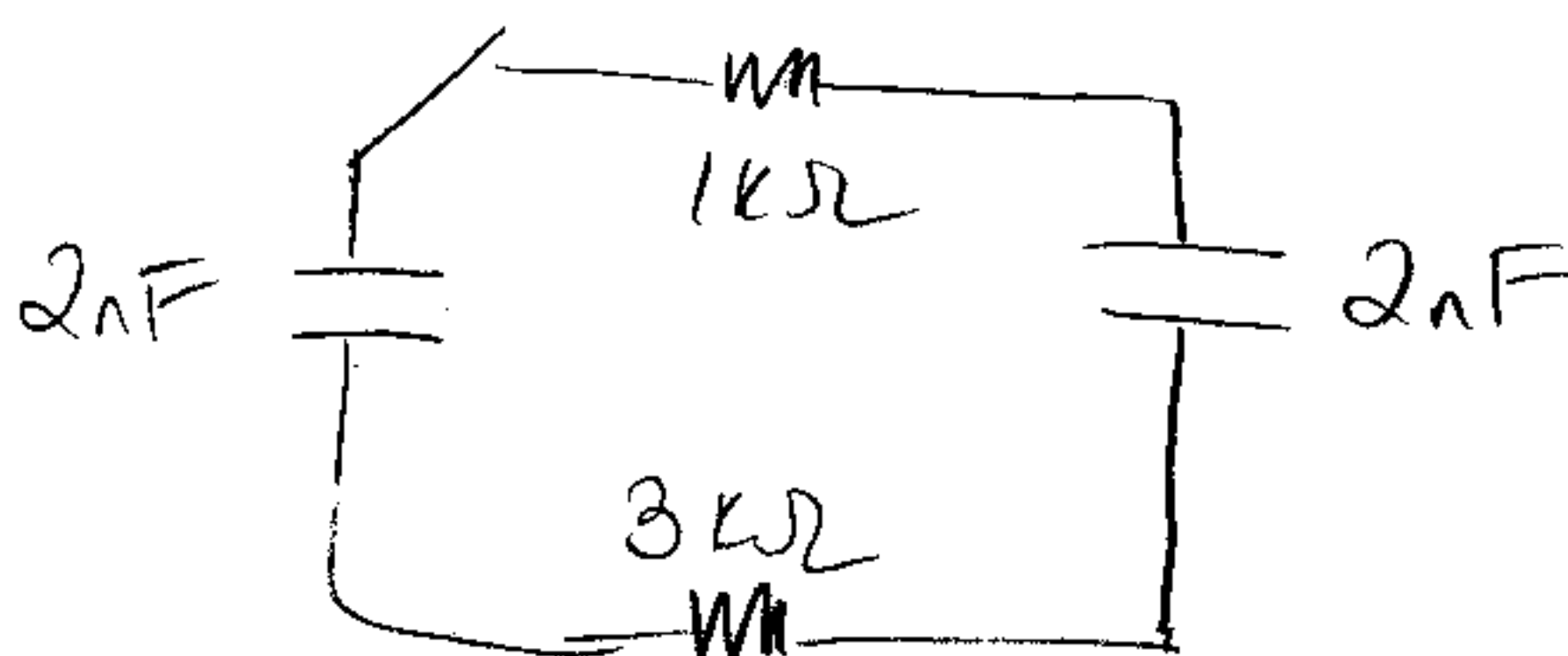Use $t \geq 0$ circuit to find $RC + V_{\text{out}, f}$.




$$RC = 4 \mu\text{s}$$

All in series,


$$R = 1\text{k} + 3\text{k} = 4\text{k}\Omega$$

$$C = \left(\frac{1}{2\text{nF}} + \frac{1}{2\text{nF}} \right)^{-1} = 1\text{nF}$$

Problem 6, Page 2

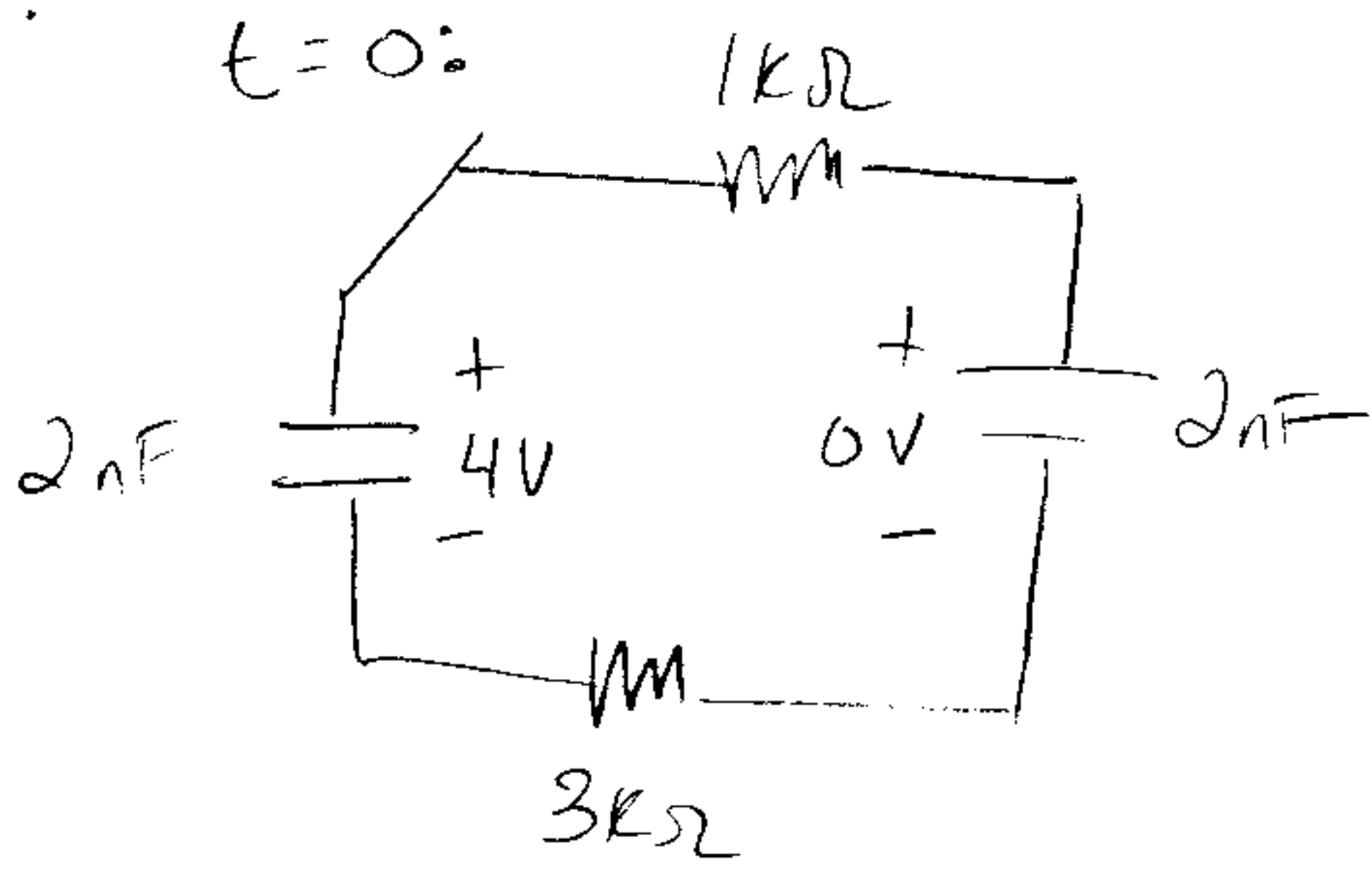

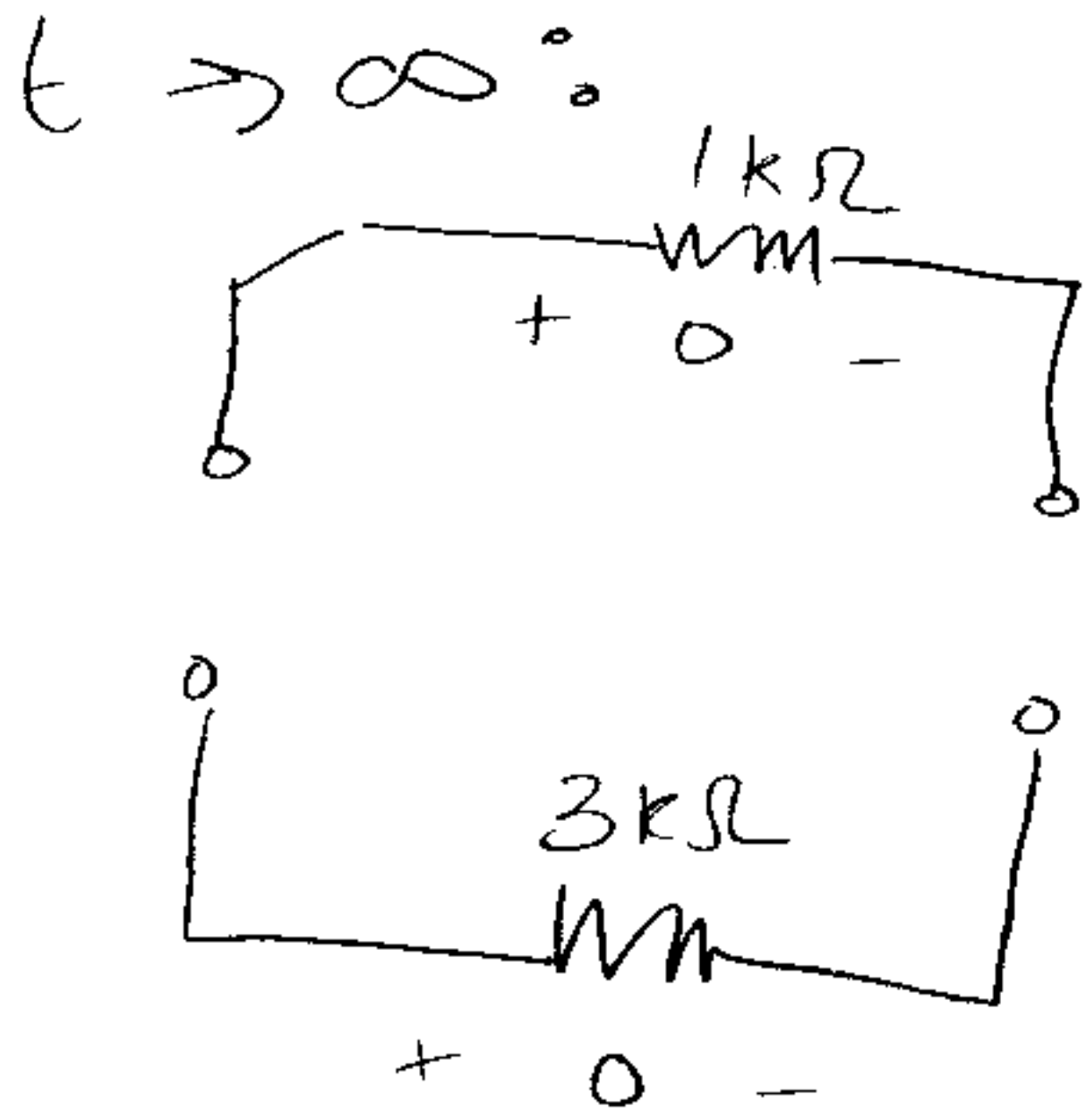Initially, left capacitor is charged & right is discharged.




Eventually, both capacitors act as open circuits. So 0A flows, so both resistors have 0V. So both capacitors have equal voltage to satisfy KVL.


Left capacitor must give $1/2$ its charge to right capacitor. Since capacitances equal, equal charge will result in equal voltage ($Q = CV$). $V_{out,f} = 1/2 V_{out}(0) = 2V$

So until $t = 4\mu s$, $V_{out}(t) = 2V + (4V - 2V)e^{-t/4\mu s}$ V.

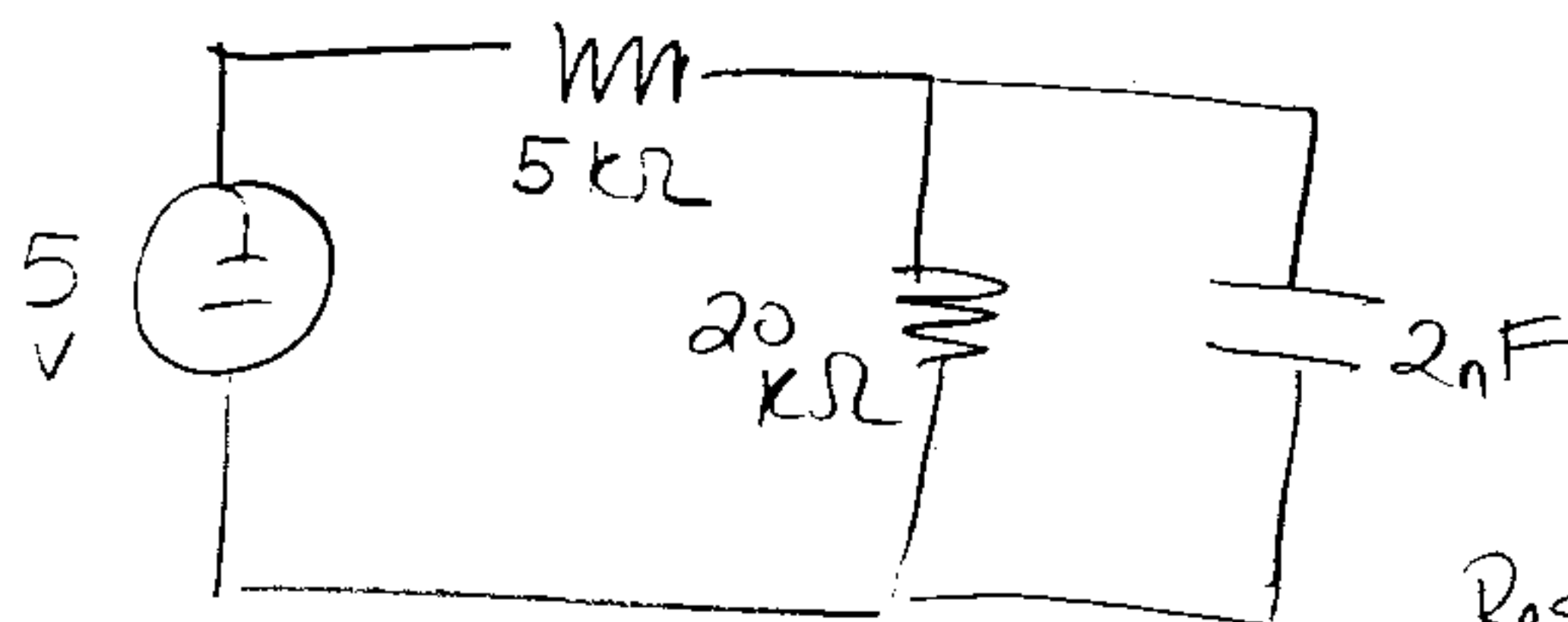At $t = 4\mu s$, switch occurs. $V_{out}(4\mu s) = 2V + 2Ve^{-\frac{4\mu s}{4\mu s}} = 2.74V$.
As $t \rightarrow \infty$, we go back to circuit at $t = 0^-$. $V_{out,f} = 4V$.



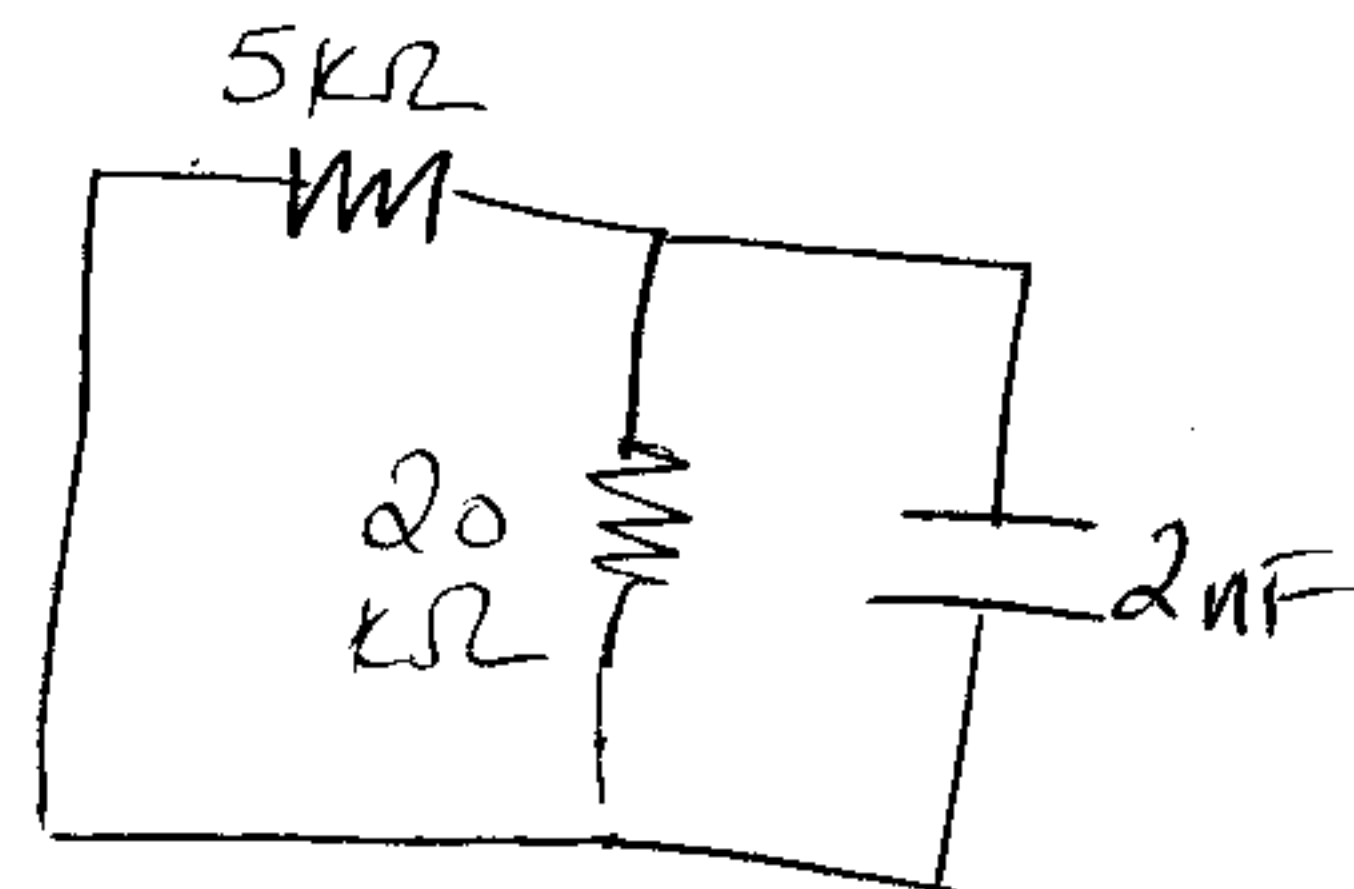To see R_{eq} , kill voltage source. Resistors in parallel.



R_{eq} is $(\frac{1}{5k\Omega} + \frac{1}{20k\Omega})^{-1} = 4k\Omega$ $RC = 8\mu s$

So after $t = 4\mu\text{s}$, $V_{\text{out}}(t) = 4\text{V} + (2.74 - 4\text{V}) e^{\frac{-(t-4\mu\text{s})}{8\mu\text{s}}}$


$$V_{\text{out}}(t) = \begin{cases} 2 + 2e^{-\frac{t}{4\mu\text{s}}} \text{ V} & 0 \leq t \leq 4\mu\text{s} \\ 4 - 1.26e^{\frac{-(t-4\mu\text{s})}{8\mu\text{s}}} & t > 4\mu\text{s} \end{cases}$$

b) We only have non zero current through the $1\text{k}\Omega$ resistor when $0 \leq t \leq 4\mu\text{s}$ (resistor disconnected when in position "1").

$V_{1\text{k}}(t) = 0$ for $t > 4\mu\text{s}$.

When in position "0",
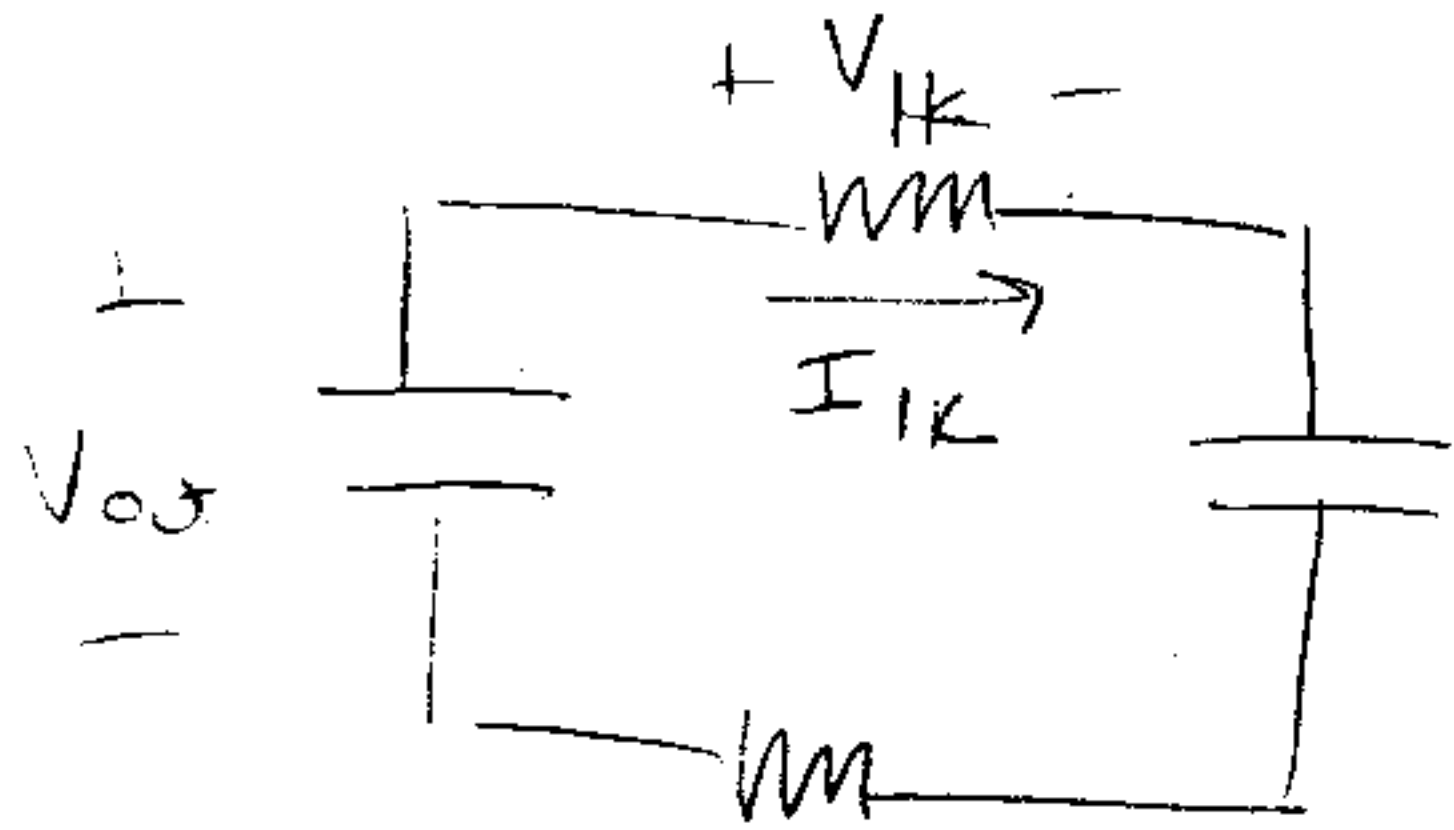
$$V_{1\text{k}}(t) = 1\text{k}\Omega I_{1\text{k}} = 1\text{k}\Omega \left(-2\text{nF} \frac{dV_{\text{out}}}{dt} \right)$$



$$= -(1 \times 10^3)(2 \times 10^{-9}) \left(\frac{-2}{4 \times 10^{-6}} e^{-\frac{t}{4\mu\text{s}}} \right) \text{ V}$$

$$= e^{-\frac{t}{4\mu\text{s}}} \text{ V}$$

So

$$V_{1\text{k}}(t) = \begin{cases} e^{-\frac{t}{4\mu\text{s}}} \text{ V} & 0 \leq t \leq 4\mu\text{s} \\ 0 & t > 4\mu\text{s} \end{cases}$$

$$c) E = \int_0^{4\mu s} P(t) dt = \int_0^{4\mu s} \frac{V_{IK}(t)^2}{1k\Omega} dt$$


$$= \int_0^{4\mu s} e^{-\frac{2t}{4\mu s}} / 1000 dt$$

$$= \frac{1}{1000} \cdot \frac{-4 \times 10^{-6}}{2} \left(e^{-\frac{2t}{4\mu s}} \right) \Big|_0^{4\mu s}$$

$$= -\frac{4 \times 10^{-6}}{2000} (e^{-2} - 1) = 1.7 \text{ nW}$$

Name _____

Problem 7: 10 Points Possible

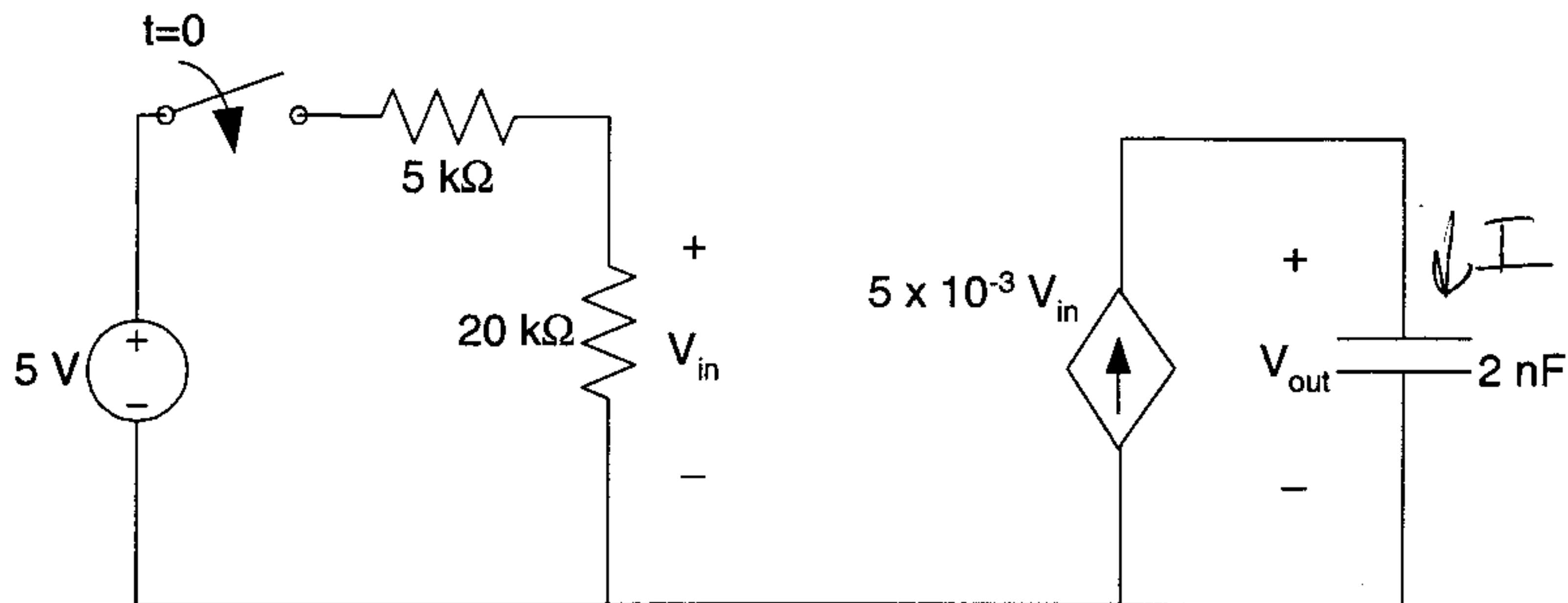

Suppose that $V_{out}(0) = 1$ V.

Find $V_{out}(t)$ for $t \geq 0$.

for $t \geq 0$,

$$I = C \frac{dV_{out}}{dt} \quad 5 \times 10^{-3} V_{in} = 2 \times 10^{-9} F \frac{dV_{out}}{dt}$$

$$V_{in} = 4V \text{ for } t \geq 0 \text{ by voltage division}$$

$$\frac{dV_{out}}{dt} = \frac{5 \times 10^{-3} \cdot 4}{2 \cdot 10^{-9}} \text{ V/s} = 10 \cdot 10^6 \text{ V/s}$$

$$V_{out}(t) = \int_0^t \frac{dV_{out}}{dt'} dt' + V_{out}(0)$$

$$= \int_0^t 10^7 dt' + 1V$$

$$= 10^7 t + 1$$