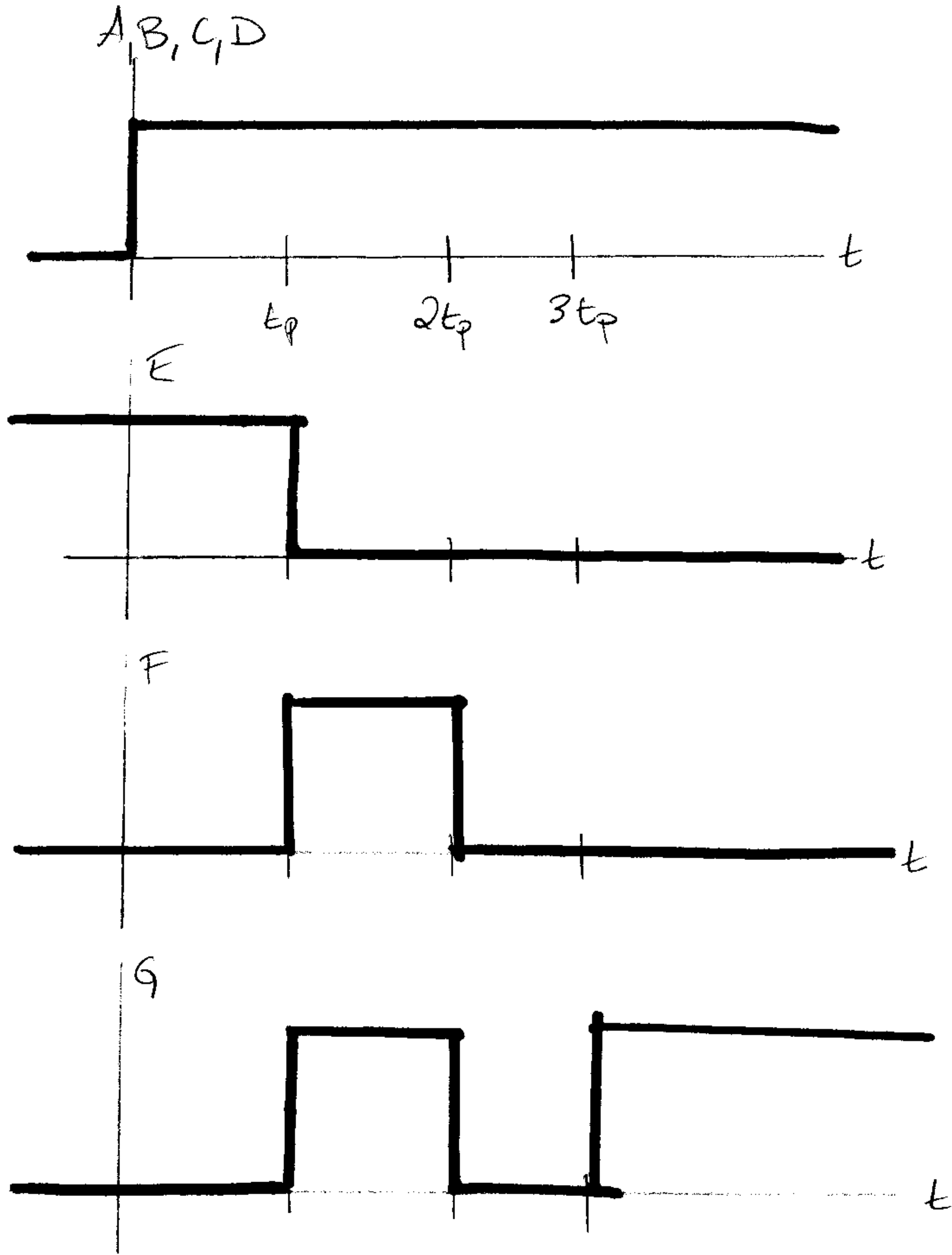



Problem 10

Practice Exam Solutions



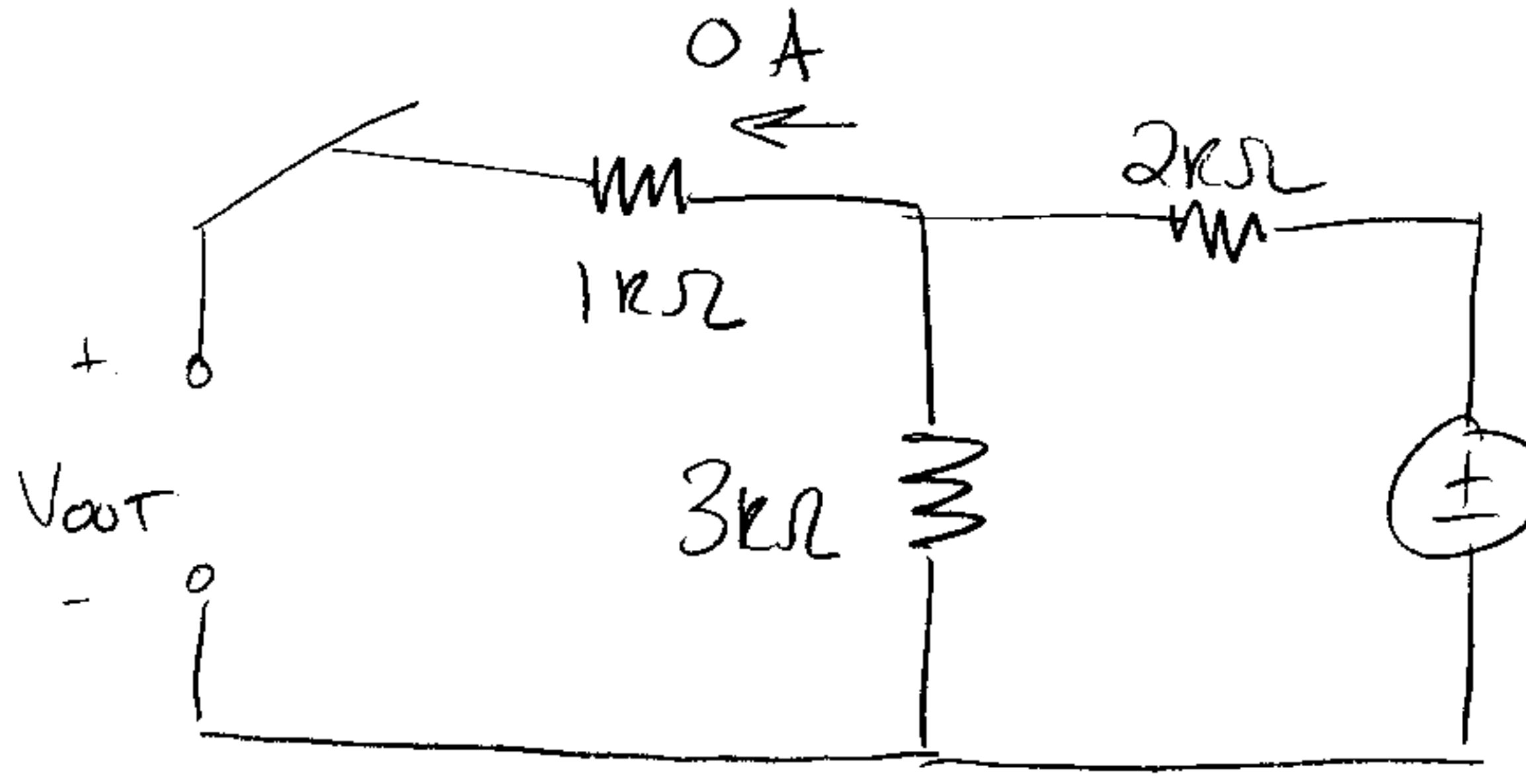
Problem 2: Need to find  $V_{OUT}(0)$ .

$t < 0$ : After a long time, capacitor is open circuit




Since 0A thru  $1k\Omega$  resistor (open circuit), voltage division of 5V over  $2k\Omega + 3k\Omega$  resistors

(they have same current):

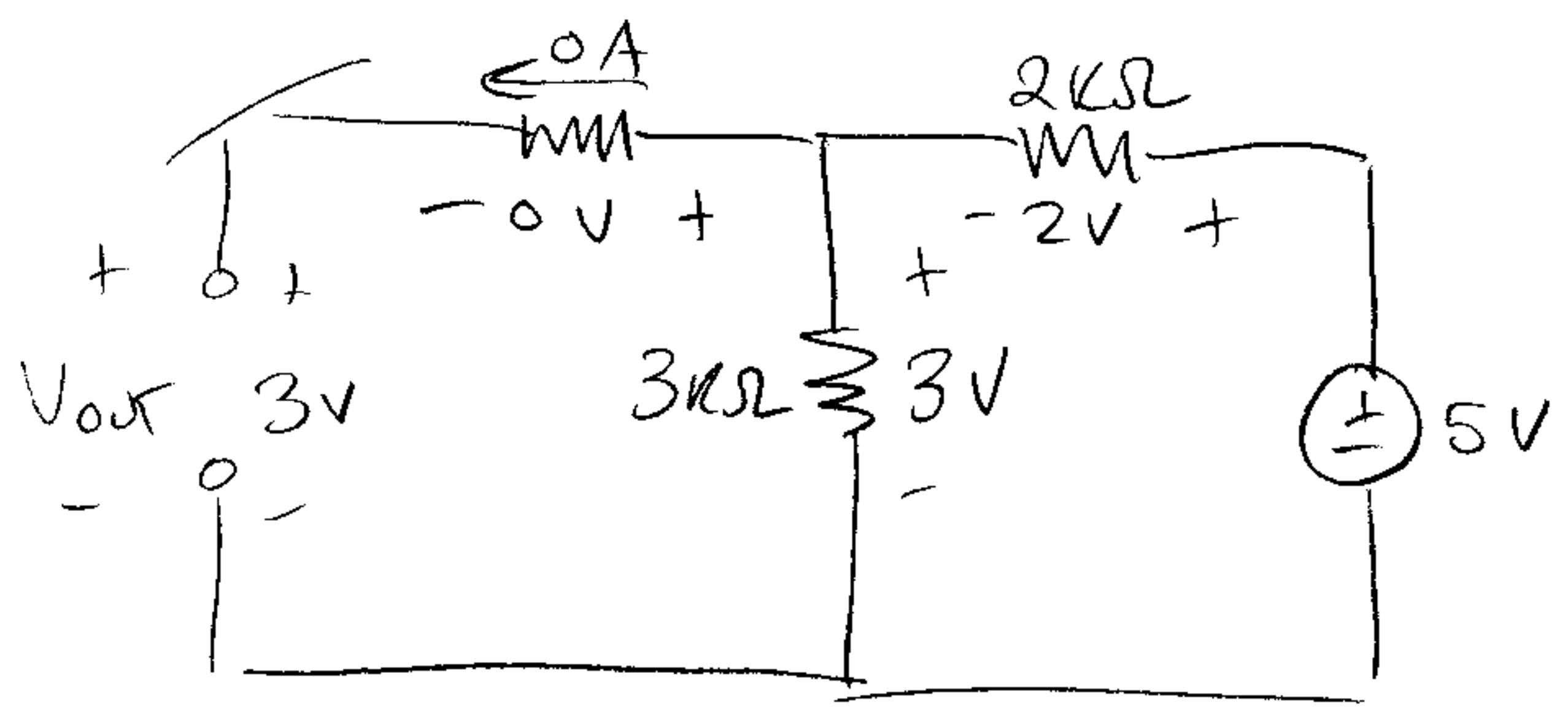

By KVL,  $V_{OUT}(0) = 3V$ .

$t \geq 0$  until  $t = 8\mu s$ :

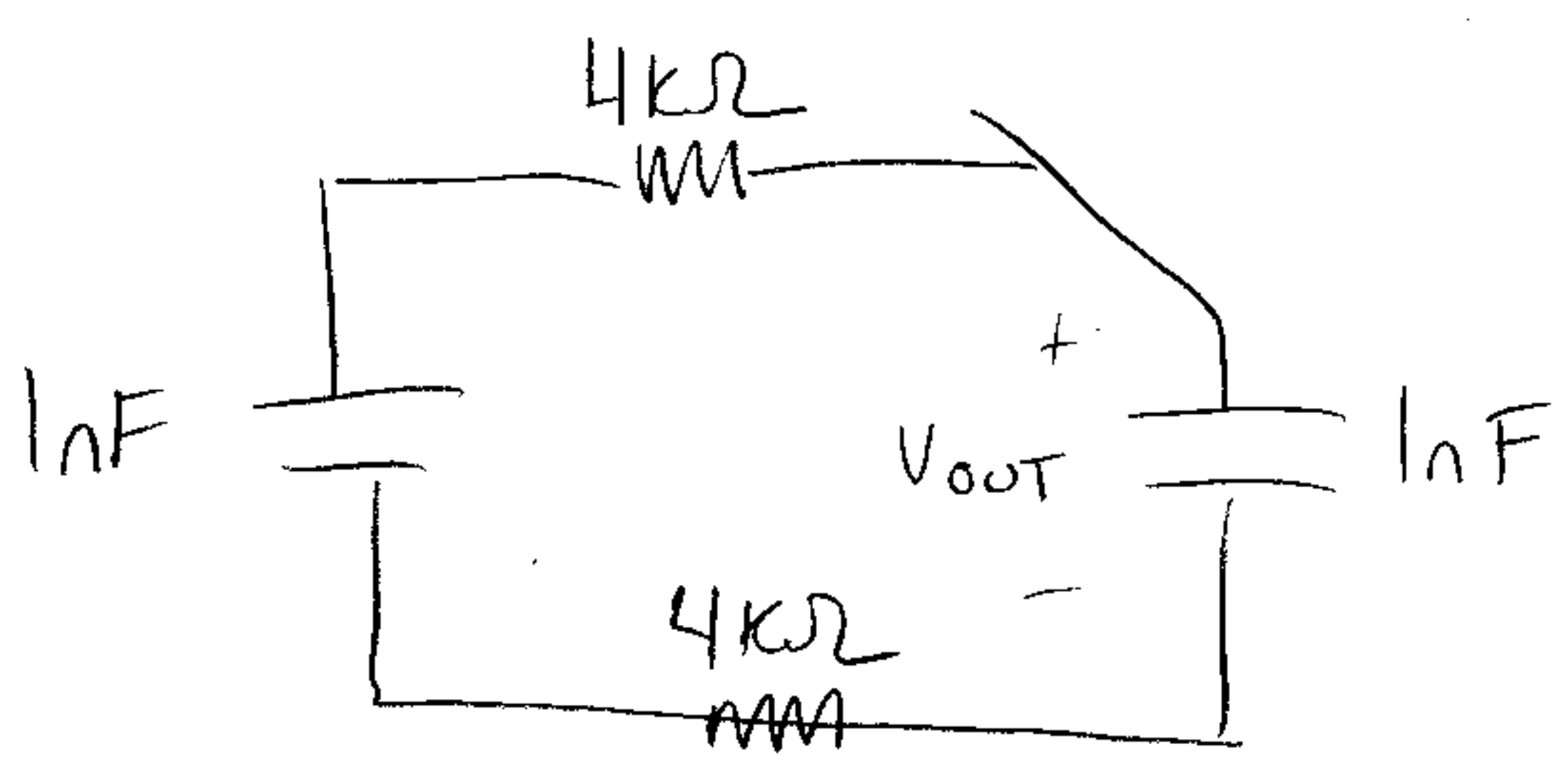


Everything in series.  
 Total resistance:  $8k\Omega$ .  
 Total capacitance:  $500pF$ .  
 $RC = 4\mu s$ .

$V_{OUT}(0) = 3V$

$V_{OUT,f} = 1.5V$  (must give  $1/2$  its charge to other capacitor)

$V_{OUT}(t) = 1.5 + (3 - 1.5)e^{-t/4\mu s}$

$t \geq 8 \mu s$ :

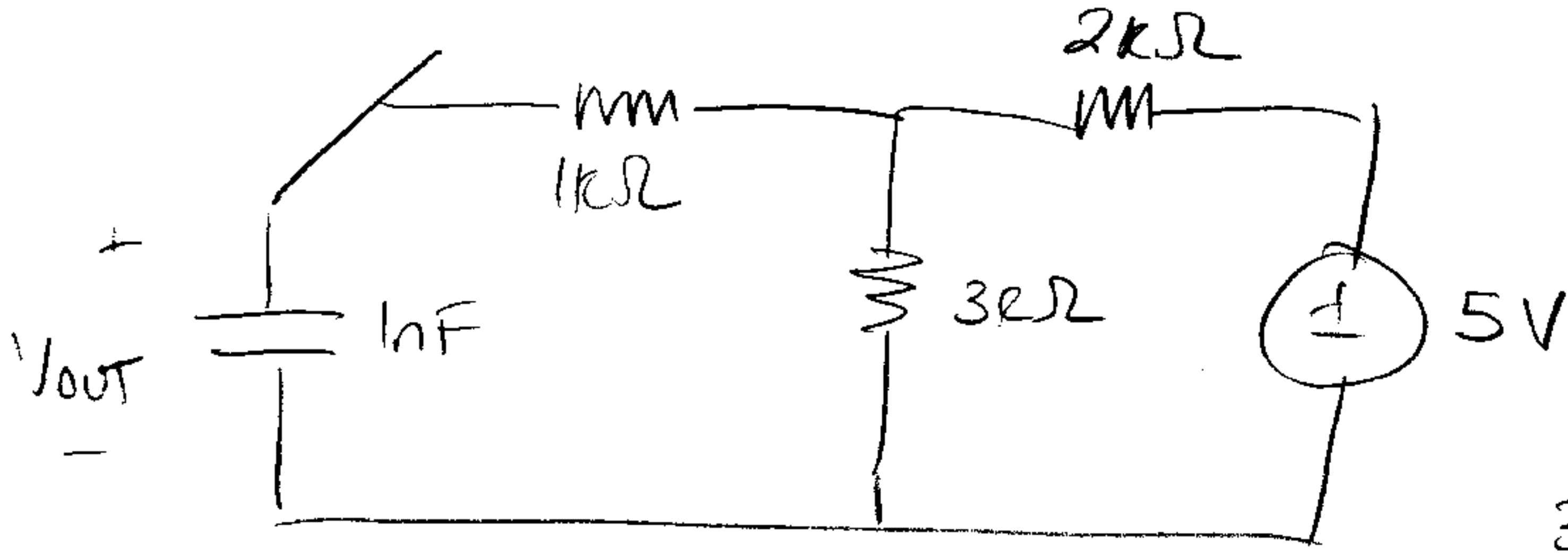

$C = 1nF$

Req: kill source  
to see that

$3k\Omega + 2k\Omega$  in parallel,  
Combo is  $(\frac{1}{3k} + \frac{1}{2k})^{-1} = 1.2k$

This in series with  $1k$  gives

$R_{eq} = 2.2k\Omega$

$V_{out}(8\mu s) = 1.5 + (3 - 1.5)e^{-\frac{8\mu s}{4\mu s}}$   
 $= 1.70V$

$V_{out_f} = 3V$  by same analysis as  $V_{out}(0)$

$V_{out}(t) = 3V + (1.7 - 3)e^{-\frac{-(t-8\mu s)}{2.2\mu s}}$


Overall,

$$V_{out}(t) = \begin{cases} 1.5 + 1.5e^{-\frac{t}{4\mu s}} & 0 \leq t \leq 8\mu s \\ 3 - 1.3e^{-\frac{-(t-8\mu s)}{2.2\mu s}} & 8\mu s \leq t \end{cases}$$

# Problem 3:

4

For  $t \geq 0$ , until  $t = 3s$ ,

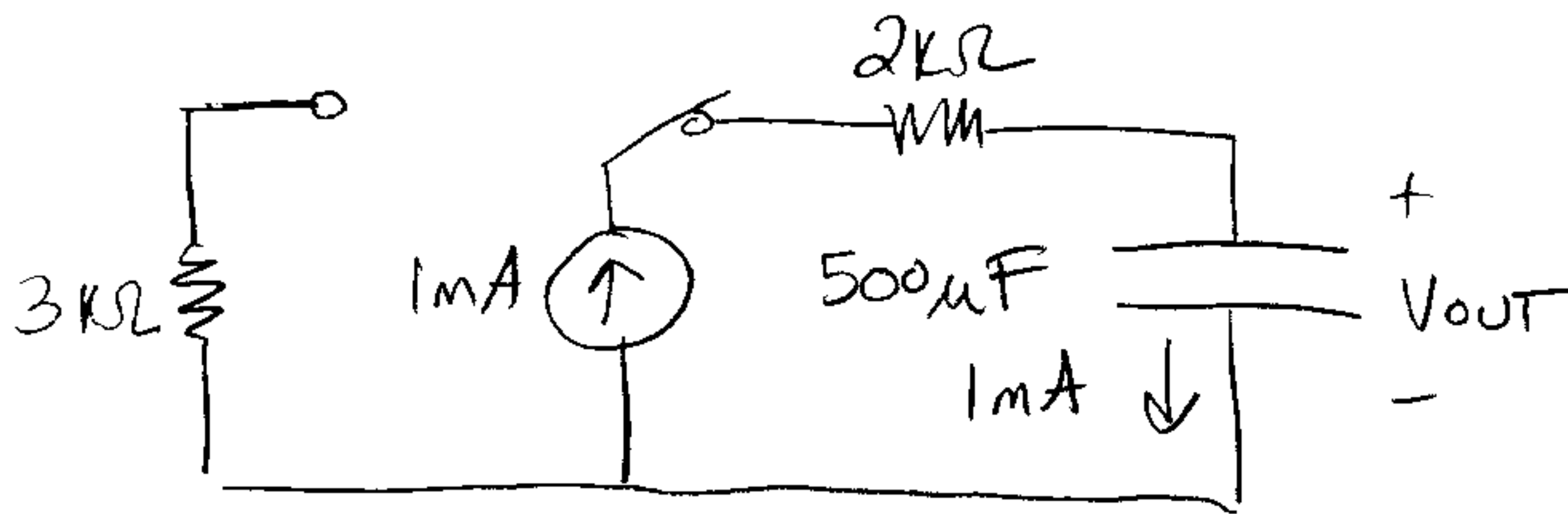


$$I = C \frac{dV}{dt}$$

$$1mA = 500\mu F \frac{dV_{out}}{dt}$$

$$V_{out}(t) = \int_0^t \frac{1mA}{500\mu F} dt' + V_{out}(0)$$

$$= \frac{1mA}{500\mu F} t + 1V = 2t + 1V$$

For  $t \geq 3s$ ,

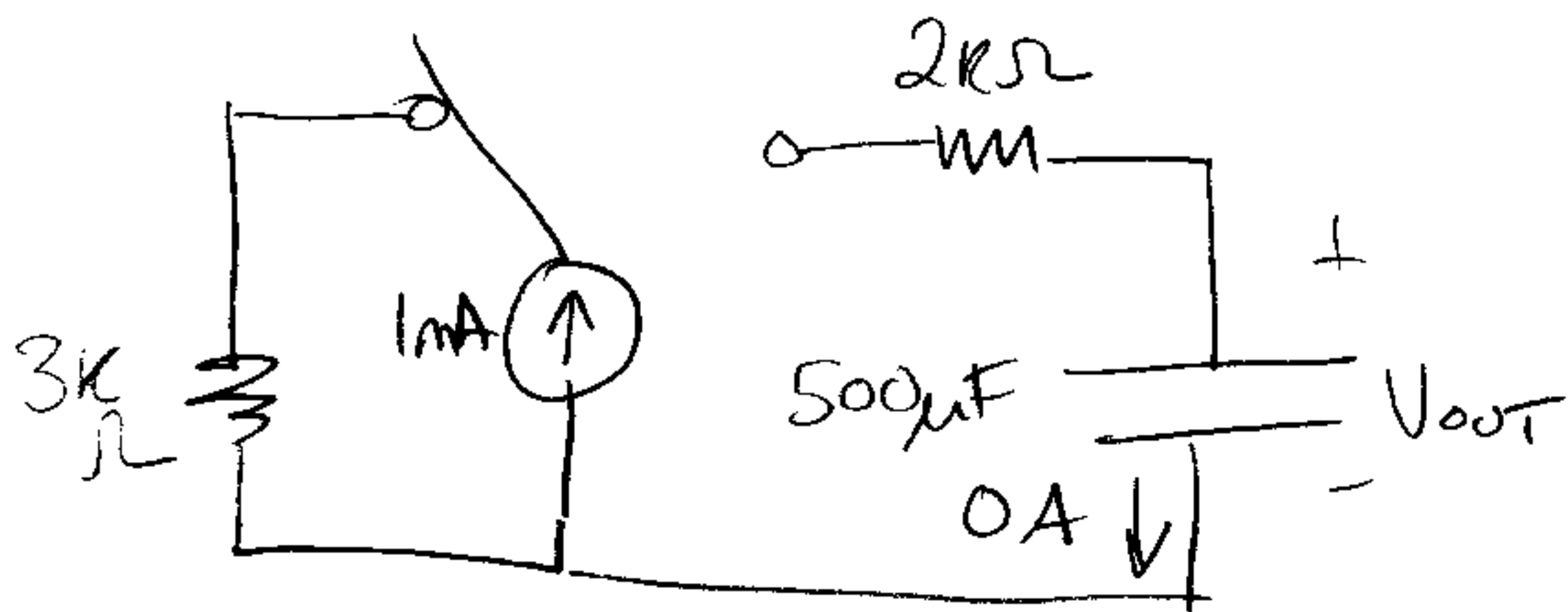


$$V_{out}(t) = \int_{3s}^t 0 dt' + V_{out}(3s)$$

$$= V_{out}(3s)$$

$$= 7V$$

$$V_{out}(t) = \begin{cases} 2t + 1V & 0 \leq t \leq 3s \\ 7V & 3s \leq t \end{cases}$$

# Problem 4:

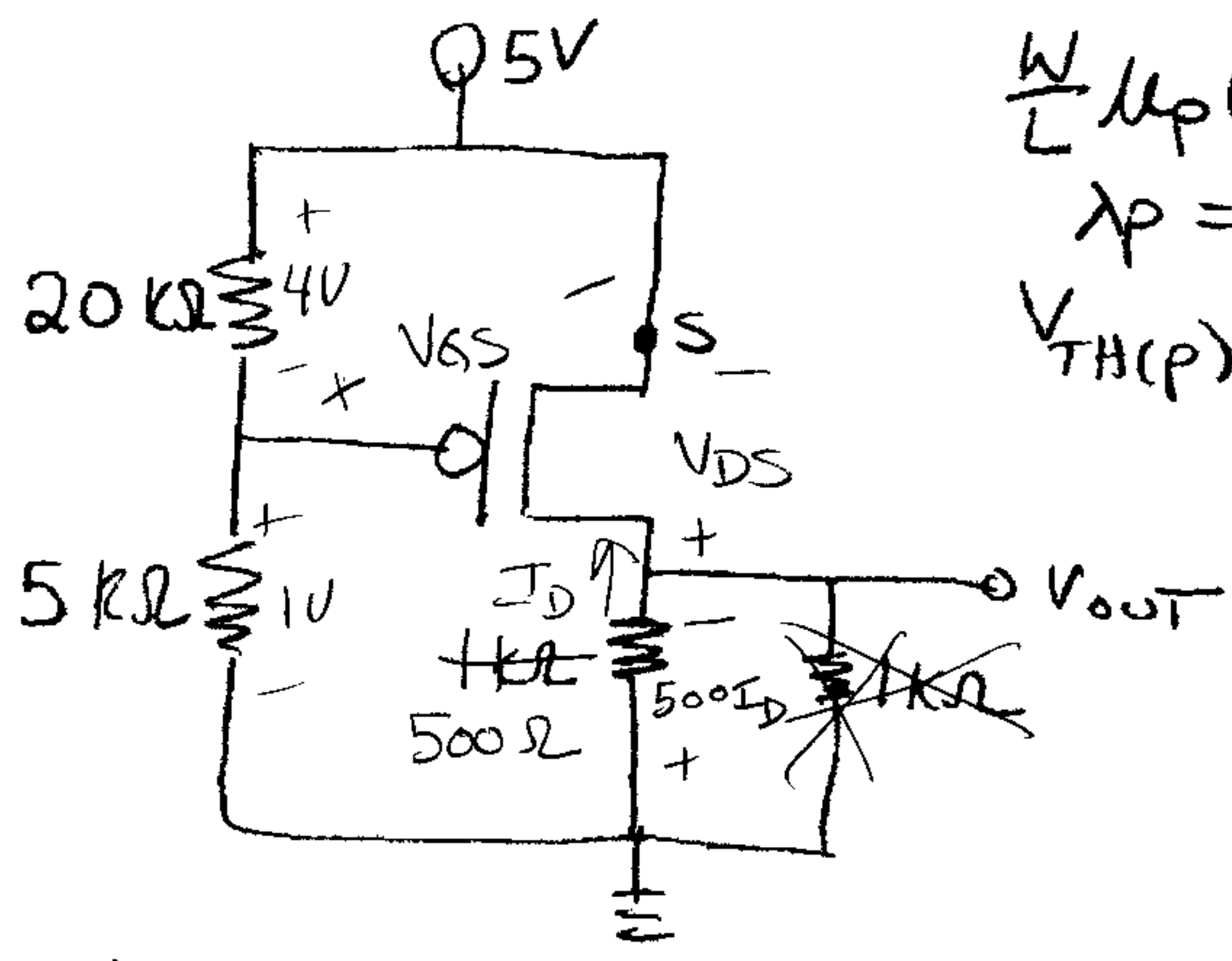

$$\frac{W}{L} \mu_p C_{ox} = 2 \text{ mA/V}^2$$

$$\lambda_p = 0$$

$$V_{TH(p)} = -1 \text{ V}$$

Find  $V_{out}$ .

By voltage division (since no current into gate)  
 $20 \text{ k}\Omega$  resistor has  $4 \text{ V}$  as shown.

By KVL,  $V_{GS} = -4 \text{ V}$       $V_{GS} < V_{TH} \Rightarrow$  not cutoff

Guess saturation (although the bigger  $V_{GS}$  is, the more likely we are in triode mode!)

$$I_D = 2 \text{ mA/V}^2 \cdot \frac{1}{2} \cdot (-4 \text{ V} - (-1 \text{ V}))^2 = -9 \text{ mA}$$

Can combine parallel  $1 \text{ k}\Omega$  resistors to one  $500 \Omega$  resistor.

KVL:  $500 \Omega \cdot I_D + V_{DS} + 5 \text{ V} = 0$       $V_{DS} = -0.5 \text{ V}$

$V_{DS} \neq V_{GS} - V_{TH}$  so must be triode mode.

## Problem 4 Cont.

(6)

$$I_D = -2\text{mA}/V^2 \left( -4V - -1V - \frac{V_{DS}}{2} \right) V_{DS}$$

From KVL,  $I_D = -\frac{5+V_{DS}}{500}$

Substitute & solve...

$$V_{DS} = \{ -6.45, -1.55 \}$$

-6.45 V impossible since then  $V_{DS} \not> V_{GS} - V_{TH}$   
(and also, associated  $I_D$  would be positive  $\Rightarrow$  can't for PMOS)


So  $V_{DS} = -1.55$ , satisfies  $V_{DS} > V_{GS} - V_{TH}$ .

$$V_{OUT} = -500 I_D \quad (\text{see diagram})$$

$$V_{OUT} = -500 \left( -\frac{5+V_{DS}}{500} \right) = \underline{\underline{3.45V}}$$

# Problem 5

7

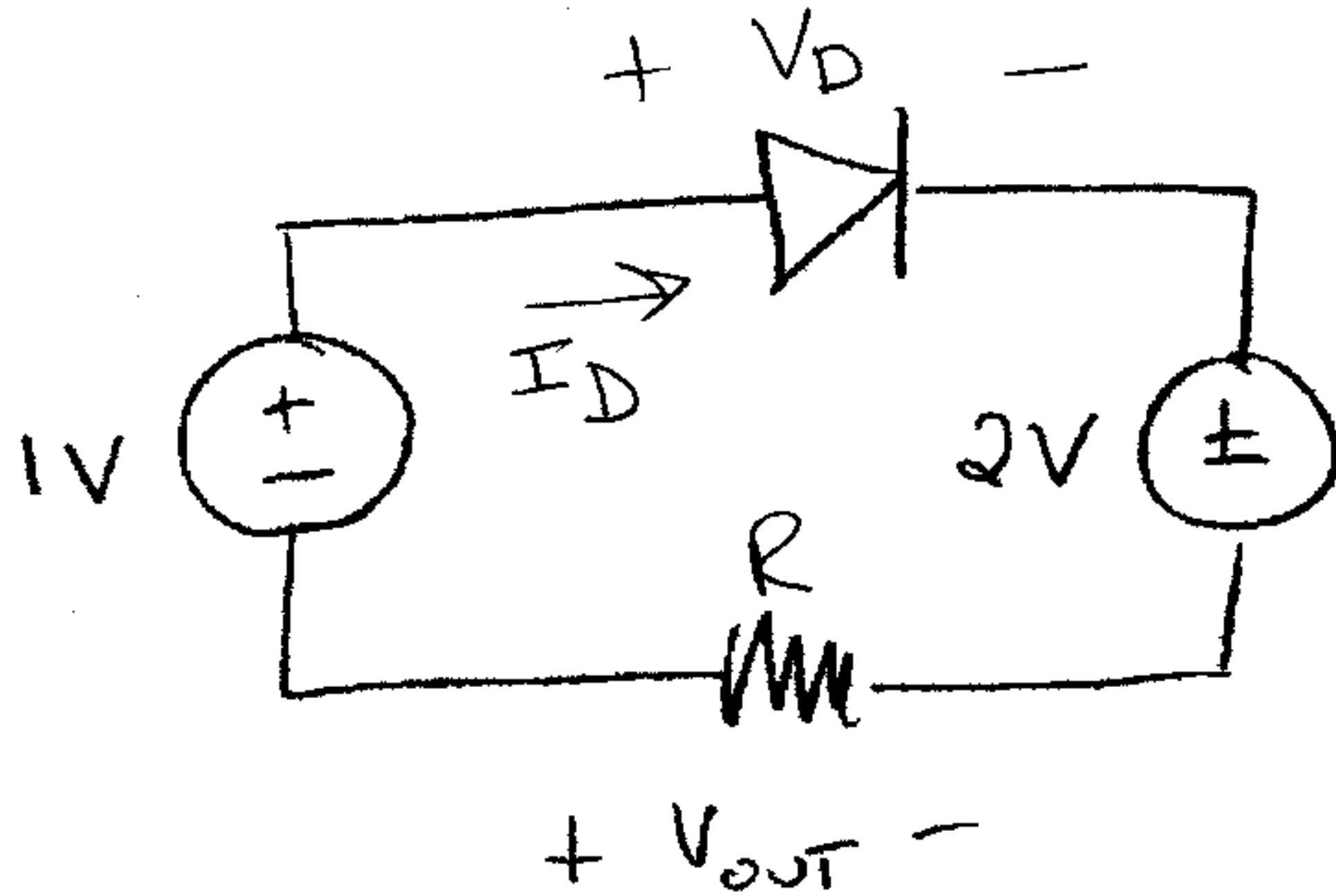

$$V_F = 0.7V$$

Use large-signal model for diode.

By KVL,

$$-1V + V_D + 2V - V_{OUT} = 0$$

By Ohm's law,

$$V_{OUT} = -RI_D$$

$$V_D = -RI_D - 1V$$

If forward bias,  $V_D = 0.7V$  and  $I_D > 0$ .

If reverse bias,  $V_D < 0.7V$  and  $I_D = 0$ .

One of these works in above equation.

If forward bias,

$$0.7 = -RI_D - 1V$$


Since  $R > 0$  &  $I_D > 0$ , impossible.

If reverse bias,

$$V_D = -1V \quad \text{possible under reverse bias,}$$

$$V_{OUT} = -RI_D = -R \cdot 0A = 0V$$

Problem 6:

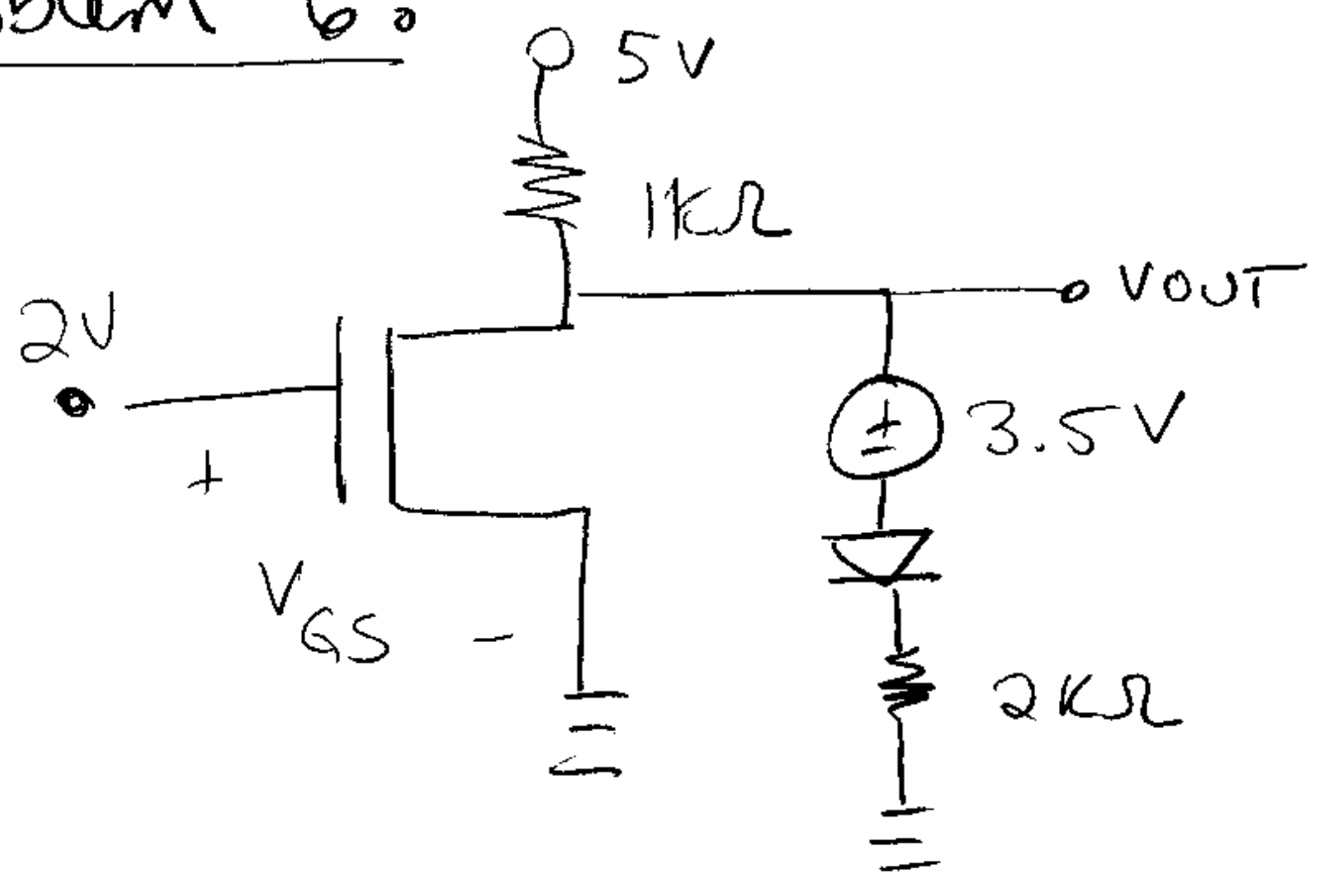

$V_{GS} = 2V$        $V_{GS} > V_{TH} \Rightarrow$  not cutoff

Guess saturation.

$I_D = 1mA / 2 \cdot (2V - 1V)^2 = 1/2 mA$  (not a joke)

Diode forward or reverse biased?


If forward, then  $V_{OUT}$  would be at least 5.5V.

This would make current flow up the 1k resistor.

Since current can't flow up the diode, current would have to flow up transistor, making  $I_D$  negative. Not possible for NMOS.

Guess reverse bias.

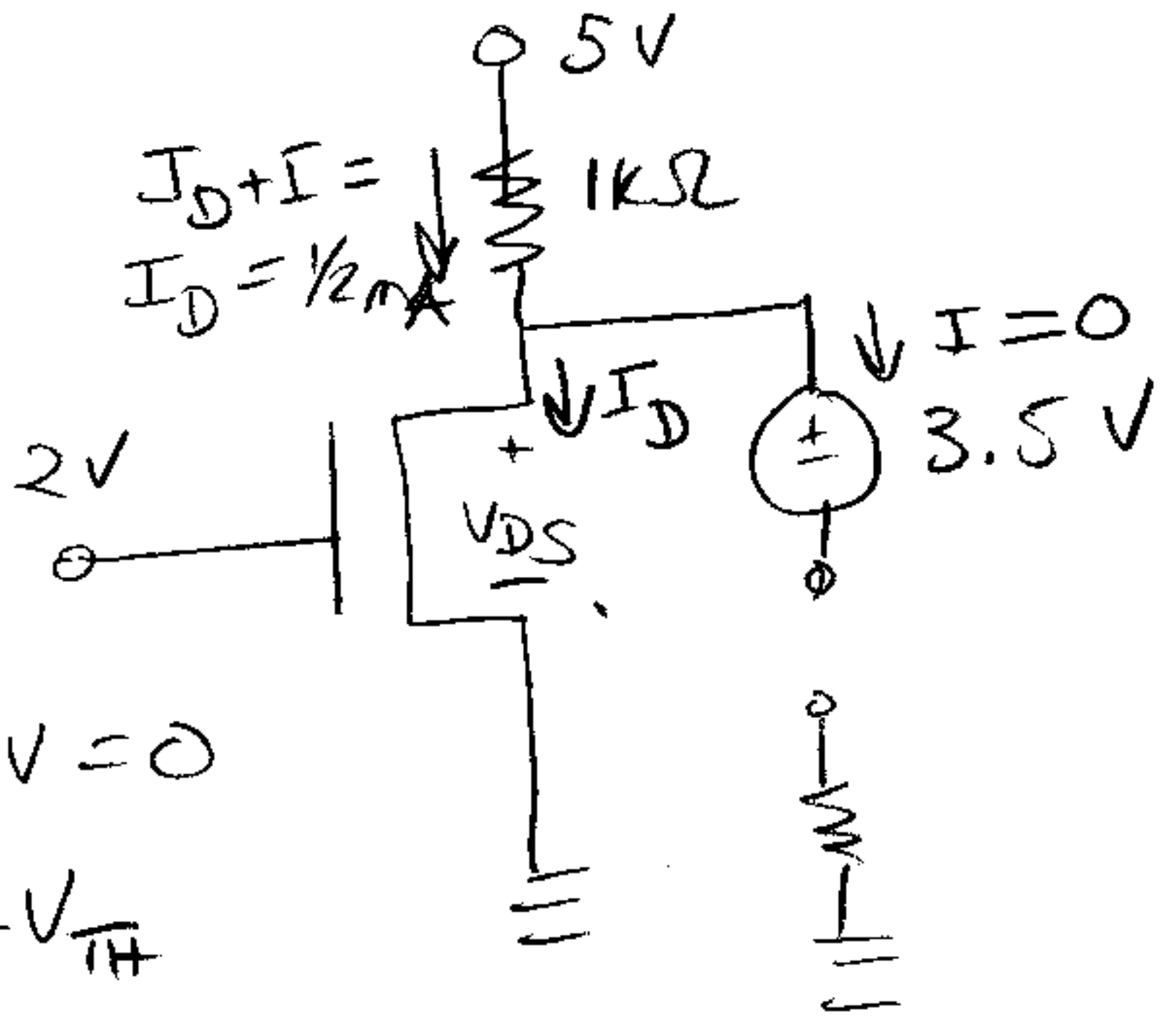Now no current thru diode branch. By KCL,  $I_D$  flows thru 1k resistor.



KVL:  $-V_{DS} - 1k\Omega \cdot 1/2 mA + 5V = 0$

$V_{DS} = 4.5V$        $V_{DS} > V_{GS} - V_{TH}$

Saturation is correct mode.  $V_{OUT} = V_{DS} = 4.5V$