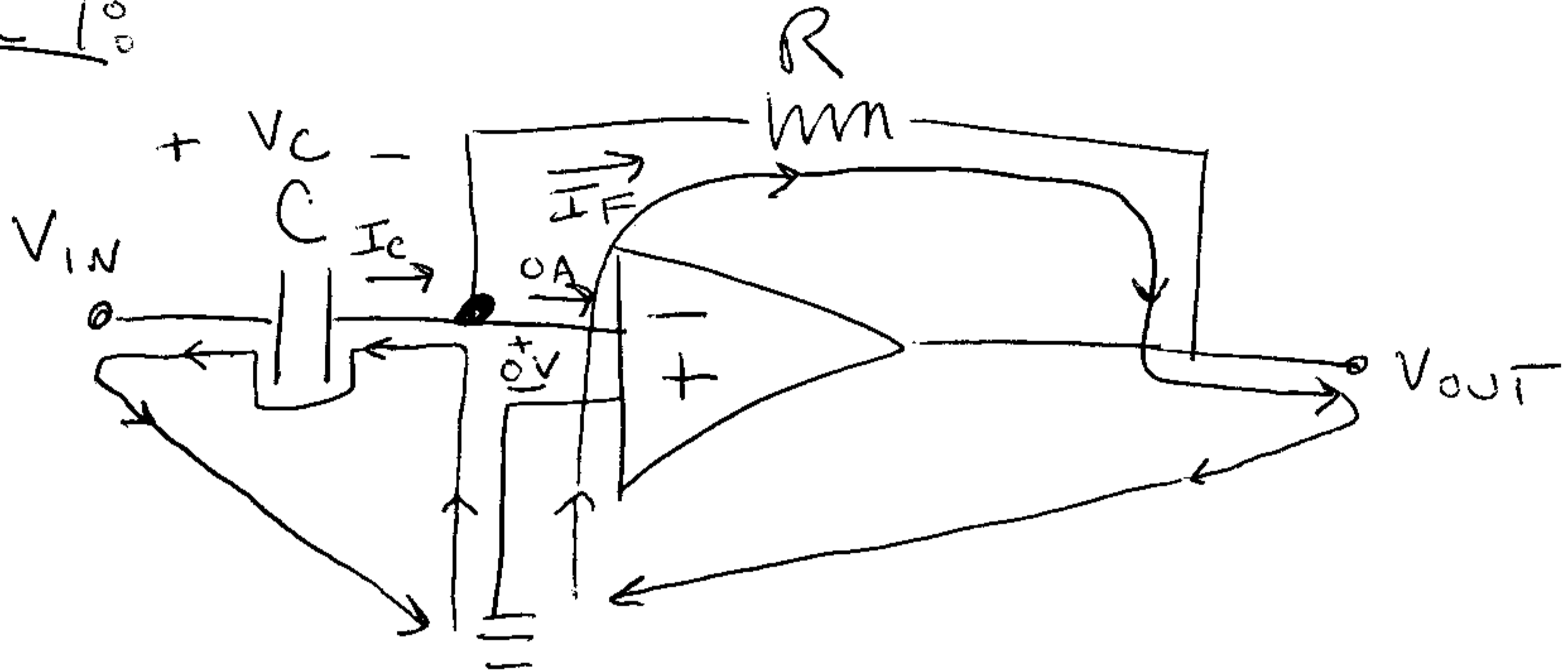


EE 42

Solutions to "Hard" MT2 Review Problems

Problem 1:

a)



KVL around input loop: $-0V - V_C + V_{IN} = 0$

$$V_C = V_{IN}$$

KCL: $I_C = I_F + OA$

$$I_C = I_F$$

Capacitor law: $I_C = C \frac{dV_C}{dt}$

$$I_F = C \frac{dV_C}{dt} = C \frac{dV_{IN}}{dt}$$


KVL around output loop:

$$-0V + I_F R + V_{OUT} = 0 \quad \Rightarrow \quad V_{OUT} = -I_F R$$


$$V_{OUT} = -RC \frac{dV_{IN}}{dt} \quad (\text{Differentiator!})$$

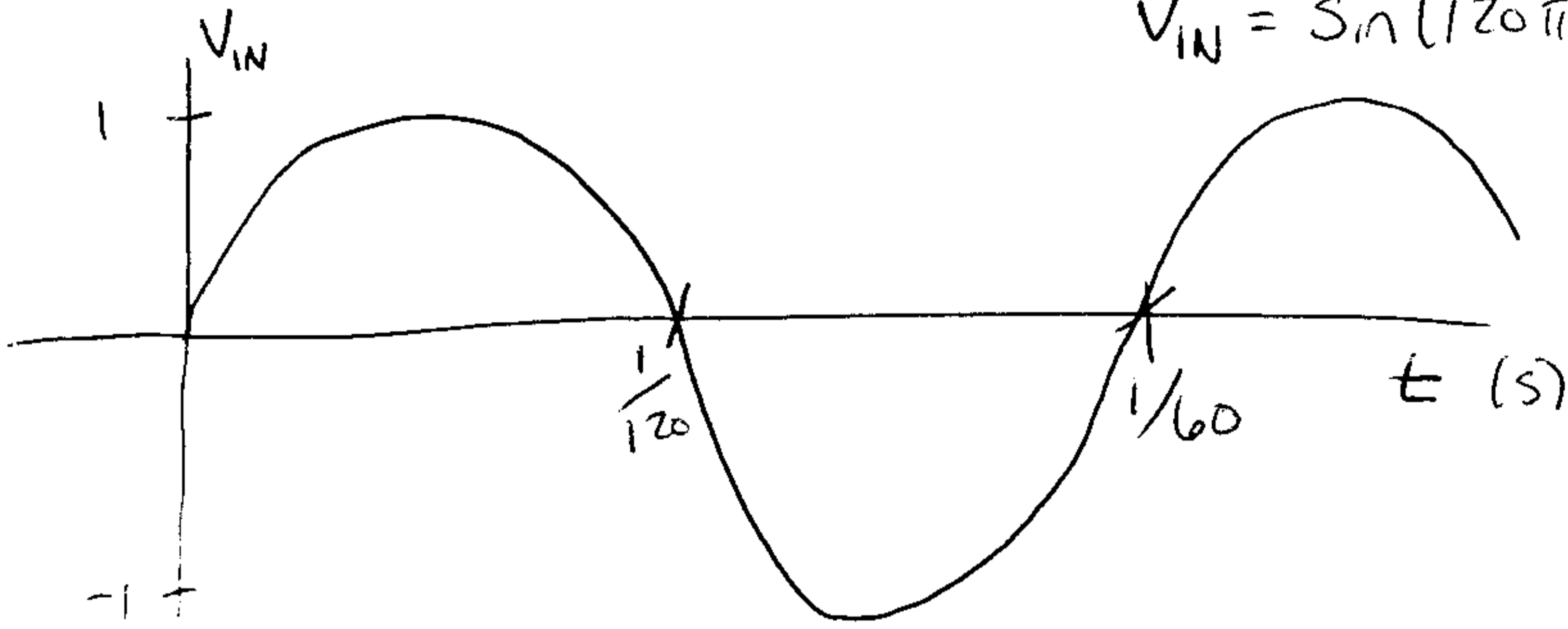b) Assume $RC=1$.

$$V_{IN} = \sin(120\pi t) + 10^{-3} \sin(120 \cdot 10^6 \pi t)$$



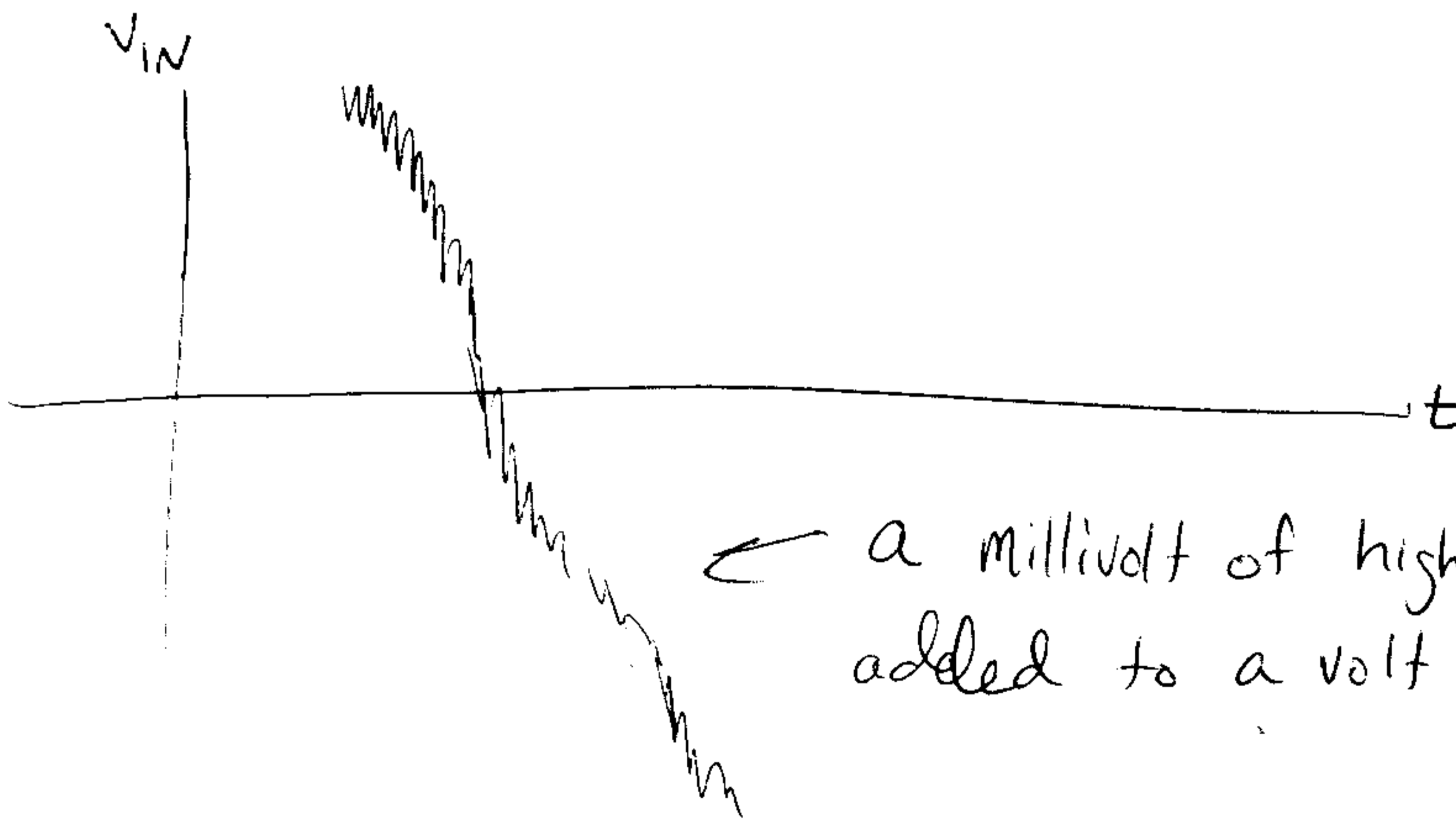The 60 Hz signal is visible; the 60 MHz sine wave is not because it is multiplied by 10^{-3} .
 If you zoomed in, it would look like




← a millivolt of high frequency added to a volt of 60 Hz

3

$$V_{out}(t) = -RC \frac{dV_{in}}{dt}$$

$$= -\left(120\pi \sin(120\pi t) + 120\pi \cdot 10^3 \cos(120\pi \cdot 10^6 t)\right)$$

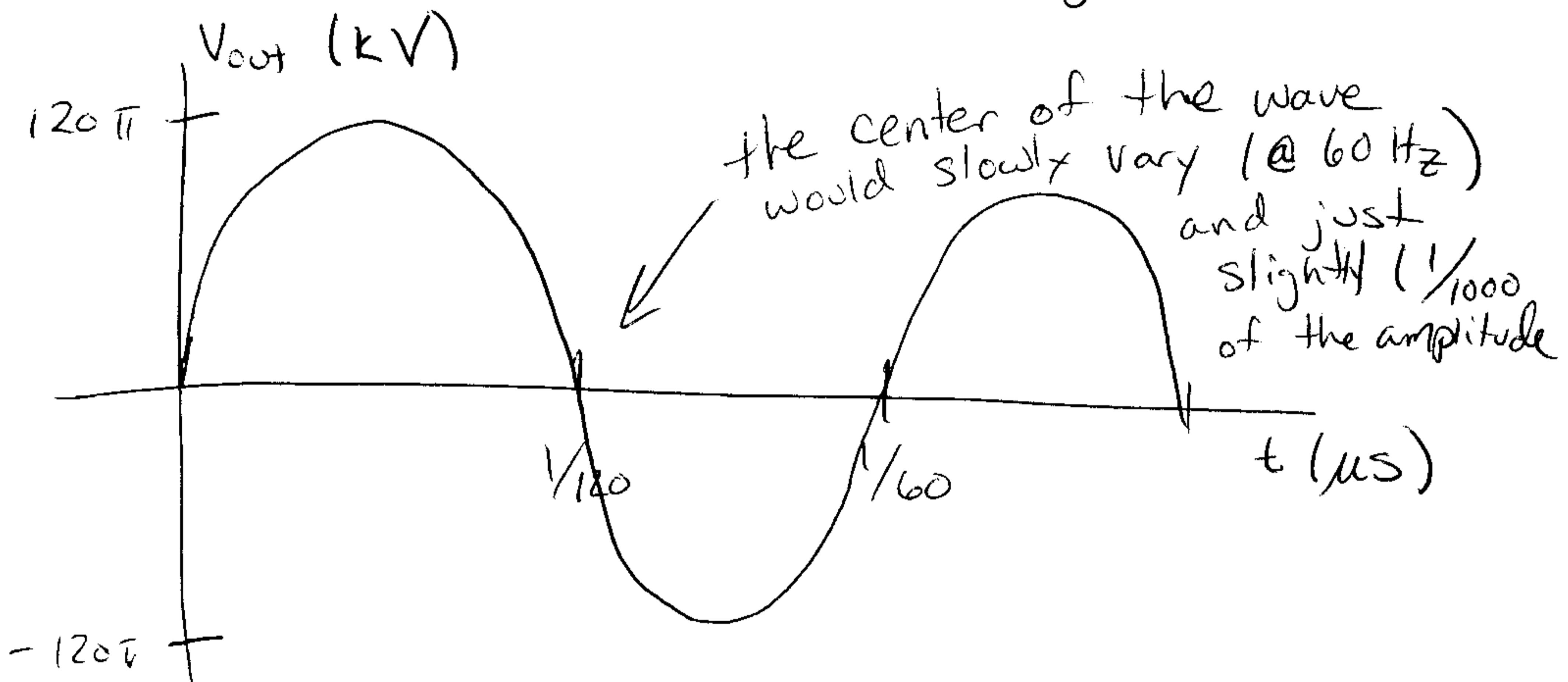
The sinusoids get amplified by their frequencies. The 60MHz noise becomes huge compared to the 60Hz signal.




Moral: Differentiators are noisy and don't work that well.

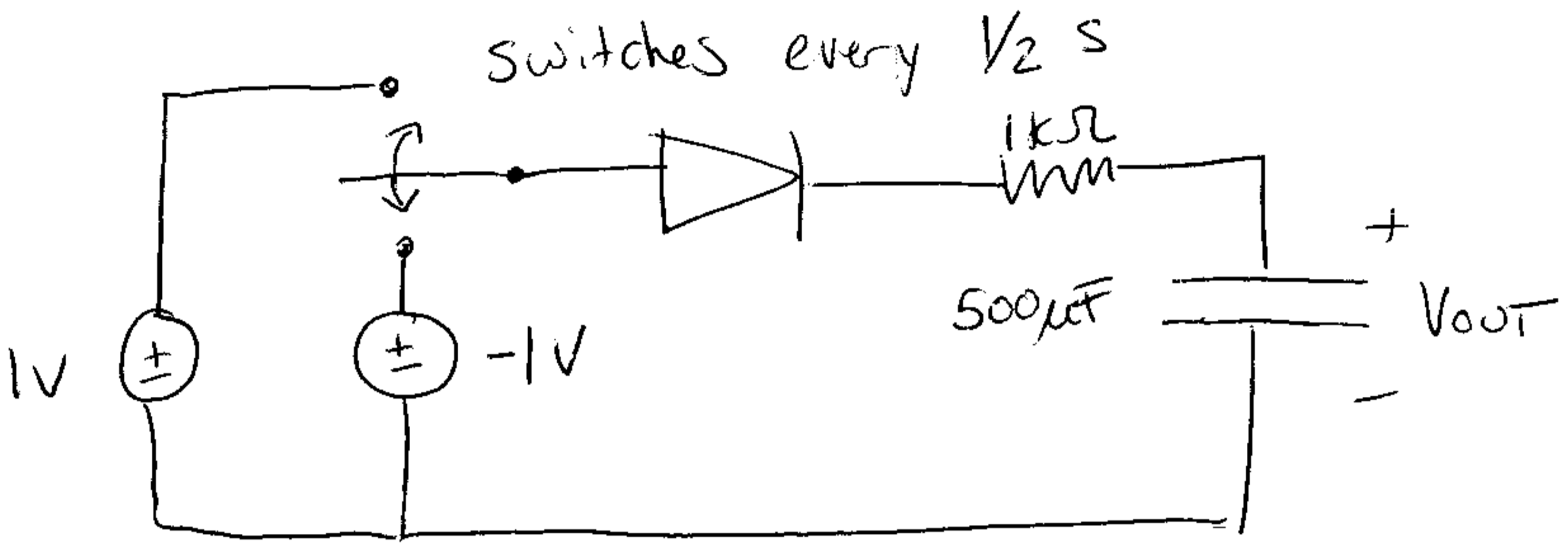Problem 2:

We can look at the V_S source as a switch that goes back & forth between $1V$ and $-1V$:




First, the V_S is at $1V$.

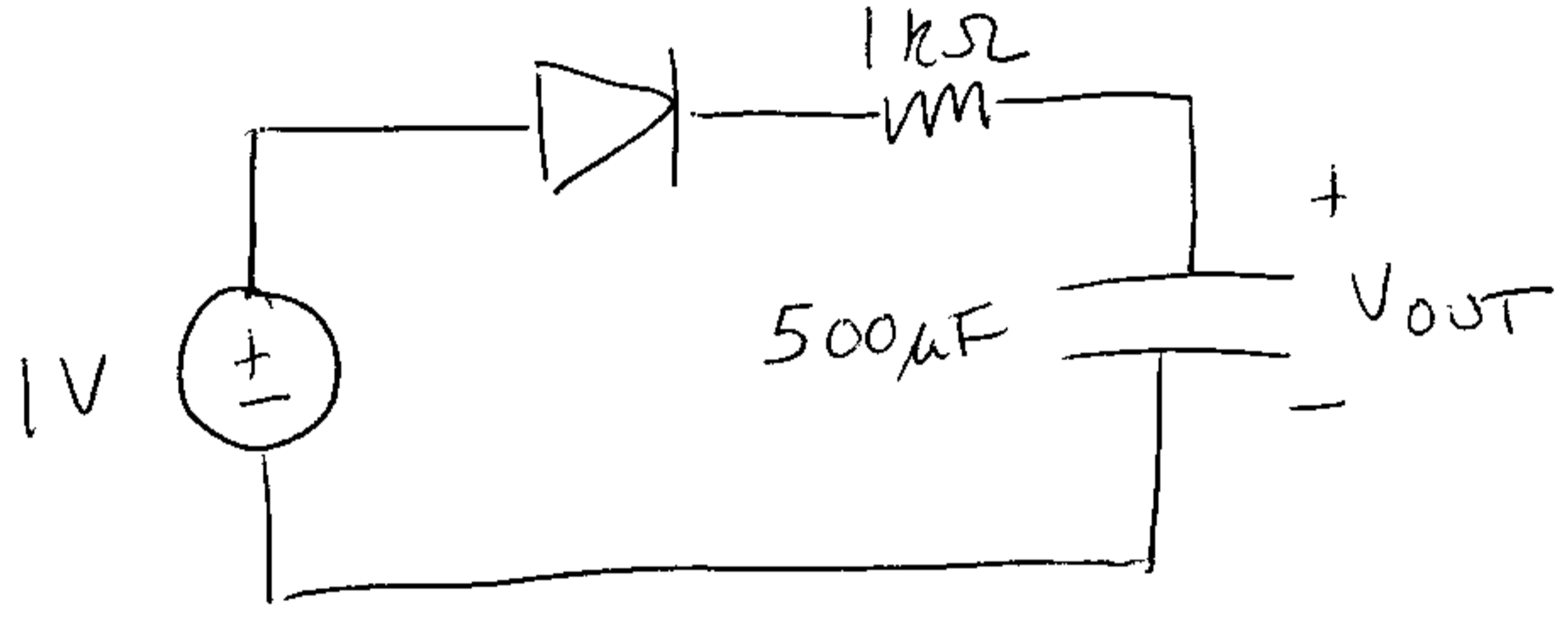


Valid for $0 < t \leq \frac{1}{2} s$

At $t=0$, $V_{out} = 0V$:

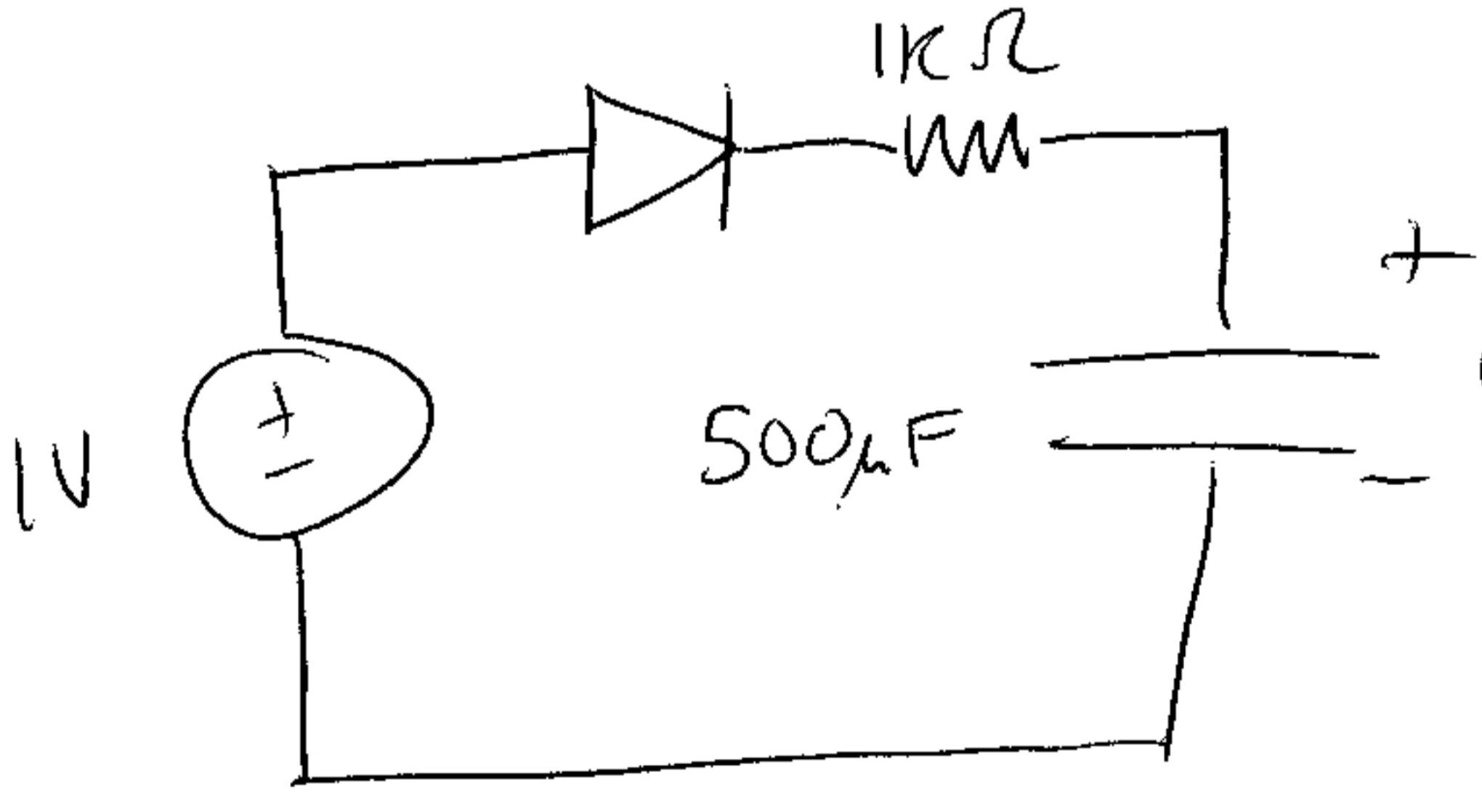

Diode cannot be reverse biased - if so, $0A$ current, so $0V$ across resistor, so $1V$ must fall over diode. Not possible for reverse bias.

↓ forward bias = wire

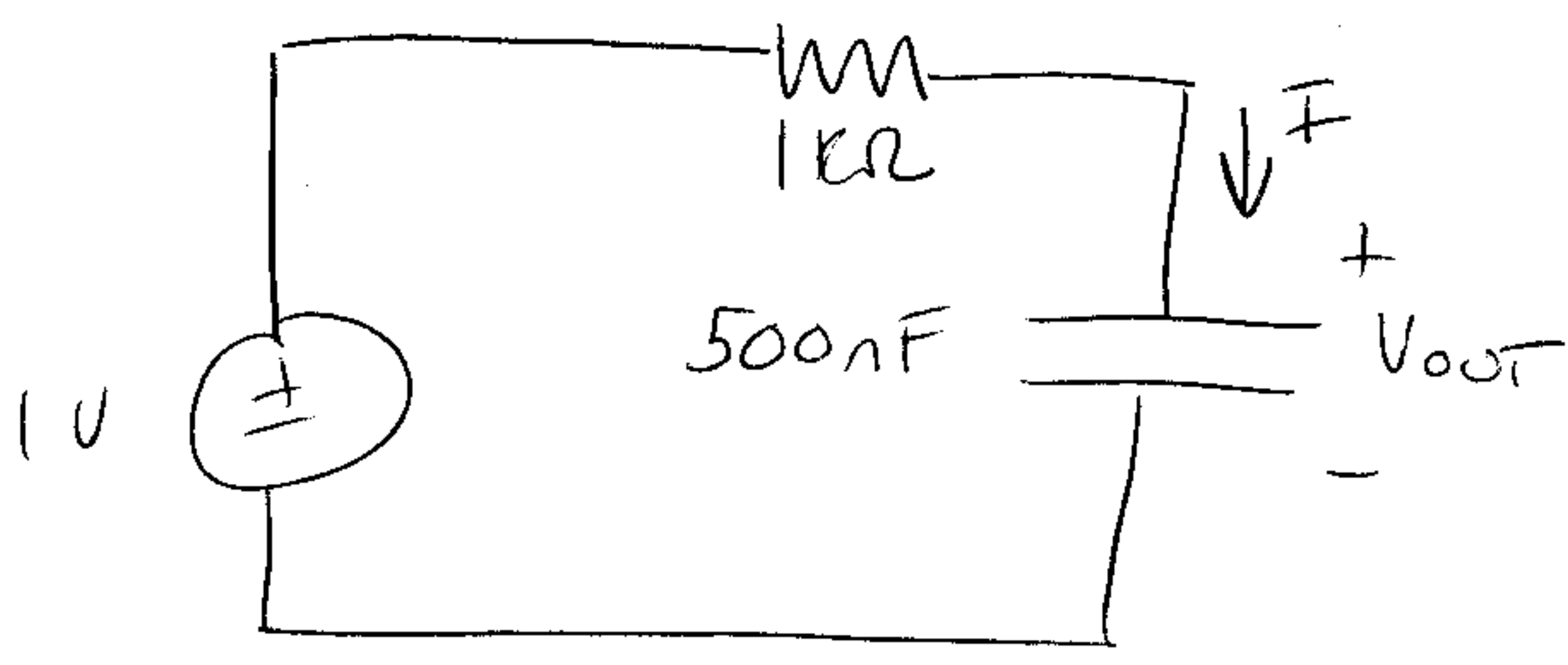

$t = 0$

RC circuit!

Will the diode ever be reverse biased?
 The current would have to be zero in that case.


Since $V_{out}(t) = 1V + (0V - 1V)e^{-t/0.5ms}$

so $I(t) = C \frac{dV_{out}}{dt} = \frac{500nF}{0.5ms} e^{-t/0.5ms} = 1mA \cdot e^{-t/0.5ms}$

Under forward bias assumption for all t from 0 to $1/2s$, diode current is always positive. So we are always forward biased in this time interval, and


$V_{out}(t) = 1 - e^{-t/0.5ms}$ for $0 < t \leq 1/2s$

Everything changes at $t = 1/2s$.

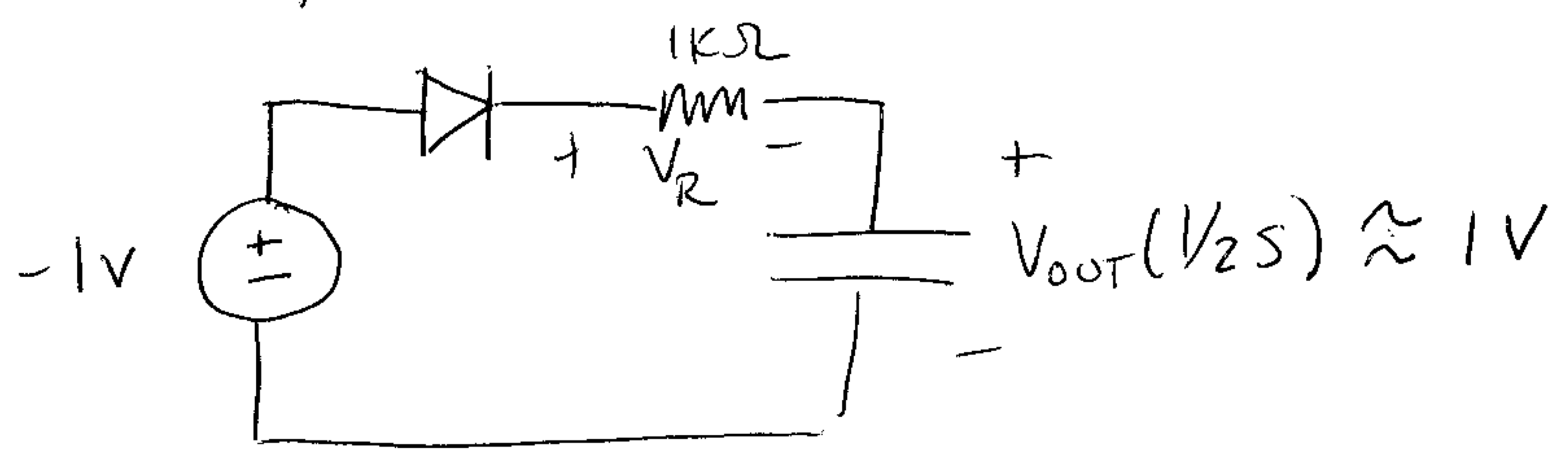

Diode cannot be forward biased since V_R would be $-2V \Rightarrow$ negative diode current


(6)

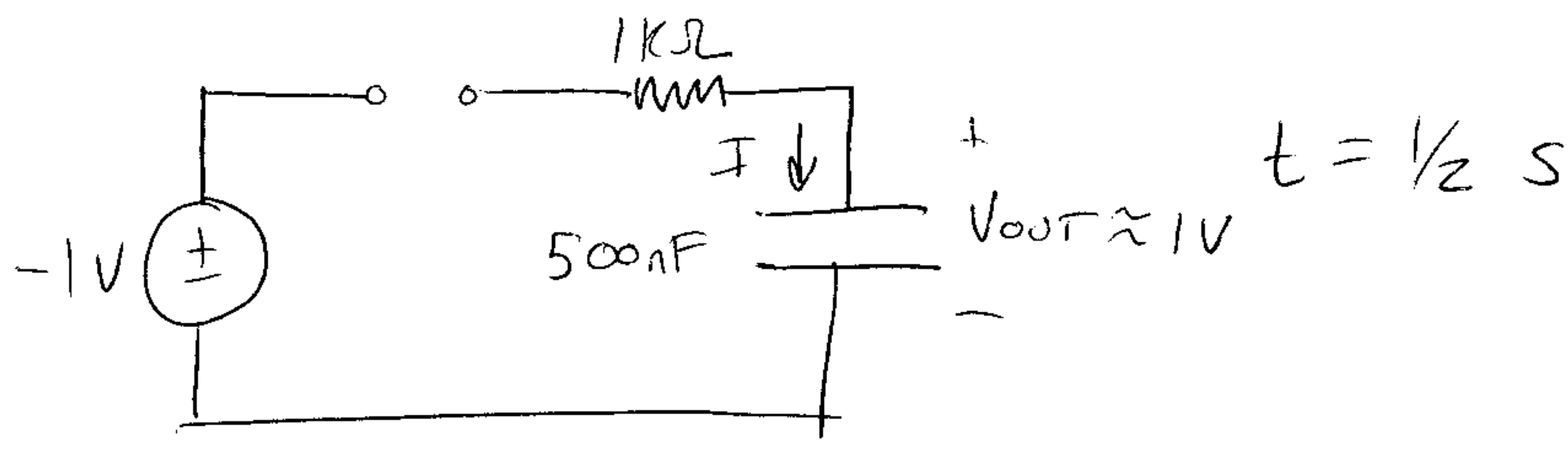


$I = 0$, V_{out} does not change,

Diode situation does not change,


until circuit switches again

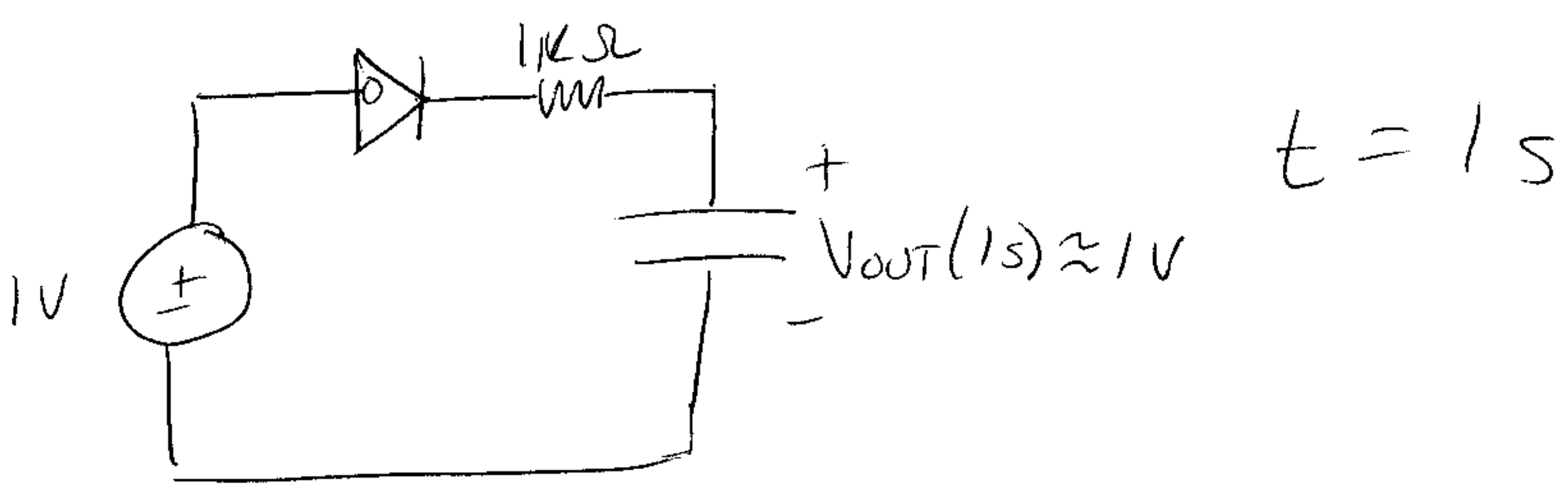


$V_{out}(1s)$ is a little less than 1V from our previous calculation. Like before, diode is forward biased. Capacitor charges even closer to 1V.

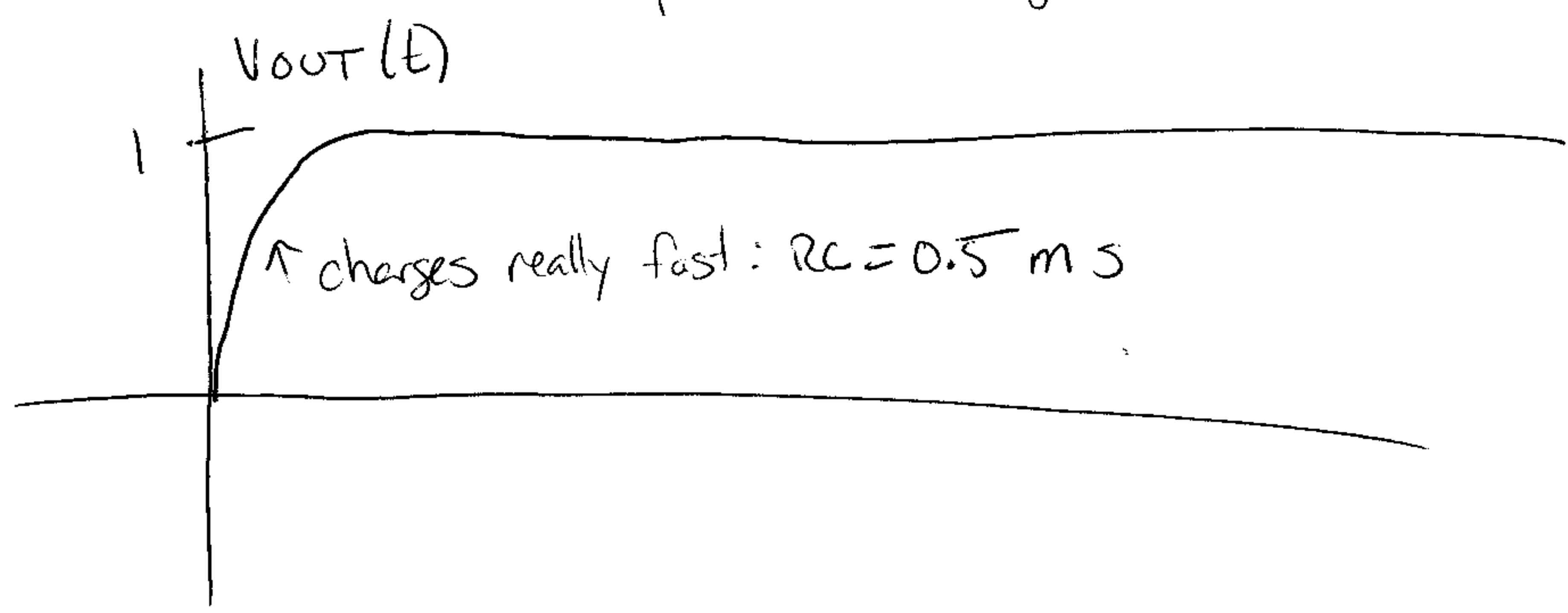

Problem 3:

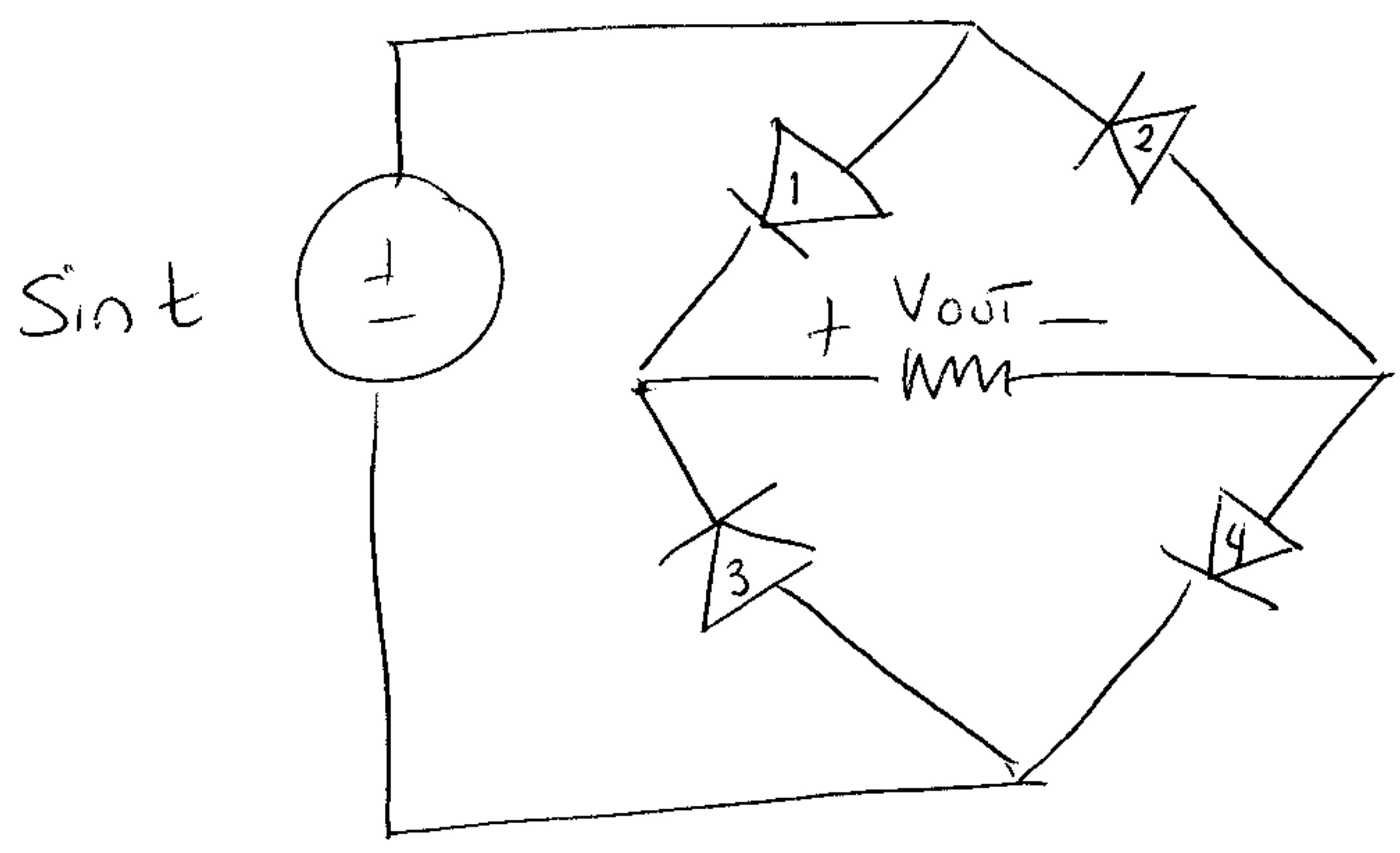


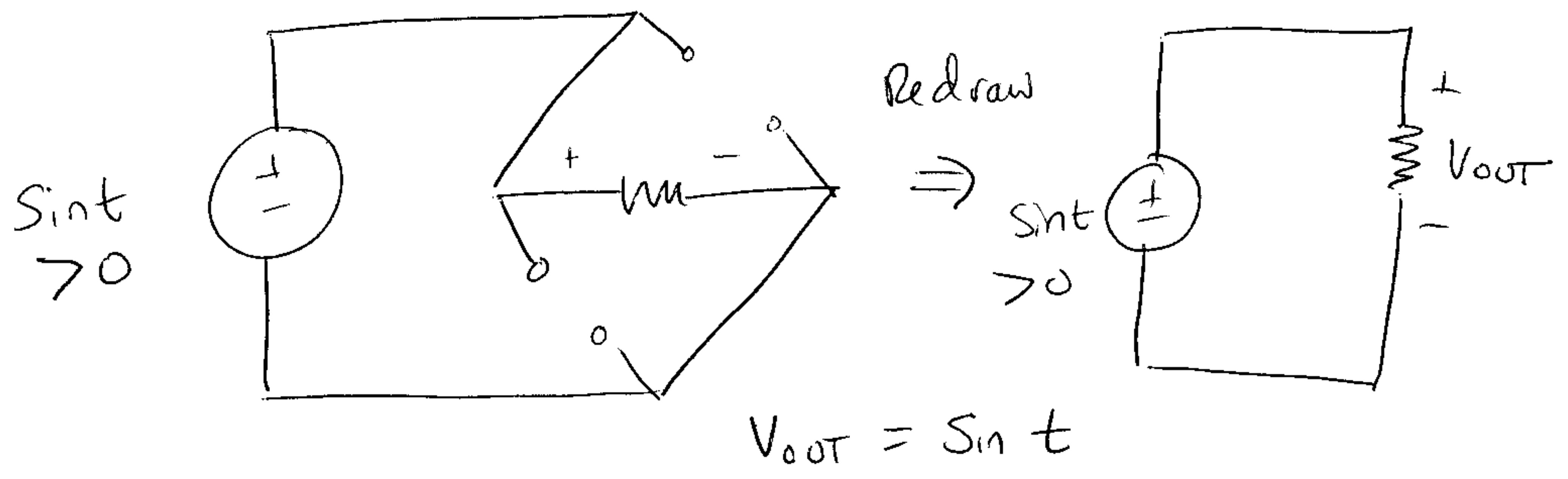When $\sin t > 0$, diodes 1 & 4 are "right-side-up" compared to the applied voltage; 2 & 3 are "upside-down".
 Guess 1 & 4 are forward biased, 2 & 3 reverse.




Roles of diodes switch when $\sin t < 0 \dots$

8

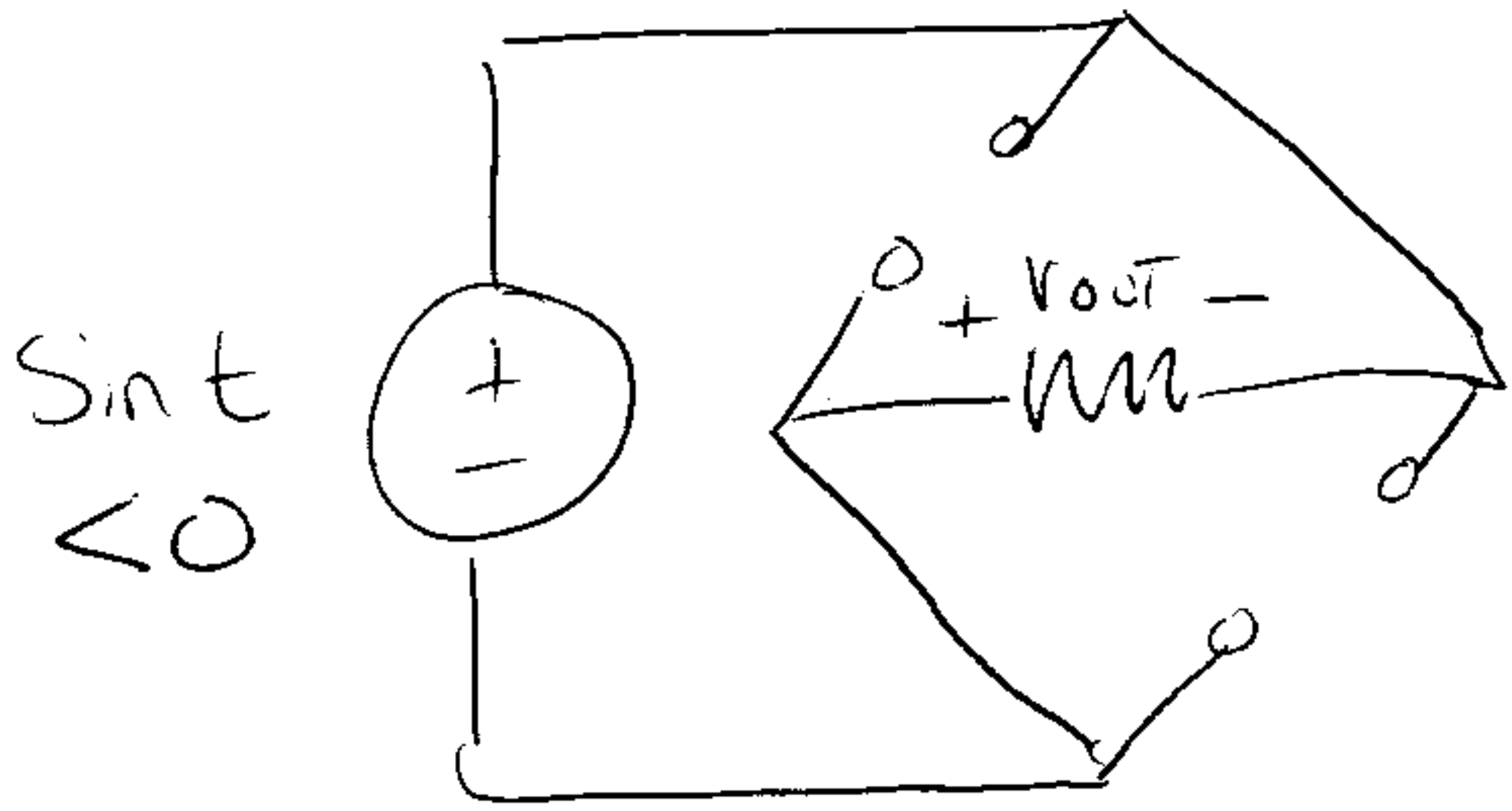

Redraw

$\Rightarrow \sin t < 0$

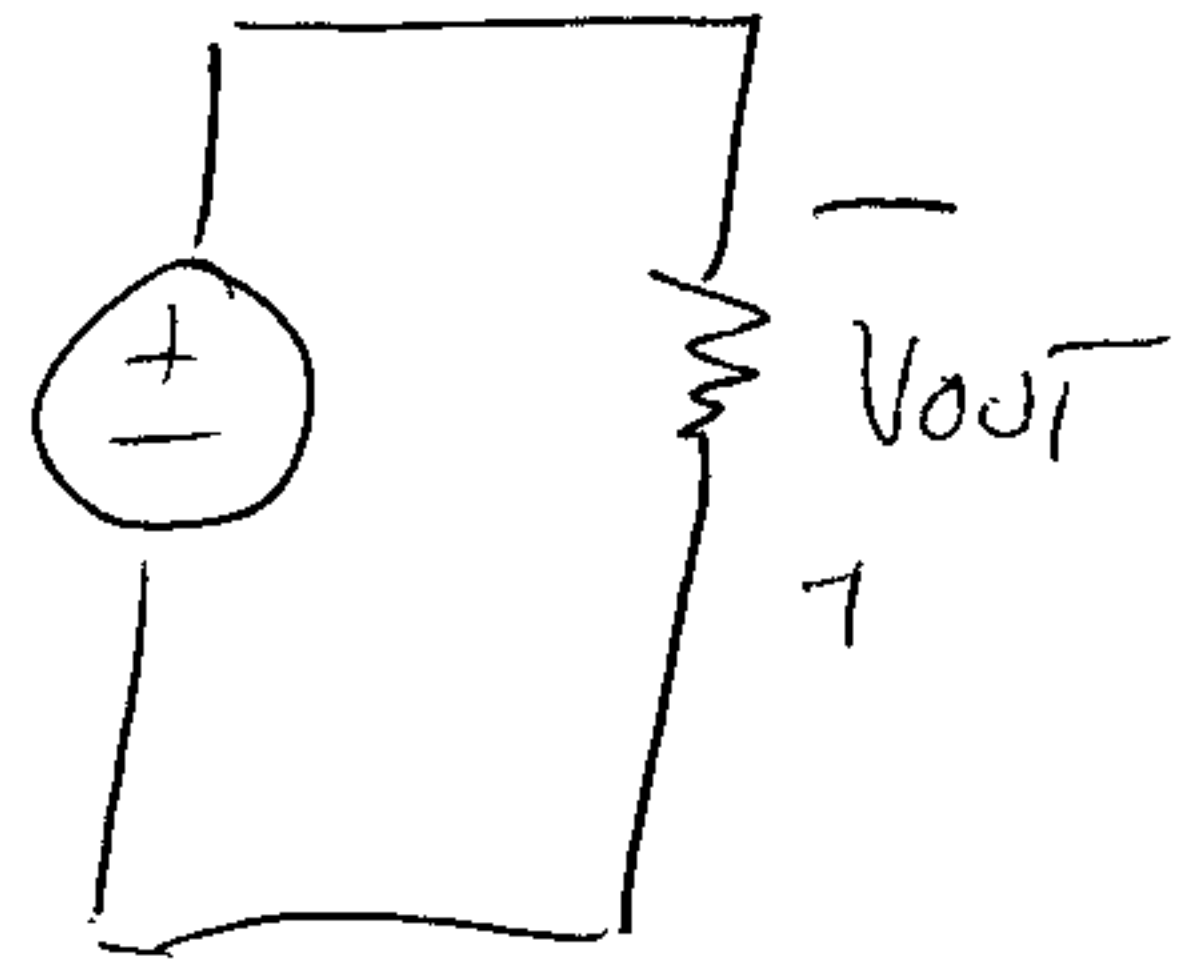


$$-V_{out} = \sin t$$

So when $\sin t$ is positive, $V_{out} = \sin t$.


" " " negative, $V_{out} = -\sin t$.

Hence $V_{out} = |\sin t|$.

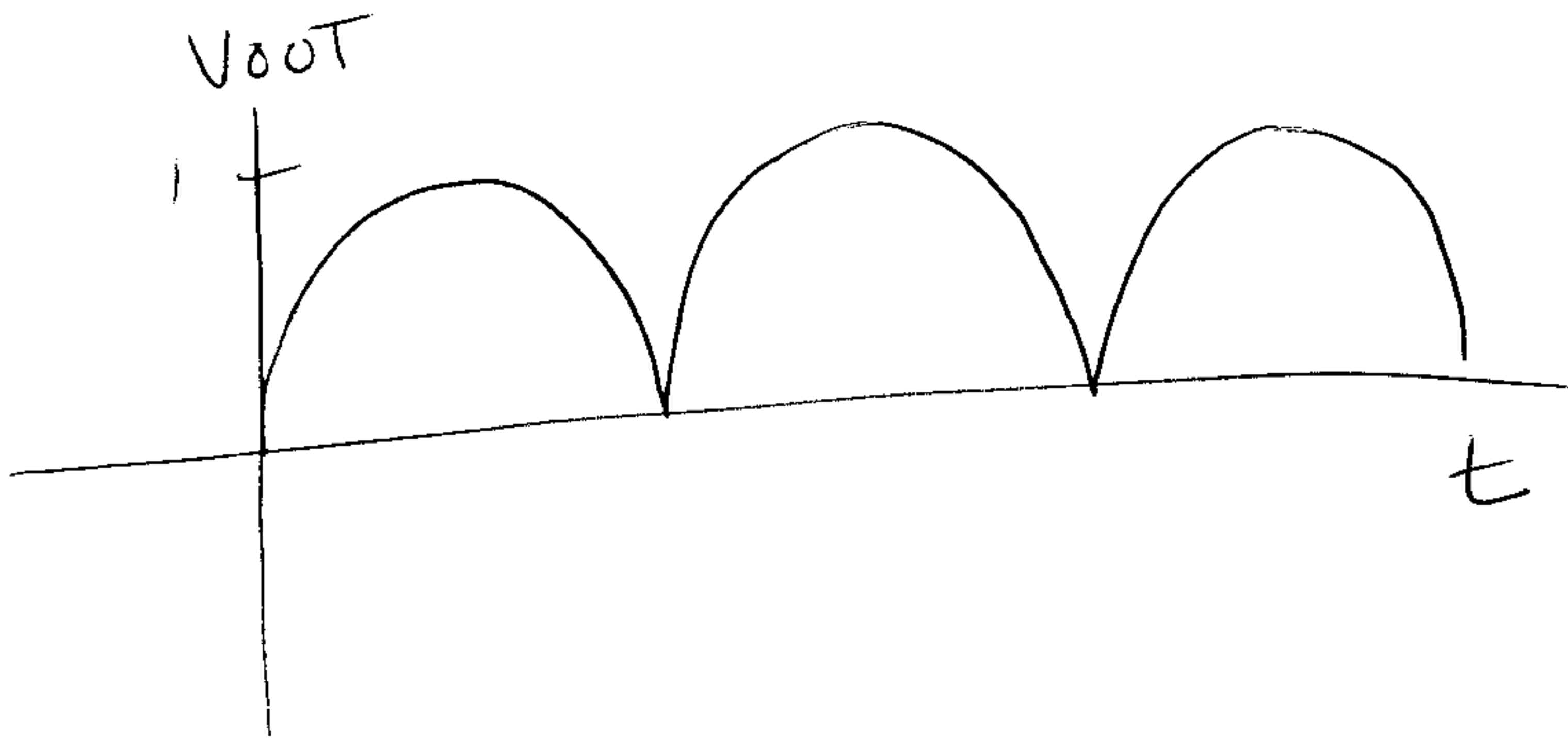

Problem 4

9

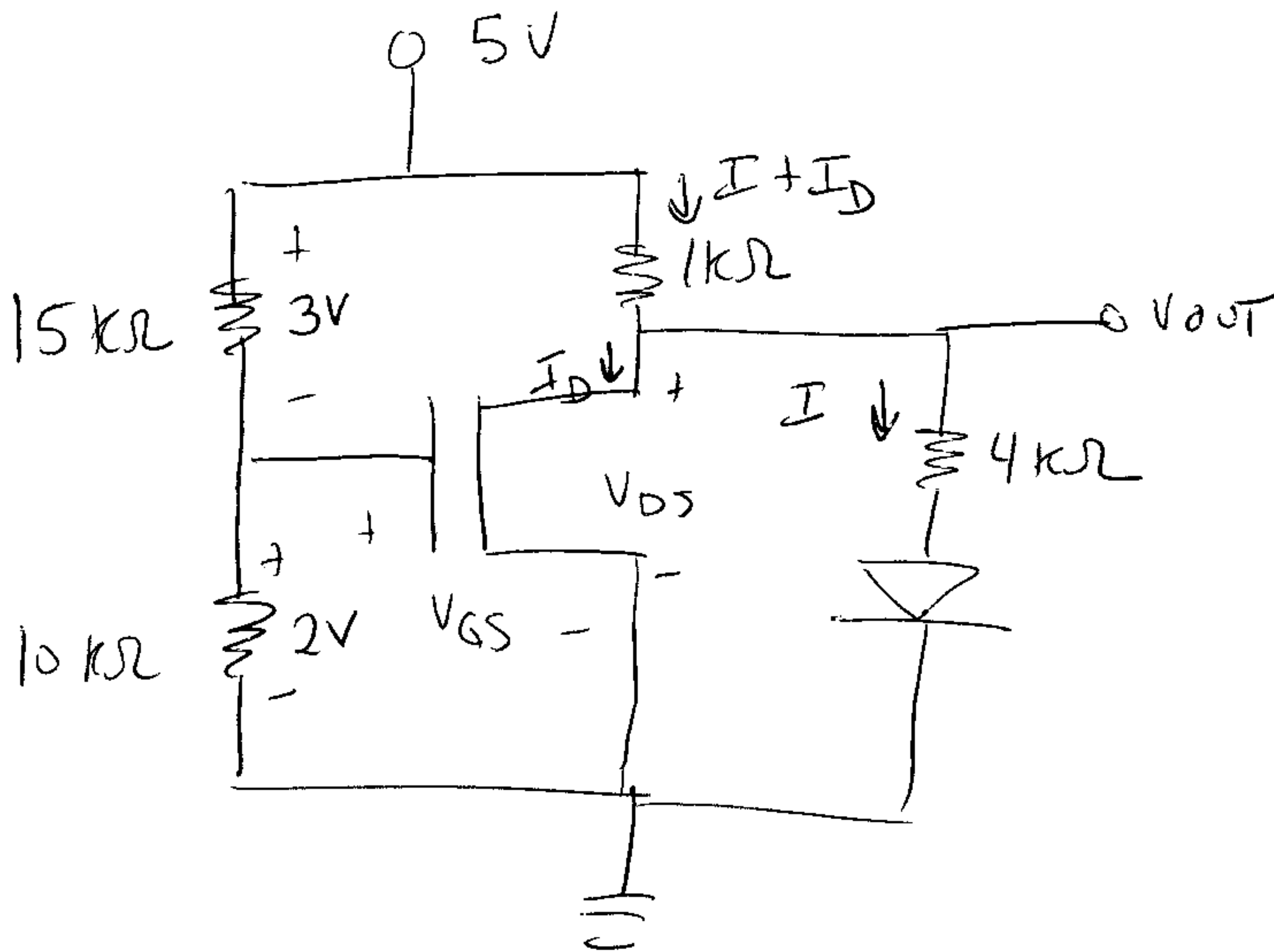

Since no current goes into/out gate, $15k\Omega + 10k\Omega$ effectively in series: voltage division gives their voltages. Guess saturation (since $V_{GS} = 2V$ means not in cutoff):


$$I_D = 1mA/V^2 \cdot \frac{1}{2} \cdot (2V - 1V)^2 = \frac{1}{2} mA$$

Need to find V_{DS} to verify saturation.

Need to deal with voltage over $4k\Omega$ resistor + diode.

Guess diode forward biased since V_{GS} little \Rightarrow

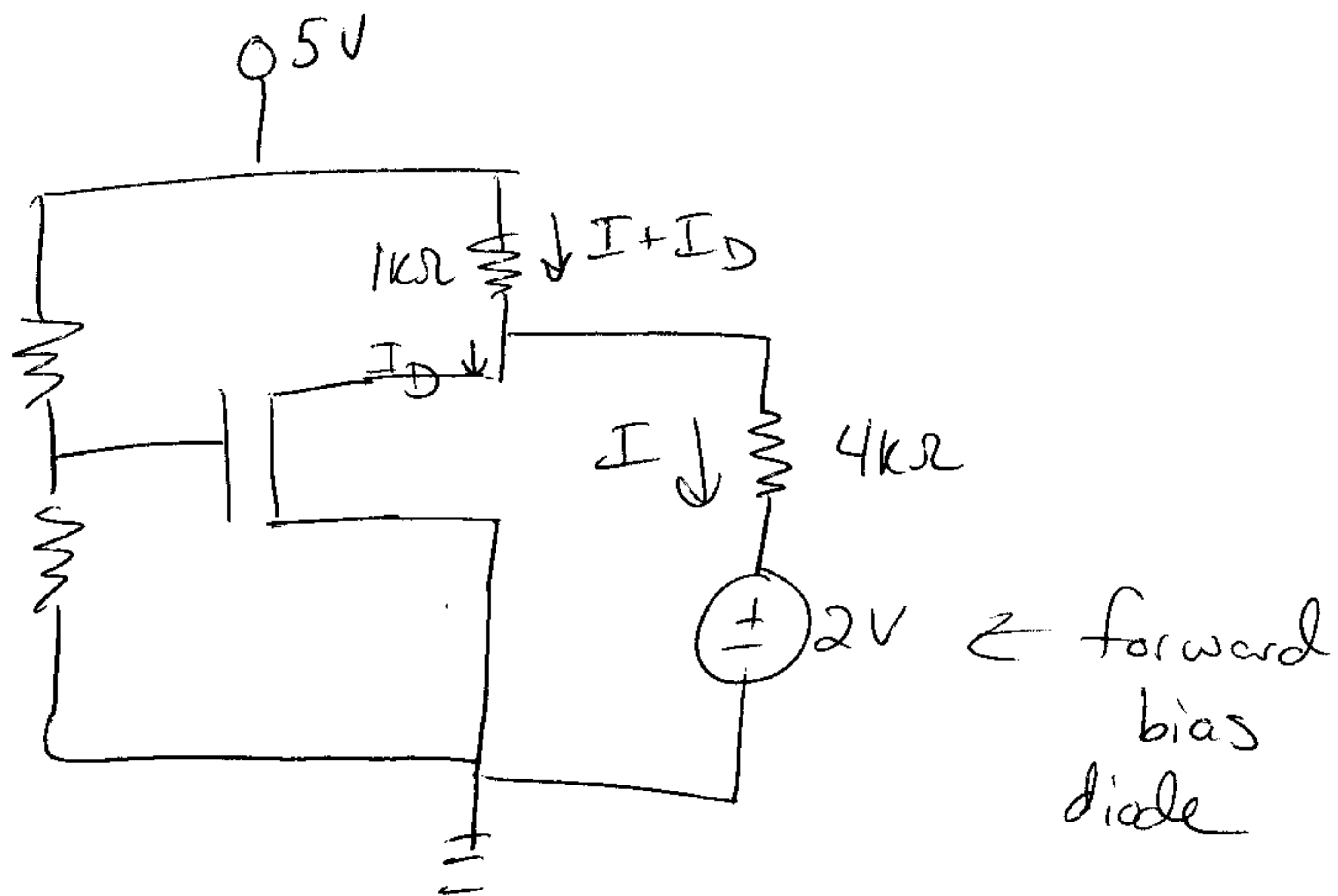V_{out} big. Find I to see if we are right.



KVL: $-2V - 4k\Omega I - 1k\Omega(I + I_D) + 5V = 0$
 (start at ground, go up)

We said $I_D = 1/2 \text{ mA}$; substitute & solve

$$I = 1/2 \text{ mA}$$

$$V_{DS} = I \cdot 4k\Omega + 2V = 4V$$

$$V_{out} = 4V$$