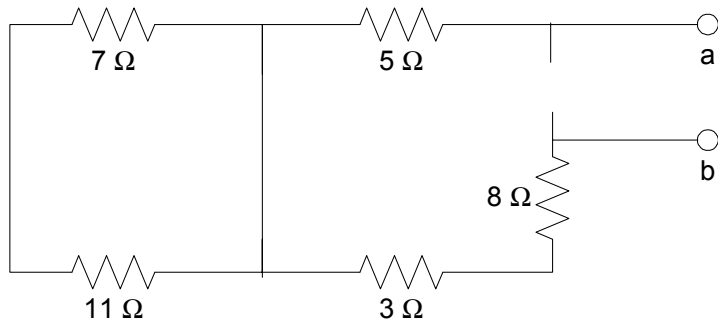



Midterm #1 Review Solutions

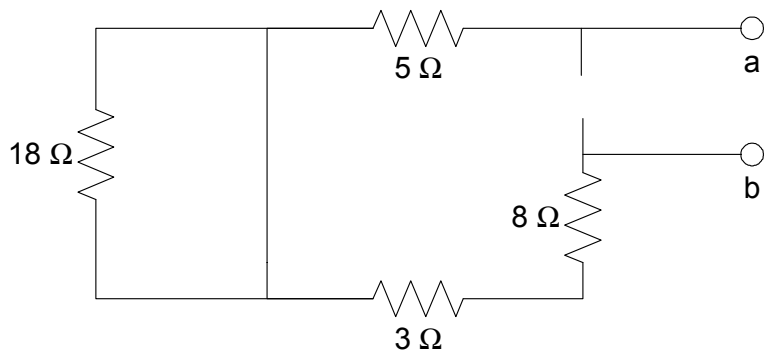Problem 1:


To find  $R_{TH}$  ( $R_N$ ), we can turn off the independent sources:




The 7 Ω and 11 Ω resistor are in series. They can be combined into a  $7\ \Omega + 11\ \Omega = 18\ \Omega$  resistor.



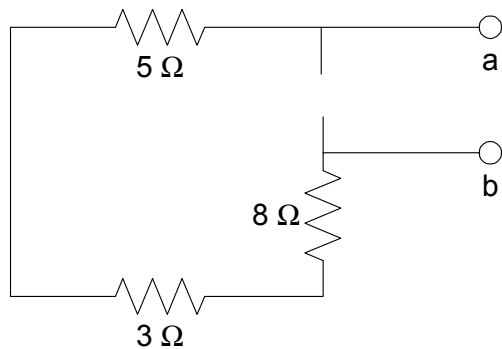Now, the 18 Ω resistor is in parallel with a wire. The resistor must have 0 V, or KVL would be violated. So we can ignore this resistor, since it has 0 V and therefore 0 A.



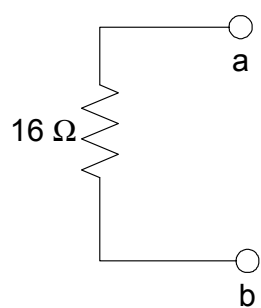
Now, the 5 Ω, 3 Ω, and 8 Ω resistors are in series since they have the same current: no current can go through the hole where the current source used to be. They combine into a  $5\ \Omega + 3\ \Omega + 8\ \Omega = 16\ \Omega$  resistor.




So,  $R_{TH} = R_N = 16\ \Omega$ .

To find  $V_{TH}$ , we find the voltage drop from a to b with the terminals left open.

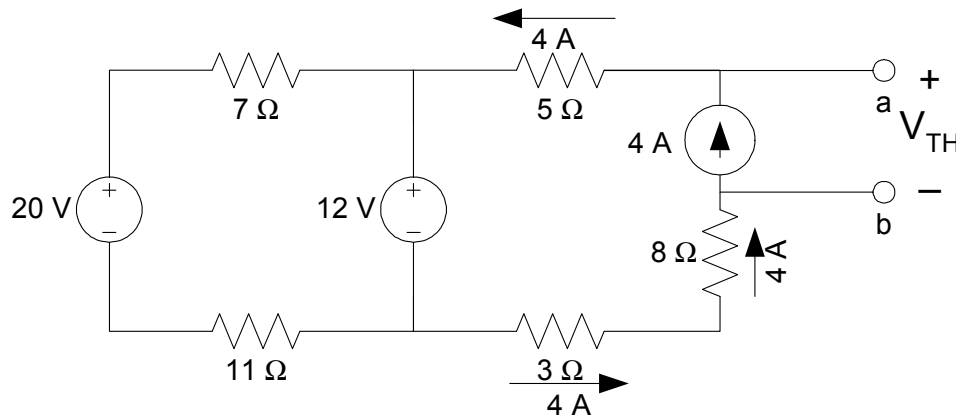With the terminals left open, the  $5\ \Omega$ ,  $3\ \Omega$ , and  $8\ \Omega$  resistors, and the current source, all share the same current. There is nowhere for the current to escape within that branch. The current source dictates that the current is  $4\ \text{A}$  as shown:



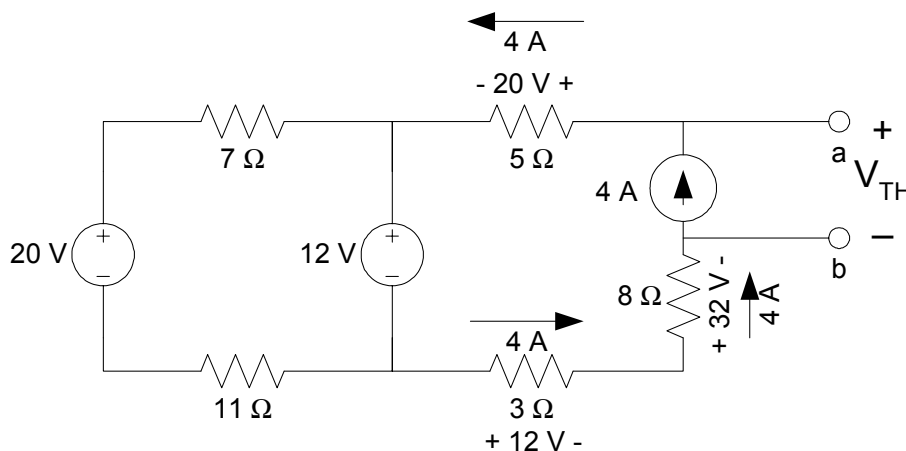The voltage over these resistors can be found using Ohm's law:



$V_{TH}$  can now be found using a KVL loop:


Starting at point a and going counter-clockwise,  
 $20\ \text{V} + 12\ \text{V} + 12\ \text{V} + 32\ \text{V} - V_{TH} = 0$

$$V_{TH} = 76\ \text{V}$$

$$I_N = V_{TH} / R_{TH} = 19/4\ \text{A}$$
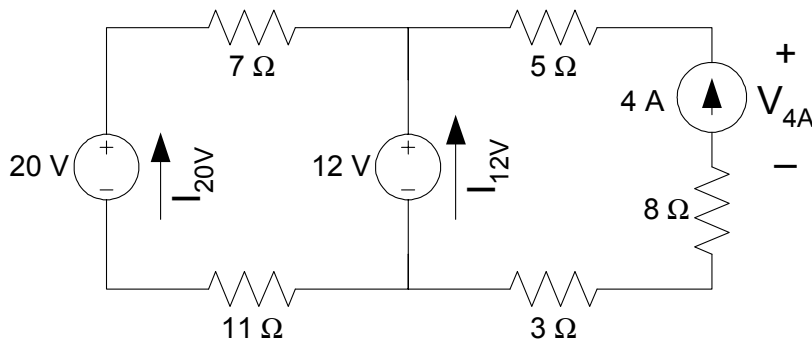
### Problem 2:

To find power generated, we need to find the current going from  $-$  to  $+$  over the device voltage and multiply these values together.



Notice that the the  $5\ \Omega$ ,  $3\ \Omega$ , and  $8\ \Omega$  resistors, and the current source, all share the same current. There is nowhere else for the current to go in that path.

The same is true for the  $7\ \Omega$  and  $11\ \Omega$  resistors, and the  $20\ \text{V}$  voltage source.

By KVL, counter-clockwise in the right hand loop,

$$(4\ \text{A})(5\ \Omega) + 12\ \text{V} + (4\ \text{A})(3\ \Omega) + (4\ \text{A})(8\ \Omega) - V_{4A} = 0$$

$$V_{4A} = 76\ \text{V}$$

By KVL, clockwise in the left hand loop,

$$(I_{20V})(7 \Omega) + 12 \text{ V} + (I_{20V})(11 \Omega) - 20 \text{ V} = 0$$

$$I_{20V} = 4/9 \text{ A}$$

By KCL at the top-middle node,

$$I_{20V} + I_{12V} + 4 \text{ A} = 0$$

$$I_{12V} = -40/9 \text{ A}$$




Now, we have the quantities we need to calculate power generated:

4 A source:  $P = (4 \text{ A})(76 \text{ V}) = 304 \text{ W}$


20 V source:  $P = (4/9 \text{ A})(20 \text{ V}) = 80/9 \text{ W}$

12 V source:  $P = (-40/9 \text{ A})(12 \text{ V}) = -160/3 \text{ W}$

**Problem 3:**

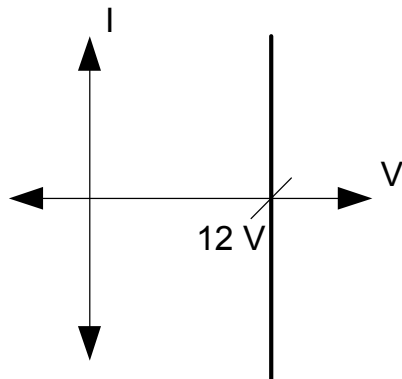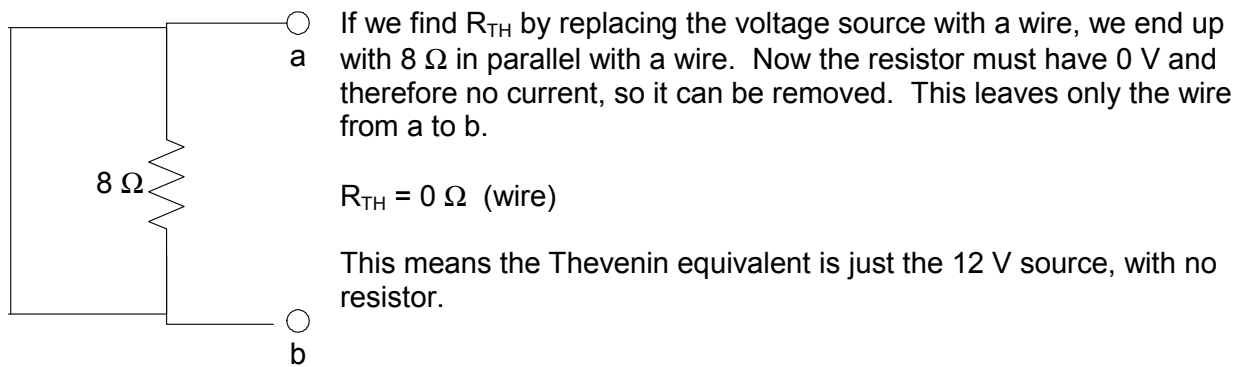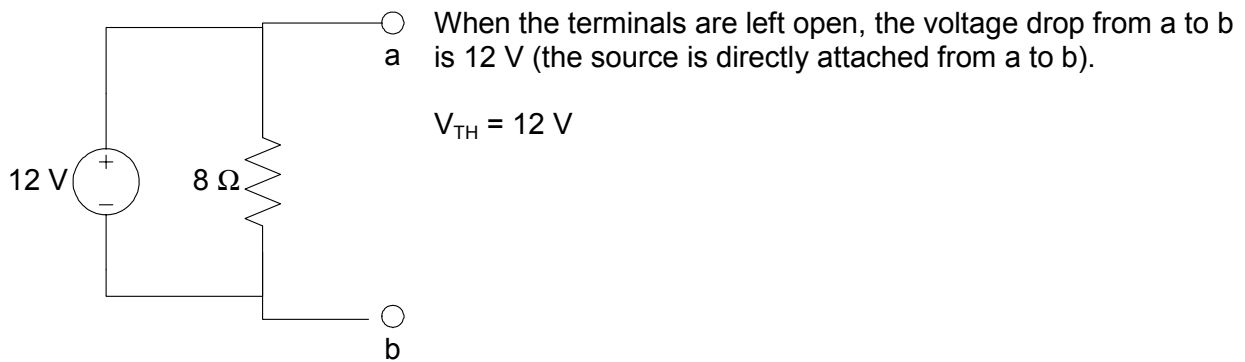

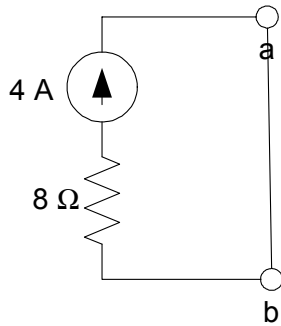The I-V graph for this circuit is a vertical line. There is no y-intercept, so  $I_N$ , and the Norton equivalent circuit, do not exist for this example.




The current flowing from a to b when the terminals are shorted is 4 A, so

$$I_N = 4 \text{ A}$$




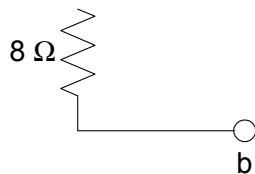If we find  $R_{TH}$  by replacing the current source with air, we end up with  $8 \Omega$  in series with air. Now the resistor must have zero current, so it can be removed. This leaves only air from a to b.



$$R_N = \infty \Omega \text{ (air)}$$

This means the Thevenin equivalent is just the 4 A source, with no resistor in parallel.

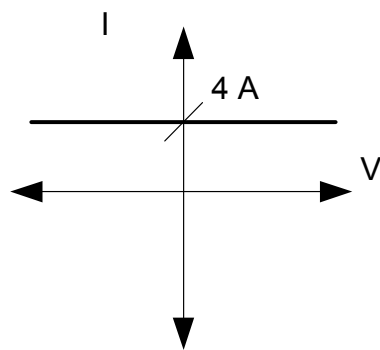


The I-V graph for this circuit is a horizontal line. There is no x-intercept, so  $V_{TH}$ , and the Thevenin equivalent circuit, do not exist for this example.
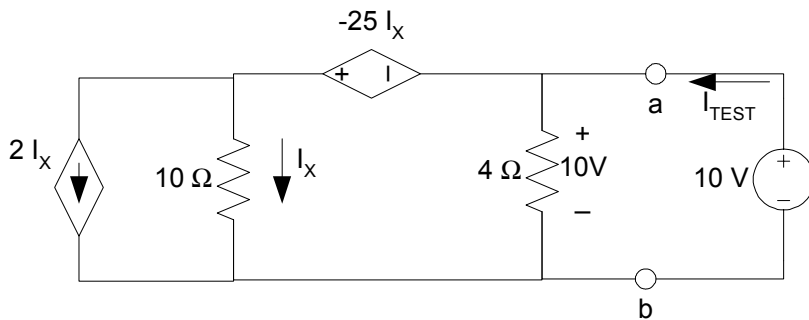
#### Problem 4:

We have no independent sources in this circuit. This means that  $V_{TH} = 0 \text{ V}$  and  $I_N = 0 \text{ A}$ .

So, the circuit is simply a resistor. To find the resistance,  $R_{TH}$ , we apply a test voltage (any voltage we want; 10 V for example) and measure the current going through the circuit:




By KVL on the right-hand loop, we see that the  $4 \Omega$  resistor has 10 V as shown.

KVL on the center loop counter-clockwise:

$$-10 \text{ V} - 25 I_x + (10 \Omega) I_x = 0$$

$$I_x = 2/7 \text{ A}$$

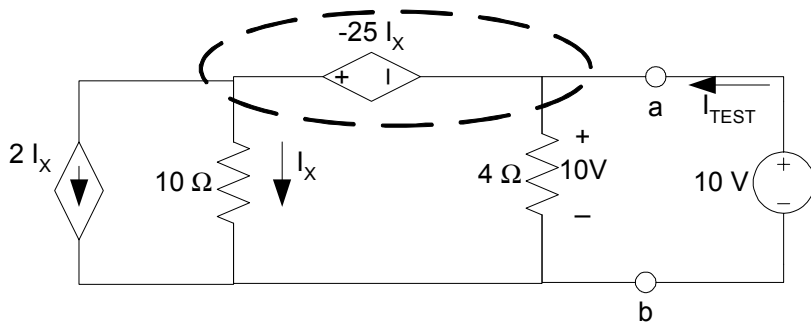

By KCL on the surface shown,


$$2 I_x + I_x + (10 \text{ V} / 4 \Omega) - I_{\text{TEST}} = 0$$

$$I_{\text{TEST}} = 37/14 \text{ A}$$

$$R_{\text{TH}} = V_{\text{TEST}} / I_{\text{TEST}} = 10 \text{ V} / (37/14 \text{ A})$$


$$R_{\text{TH}} = 140/37 \Omega$$

**Problem 5:**

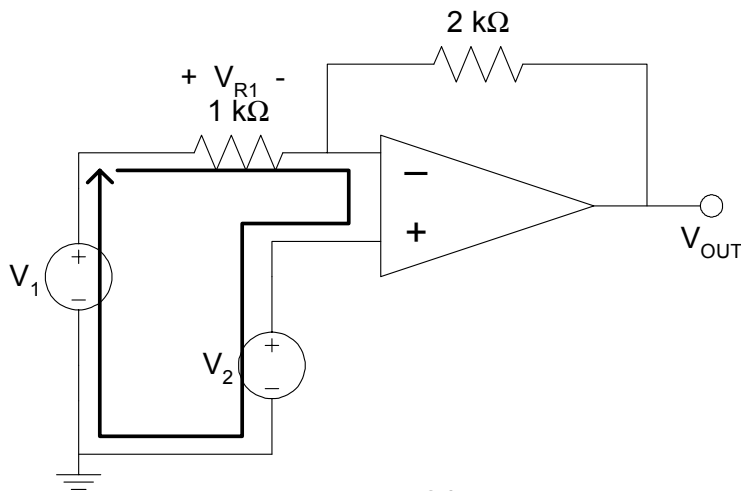

By KVL around the input loop shown,
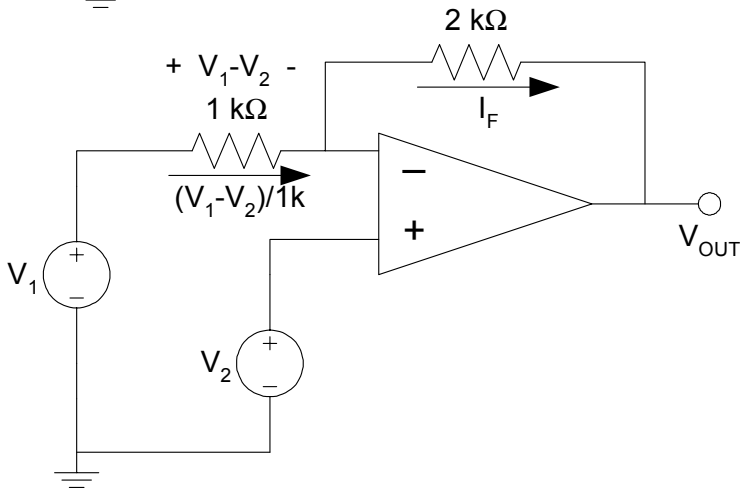
$$V_{R1} + V_2 - V_1 = 0 \quad \text{so} \quad V_{R1} = V_1 - V_2$$




By KCL,  $I_F - (V_1 - V_2)/1k = 0$ , since the current into the op-amp input is 0 A.

$$I_F = (V_1 - V_2)/1k$$


By KVL around the loop shown,

$$-V_2 + 0 \text{ V} + (2 \text{ k}\Omega)I_F + V_{\text{OUT}} = 0$$

$$V_{\text{OUT}} = 3 V_2 - 2 V_1$$

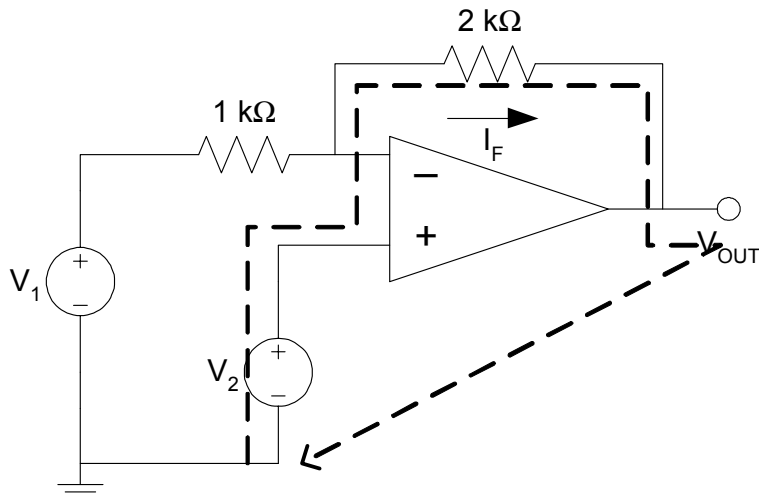

**Problem 6:**

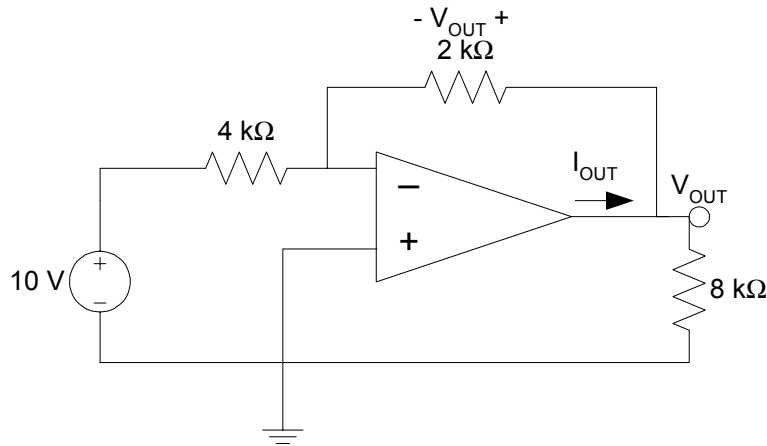

Since this is an inverting amplifier, we know immediately that

$$V_{OUT} = -(2 \text{ k}\Omega / 4 \text{ k}\Omega) 10 \text{ V}$$

$$V_{OUT} = -5 \text{ V}$$

Also, note that the right side of the 2 kΩ resistor is at voltage  $V_{OUT}$ , and the left side is at ground. (Trace from the left side to ground; you only go over the op-amp inputs, a drop of 0 V).

KCL equation at the  $V_{OUT}$  node:  $V_{OUT} / 8 \text{ k}\Omega + V_{OUT} / 2 \text{ k}\Omega - I_{OUT} = 0$   $I_{OUT} = -25/8 \text{ A}$

**Problem 7:**

The input is 5 V at  $t = 0$ , and decays exponentially to 0 V. The threshold voltage is 2 V, so the output will be at the high rail until the input gets down to around 2 V, then the output will quickly transition down to the low rail.

The output will be at a rail unless the output voltage given by the linear region formula is between the rails. So the amplifier will be in the linear region when:

$$V_{OUT}(t) = A(V_+ - V_-) = 1000(V_{IN}(t) - 2 \text{ V}) \quad \text{is between 0 V and 5 V}$$

The linear region is entered when this quantity is exactly 5 V:

$$5 \text{ V} = 1000(5e^{-4000t} \text{ V} - 2 \text{ V})$$

$$t = -1/4000 \ln(2.005 / 5)$$


$$t = 228.45 \text{ }\mu\text{s}$$

The linear region is over when this quantity is exactly 0 V:

$$0 \text{ V} = 1000(5e^{-4000t} \text{ V} - 2 \text{ V})$$

$$t = -1/4000 \ln(2 / 5)$$

$$t = 229.07 \text{ }\mu\text{s}$$

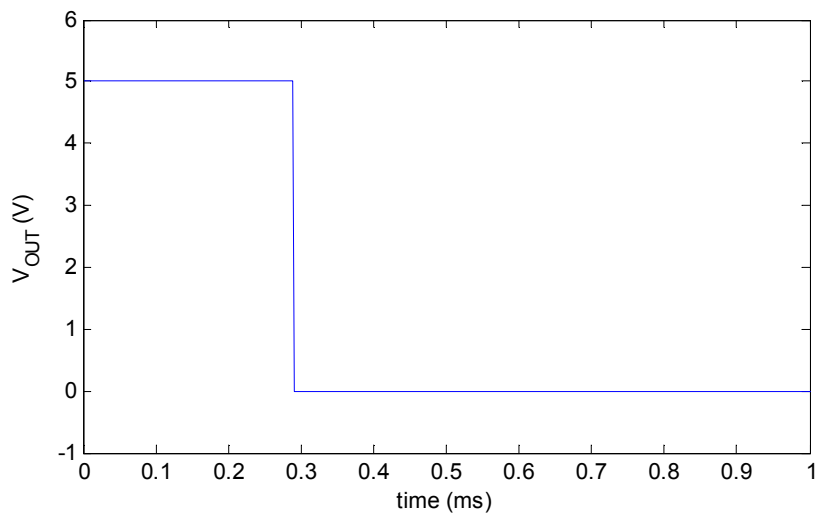

The comparator is in the linear region for 620 ns.