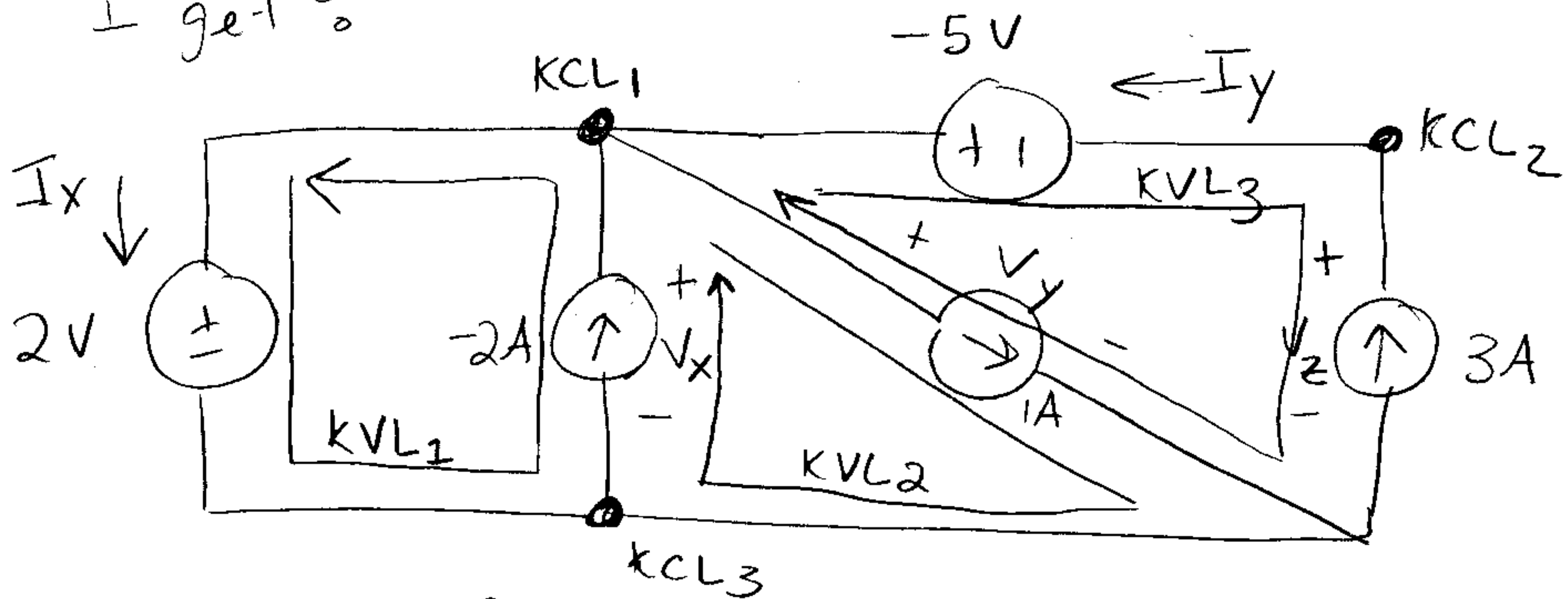


EE 42

Homework Solutions #1

Problem 1:

Writing KVL equations (assigning my own variable names to things I don't know), I get:



$$\text{KVL}_1: 2V + V_x = 0$$

$$\text{KVL}_2: V_y - V_x = 0$$

$$\text{KVL}_3: -5V + V_z - V_y = 0$$

There are no contradictions in these equations.

Writing KCL, assigning variables to unknown currents,

$$\text{KCL}_1: I_x - 2A - I_y + 1 = 0$$

$$\text{KCL}_2: I_y - 3A = 0$$


$$\text{KCL}_3: -I_x - 2A - 1A + 3A = 0$$

(2)

There are no contradictions in these equations either.

Neither KVL nor KCL are violated.

Problem 20

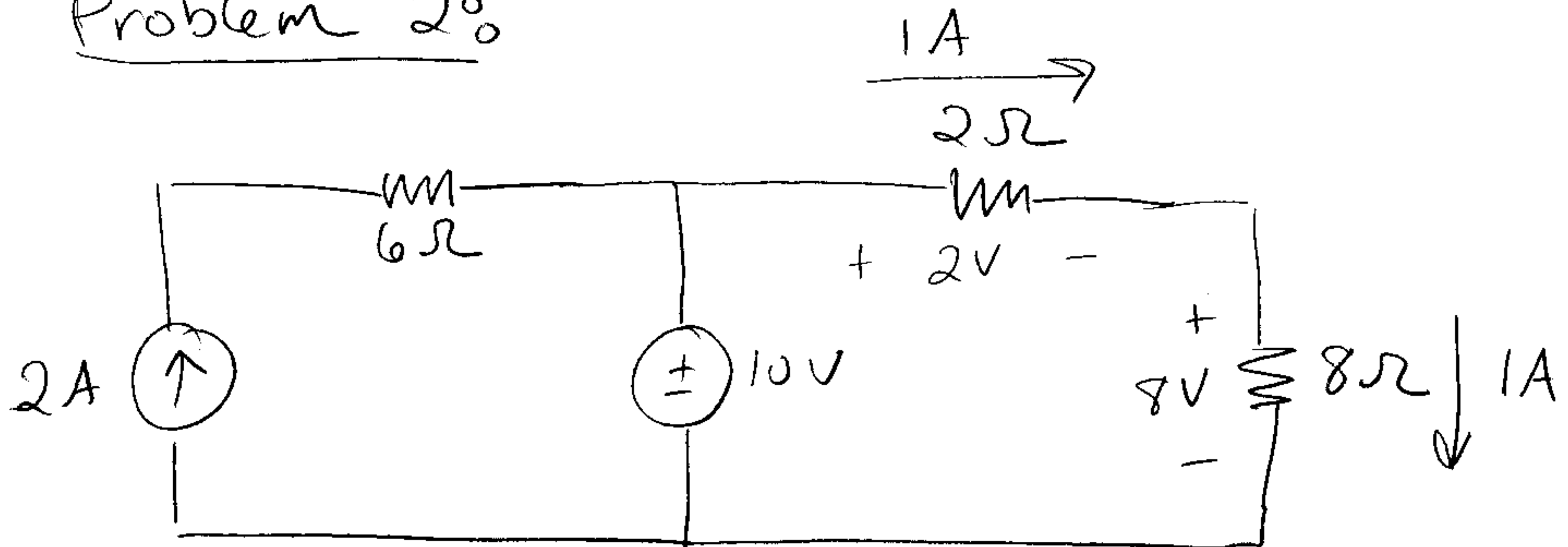


I have 10 V over a pair of series resistors (2Ω & 8Ω). Using voltage division, the voltage over the 2Ω resistor is

$$10V \cdot \frac{2\Omega}{2\Omega + 8\Omega} = 2V. \text{ The } 8\Omega \text{ resistor takes}$$

8V. The polarity is determined by the 10 V source, so the resistor voltage drops cancel the 10 V source.

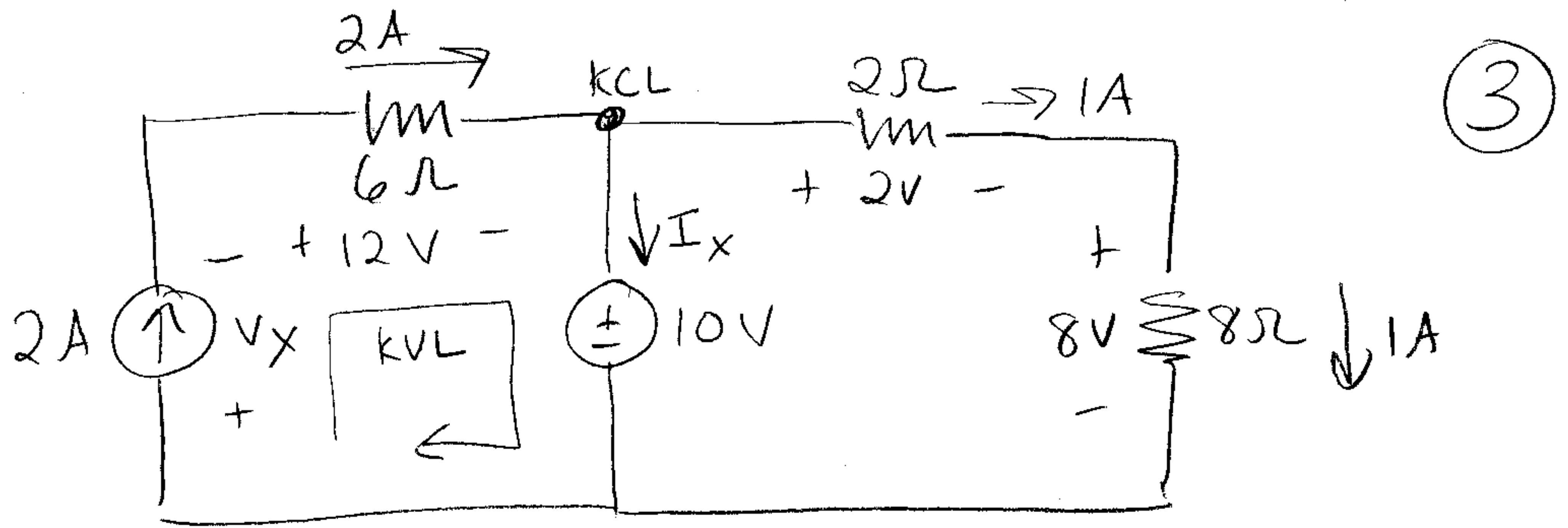Using Ohm's law, the current through each resistor is 1A, from + to -. (You could also determine this by combining the series resistors.)



Notice that the entire 2A of current from the current source must go through the 6Ω resistor (it has nowhere else to go, and current doesn't disappear). By Ohm's law, 12V falls over the resistor with polarity shown.

Now I have all the V and I values for resistors. Still need I for 10V source and V for 2A source. I will give names to these unknowns, and give them the polarity that will result in power absorbed (current flows + to -). By KCL,

$$-2A + I_x + 1A = 0 \Rightarrow I_x = 1A$$

By KVL,

$$V_x + 12V + 10V = 0 \quad V_x = -22V$$

Find power absorbed:

$$P_{2A} = (2A)(-22V) = -44W$$

$$P_{6\Omega} = (2A)(12V) = 24W$$


$$P_{10V} = (1A)(10V) = 10W$$

$$P_{2\Omega} = (1A)(2V) = 2W$$

$$P_{8\Omega} = (1A)(8V) = 8W$$

As expected, all resistors absorb (positive) power. The 10V source also absorbs ^{positive} power! The 2A source absorbs negative power, which means it generates 44W of power.

Problem 3:

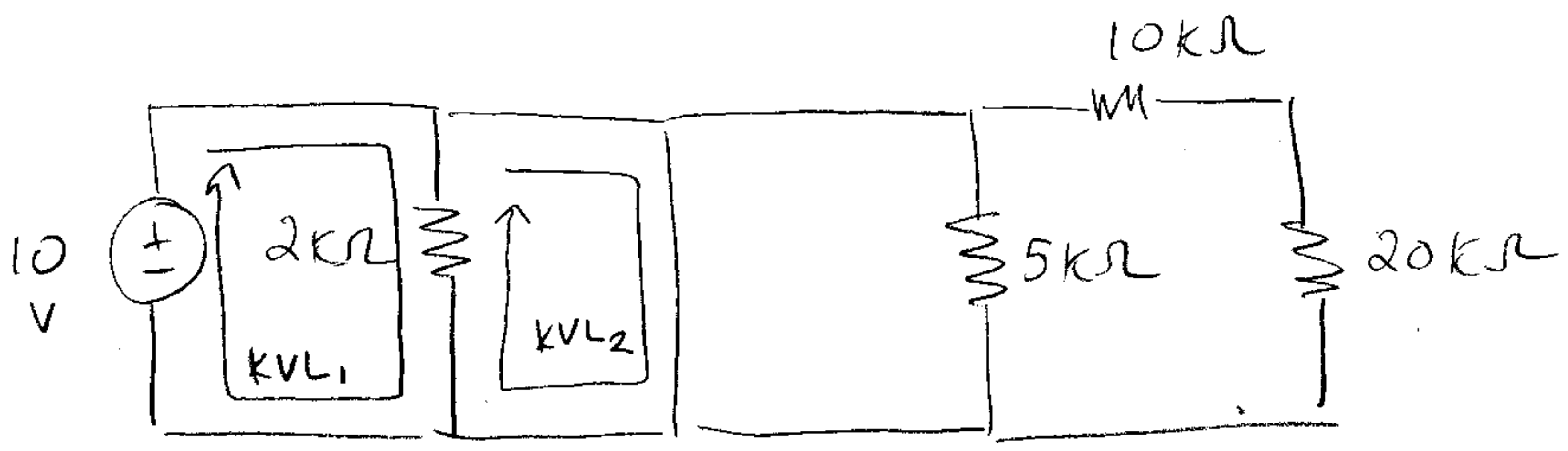

KVL₁ says the 2kΩ resistor should carry 10V.


KVL₂ says the 2kΩ resistor should carry 0V.

5

This is a contradiction: KVL is violated.


In real life, KVL is never violated.

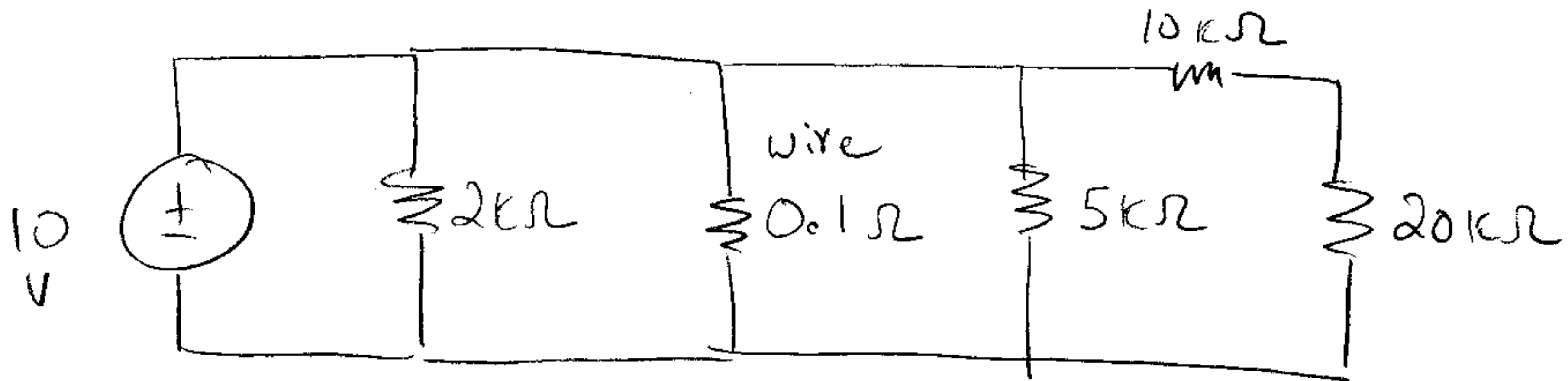The wire acts like a very small resistance:



According to Ohm's law, the wire should get 100 A. This wouldn't likely happen - either the wire would melt, the 10 V source would blow a fuse, or the 10 V source would reduce its voltage so that its max current is not exceeded.


Problem 4:

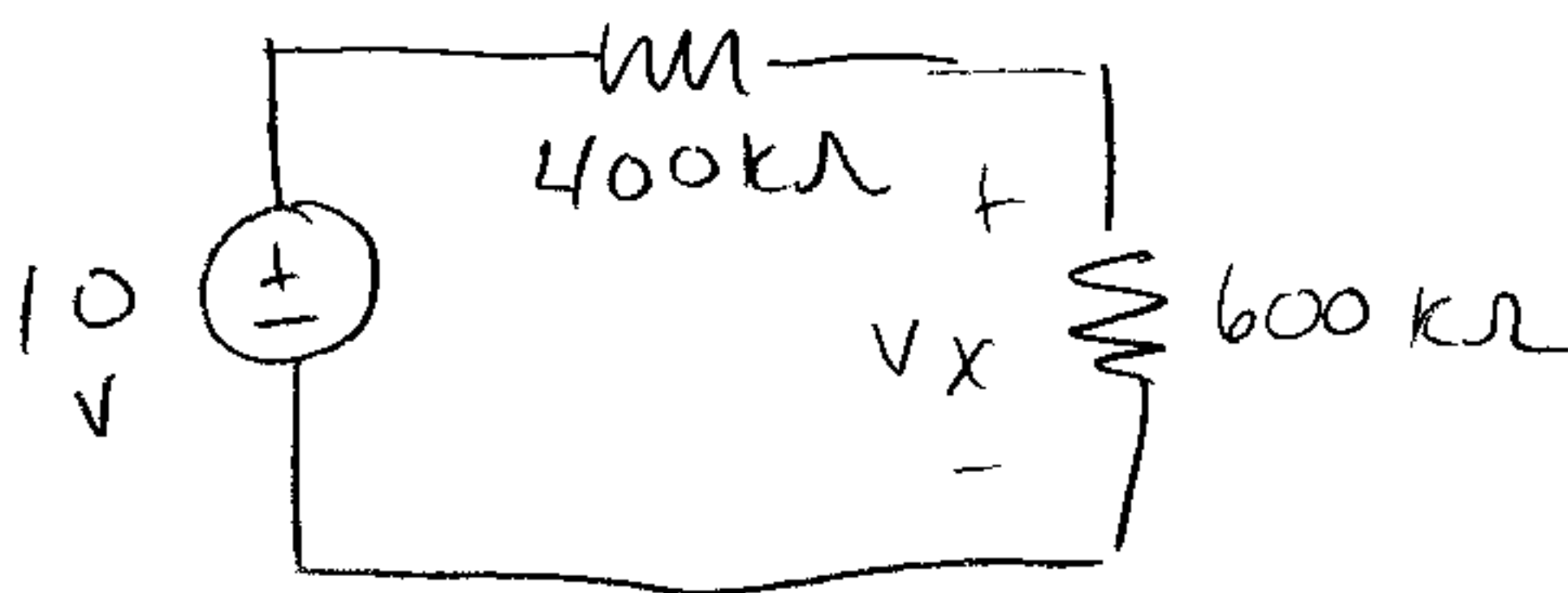

By voltage division,

$$V_x = 10V \cdot \frac{600k\Omega}{400k\Omega + 600k\Omega} = 6V$$

(6)

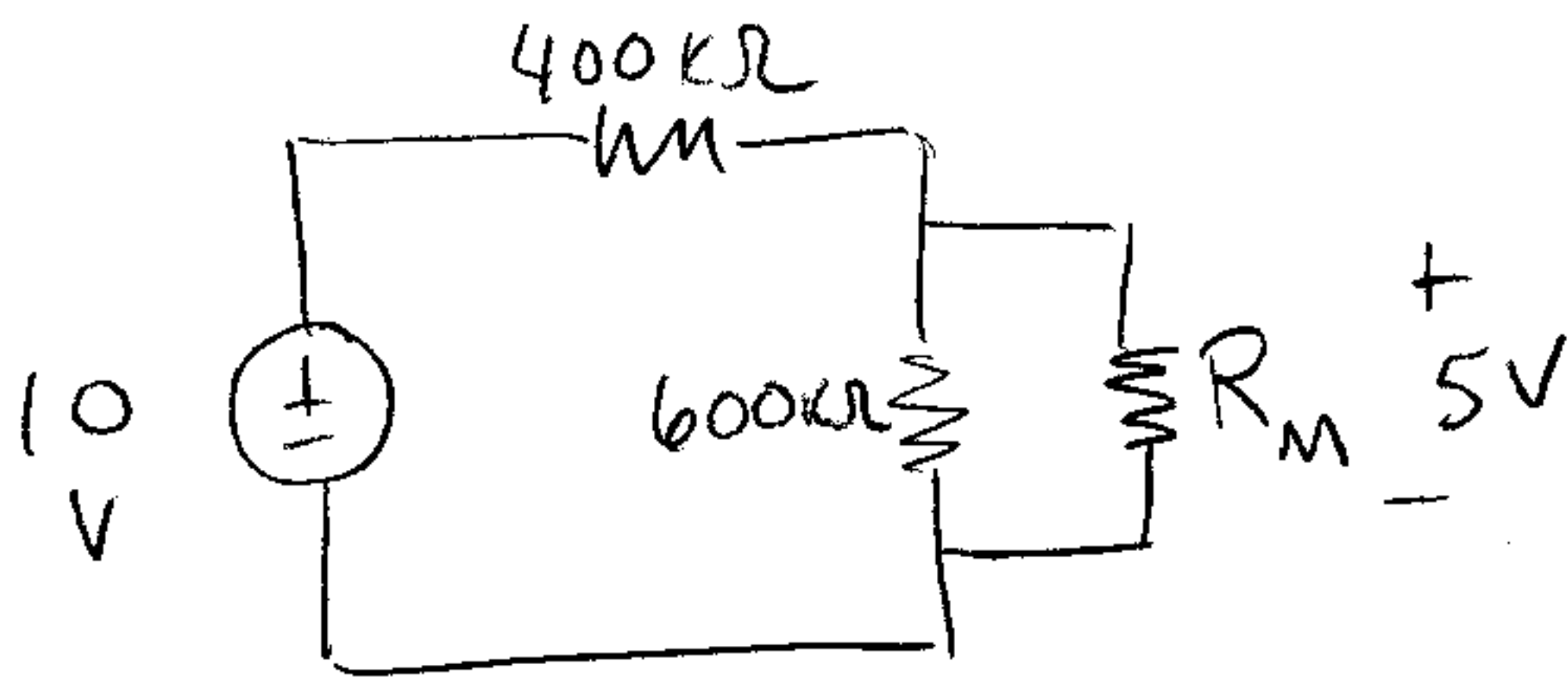


With the voltmeter in, all voltages and currents get changed. Now, the voltage across the $600\text{k}\Omega$ is 5V .

We could combine the $600\text{k}\Omega$ & R_M in parallel:

$$R_{eq} = \left(\frac{1}{600\text{k}\Omega} + \frac{1}{R_M} \right)^{-1} = \frac{R_M \cdot 600\text{k}\Omega}{R_M + 600\text{k}\Omega}$$

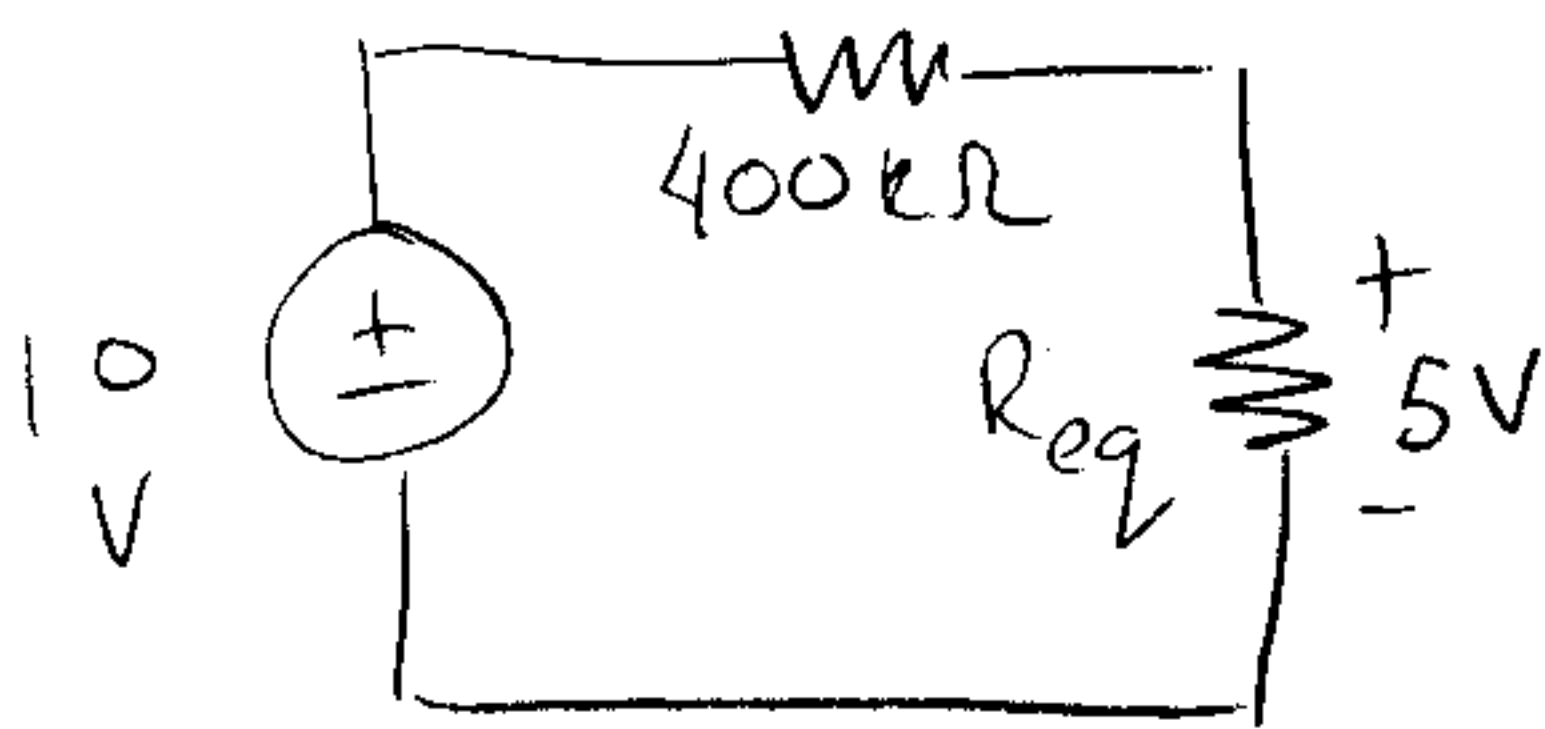That R_{eq} has the same voltage as the original parallel resistors:



By voltage division,

$$5\text{V} = 10\text{V} \cdot \frac{R_{eq}}{400\text{k}\Omega + R_{eq}}$$

$$\text{So } R_{eq} = 400\text{k}\Omega.$$

Now we know


$$R_{eq} = 400\text{k}\Omega = \frac{R_M \cdot 600\text{k}\Omega}{R_M + 600\text{k}\Omega} \quad \text{so } R_M = 1.2\text{M}\Omega$$

Problem 5:


One could use nodal analysis.

I prefer to piece together clues:

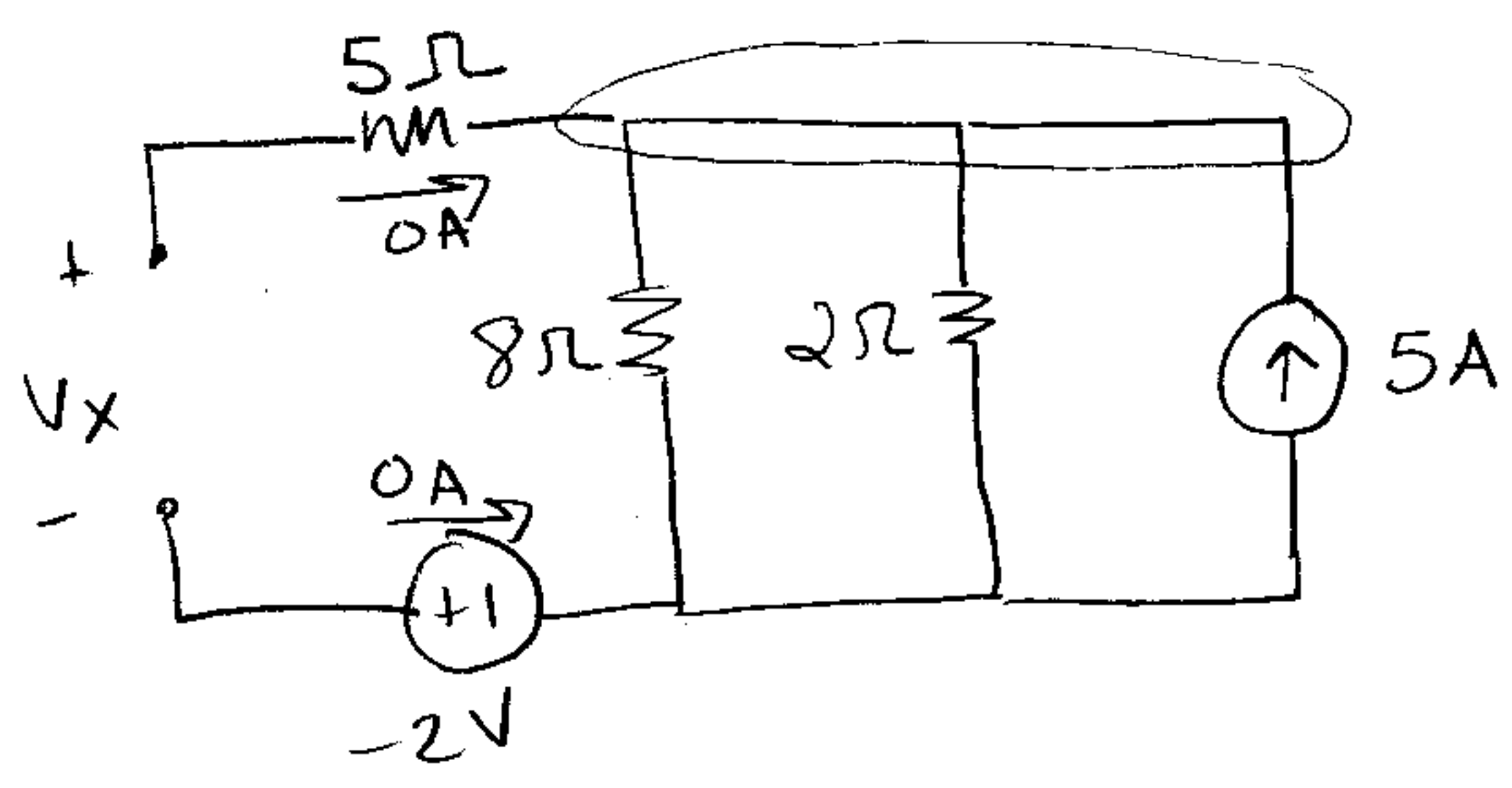- There can be no current through the hole in the circuit. So there is no current in the 5Ω resistor or in the $-2V$ source.



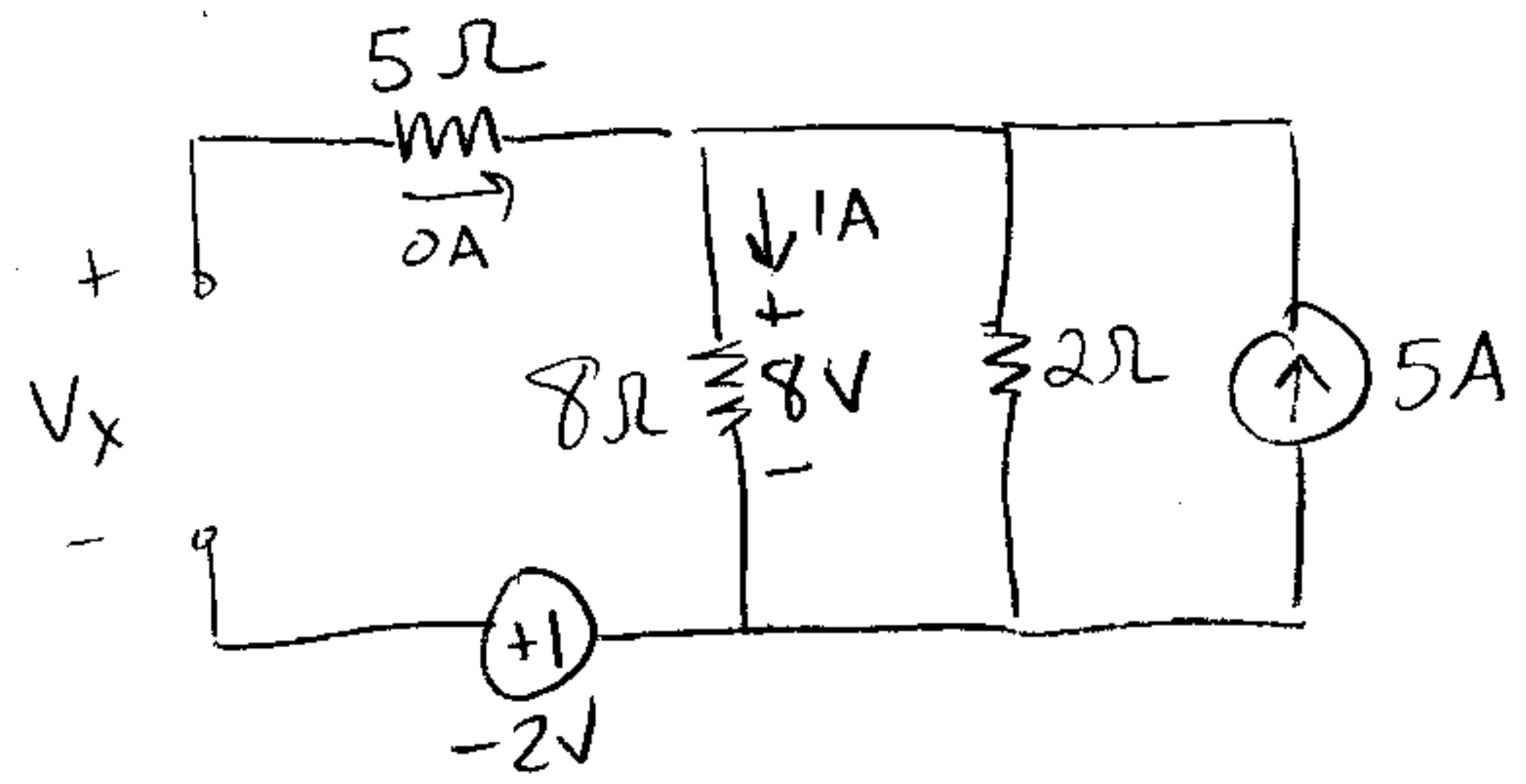- By KCL at the circled node, $5A$ goes in, and no current can enter the 5Ω resistor. So all $5A$ is divided between the 8Ω and 2Ω resistors.



- By current division, the 8Ω resistor gets $1A$ ($5A \cdot \frac{2\Omega}{8\Omega + 2\Omega} = 1A$). Therefore, the 8Ω resistor gets $8V$.

(You could also combine the resistors in parallel to reach this conclusion.)

• By KVL, $V_x + -2V - 8V - \textcircled{0V} = 0$

the 5Ω resistor has $0V$, by ohm's law

So $V_x = 10V$.