

University of California at Berkeley  
 College of Engineering  
 Department of Electrical Engineering and Computer Science

EECS 150  
 Fall 2000

R. H. Katz

**Problem Set # 4 - Solution**

1a) Inputs: n\_of\_d[1:0]  
           n\_of\_n[2:0]  
 Outputs: d\_out[1:0]  
           n\_out[2:0]  
           no\_change

b) The d\_out bits tell how many dimes should be given: 00 for none, 01 for one, and 10 for two. Three dimes should never be given so 11 is undefined.

The n\_out bits are similar to dimes\_out: 000 for none, 001 for one, 010 for two, 011 for three, 101 for four, and 110 for five. Anything else is undefined.

no\_change will be 1 if it is not possible to return change and 0 if it is. If no\_change is 1, we don't care about all the other outputs. I'm assuming that the larger system will ignore the other output signals when no\_change is 1.

c)

n_of_d1	n_of_d0	n_of_n2	n_of_n1	n_of_n0	d_out1	d_out0	n_out2	n_out1	n_out0	no_change
0	0	0	0	0	x	x	x	x	x	1
0	0	0	0	1	x	x	x	x	x	1
0	0	0	1	0	x	x	x	x	x	1
0	0	0	1	1	x	x	x	x	x	1
0	0	1	0	0	x	x	x	x	x	1
0	0	1	0	1	x	x	1	0	1	0
0	0	1	1	0	x	x	1	0	1	0
0	0	1	1	1	x	x	1	0	1	0
0	1	0	0	0	x	x	x	x	x	1
0	1	0	0	1	x	x	x	x	x	1
0	1	0	1	0	x	x	x	x	x	1
0	1	0	1	1	0	1	0	1	1	0
0	1	1	0	0	0	1	0	1	1	0
0	1	1	0	1	0	1	0	1	1	0
0	1	1	1	0	0	1	0	1	1	0
0	1	1	1	1	0	1	0	1	1	0
1	0	0	0	0	x	x	x	x	x	1
1	0	0	0	1	1	0	0	0	1	0
1	0	0	1	0	1	0	0	0	1	0
1	0	0	1	1	1	0	0	0	1	0
1	0	1	0	0	1	0	0	0	1	0
1	0	1	0	1	1	0	0	0	1	0

1	0	1	1	0	1	0	0	0	1	0
1	0	1	1	1	1	0	0	0	1	0
1	1	0	0	0	x	x	x	x	x	1
1	1	0	0	1	1	0	0	0	1	0
1	1	0	1	0	1	0	0	0	1	0
1	1	0	1	1	1	0	0	0	1	0
1	1	1	0	0	1	0	0	0	1	0
1	1	1	0	1	1	0	0	0	1	0
1	1	1	1	0	1	0	0	0	1	0
1	1	1	1	1	1	0	0	0	1	0

**d\_out1:**

	n_of_d0 n_of_n2	n_of_n1 n_of_n0	00	01	11	10
n_of_d1=0			x	x	x	x
			x	x	x	x
			0	0	0	0
			x	x	0	x

	n_of_d0 n_of_n2	n_of_n1 n_of_n0	00	01	11	10
n_of_d1=1			x	1	1	1
			1	1	1	1
			1	1	1	1
			x	1	1	1

**d\_out1 = n\_of\_d1**

**d\_out0:**

	n_of_d0 n_of_n2	n_of_n1 n_of_n0	00	01	11	10
n_of_d1=0			x	x	x	x
			x	x	x	x
			1	1	1	1
			x	x	1	x

	n_of_d0 n_of_n2	n_of_n1 n_of_n0	00	01	11	10
n_of_d1=1			x	0	0	0
			0	0	0	0
			0	0	0	0
			x	0	0	0

**d\_out0 = n\_of\_d1'**

**n\_out2:**

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=0$			00	x	x	x	x
			01	x	1	1	1
			11	0	0	0	0
			10	x	x	0	x

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=1$			00	x	0	0	0
			01	0	0	0	0
			11	0	0	0	0
			10	x	0	0	0

**$n\_out2 = n\_of\_d1 \cdot n\_of\_d0$**

**n\_out1:**

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=0$			00	x	x	x	x
			01	x	0	0	0
			11	1	1	1	1
			10	x	x	1	x

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=1$			00	x	1	1	1
			01	1	1	1	1
			11	1	1	1	1
			10	x	1	1	1

**$d\_out1 = n\_of\_d1 + n\_of\_d0$**



**n\_out0:**

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=0$			00	x	x	x	x
			01	x	1	1	1
			11	x	x	x	x
			10	x	x	x	x

	$n\_of\_d0 n\_of\_n2$	$n\_of\_n1 n\_of\_n0$	00	01	11	10	
$n\_of\_d1=1$			00	x	1	1	1
			01	1	1	1	1
			11	1	1	1	1
			10	x	1	1	1


**$n\_out0 = 1$**

**no\_change:**

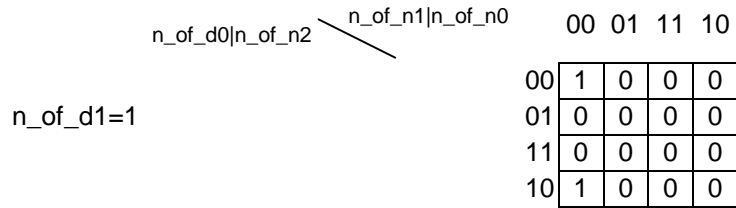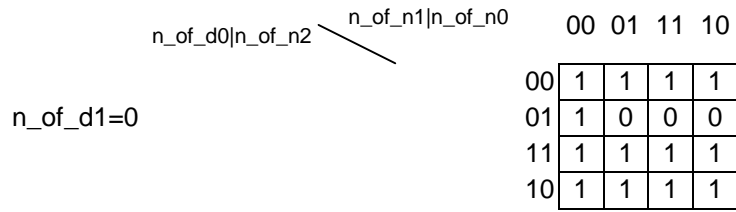

$$no\_change = n\_of\_d1' \cdot n\_of\_d0 + n\_of\_d1' \cdot n\_of\_n2' + n\_of\_d1' \cdot n\_of\_n1 \cdot n\_of\_n0 + n\_of\_n2' \cdot n\_of\_n1' \cdot n\_of\_n0'$$

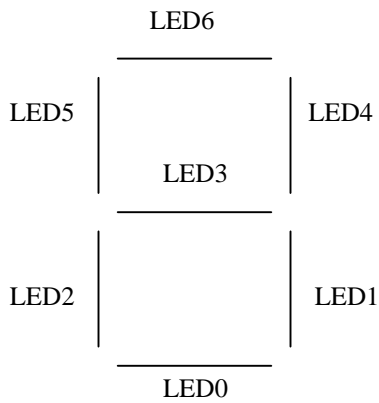2) This is the way I am labeling the display:



A	B	C	D	L6	L5	L4	L3	L2	L1	L0
0	0	0	0	1	1	1	0	1	1	1
0	0	0	1	1	0	0	0	0	0	0
0	0	1	0	1	0	0	1	0	0	0
0	0	1	1	1	0	0	1	0	0	1
0	1	0	0	0	1	1	1	0	0	0
0	1	0	1	0	0	0	1	1	1	0
0	1	1	0	0	0	1	1	1	0	0
0	1	1	1	0	1	0	1	0	1	0
1	0	0	0	0	1	1	0	1	1	0
1	0	0	1	0	1	1	1	1	1	0
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

L6:

AB \ CD	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	X	X	X	X
10	0	0	X	X

$$L6 = A'B'$$

L5:

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	0	1	0
11	X	X	X	X
10	1	1	X	X

$$L5 = A + C'D' + BCD$$

L4:

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	0	0	1
11	X	X	X	X
10	1	1	X	X

$$L4 = A + C'D' + BCD'$$

L3:

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	1	1
11	X	X	X	X
10	0	1	X	X

$$L3 = C + B + AD$$

L2:

AB \ CD	00	01	11	10
00	1	0	0	0
01	0	1	0	1
11	X	X	X	X
10	1	1	X	X

$$L2 = A + B'C'D' + BC'D + BCD'$$

L1:

AB \ CD	00	01	11	10
00	1	0	0	0
01	0	1	1	0
11	X	X	X	X
10	1	1	X	X


$$L1 = A + BD + B'C'D$$

L0:

AB \ CD	00	01	11	10
00	1	0	1	0
01	0	0	0	0
11	X	X	X	X
10	0	0	X	X

$$L0 = A'B'C'D' + B'CD$$

L5 AND L6

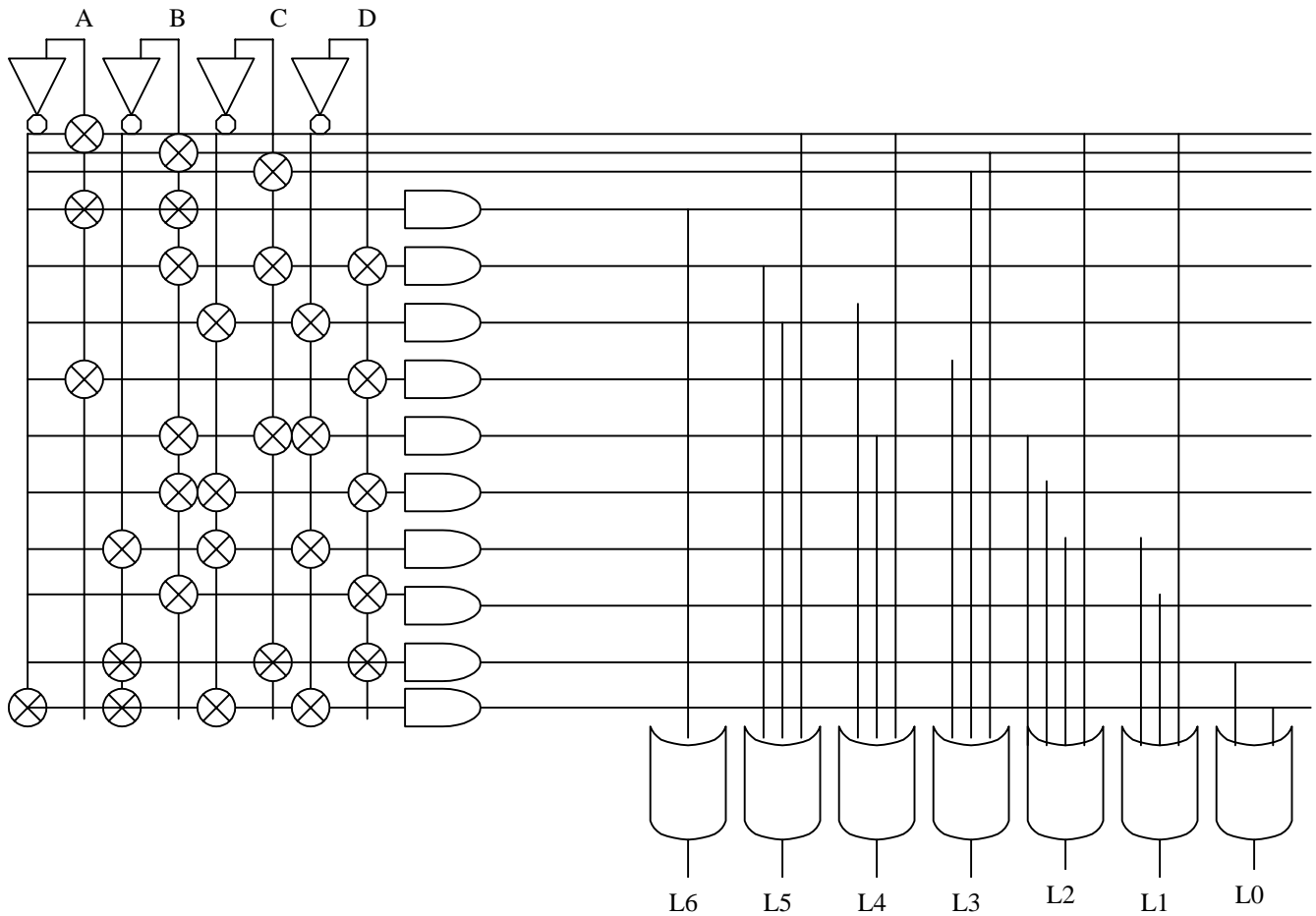

3a)


A	B	C	D0	D1	Z
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	0	1	1
1	1	0	1	0	0
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

AB	CD0		D1=0	
	00	01	11	10
00	0	0	1	0
01	0	0	1	1
11	0	0	1	1
10	1	0	1	0

AB	CD0		D1=1	
	00	01	11	10
00	0	0	1	0
01	0	1	0	1
11	1	1	1	1
10	0	0	1	1

$$Z = AB'C'D_0'D_1' + BCD_1' + B'CD_0 + BC'D_0D_1 + ABD_1 + BCD_0' + ACD_1$$

b, c)

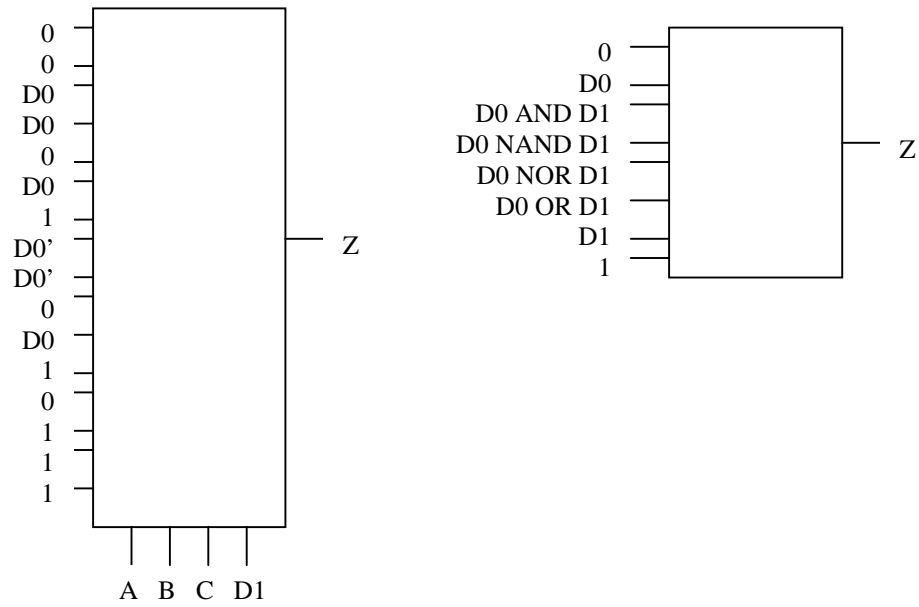

d) In terms of logic gates, the implementation in part a) will be the best.