

University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science

EECS 150
 Fall 2000

R. H. Katz

Solutions Set # 2

1. Simplify the following expressions using the laws and theorems of Boolean Algebra:

$$\begin{aligned} \text{(a) } S(A,B,C) &= A' B' C + A' B C' + A B' C' + A B C \\ &= A' (B' C + B C') + A (B' C' + B C) \\ &= A' (B \text{ XOR } C) + A ((B \text{ XOR } C)') \\ &= A \text{ XOR } B \text{ XOR } C \end{aligned}$$

$$\begin{aligned} \text{(b) } F(A,B,C) &= A' B' C' + A' B' C + A B' C' + A B' C + A B C' + A B C \\ &= A' B' (C' + C) + A B' (C' + C) + A B (C' + C) \\ &= A' B' + A B' + A B \\ &= A' B' + A B' + A B' + A B \\ &= B' (A' + A) + A (B' + B) \\ &= B' + A \end{aligned}$$

$$\begin{aligned} \text{(c) } G(A,B,C,D) &= A' B' C' D' + A' B' C D' + A B' C' D' + A B' C D + A B C' D' + A B C D \\ &= A' B' D' (C' + C) + A C' D' (B' + B) + A C D (B' + B) \\ &= A' B' D' + A C' D' + A C D \\ &= A' B' D' + A ((C \text{ XOR } D)') \end{aligned}$$

2. Use K-maps on the expressions of Problem 1. Show your work in K-map form. For 1(a)-(c):

(a) Find the minimized sum of products form.

1a)

$C \backslash AB$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S = A' B' C + A' B C' + A B C + A B C'$$

1b)

$C \backslash AB$	00	01	11	10
0	1	0	1	1
1	1	0	1	1

$$F = B' + A$$

1c)

CD\AB	00	01	11	10
00	1	0	1	1
01	0	0	0	0
11	0	0	1	1
10	1	0	0	0

$$G = AC'D' + ACD + A'B'D'$$

(b) Find the minimized product of sums form.

1a)

C\AB	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\begin{aligned} S' &= A'B'C' + A'BC + ABC' + AB'C \\ &= (A'B'C')' (A'BC)' (ABC')' (AB'C)' \\ &= (A + B + C) (A + B' + C') (A' + B' + C) (A' + B + C') \end{aligned}$$

1b)

C\AB	00	01	11	10
0	1	0	1	1
1	1	0	1	1

$$\begin{aligned} F' &= BA' \\ &= A + B' \end{aligned}$$

1c)

CD\AB	00	01	11	10
00	1	0	1	1
01	0	0	0	0
11	0	0	1	1
10	1	0	0	0

$$\begin{aligned} G' &= C'D + A'B + A'D + ACD' \\ &= (C'D)' (A'B)' (A'D)' (ACD')' \\ &= (C + D') (A + B') (A + D') (A' + C' + D) \end{aligned}$$

(c) Find the minimized sum of products form of the function's complement.

k-maps are the same from part b

1a) $S' = A'B'C' + A'BC + ABC' + AB'C$

1b) $F' = A'B$

1c) $G' = A'D + A'B + C'D + ACD'$

(d) Find the minimized product of sums form of the function's complement.

K-maps are the same from part a


1a) $F = A'B'C + A'BC' + ABC + AB'C'$
 $F' = (A + B + C')(A + B' + C)(A' + B' + C')(A' + B + C)$

1b) $F = A + B'$
 $F' = A'B$


1c) $G = AC'D' + ACD + A'B'D'$
 $G' = (A' + C + D)(A' + C' + D')(A + B + D)$

3i)

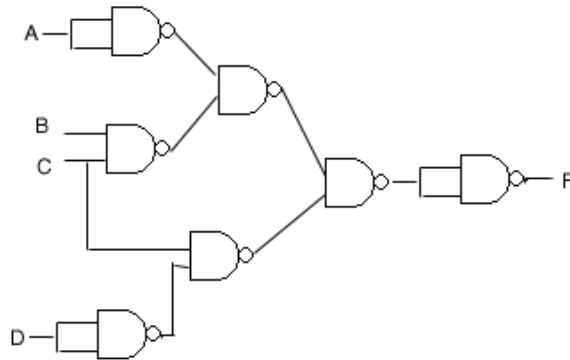a) One possible solution: $F(A,B,C,D) = (A + (B C)) (C' + D) = ((A' (B C)')') (C D')')$



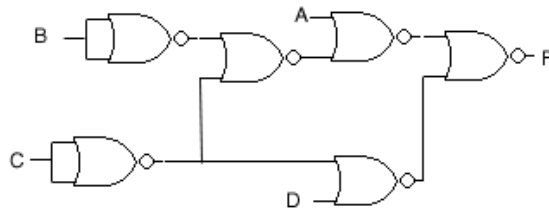b) One possible solution: $F(A,B,C,D) = (A + (B C)) (C' + D) = ((A + (B'+C'))') + (C' + D)')$




c) $F = AC' + AD + BCD$
d) $F = (A+B)(A+C)(C'+D)$

CD \ AB	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	1	1	1
10	0	0	0	0


e) The simplest implementation is the NOR gate implementation. It uses the least gates of all the above implementations.

3ii)

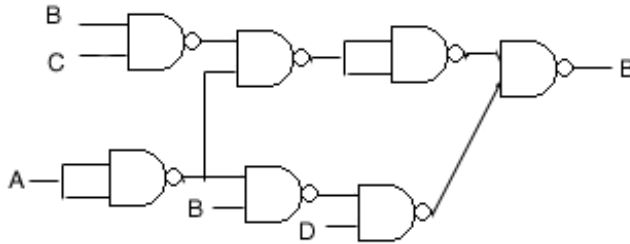a) One possible solution: $G(A,B,C,D) = ((A+B')D) + (A+(BC)) = ((A'B')D)' ((A'(BC)')')'$



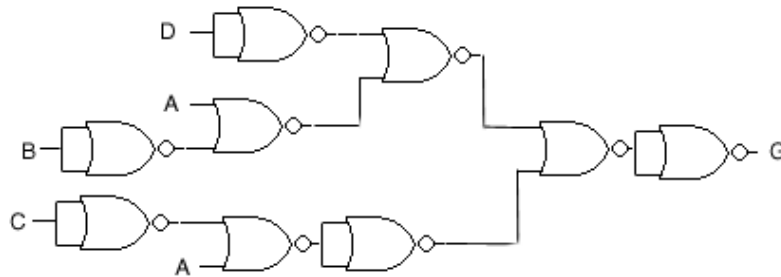b) One possible solution: $G(A,B,C,D) = ((A+B')D) + (A+(BC)) = (((A+B')' + D')' + ((B' + C')' + A)')'$



c) $G = A + BC + B'D$

d) $G = (A+B'+C)(A+B+D)$

CD \ AB	AB			
	00	01	11	10
00	0	0	1	1
01	1	0	1	1
11	1	1	1	1
10	0	1	1	1

e) The sum of products implementation is the simplest to implement in this case. It uses the least gates of the four implementations.

4a)

A	B	C	D	W	X	Y	Z
0	0	0	0	X	X	X	X
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	X	X	X	X
0	1	0	1	0	1	0	0
0	1	1	0	0	0	0	1
0	1	1	1	0	0	0	1
1	0	0	0	X	X	X	X
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	X	X	X	X
1	1	0	1	1	1	0	0
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	0

4b)

$$W = AC'$$

$$X = BC' + AB + AD'$$

CD \ AB	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	0	0	0	0
10	0	0	0	0

CD \ AB	00	01	11	10
00	X	X	X	X
01	0	1	1	0
11	0	0	1	0
10	0	0	1	1

$$Y = AB'CD$$

$$Z = BD' + A'BC$$

CD \ AB	00	01	11	10
00	X	X	X	X
01	0	0	0	0
11	0	0	0	1
10	0	0	0	0

CD \ AB	00	01	11	10
00	X	X	X	X
01	0	0	0	0
11	0	1	0	0
10	0	1	1	0

4c) $W = A+C'$ $X = (A+C')(B+D')$ $Y = AB'CD$ $Z = BC(B'+D')$

5a)

A	B	C	D	By2	By3	By6
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	0
0	1	1	0	1	1	1
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	0
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

5b) By2 = D'

CD \ AB	00	01	11	10
00	1	1	X	1
01	0	0	X	0
11	0	0	X	0
10	1	1	X	1

By3 = A'B'C'D' + A'B'CD + AC'D + BCD'

CD \ AB	00	01	11	10
00	1	0	X	0
01	0	0	X	1
11	1	0	X	0
10	0	1	X	0

By6 = A'B'C'D' + BCD'

CD \ AB	00	01	11	10
00	1	0	X	0
01	0	0	X	0
11	0	0	X	0
10	0	1	X	0

5c) By2 cannot be simplified any further.

By3 can be rewritten as $A'B'(C'D' + CD) + AC'D + BCD'$ or $A'B'(\overline{C'D'} \text{ XOR } CD) + AC'D + BCD'$

By6 can be rewritten as $D'(A'B'C' + BC)$ but is not that much simpler than the original other than the fact that the four input AND gate can be replaced by a three input AND gate.