

CS 150
Lab Lecture 2

Schematic Entry & Simulation, Part 010₂
Finite State Machines
Laura Todd, 9-8-2000

DON'T
PANIC

Homework Quiz

- NMP - Not My Problem. ;P

CS 150 - Fall 00 - Lab Lecture 2

2

Overview

- Homework Quiz ✓
- Administrivia
- Objectives
- Prelab
- Brief Description
- To-do
- Hints, tips, and tricks

CS 150 - Fall 00 - Lab Lecture 2

3

Administrivia

■ Discussion Sections:

■ Monday	1-2	285 Cory
■ Tuesday	1-2	310 Soda
■ Wednesday	1-2	71 Evans
■ Wednesday	2-3	4 Evans
■ Thursday	1-2	310 Soda

■ Office Hours (TAs)

■ Laura	Wed 3-4	204b Cory
■ Jimmy	Tu 4-5	204b Cory
■ Norm	Th 3:30-5	204b Cory
■ Po	Th 1-2	204b Cory
■ Ramki	F 9:30-11:30	tentatively 464 Soda

CS 150 - Fall 00 - Lab Lecture 2

4

Objectives

- Practice using Xilinx software
- Enter a FSM design from logic equations
- Simulate the FSM
- Work in a group

CS 150 - Fall 00 - Lab Lecture 2

5

Prelab

■ Get a partner in YOUR lab section

- For the first few labs, your partner must be from your own lab section

■ Complete the IN1 and IN2 blocks

■ Write a script file to test your design

■ Why do we have a prelab assignment?

- Because there's lots to do, maybe more than you can do in 3 hours
- Much of the design work can be done on paper beforehand

CS 150 - Fall 00 - Lab Lecture 2

6


Brief Description - the "High Level Spec"

- The high-level spec is a description of the problem in "plain English"
 - This is a very general description of the system you're trying to build, in our case, a combination lock
 - Our lock will have a RESET button, an ENTER button, and two binary switches: CODE1 and CODE0.
 - To open the lock, the user must enter a pair of 2-bit codes. (ie. 01 <enter> 11 <enter>)
 - If the user enters the right codes, the lock will OPEN, otherwise it will indicate an ERROR
 - Designing from a high-level specs is like those old math word problems: you have to come up with a way to get the answer all on your own. But don't despair, we do it for you this time!

CS.150 - Fall '00 - Lab Lecture 2

7

 Brief Description - Lower Levels: Down the rabbit hole...




System-level view: these are the building blocks we need

CS.150 - Fall '00 - Lab Lecture 2

8

Brief Description - the Clock

 - The "clock" keeps the FSM synchronized.




- When the clock goes "BONG!" the FSM will change state
- During the part of the clock marked with orange, the logic has time to figure out what it's next state is going to be
- When the clock signal value goes from "0" to "1", we call that a rising edge. The time from one rising edge to another is called the "clock cycle" time.
- Let's look at the FSM for the lab→

CS.150 - Fall '00 - Lab Lecture 2

9

 Brief Description - Lower Levels: Round and round she goes...



Logical view: the finite state machine

CS.150 - Fall '00 - Lab Lecture 2

10

Brief Description - the IN* blocks

- The IN1 and IN2 blocks compare the code the user inputs to the "secret" code that will open the lock.
 - If code matches, assert a TRUE on the output (COM*)
 - Otherwise, assert a FALSE
- Choose your own combination. Write it down.
- The two combinations must be different:
 - Good: 01 11
 - Bad: 10 10
- IN1 and IN2 are very simple blocks. Just some AND gates and inverters.

CS.150 - Fall '00 - Lab Lecture 2

11

Brief Description - MyCLB

- CLB = Combinational Logic Block => and, or, inv...
- The MyCLB block acts as the controller for our lock, it's the brains
- Truth table and logic equations are in the printout
 - You're expected to implement this block during lab time.
- This block is a little messy:
 - So, keep your schematic neat (it'll be easier to debug)
 - Watch for mis-labeled wires
- KISS-Keep It Simple, Stupid
 - Use the "multi-level" equations, they're much easier to debug
 - But take the time to understand them!


CS.150 - Fall '00 - Lab Lecture 2

12

Brief Description - MyDFF

■ What the heck are D flip-flops????

 - Remember sequential logic? We need a way of saving the current state!
- Welcome to the world of memory!
- D flip-flops are memory elements
- Put what you want to save on the D pin
- When the clock has a rising edge the DFF will look at the value on D and move it to Q
- Now until the next rising edge on the clock, Q will remain the same, giving us a saved output



- This is the simple version: lots more later in class!

CS150 - Fall 00 - LabLecture 2

13

ToDo's - What you need for credit

- Enter the IN1, IN2, MyCLB schematics
- Make a test script for your CLB. Run it. Make sure it's correct. (You want this to work, don't you?)
- Make the MyDFF block.
- Wire up all the individual pieces you just made.
- Write a script to simulate scenarios on the full lock
 - Successful/Unsuccessful entries of the combination
 - Use of the RESET and ENTER buttons
 - Do all the paths on the state diagram work correctly?
 - Create a log file to show your TA

CS150 - Fall 00 - LabLecture 2

14

Hints, Tips, and Tricks

- Buses are your friends.
 - CS150 buses: collections of wires that have a similar purpose
 - Usually same wire name + a number, as in DATA7, DATA6, ... DATA1, DATA0
 - Simplify, simplify, simplify...
- Scripts are your friends.
 - Note: the pipe character "|" will comment out a line.
- Don't print things!
- Xilinx software is buggy. When in doubt, restart it.

CS150 - Fall 00 - LabLecture 2

15

The End... for now.

**DON'T
PANIC**

Ya ain't seen nuthin' yet...