

# EECS150 Fall 2000 Lab6 - Nasty Realities

by Sammy Sy

Don't let the title scare you. Even though the final project might be nasty, this lab is not.

## Sections

- Some information on the electrical components in this lab
- Capacitance vs Propagation delay
- Reflection and Termination
- Capacitive Coupling
- Extra Xilinx tips

## Components (1)

- Breadboard
- Which holes are connected with which?



## Components (2)

- Ribbon cable
- Is interference a problem?
- We'll find out




## Components (3)

- Resistors and capacitors
- Time to figure out how those colors on resistors and numbers on capacitors mean
- Detailed description on the lab handout
- Example: red-black-brown = 200 ohm (red = 2, black = 0, brown 1)
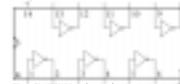
## Components (4)

- 74F04PC hex inverter chip
- Essentially just a bunch of inverter gates
- Remember an inverter requires input, **and VCC and GND.**



## Components (5)

- We also need a bunch of normal wires to hook them up
- Remind yourself how to play with the pulse generator
- More practice with the mighty oscilloscope

## What to do in this lab

- You will be building several simple circuits to measure gate delays, and observe how reflection and capacitance affect electrical signals.
- The lab handout gives you the step-by-step procedures.
- Some motivations.

## Capacitance vs Propagation delay (1)

- Capacitance is evil
- Why?
- It limits how fast a gate transition can take place.
- In fact, all conductors are subject to this evilness - for example, two wires together.

## Capacitance vs Propagation delay (2)

- Ring oscillator
- No stable state
- Therefore, those inverters will be switching as fast as their capacitance allows.
- $T = 2 * \text{delay} * N$



## Reflection and Termination (1)

- What's reflection?
- If you view electrical signal as propagation of E&M waves, then a wire is no different than optical fiber.
- When the signal hits a dead end, it bounces back and interferes with itself.
- Can be solved by proper termination.

## Reflection and Termination (2)

- Terminate by eliminating those dead ends.
- Add some load (i.e.: resistance).
- I once heard that TV cable companies detect undesired "fanouts" by sending a strong pulse to the wire and count the number of reflections received.
- Now you can outsmart them.



### Capacitive Coupling (1)

- Recall the ribbon cable
- Signal on wire interferes with the neighboring wires. It's especially noticeable in long and crowded wires.
- An undriven wire is more easily affected.



### Capacitive Coupling (2)

- For example, say we have 3 wires A, B and C arranged linearly (i.e. B is between A and B).
- Let A = some signal
- Let B = undriven
- Let C = some other signal
- Because B is undriven, it's easily influenced by A and C



### Capacitive Coupling (3)

- Simultaneously, B affects A and C.
- We can introduce a "shield" to protect the signals in A and C.
- If we ground B, it becomes much less likely to be manipulated by A and C.
- Thus, A and C won't step onto each others' toes.



### Xilinx Tips (1)

- This lab doesn't need Xilinx (relieved!)
- Difference between FDC and FDR (similarly applies to CC8CE vs CC8RE, etc)
- FDC = D-type flipflop with *asynchronous* clear
- FDR = D-type flipflop with *synchronous* reset



### Xilinx Tips (2)

- Keep the clock signal clean!
- Read the implementation log
- Once you've made something into a macro, the original schematic file is not used by the project anymore.
- Ground yourself