

Sequential Logic Examples

- Finite State Machine Concept
 - FSMs are the decision making logic of digital designs
 - Partitioning designs into datapath and control elements
 - When inputs are sampled and outputs asserted
- Basic Design Approach: 4-step Design Process
- Implementation Examples and Case Studies
 - Finite-string pattern recognizer
 - Complex counter
 - Traffic light controller
 - Door combination lock

CS 150 - Fall 2000 - Sequential Logic Examples - 1

General FSM Design Procedure

- (1) Determine inputs and outputs
- (2) Determine possible states of machine
 - - State minimization
- (3) Encode states and outputs into a binary code
 - - State assignment or state encoding
 - - Output encoding
 - - Possibly input encoding (if under our control)
- (4) Realize logic to implement functions for states and outputs
 - - Combinational logic implementation and optimization
 - - Choices in steps 2 and 3 have large effect on resulting logic

CS 150 - Fall 2000 - Sequential Logic Examples - 2

Finite String Pattern Recognizer (Step 1)

- Finite String Pattern Recognizer
 - One input (X) and one output (Z)
 - Output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen
- Step 1: Understanding the Problem Statement
 - Sample input/output behavior:


X: 00101010010 ...
Z: 00010101000 ...

X: 11011010010 ...
Z: 00000001000 ...

CS 150 - Fall 2000 - Sequential Logic Examples - 3

Finite String Pattern Recognizer (Step 2)

- Step 2: Draw State Diagram
 - For the strings that must be recognized, i.e., 010 and 100
 - Moore implementation

 


CS 150 - Fall 2000 - Sequential Logic Examples - 4

Finite String Pattern Recognizer (Step 2, cont'd)

- Exit conditions from state S3: have recognized ...010
 - If next input is 0 then have ...0100 = ...100 (state S6)
 - If next input is 1 then have ...0101 = ...01 (state S2)

Exit conditions from S1: recognizes strings of form ...0 (no 1 seen); loop back to S1 if input is 0

Exit conditions from S4: recognizes strings of form ...1 (no 0 seen); loop back to S4 if input is 1

 


CS 150 - Fall 2000 - Sequential Logic Examples - 5

Finite String Pattern Recognizer (Step 2, cont'd)

- S2 and S5 still have incomplete transitions
 - S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
 - S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case

- Reuse states as much as possible
 - Look for same meaning
 - State minimization leads to smaller number of bits to represent states
- Once all states have complete set of transitions we have final state diagram

 

CS 150 - Fall 2000 - Sequential Logic Examples - 6

Finite String Pattern Recognizer (Step 3)

Verilog description including state assignment (or state encoding)

```

module string (clk, X, rst, Q0, Q1, Q2, Z);
  input clk, X, rst;
  output Q0, Q1, Q2, Z;

  reg state[0:2];

  `define S0 = {0,0,0}; //reset state
  `define S1 = {0,0,1}; //strings ending in ...0
  `define S2 = {0,1,0}; //strings ending in ...01
  `define S3 = {0,1,1}; //strings ending in ...010
  `define S4 = {1,0,0}; //strings ending in ...1
  `define S5 = {1,0,1}; //strings ending in ...10
  `define S6 = {1,1,0}; //strings ending in ...100

  assign Q0 = state[0];
  assign Q1 = state[1];
  assign Q2 = state[2];
  assign Z = (state == `S3);

  always @(posedge clk) begin
    if rst state = `S0;
    else
      case (state)
        `S0: if (X) state = `S4 else state = `S1;
        `S1: if (X) state = `S2 else state = `S1;
        `S2: if (X) state = `S4 else state = `S3;
        `S3: if (X) state = `S2 else state = `S6;
        `S4: if (X) state = `S4 else state = `S5;
        `S5: if (X) state = `S2 else state = `S6;
        `S6: state = `S6;
        default: begin
          $display ("invalid state reached");
          state = 3'bxxx;
        endcase
      endcase
    end
  end
endmodule

```

CS 150 - Fall 2000 - Sequential Logic Examples - 7

Finite String Pattern Recognizer

Review of Process

- Understanding problem
 - Write down sample inputs and outputs to understand specification
- Derive a state diagram
 - Write down sequences of states and transitions for sequences to be recognized
- Minimize number of states
 - Add missing transitions; reuse states as much as possible
- State assignment or encoding
 - Encode states with unique patterns
- Simulate realization
 - Verify I/O behavior of your state diagram to ensure it matches specification

CS 150 - Fall 2000 - Sequential Logic Examples - 8

Complex Counter

Synchronous 3-bit counter has a mode control M

- When M = 0, the counter counts up in the binary sequence
- When M = 1, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111
 Gray: 000, 001, 011, 010, 110, 111, 101, 100

Valid I/O behavior (partial)


Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

CS 150 - Fall 2000 - Sequential Logic Examples - 9

Complex Counter (State Diagram)

Deriving State Diagram

- One state for each output combination
- Add appropriate arcs for the mode control

 

CS 150 - Fall 2000 - Sequential Logic Examples - 10

Complex Counter (State Encoding)

Verilog description including state encoding

```

module string (clk, M, rst, Z0, Z1, Z2);
  input clk, X, rst;
  output Z0, Z1, Z2;

  reg state[0:2];

  `define S0 = {0,0,0};
  `define S1 = {0,0,1};
  `define S2 = {0,1,0};
  `define S3 = {0,1,1};
  `define S4 = {1,0,0};
  `define S5 = {1,0,1};
  `define S6 = {1,1,0};
  `define S7 = {1,1,1};

  assign Z0 = state[0];
  assign Z1 = state[1];
  assign Z2 = state[2];

  always @(posedge clk) begin
    if rst state = `S0;
    else
      case (state)
        `S0: state = `S1;
        `S1: if (M) state = `S3 else state = `S2;
        `S2: if (M) state = `S6 else state = `S3;
        `S3: if (M) state = `S2 else state = `S4;
        `S4: if (M) state = `S0 else state = `S5;
        `S5: if (M) state = `S4 else state = `S6;
        `S6: if (M) state = `S7 else state = `S7;
        `S7: if (M) state = `S5 else state = `S0;
      endcase
    end
  end
endmodule


```

CS 150 - Fall 2000 - Sequential Logic Examples - 11

Traffic Light Controller as Two Communicating FSMs


Without Separate Timer

 - S0 would require 7 states
- S1 would require 3 states
- S2 would require 7 states
- S3 would require 3 states
- S1 and S3 have simple transformation
- S0 and S2 would require many more arcs
 - C could change in any of seven states



By Factoring Out Timer


- Greatly reduce number of states
 - 4 instead of 20
- Counter only requires seven or eight states
 - 12 total instead of 20

 

CS 150 - Fall 2000 - Sequential Logic Examples - 12

Communicating Finite State Machines


- One machine's output is another machine's input

 

CS 150 - Fall 2000 - Sequential Logic Examples - 13

Datapath and Control

- Digital hardware systems = data-path + control
 - Datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - Control: FSM generating sequences of control signals that instructs datapath what to do next

 

CS 150 - Fall 2000 - Sequential Logic Examples - 14

Digital Combinational Lock

- Door Combination Lock:
 - Punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - Inputs: sequence of input values, reset
 - Outputs: door open/close
 - Memory: must remember combination or always have it available
 - Open questions: how do you set the internal combination?
 - Stored in registers (how loaded?)
 - Hardwired via switches set by user

CS 150 - Fall 2000 - Sequential Logic Examples - 15

Implementation in Software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value ( ));
    v1 = read_value ( );
    if (v1 != c[1]) then error = 1;

    while (!new_value ( ));
    v2 = read_value ( );
    if (v2 != c[2]) then error = 1;


    while (!new_value ( ));
    v3 = read_value ( );
    if (v3 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```

CS 150 - Fall 2000 - Sequential Logic Examples - 16

Determining Details of the Specification


- How many bits per input value?
- How many values in sequence?
- How do we know a new input value is entered?
- What are the states and state transitions of the system?

 

CS 150 - Fall 2000 - Sequential Logic Examples - 17

Digital Combination Lock State Diagram


- States: 5 states
 - Represent point in execution of machine
 - Each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - Changes of state occur when clock says its ok
 - Based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed

 

CS 150 - Fall 2000 - Sequential Logic Examples - 18

Datapath and Control Structure

- Datapath**
 - Storage registers for combination values
 - Multiplexer
 - Comparator
- Control**
 - Finite-state machine controller
 - Control for data-path (which value to compare)

 

CS 150 - Fall 2000 - Sequential Logic Examples - 19

State Table for Combination Lock


- Finite-State Machine**
 - Refine state diagram to take internal structure into account
 - State table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...
0	1	1	S3	OPEN	-	open
...

CS 150 - Fall 2000 - Sequential Logic Examples - 20

Encodings for Combination Lock

- Encode state table**
 - State can be: S1, S2, S3, OPEN, or ERR
 - Needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - And as many as 5: 00001, 00010, 00100, 01000, 10000
 - Choose 4 bits: 0001, 0010, 0100, 1000, 0000
 - Output mux can be: C1, C2, or C3
 - Needs 2 to 3 bits to encode
 - Choose 3 bits: 001, 010, 100
 - Output open/closed can be: open or closed
 - Needs 1 or 2 bits to encode
 - Choose 1 bit: 1, 0

 


reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...
0	1	1	0100	1000	-	1
...

CS 150 - Fall 2000 - Sequential Logic Examples - 21

Datapath Implementation for Combination Lock



- Multiplexer**
 - Easy to implement as combinational logic when few inputs
 - Logic can easily get too big for most PLDs

 

CS 150 - Fall 2000 - Sequential Logic Examples - 22

Datapath Implementation (cont'd)


- Tri-State Logic**
 - Utilize a third output state: "no connection" or "float"
 - Connect outputs together as long as only one is "enabled"
 - Open-collector gates can only output 0, not 1
 - Can be used to implement logical AND with only wires

  

CS 150 - Fall 2000 - Sequential Logic Examples - 23

Tri-State Gates

- Third value**
 - Logic values: "0", "1"
 - Don't care: "X" (must be 0 or 1 in real circuit!)
 - Third value or state: "Z" - high impedance, infinite R, no connection
- Tri-state gates**
 - Additional input - output enable (OE)
 - Output values are 0, 1, and Z
 - When OE is high, the gate functions normally
 - When OE is low, the gate is disconnected from wire at output
 - Allows more than one gate to be connected to the same output wire
 - As long as only one has its output enabled at any one time (otherwise, sparks could fly)

 

	In	OE	Out
non-inverting	X	0	Z
tri-state	0	1	0
buffer	1	1	1


CS 150 - Fall 2000 - Sequential Logic Examples - 24

Tri-State and Multiplexing

When Using Tri-State Logic

 
- (1) Never more than one "driver" for a wire at any one time (pulling high and low at same time can severely damage circuits)
- (2) Only use value on wire when its being driven (using a floating value may cause failures)

Using Tri-State Gates to Implement an Economical Multiplexer




Open-Collector Gates and Wired-AND

- Open collector:** another way to connect gate outputs to same wire
 - Gate only has the ability to pull its output low
 - Cannot actively drive wire high (default - pulled high through resistor)
 - Wired-AND can be implemented with open collector logic**
 - If A and B are "1", output is actively pulled low
 - If C and D are "1", output is actively pulled low
 - If one gate output is low and the other high, then low wins
 - If both outputs are "1", the wire value "floats", pulled high by resistor
 - Low to high transition usually slower than if gate pulling high
- Hence, the two NAND functions are ANDed together

 

Digital Combination Lock (New Datapath)

 - Decrease number of inputs
- Remove 3 code digits as inputs
 - Use code registers
 - Make them loadable from value
 - Need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - Could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



Section Summary

- FSM Design**
 - Understanding the problem
 - Generating state diagram
 - Implementation using synthesis tools
 - Iteration on design/specification to improve qualities of mapping
 - Communicating state machines
 - Four case studies**
 - Understand I/O behavior
 - Draw diagrams
 - Enumerate states for the "goal"
 - Expand with error conditions
 - Reuse states whenever possible
- CS 150 - Fall 2000 - Sequential Logic Examples - 28