

Implementation Strategies

ROM-based Design

Example: BCD to Excess 3 Serial Converter

BCD	Excess 3 Code
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111
0101	1000
0110	1001
0111	1010
1000	1011
1001	1100

Conversion Process

Bits are presented in bit serial fashion starting with the least significant bit


Single input X, single output Z

Xilinx FPGAs - 38

Implementation Strategies

Present State	Next State		Output	
	X=0	X=1	Z=0	Z=1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	--	1	--

State Transition Table

 


Derived State Diagram

Xilinx FPGAs - 39

Implementation Strategies

ROM-based Implementation

ROM Address	ROM Outputs			
X Q2 Q1 Q0	Z	D2	D1	D0
0 0 0 0	1	0	0	1
0 0 0 1	1	0	1	1
0 0 1 0	0	1	0	0
0 0 1 1	0	1	0	1
0 1 0 0	1	1	0	1
0 1 0 1	0	0	0	0
0 1 1 0	1	0	0	0
0 1 1 1	X	X	X	X
1 0 0 0	0	0	1	0
1 0 0 1	0	1	0	0
1 0 1 0	1	1	0	0
1 0 1 1	1	1	0	1
1 1 0 0	0	1	1	0
1 1 0 1	1	1	0	0
1 1 1 0	X	X	X	X
1 1 1 1	X	X	X	X

 

Circuit Level Realization
74175 = 4 x positive edge triggered D FFs


Truth Table/ROM I/Os

In ROM-based designs, no need to consider state assignment

Xilinx FPGAs - 40

Implementation Strategies

 Timing Behavior for input strings 0000(0) and 1110(7)



Xilinx FPGAs - 41

Implementation Strategies

PLA-based Design

State Assignment with NOVA

```

0 S0 S1 1
1 S0 S2 0
0 S1 S3 1
1 S1 S4 0
0 S2 S4 0
1 S2 S4 1
0 S3 S5 0
1 S3 S5 1
0 S4 S5 1
1 S4 S6 0
0 S5 S0 0
1 S5 S0 1
0 S6 S0 1
  
```

NOVA input file

```

S0 = 000
S1 = 001
S2 = 011
S3 = 110
S4 = 100
S5 = 111
S6 = 101
  
```

NOVA derived state assignment

9 product term implementation

Xilinx FPGAs - 42

Implementation Strategies

```

.i 4 Espresso Inputs .i 4 Espresso Outputs
.o 4 .o 4
.ilb x q2 q1 q0 .ilb x q2 q1 q0
.ob d2 d1 d0 z .ob d2 d1 d0 z
.p 16 .p 9
0 000 001 1 0001 0100
1 000 011 0 10-0 0100
0 001 110 1 01-0 0100
1 001 100 0 1-1- 0001
0 011 100 0 -0-1 1000
1 011 100 1 0-0- 0001
0 110 111 0 -1-0 1000
1 110 111 1 --10 0100
0 100 111 1 ---0 0010
1 100 101 0 .e
0 111 000 0
1 111 000 1
0 101 000 1
1 101 --- -
0 010 --- -
1 010 --- -
.e
  
```

Xilinx FPGAs - 43


Implementation Strategies

$$D2 = \overline{Q2} \cdot Q0 + Q2 \cdot \overline{Q0}$$

$$D1 = \overline{X} \cdot Q2 \cdot Q1 \cdot Q0 + X \cdot \overline{Q2} \cdot Q0 + X \cdot Q2 \cdot \overline{Q0} + Q1 \cdot Q0$$

$$D0 = Q0$$
 
$$Z = X \cdot Q1 + \overline{X} \cdot \overline{Q1}$$



Implementation Strategies


10H8 PAL: 10 inputs, 8 outputs, 2 product terms per OR gate

$$D1 = D11 + D12$$


$$D11 = \overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0 + X \cdot \overline{Q2} \cdot \overline{Q0}$$

$$D12 = \overline{X} \cdot Q2 \cdot \overline{Q0} + Q1 \cdot \overline{Q0}$$

 - 0. $Q2 \cdot Q0$
- 1. $Q2 \cdot \overline{Q0}$
- 8. $X \cdot Q2 \cdot Q1 \cdot Q0$
- 9. $X \cdot Q2 \cdot \overline{Q0}$
- 16. $\overline{X} \cdot Q2 \cdot \overline{Q0}$
- 17. $Q1 \cdot \overline{Q0}$
- 24. D11
- 25. D12
- 32. Q0
- 33. not used
- 40. $X \cdot Q1$
- 41. $X \cdot \overline{Q1}$




Implementation Strategies

 

Implementation Strategies

Registered PAL Architecture

Buffered Input or product term

 

$$\overline{D2} = Q2 \cdot Q0 + \overline{Q2} \cdot \overline{Q0}$$

$$\overline{D1} = \overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0 + X \cdot Q2 + X \cdot Q0 + Q2 \cdot Q0 + Q1 \cdot Q0$$

$$\overline{D0} = Q0$$


$$\overline{Z} = X \cdot \overline{Q1} + \overline{X} \cdot Q1$$

Negative Logic Feedback


Xilinx FPGAs - 47

Implementation Strategies

Programmable Output Polarity/XOR PALs

 

 
Advantage of XOR PAL: Parity and Arithmetic Operations



Implementation Strategies

Example of XOR PAL

Example of Registered PAL

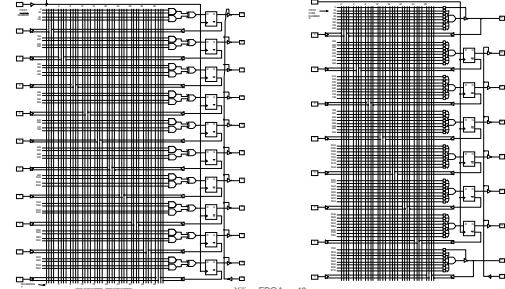

Specifying PALs with ABEL

```

PI0H8 PAL
module bod2excess3
title 'BCD to Excess 3 Code Converter State Machine'
ul device 'pi0h8';

*Input Pins
X,Q2,Q1,Q0,D11i,D12i pin 1,2,3,4,5,6;

*Output Pins
D2,D10,D12o,D1,D0,Z pin 19,18,17,16,15,14;

INSTATE = {Q2, Q1, Q0};
S0 = [0, 0, 0];
S1 = [0, 0, 1];
S2 = [0, 1, 1];
S3 = [1, 1, 0];
S4 = [1, 0, 0];
S5 = [1, 1, 1];
S6 = [1, 0, 1];

equations
D2 = (Q2 & Q0) # (Q2 & !Q0);
D1 = D11i # D12i;
D10 = (!X & !Q2 & !Q1 & Q0) # (X & !Q2 & !Q0);
D12o = (!X & Q2 & !Q0) # (Q1 & !Q0);
D0 = !Q0;
Z = (X & Q1) # (!X & !Q1);

end bod2excess3;
Xilinx FPGAs - 50
    
```

Explicit equations for partitioned output functions

Specifying PALs with ABEL

```

PI2H6 PAL
module bod2excess3
title 'BCD to Excess 3 Code Converter State Machine'
ul device 'pi2h6';

*Input Pins
X, Q2, Q1, Q0 pin 1, 2, 3, 4;

*Output Pins
D2, D1, D0, Z pin 17, 18, 16, 15;

INSTATE = {Q2, Q1, Q0}; OUTSTATE = {D2, D1, D0};
S0in = [0, 0, 0]; S0out = [0, 0, 0];
S1in = [0, 0, 1]; S1out = [0, 0, 1];
S2in = [0, 1, 1]; S2out = [0, 1, 1];
S3in = [1, 1, 0]; S3out = [1, 1, 0];
S4in = [1, 0, 0]; S4out = [1, 0, 0];
S5in = [1, 1, 1]; S5out = [1, 1, 1];
S6in = [1, 0, 1]; S6out = [1, 0, 1];

equations
D2 = (!Q2 & Q0) # (Q2 & !Q0);
D1 = (!X & !Q2 & !Q1 & Q0) # (X & !Q2 & !Q0) #
    (!X & Q2 & !Q0) # (Q1 & !Q0);
D0 = !Q0;
Z = (X & Q1) # (!X & !Q1);

end bod2excess3;
Xilinx FPGAs - 51
    
```

Simpler equations

Specifying PALs with ABEL

```

PI6R4 PAL
module bod2excess3
title 'BCD to Excess 3 Code Converter'
ul device 'pi6r4';

*Input Pins
Clk, Reset, X, IOE pin 1, 2, 3, 11;

*Output Pins
D2, D1, D0, Z pin 14, 15, 16, 13;

SREG = {D2, D1, D0};
S0 = [0, 0, 0];
S1 = [0, 0, 1];
S2 = [0, 1, 1];
S3 = [1, 1, 0];
S4 = [1, 0, 0];
S5 = [1, 1, 1];
S6 = [1, 0, 1];

state diagram SREG
state S0: if Reset then S0
    else if X then S2 with Z = 0
    else S1 with Z = 1
state S1: if Reset then S0
    else if X then S4 with Z = 0
    else S3 with Z = 1
state S2: if Reset then S0
    else if X then S4 with Z = 1
    else S4 with Z = 0
state S3: if Reset then S0
    else if X then S5 with Z = 1
    else S5 with Z = 0
state S4: if Reset then S0
    else if X then S6 with Z = 0
    else S5 with Z = 1
state S5: if Reset then S0
    else if X then S0 with Z = 1
    else S0 with Z = 0
state S6: if Reset then S0
    else if !X then S0 with Z = 1
    else S0 with Z = 0


end bod2excess3;
Xilinx FPGAs - 52
    
```

FSM Design with Counters

Synchronous Counters: CLR, LD, CNT

Four kinds of transitions for each state:

 
- (1) to State 0 (CLR)
- (2) to next state in sequence (CNT)
- (3) to arbitrary next state (LD)
- (4) loop in current state



Careful state assignment is needed to reflect basic sequencing of the counter

FSM Design with Counters

Excess 3 Converter Revisited

 

Note the sequential nature of the state assignments

FSM Design with Counters

Excess 3 Converter

Inputs/Current State			Next State			Outputs							
X	Q2	Q1	Q0	Q2	Q1	Q0	Z	CLR	LD	EN	C	B	A
0	0	0	0	0	0	1	1	1	1	1	X	X	X
0	0	0	1	0	1	0	1	1	1	1	X	X	X
0	0	1	0	0	1	1	0	1	1	1	X	X	X
0	0	1	1	0	0	0	0	X	X	X	X	X	X
0	1	0	0	1	0	1	1	1	1	1	X	X	X
0	1	0	1	0	1	1	0	1	0	X	0	1	0
0	1	1	0	0	0	0	1	0	X	X	X	X	X
0	1	1	1	X	X	X	X	X	X	X	X	X	X
1	0	0	0	1	0	0	1	0	X	1	0	0	0
1	0	0	1	0	1	0	1	0	X	1	0	1	0
1	0	1	0	0	1	1	1	1	1	1	X	X	X
1	0	1	1	0	0	1	0	X	X	X	X	X	X
1	1	0	0	1	0	1	1	1	1	1	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

CLR signal dominates LD which dominates Count

Implementing FSMs with Counters

```


.i 5          Espresso Input File .i 5
.o 7          .o 7
.ilb res x q2 q1 q0 .ilb res x q2 q1 q0
.ob z clr ld en c b a .ob z clr ld en c b a
.p 17        .p 10
1---- -0---- 0-001 0101101
00000 1111--- -0-01 1000000
00001 1111--- -11-0 1000000
00010 0111--- 0-0-0 0101100
00011 00----- -000- 1010000
00100 0111--- -0--0 0010000
00101 110-011 0-10- 0101011
00110 10----- --11- 1000000
00111 ----- -11-- 0010000
01000 010-100 -1-1- 1010000
01001 010-101 .e
01010 1111---
01011 10-----
01100 1111---
01101 0111---
01110 -----
01111 -----
.e
    
```

Excess 3 Converter

Espresso Output File

Xilinx FPGAs - 56

FSM Implementation with Counters

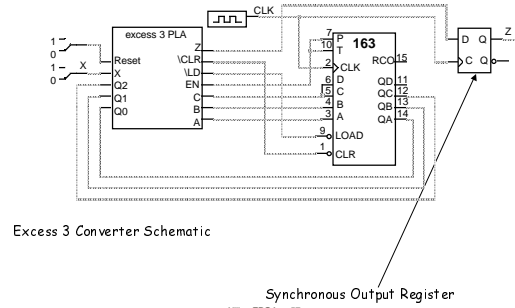

Implementation Strategies

Xilinx LCA Architecture

Implementing the BCD to Excess 3 FSM

$$Q2+ = \overline{Q2} \cdot Q0 + Q2 \cdot \overline{Q0}$$

$$Q1+ = \overline{X} \cdot \overline{Q2} \cdot \overline{Q1} \cdot Q0 + X \cdot \overline{Q2} \cdot \overline{Q0} + \overline{X} \cdot Q2 \cdot \overline{Q0} + Q1 \cdot \overline{Q0}$$

$$Q0+ = \overline{Q0}$$

$$Z = Z \cdot Q1 + \overline{X} \cdot \overline{Q1}$$

No function more complex than 4 variables
4 FFs implies 2 CLB's

Synchronous Mealy Machine


Global Reset to be used

Place Q2+, Q0+ in once CLB

Q1, Z in second CLB
maximize use of direct & general purpose interconnections

Xilinx FPGAs - 58

Implementing the BCD to Excess 3 FSM

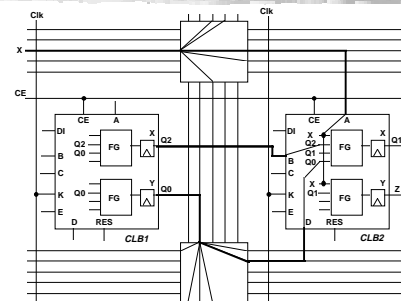

Design Case Study

Traffic Light Controller

Decomposition into primitive subsystems


- Controller FSM
 - next state/output functions
 - state register
- Short time/long time interval counter
- Car Sensor
- Output Decoders and Traffic Lights

Xilinx FPGAs - 60


Design Case Study

Traffic Light Controller

Block Diagram

 

Design Case Study

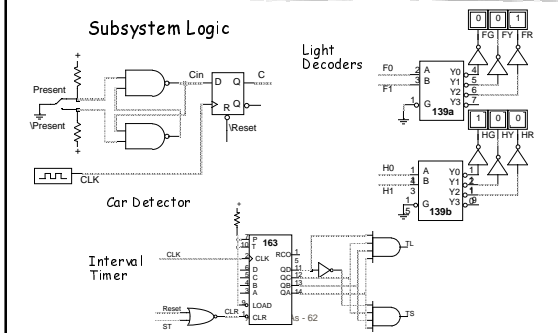

Design Case Study

State Assignment: $HG = 00, HY = 10, FG = 01, FY = 11$

$$P1 = C TL \bar{Q1} + \bar{T}S Q1 Q0 + \bar{C} Q1 Q0 + \bar{T}S Q1 Q0$$

$$P0 = TS Q1 \bar{Q0} + Q1 Q0 + \bar{T}S Q1 Q0$$

$$ST = C TL \bar{Q1} + \bar{C} Q1 Q0 + TS Q1 \bar{Q0} + TS Q1 Q0$$

$$HL[1] = TS Q1 Q0 + \bar{Q1} Q0 + \bar{T}S Q1 Q0$$

$$HL[0] = \bar{T}S Q1 \bar{Q0} + TS Q1 \bar{Q0}$$

Next State Logic

$$FL[1] = \bar{Q0}$$

$$FL[0] = TS Q1 Q0 + \bar{T}S Q1 Q0$$

PAL/PLA Implementation:

5 inputs, 7 outputs, 8 product terms


PAL 22V10 -- 11 inputs, 10 prog. I/Os, 8 to 14 prod terms per OR

ROM Implementation:

32 word by 8-bit ROM (256 bits)

Reset may double ROM size

Design Case Study

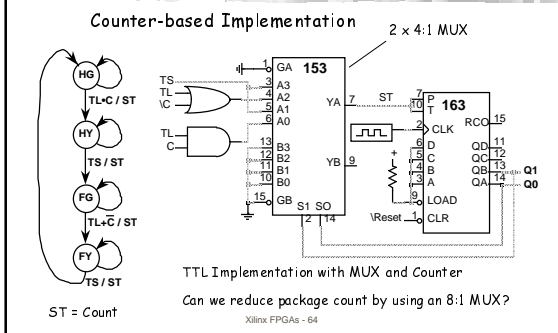


Design Case Study

Counter-based Implementation

Dispense with direct output functions for the traffic lights

 Why not simply decode from the current state?



Design Case Study

LCA-Based Implementation

Discrete Gate Method:

None of the functions exceed 5 variables

P1, ST are 5 variable (1 CLB each)

P0, HL1, HL0, FLO are 3 variable (1/2 CLB each)


FL1 is 1 variable (1/2 CLB)

4 1/2 CLBs total

Design Case Study

LCA-Based Implementation

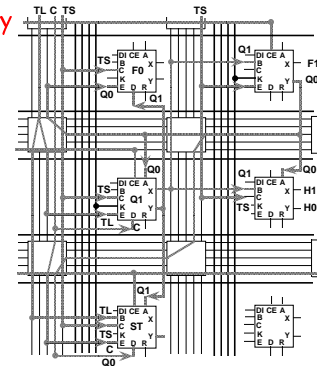Placement of functions selected to maximize the use of direct connections



Design Case Study

LCA-Based Implementation

Counter/Multiplexer Method:

4:1 MUX, 2 Bit Upcounter

MUX: six variables (4 data, 2 control)
but this is the kind of 6 variable function that can be implemented in 1 CLB!

2nd CLB to implement $TL \cdot C$ and $TL + C'$

But note that ST/Cnt is really a function of TL, C, TS, Q1, Q0
1 CLB to implement this function of 5 variables!

2 Bit Counter: 2 functions of 3 variables (2 bit state + count)
Also implemented in one CLB

Traffic light decoders: functions of 2 variables (Q1, Q0)
2 per CLB = 3 CLB for the six lights

Total count = 5 CLBs