

Hardware Description Languages

- Describe hardware at varying levels of abstraction
- Structural description
 - Textual replacement for schematic
 - Hierarchical composition of modules from primitives
- Behavioral/functional description
 - Describe what module does, not how
 - Synthesis generates circuit for module
- Simulation semantics

CS 150 - Fall 2000 - Hardware Description Languages - 1

HDLs

- Abel (circa 1983) - developed by Data-I/O
 - Targeted to programmable logic devices
 - Not good for much more than state machines
- ISP (circa 1977) - research project at CMU
 - Simulation, but no synthesis
- Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
 - Similar to Pascal and C
 - Delays is only interaction with simulator
 - Fairly efficient and easy to write
 - IEEE standard
- VHDL (circa 1987) - DoD sponsored standard
 - Similar to Ada (emphasis on re-use and maintainability)
 - Simulation semantics visible
 - Very general but verbose
 - IEEE standard

Verilog

- Supports structural and behavioral descriptions
- Structural
 - Explicit structure of the circuit
 - E.g., each logic gate instantiated and connected to others
- Behavioral
 - Program describes input/output behavior of circuit
 - Many structural implementations could have same behavior
 - E.g., different implementation of one Boolean function
- We'll only be using behavioral Verilog in DesignWorks
 - Rely on schematic when we want structural descriptions

CS 150 - Fall 2000 - Hardware Description Languages - 3

Structural Model

```
module xor_gate (out, a, b);
  input  a, b;
  output out;
  wire  abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);

endmodule
```

CS 150 - Fall 2000 - Hardware Description Languages - 4

Simple behavioral model

- Continuous assignment

```
module xor_gate (out, a, b);
  input  a, b;
  output out;
  reg    out;

  assign #6 out = a ^ b;
endmodule
```

simulation register -
keeps track of
value of signal

delay from input change
to output change

CS 150 - Fall 2000 - Hardware Description Languages - 5

Simple Behavioral Model

- always block

```
module xor_gate (out, a, b);
  input  a, b;
  output out;
  reg    out;

  always @(a or b) begin
    #6 out = a ^ b;
  end
endmodule
```

specifies when block is executed
I.e., triggered by which signals

CS 150 - Fall 2000 - Hardware Description Languages - 6

Driving a Simulation

```
module stimulus (x, y);
  output      x, y;
  reg [1:0]   cnt;

  initial begin
    cnt = 0;
    repeat (4) begin
      #10 cnt = cnt + 1;
      $display ("% time=%d, x=%b, y=%b, cnt=%b",
        $time, x, y, cnt); end
      #10 $finish;
    end

    assign x = cnt[1];
    assign y = cnt[0];
  endmodule
```

2-bit vector

initial block executed only once at start of simulation


print to a console

directive to stop simulation

CS 150 - Fall 2000 - Hardware Description Languages - 7

Complete Simulation

- Instantiate stimulus component and device to test in a schematic

 

CS 150 - Fall 2000 - Hardware Description Languages - 8

Comparator Example

```
module Compare1 (A, B, Equal, Alarger, Blarger);
  input  A, B;
  output Equal, Alarger, Blarger;

  assign #5 Equal = (A & B) | (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

CS 150 - Fall 2000 - Hardware Description Languages - 9

More Complex Behavioral Model

```
module life (n0, n1, n2, n3, n4, n5, n6, n7, self, out);
  input  n0, n1, n2, n3, n4, n5, n6, n7, self;
  output out;
  reg    out;
  reg [7:0] neighbors;
  reg [3:0] count;
  reg [3:0] i;

  assign neighbors = {n7, n6, n5, n4, n3, n2, n1, n0};

  always @(neighbors or self) begin
    count = 0;
    for (i = 0; i < 8; i = i+1) count = count + neighbors[i];
    out = (count == 3);
    out = out | ((self == 1) & (count == 2));
  end
endmodule
```

CS 150 - Fall 2000 - Hardware Description Languages - 10

Hardware Description Languages vs. Programming Languages

- Program Structure
 - Instantiation of multiple components of the same type
 - Specify inter connections between modules via schematic
 - Hierarchy of modules
- Assignment
 - Continuous assignment (logic always computes)
 - Propagation delay (computation takes time)
 - Timing of signals is important (when does computation have its effect)
- Data structures
 - Size explicitly spelled out - no dynamic structures
 - No pointers
- Parallelism
 - Hardware is naturally parallel (must support multiple threads)
 - Assignments can occur in parallel (not just sequentially)

CS 150 - Fall 2000 - Hardware Description Languages - 11

Hardware Description Languages and Combinational Logic

- Modules: specification of inputs, outputs, bidirectional, and internal signals
- Continuous assignment: a gate's output is a function of its inputs at all times (doesn't need to wait to be "called")
- Propagation delay: concept of time and delay in input affecting gate output
- Composition: connecting modules together with wires
- Hierarchy: modules encapsulate functional blocks
- Specification of don't care conditions (accomplished by setting output to "x")

CS 150 - Fall 2000 - Hardware Description Languages - 12

Hardware Description Languages and Sequential Logic

- Flip-Flops
 - Representation of clocks - timing of state changes
 - Asynchronous vs. synchronous
- FSMs
 - Structural view (FFs separate from combinational logic)
 - Behavioral view (synthesis of sequencers)
- Data-paths = ALUs + registers
 - Use of arithmetic/logical operators
 - Control of storage elements
- Parallelism
 - Multiple state machines running in parallel
- Sequential don't cares

CS 150 - Fall 2000 - Hardware Description Languages - 13

Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock edge

```

module dff (clk, d, q);
    input  clk, d;
    output q;
    reg   q;

    always @(posedge clk)
        q = d;
endmodule
    
```

CS 150 - Fall 2000 - Hardware Description Languages - 14

More Flip-flops

- Synchronous/asynchronous reset/set
 - Single thread that waits for the clock
 - Three parallel threads - only one of which waits for the clock

```

module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge clk)
        if (reset) q = 1'b0;
        else if (set) q = 1'b1;
        else q = d;
endmodule

module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge reset)
        q = 1'b0;
    always @(posedge set)
        q = 1'b1;
    always @(posedge clk)
        q = d;
endmodule
    
```

CS 150 - Fall 2000 - Hardware Description Languages - 15

Structural View of an FSM

- Traffic light controller: two always blocks - flip-flops separate from logic

```

module FSM (HL, FL, ST, clk, C, TS, TL);
    output [2:0] HL, FL;
    output ST;
    input clk;
    input C, TS, TL;
    reg [1:0] present_state;
    reg [1:0] next_state;

    initial begin HL = 3'b001; FL = 3'b100; present_state = 2'b00; end

    always @(posedge clk) // registers
        present_state = next_state;

    always @(present_state or C or TS or TL)
        // compute next-state and output logic whenever state or inputs change
        // put equations here for next_state[1:0], HL[2:0], FL[2:0], and ST
        // as functions of C, TS, TL, and present_state[1:0]
endmodule
    
```

CS 150 - Fall 2000 - Hardware Description Languages - 16

Behavioral View of an FSM

- Specification of inputs, outputs, and state elements

```

module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, clk);
    output HR;
    output HY;
    output HG;
    output FR;
    output FY;
    output FG;
    output ST;
    input TS;
    input TL;
    input C;
    input reset;
    input clk;

    reg [6:1] state;
    reg ST;

    `define highwaygreen 6'b001100
    `define highwayyellow 6'b010100
    `define farmroadgreen 6'b100001
    `define farmroadyellow 6'b100010

    assign HR = state[6];
    assign HY = state[5];
    assign HG = state[4];
    assign FR = state[3];
    assign FY = state[2];
    assign FG = state[1];
endmodule
    
```

specify state bits and codes for each state as well as connections to outputs

CS 150 - Fall 2000 - Hardware Description Languages - 17

Behavioral View of an FSM (cont'd)

```

initial begin state = `highwaygreen; ST = 0; end

always @(posedge clk)
    begin
        if (reset)
            begin state = `highwaygreen; ST = 1; end
        else
            begin
                ST = 0;
                case (state)
                    `highwaygreen:
                        if (TL & C) begin state = `highwayyellow; ST = 1; end
                    `highwayyellow:
                        if (TS) begin state = `farmroadgreen; ST = 1; end
                    `farmroadgreen:
                        if (TL | !C) begin state = `farmroadyellow; ST = 1; end
                    `farmroadyellow:
                        if (TS) begin state = `highwaygreen; ST = 1; end
                endcase
            end
    end
endmodule
    
```

case statement triggered by clock edge

CS 150 - Fall 2000 - Hardware Description Languages - 18

Timer for Traffic Light Controller

Another FSM

```

module Timer(TS, TL, ST, Clk);
  output TS;
  output TL;
  input  ST;
  input  Clk;
  integer value;

  assign TS = (value >= 4); // 5 cycles after reset
  assign TL = (value >= 14); // 15 cycles after reset

  always @(posedge ST) value = 0; // async reset

  always @(posedge Clk) value = value + 1;

endmodule

```

CS 150 - Fall 2000 - Hardware Description Languages - 19

Complete Traffic Light Controller

Tying it all together (FSM + timer)

```

module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);
  output HR, HY, HG, FR, FY, FG;
  input  reset, C, Clk;

  Timer part1(TS, TL, ST, Clk);
  FSM part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
endmodule

```

CS 150 - Fall 2000 - Hardware Description Languages - 20

Verilog FSM - Reduce 1s example

Moore machine


```

`define zero 0
`define one1 1
`define twos 2
// state assignment

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg [2:1] state; // state variables
  reg [2:1] next_state;

  always @(posedge clk)
    if (reset) state = `zero;
    else state = next_state;

```

 

CS 150 - Fall 2000 - Hardware Description Languages - 21

Moore Verilog FSM (cont'd)

```

always @(in or state)
case (state)
`zero:
  // last input was a zero
  begin
    if (in) next_state = `one1;
    else next_state = `zero;
  end
`one1:
  // we've seen one 1
  begin
    if (in) next_state = `twos;
    else next_state = `zero;
  end
`twos:
  // we've seen at least 2 ones
  begin
    if (in) next_state = `twos;
    else next_state = `zero;
  end
endcase

always @(state)
case (state)
`zero: out = 0;
`one1: out = 0;
`twos: out = 1;
endcase
endmodule

```

crucial to include all signals that are input to state and output equations

note that output only depends on state

CS 150 - Fall 2000 - Hardware Description Languages - 22

Mealy Verilog FSM


```

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  `register state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = `zero;
    else state = next_state;

  always @(in or state)
    case (state)
    `zero: // last input was a zero
      begin
        out = 0;
        if (in) next_state = `one;
        else next_state = `zero;
      end
    `one: // we've seen one 1
      if (in) begin
        next_state = `one; out = 1;
      end else begin
        next_state = `zero; out = 0;
      end
    endcase
endmodule

```

 

CS 150 - Fall 2000 - Hardware Description Languages - 23

Synchronous Mealy Machine

```

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = `zero;
    else
      case (state)
      `zero: // last input was a zero
        begin
          out = 0;
          if (in) state = `one;
          else state = `zero;
        end
      `one: // we've seen one 1
        if (in) begin
          state = `one; out = 1;
        end else begin
          state = `zero; out = 0;
        end
      endcase
endmodule

```

CS 150 - Fall 2000 - Hardware Description Languages - 24