

# CS 150 Lab Lecture 2

Schematic Entry & Simulation, Part 010<sub>2</sub>  
Finite State Machines  
Laura Todd, 1-26-01



I hope not...

## Prelab


- ⌘ Get a partner in **YOUR** lab section
- ⌘ Complete the **IN1** and **IN2** blocks
- ⌘ Write a script file to test your design

## Overview

- ⌘ Objectives
- ⌘ Prelab
- ⌘ Brief Description
- ⌘ To-do
- ⌘ Hints, tips, and tricks
 
## Brief Description - "High Level Spec"


- ⌘ The high-level spec is a description of the problem in "plain English"
- ☑ This is a very general description of the system you're trying to build, in our case, a combination lock.



## Objectives

- ⌘ Practice using Xilinx software
- ⌘ Enter a graphical gate schematic from logic equations
- ⌘ Simulate the schematic
- ⌘ Practice high-level description-to-gates design flow
- ⌘ Work in a group


## Brief Description - Block Diagram

 

System-level view: these are the building blocks we need
 
## Brief Description - the Clock

- ⌘ The "clock" keeps the FSM synchronized.




- ⌘ When the clock goes "BONG!" the FSM will change state
- ⌘ The time from one rising edge to another is called the "clock cycle" time.

## Brief Description - MyCLB

- ⌘ CLB = Combinational Logic Block => AND, OR, INV...
- ⌘ The MyCLB block acts as the controller for our lock, it's the brains
- ⌘ Truth table and logic equations are in the printout
  - ☑ Implement this block during lab time.
- ⌘ KISS-Keep It Simple & Stupid
  - ☑ Use the "multi-level" equations, they're much easier to debug

## Brief Description - FSM

 


Logical view: the finite state machine
 
## Brief Description - MyDFF

- ⌘ What the heck are D flip-flops????

- ☑ D flip-flops are memory elements
- ☑ Put what you want to save on D
- ☑ When the clock has a rising edge the DFF will look at the value on D and move it to Q
- ☑ Now until the next rising edge on the clock, Q will remain the same, giving us a saved output



- ⌘ This is the simple version: lots more later in class!
- ⌘ Lab uses the "FDR" model.
  - ☑ R stands for "Reset to Zero"

## Brief Description - the IN\* blocks

- ⌘ The IN1 and IN2 blocks compare the code the user inputs to the "secret" code that will open the lock.
- ⌘ Choose your own combination. Write it down.
- ⌘ The two combinations must be different:
  - ☑ Good: 01 11
  - ☑ Bad: 10 10
- ⌘ IN1 and IN2 are very simple blocks. Just some AND gates and inverters.


## ToDo's - What you need for credit

- ⌘ Enter the IN1, IN2, MyCLB schematics
- ⌘ Make a test script for your CLB. Run it. Make sure it's correct.
- ⌘ Make the MyDFF block.
- ⌘ Wire up all the individual pieces you just made.
- ⌘ Write a script to simulate scenarios on the full lock
  - ☑ Successful/Unsuccessful entries of the combination
  - ☑ Use of the RESET and ENTER buttons
  - ☑ Do all the paths on the state diagram work correctly?
  - ☑ Create a log file to show your TA

## Hints, Tips, and Tricks

- ⌘ Buses are your friends.
  - ☒ CS150 buses: collections of wires that have a similar purpose
  - ☒ Usually same wire name + a number, as in DATA7, DATA6, ... DATA1, DATA0
  - ☒ Simplify, simplify, simplify...
- ⌘ Scripts are your friends.
  - ☒ Note: the pipe character "|" will comment out a line.
- ⌘ Don't print things!
- ⌘ Xilinx software is buggy. When in doubt, restart it.
- ⌘ Don't draw spaghetti wires =>
  - ☒ Too easy to mislabel wires
  - ☒ Harder to debug

## Hints, Tips, and Tricks

 

Spaghetti vs. Not Spaghetti

The End... for now.

DON'T  
PANIC

Ya ain't seen nuthin' yet...