
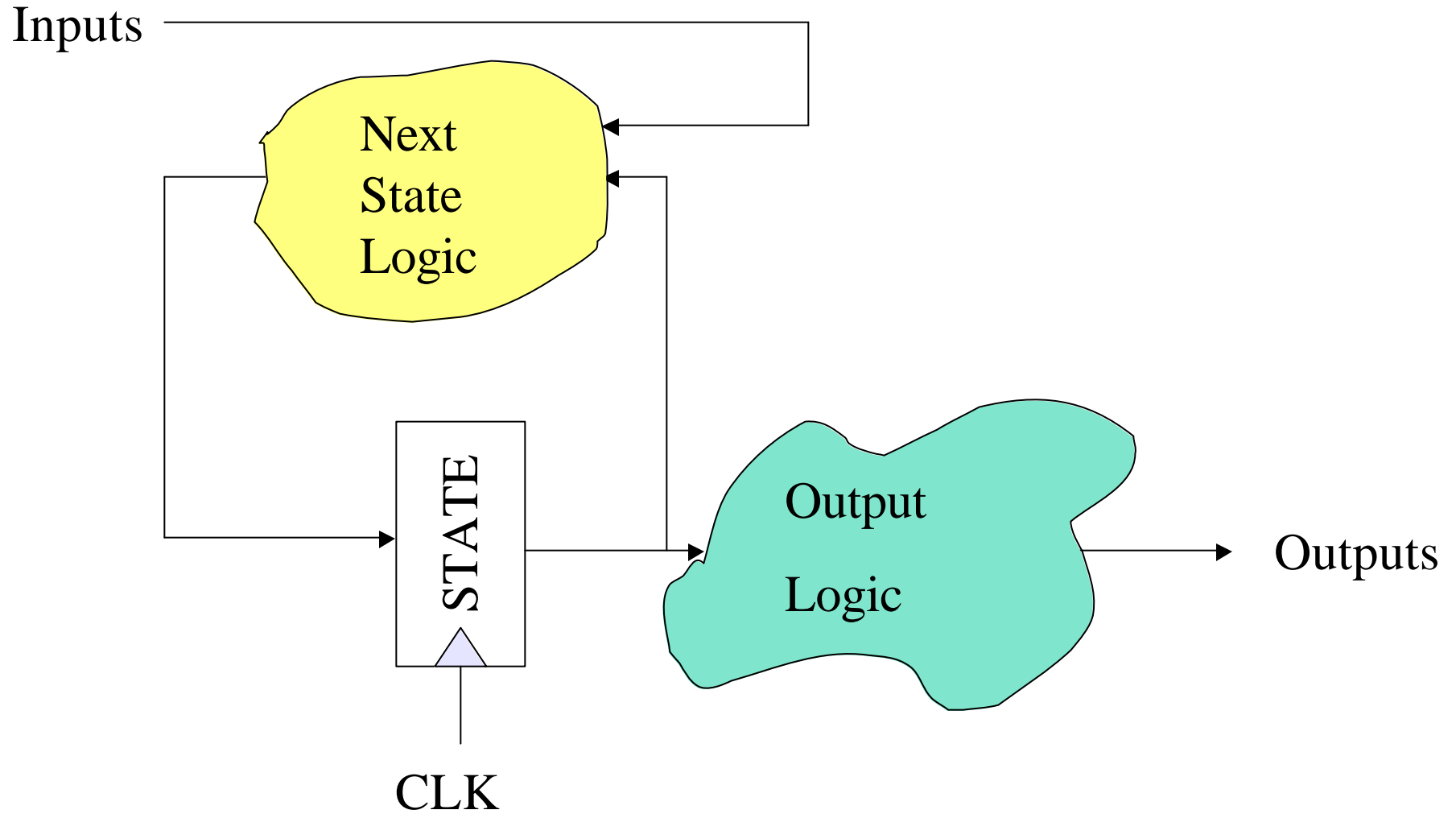


FSMs in Verilog and other random things

9/27/02

FSM structure

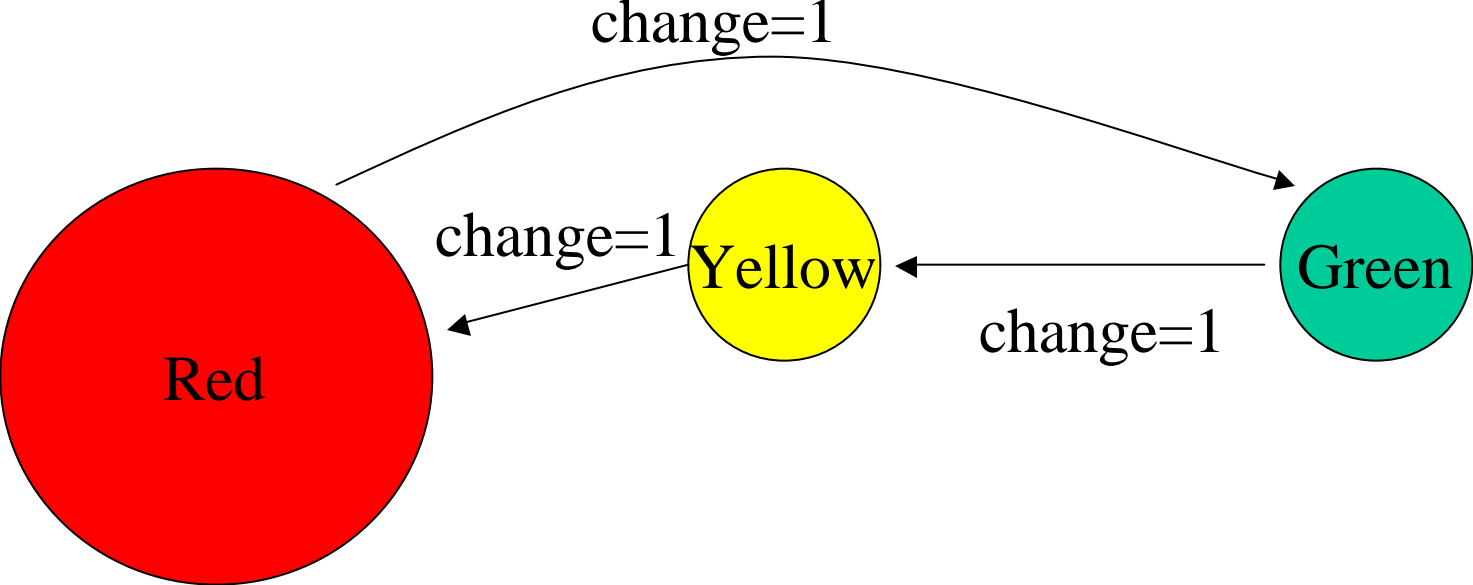





```
module trafficLightFSM(clk,reset,change,red,yellow,green);
    input clk,reset,change;
    output red,yellow,green;
    reg red,yellow,green;
    reg [1:0] curState,nextState;
    parameter showRed = 2'b00, showYellow = 2'b01;
    parameter showGreen = 2'b10;

    // state register
    always @(posedge clk)
        if (reset==1'b1) curState <= 2'b0;
        else curState <= nextState;
```

```
// next state logic
// dependent only on the current state and input
always @(curState or change)
begin
    nextState = showRed; // default state
    case (curState)
        showRed: if (change) nextState=showGreen;
        showYellow: if (change) nextState=showRed;
                    else nextState=showYellow;
        showGreen: if (change) nextState=showYellow;
                    else nextState=showGreen;
    endcase
end
```


```
// Output Logic: dependent ONLY on state
always @(curState) begin
    // *ALWAYS* put default output values
    red=1'b0; green=1'b0; yellow=1'b0;
    case (curState)
        showRed: red=1'b1;
        showYellow: yellow=1'b1;
        showGreen: green=1'b1;
    endcase
end
endmodule
```

Edge Detector

  

Non-blocking
 
```
always @(posedge clk)
begin
    E <= ~A;
    C <= ~E;
end
```



Blocking

```
always @(posedge clk)
begin
    E = ~A;
    C = ~E;
end
```

