

1. Design a 4-bit right-shifter using only 2:1 multiplexers. The shifter accepts a 4-bit input, A, a 2 bit shift amount, shamt_{1:0}, and a single bit indicating if this is a logical shift or an arithmetic shift, L.

