

EECS150 - Digital Design

Lecture 8 – High Level Design (Part 2)

Multipliers (part 1): Design Example

Sep. 24, 2013

Prof. Ronald Fearing

Electrical Engineering and Computer
Sciences

University of California, Berkeley

(slides courtesy of Prof. John Wawrzynek)

<http://www-inst.eecs.berkeley.edu/~cs150>


Fall 2013

EECS150 - Lec08-mult1

Page 1

Outline


- Recap: high level design intro

 

- List processor, conclusion and optimization
- Multiplier example

List Processor Architecture #1

Direct implementation of RTL description:

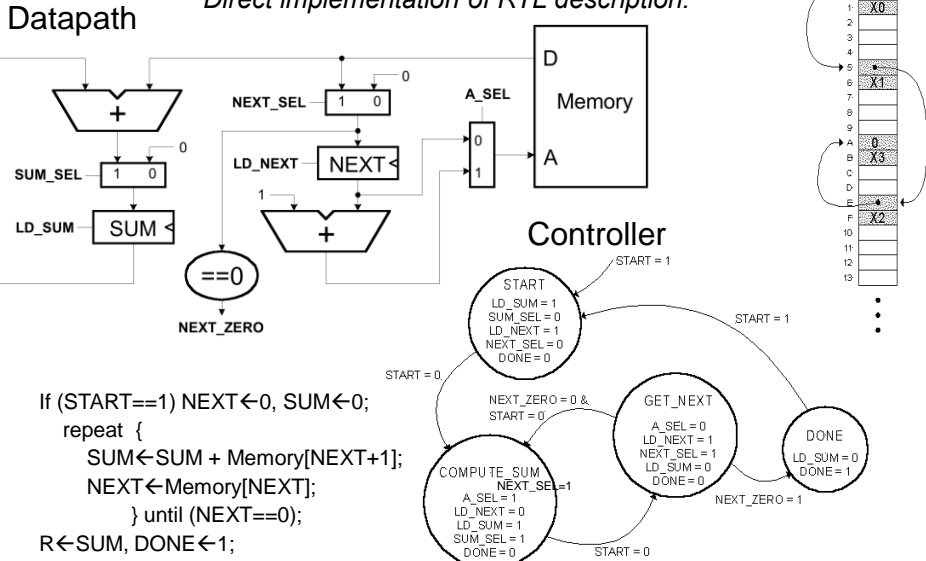


Fall 2013


EECS150 - Lec07-hld1

Page 3

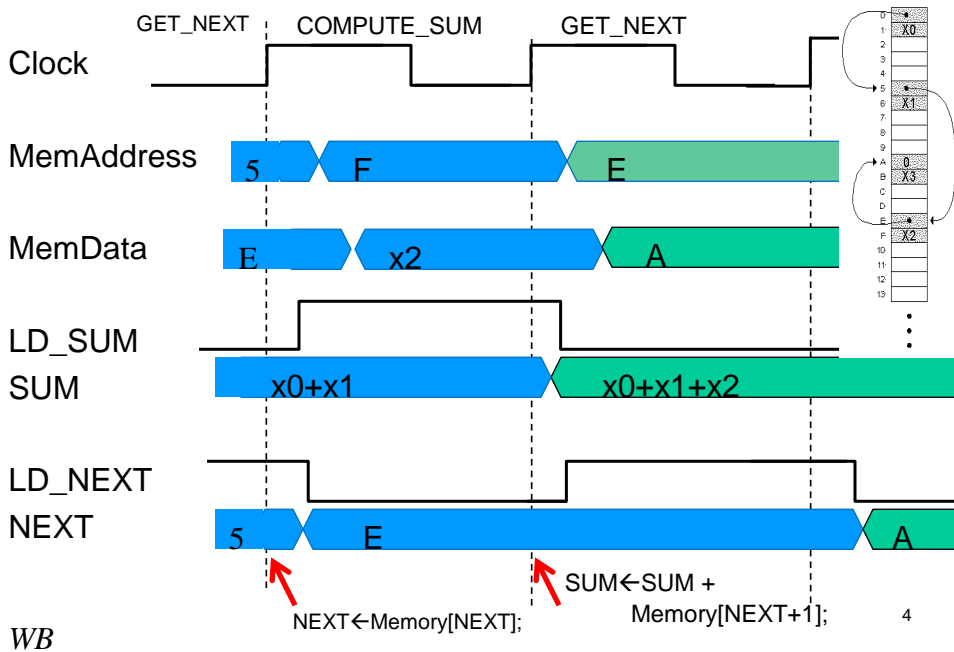operational timing diagram for list processor



4. Analysis of Performance

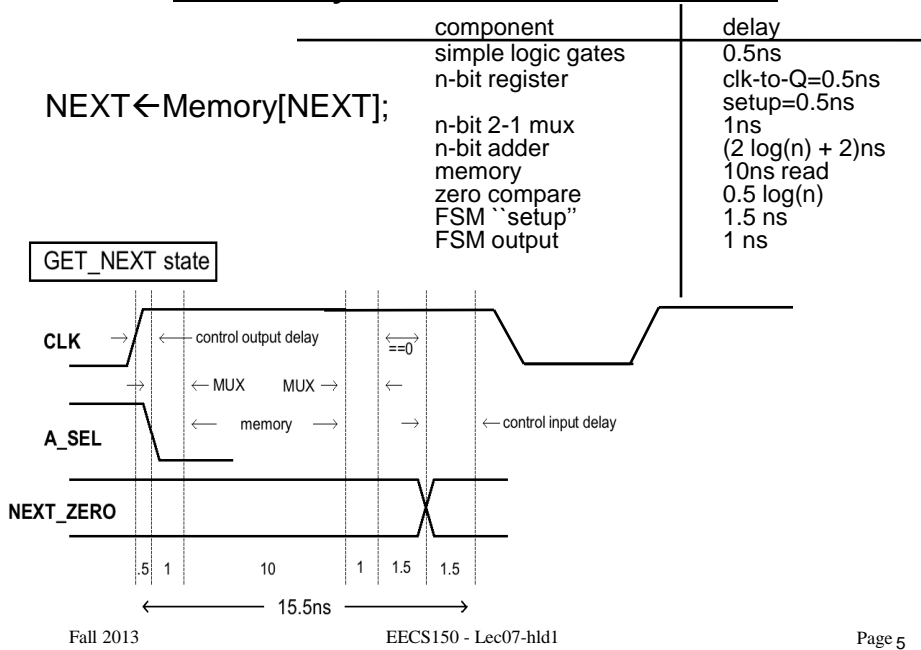


4. Analysis of Performance

SUM ← SUM + Memory[NEXT+1];

component	delay
simple logic gates	0.5ns
n-bit register	clk-to-Q=0.5ns setup=0.5ns
n-bit 2-1 mux	1ns
n-bit adder	(2 log(n) + 2)ns
memory	10ns read
zero compare	0.5 log(n)

?

4. Analysis of Performance

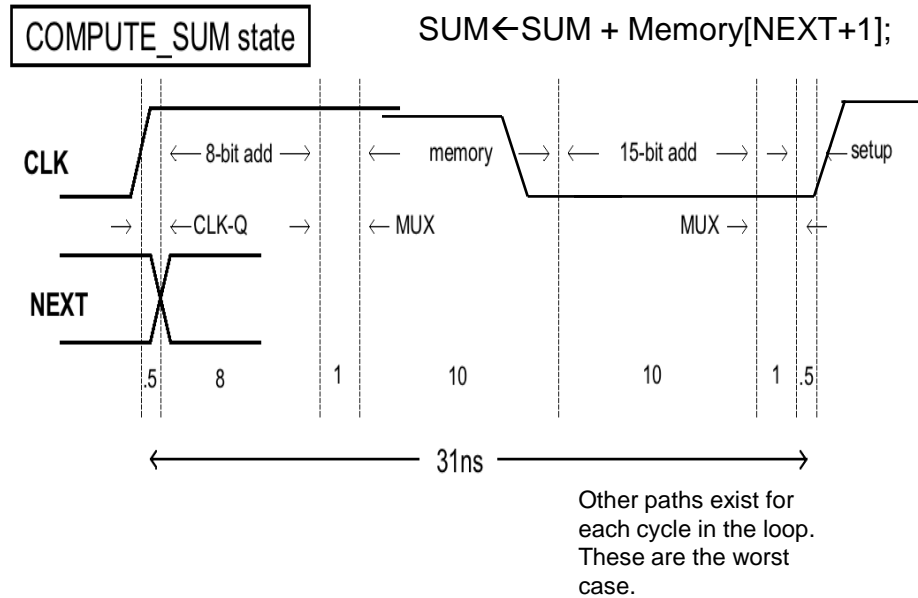

Fall 2013

EECS150 - Lec07-hld1

Page 7

4. Analysis of Performance

- Detailed timing:
 - clock period (T) = max (clock period for each state)
 - $T > 31\text{ns}$, $F < 32\text{ MHz}$
- Observation:
 - COMPUTE_SUM state does most of the work. Most of the components are inactive in GET_NEXT state.
 - GET_NEXT does: Memory access + ...
 - COMPUTE_SUM does: 8-bit add, memory access, 15-bit add + ...
- Conclusion:
 - Move one of the adds to GET_NEXT.

Fall 2013

EECS150 - Lec07-hld1

Page 8


5. Optimization

- Add new register named *NUMA*, for address of number to add.
- Update code to reflect our change (note still 2 cycles per iteration):

```


If (START==1) NEXT←0, SUM←0, NUMA←1;
repeat {
    SUM←SUM + Memory[NUMA];
    NUMA←Memory[NEXT] + 1,
    NEXT←Memory[NEXT];
} until (NEXT==0);
R←SUM, DONE←1;
    
```

} one cycle

 

5. Optimization

- Architecture #2:

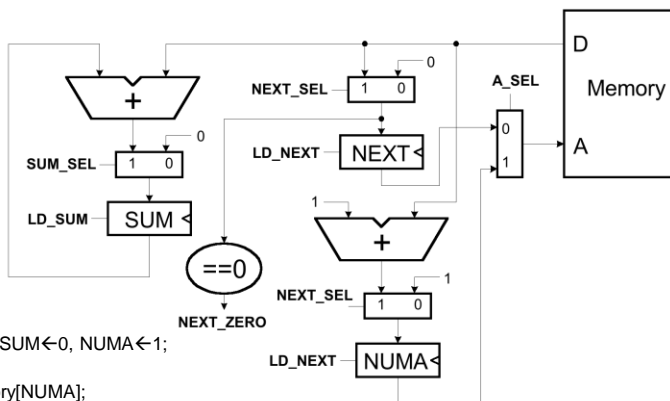


```

If (START==1) NEXT←0, SUM←0, NUMA←1;
repeat {
    SUM←SUM + Memory[SUM];
    NUMA←Memory[NEXT] + 1, NEXT←Memory[NEXT];
} until (NEXT==0);
R←SUM, DONE←1;
    
```

- Incremental cost: addition of another register and mux.

5. Optimization, Architecture #2

COMPUTE_SUM state

 


- New timing:
Clock Period (T) = max (clock period for each state)

$T > 23\text{ns}, F < 43\text{Mhz}$

- Is this worth the extra cost?
- Can we lower the cost?

GET_NEXT state

 


- Notice that the circuit now only performs one add operation per cycle, but have two adders. Why not share 1 adder for both cycles?

Fall 2013

EECS150 - Lec07-hld1

Page11

5. Optimization, Architecture #3

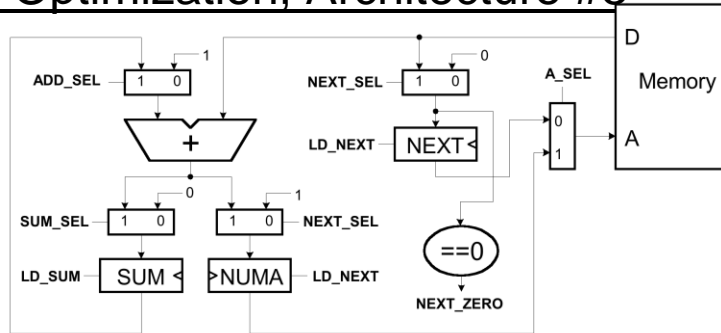

- Incremental cost:
 - Addition of another mux and control (ADD_SEL). Removal of an 8-bit adder.
- Performance:
 - No change.
- Change is definitely worth it.

[Except wiring is more limit than computation...]

Fall 2013

EECS150 - Lec07-hld1

Page12

Resource Utilization Charts

- One way to visualize these (and other possible) optimizations is through the use of a *resource utilization charts*.
- These are used in high-level design to help schedule operations on shared resources.
- Resources are listed on the y-axis. Time (in cycles) on the x-axis.
- CPU Example:

memory	fetch A1		fetch A2				
bus		fetch A1		fetch A2			
register-file		read B1		read B2			
ALU			A1+B1		A2+B2		
<i>cycle</i>	1	2	3	4	5	6	7

- Our list processor has two shared resources: memory and adder

Fall 2013

EECS150 - Lec07-hld1

Page13

List Example Resource Scheduling

- Unoptimized solution: 1. $SUM \leftarrow SUM + Memory[NEXT+1]$; 2. $NEXT \leftarrow Memory[NEXT]$;

memory	fetch x	fetch next	fetch x	fetch next
adder1	next+1		next+1	
adder2	sum		sum	
	1	2	1	2

- Optimized solution: 1. $SUM \leftarrow SUM + Memory[NUMA]$;
2. $NEXT \leftarrow Memory[NEXT]$, $NUMA \leftarrow Memory[NEXT]+1$;

memory	fetch x	fetch next	fetch x	fetch next
adder	sum	numa	sum	numa

- How about the other combination: [add x register](#)

memory	fetch x	fetch next	fetch x	fetch next
adder	numa	sum	numa	sum

1. $X \leftarrow Memory[NUMA]$, $NUMA \leftarrow NEXT+1$;
2. $NEXT \leftarrow Memory[NEXT]$, $SUM \leftarrow SUM+X$;

- Does this work? If so, a very short clock period. Each cycle could have *independent* fetch and add. $T = \max(T_{mem}, T_{add})$ instead of $T_{mem} + T_{add}$.

Fall 2013

EECS150 - Lec07-hld1

Page 14

List Example Resource Scheduling

- Schedule one loop iteration followed by the next:

Memory	next ₁		x ₁		next ₂		x ₂		
adder		numa ₁		sum ₁		numa ₂		sum ₂	

- How can we overlap iterations? next₂ depends on next₁.
 - "slide" second iteration into first (4 cycles per result):

Memory	next ₁		x ₁	next ₂		x ₂			
adder		numa ₁		sum ₁	numa ₂		sum ₂		

-or further:

Memory	next ₁	next ₂	x ₁	x ₂	next ₃	next ₄	x ₃	x ₄	
adder		numa ₁	numa ₂	sum ₁	sum ₂	numa ₃	numa ₄	sum ₃	sum ₄

The repeating pattern is 4 cycles. Not exactly the pattern what we were looking for. But does it work correctly?

List Example Resource Scheduling

- In this case, first spread out, then pack.

Memory	next ₁			x ₁		
adder		numa ₁			sum ₁	


Memory	next ₁		next ₂	x ₁	next ₃	x ₂	next ₄	x ₃	
adder		numa ₁		numa ₂	sum ₁	numa ₃	sum ₂	numa ₄	sum ₃

- X ← Memory[NUMA], NUMA ← NEXT+1;
- NEXT ← Memory[NEXT], SUM ← SUM+X;

- Three different loop iterations active at once.
- Short cycle time (no dependencies within a cycle)
- full utilization (only 2 cycles per result)
- Initialization: x=0, numa=1, sum=0, next=memory[0]
- Extra control states (out of the loop)
 - one to initialize next, clear sum, set numa
 - one to finish off. 2 cycles after next==0.

5. Optimization, Architecture #4

- Datapath:

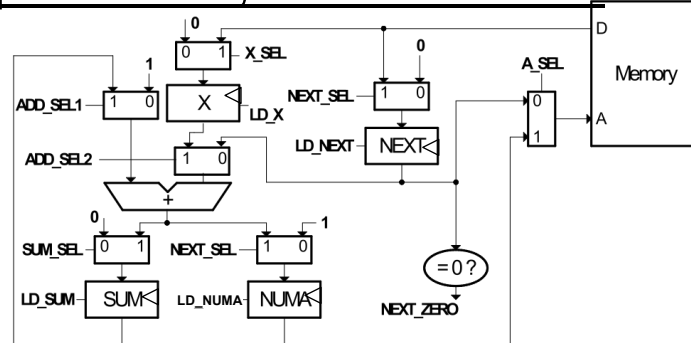

- Incremental cost:
 - Addition of another register & mux, adder mux, and control.
- Performance: find max time of the four actions
 - $X \leftarrow \text{Memory}[\text{NUMA}]$, $0.5 + 1 + 10 + 1 + 0.5 = 13\text{ns}$
 $\text{NUMA} \leftarrow \text{NEXT} + 1$; same for all $\rightarrow T > 13\text{ns}, F < 77\text{MHz}$
 - $\text{NEXT} \leftarrow \text{Memory}[\text{NEXT}]$,
 $\text{SUM} \leftarrow \text{SUM} + X$;

Fall 2013

EECS150 - Lec07-hld1

Page 17

Other Optimizations

- Node alignment restriction:
 - If the application of the list processor allows us to restrict the placement of nodes in memory so that they are aligned on even multiples of 2 bytes.
 - NUMA addition can be eliminated.
 - Controller supplies “0” for low-bit of memory address for NEXT, and “1” for X.
 - Furthermore, if we could use a memory with a 16-bit wide output, then could fetch entire node in one cycle:

$$\{\text{NEXT}, X\} \leftarrow \text{Memory}[\text{NEXT}], \text{SUM} \leftarrow \text{SUM} + X;$$

\rightarrow execution time cut in half (half as many cycles)

Spring 2012

EECS150 - Lec07-hld1


Page 18

List Processor Conclusions

- Through careful optimization:
 - clock frequency increased from 32MHz to 77MHz
 - little cost increase.
- “Scheduling” was used to overlap and to maximize use of resources.
- Questions:
 - Consider the design process we went through:
 - Could a computer program go from RTL description to circuits automatically?
 - Could a computer program derive the optimizations that we did?
 - It is the goal of “High-Level Synthesis” to do similar transformations and automatic mappings. “C-to-gates” compilers are an example.

Multiplier Example


Multiplication

 

*Many different circuits exist for multiplication.
Each one has a different balance between **speed** (performance) and amount of **logic** (cost).*

Array Multiplier

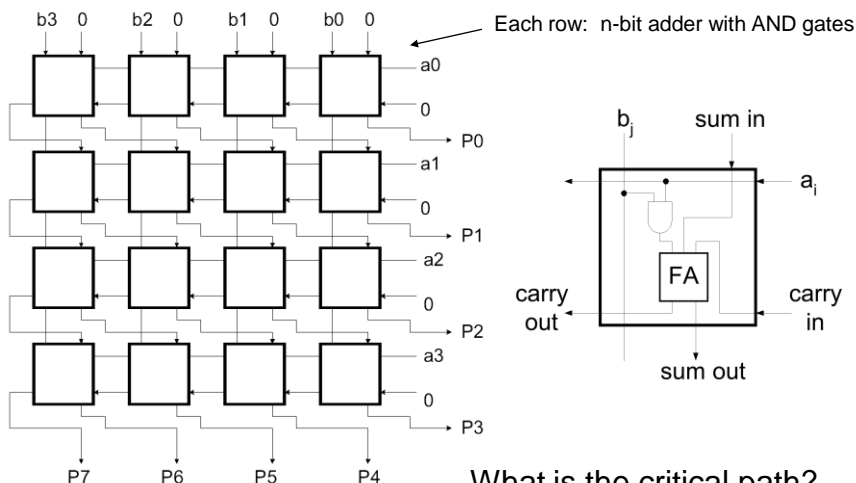
Single cycle multiply: Generates all n partial products simultaneously.



What is the critical path?

Bit-Serial Multiplier

 - Example, Bit-serial multiplier (n^2 cycles, one bit of result per n cycles):



- Control Algorithm:

```
repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}
```


Note: The occurrence of a control signal x means $x=1$. The absence of x means $x=0$.

Controller using Counters

- **State Transition Diagram:**


- Assume presence of two binary counters. An “i” counter for the outer loop and “j” counter for inner loop.
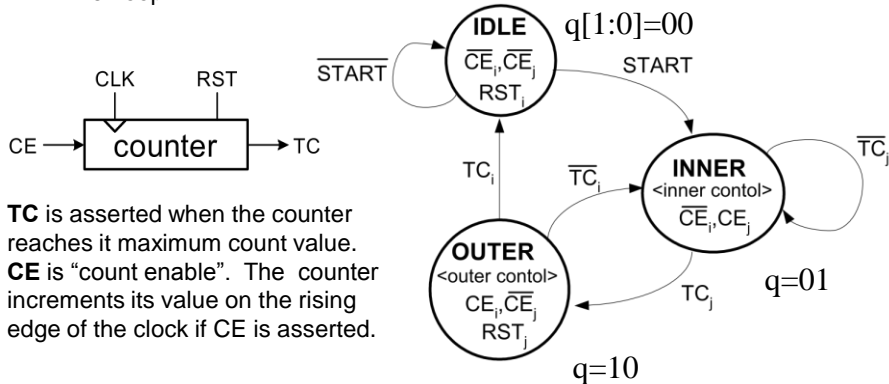
```
repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}
```



Controller using Counters

- **Controller circuit implementation:**

 

- **Outputs:**

$$\begin{aligned} CE_i &= q_2 \\ CE_j &= q_1 \\ RST_i &= q_0 \\ RST_j &= q_2 \end{aligned}$$

$$\begin{aligned} \text{shiftA} &= q_1 \\ \text{shiftB} &= q_2 \\ \text{shiftLOW} &= q_2 \\ \text{shiftHI} &= q_1 + q_2 \\ \text{reset} &= q_2 \\ \text{selectSUM} &= q_1 \end{aligned}$$

Fall 2013

EECS150 - Lec08-mult1

Page25

Conclusions

- List processor: scheduling of resources and minimizing combinational delay stages
- binary multiplier: full parallel vs complete serial