

EECS150 - Digital Design

Lecture 20 –Timing Part 1

Nov. 5, 2013

Prof. Ronald Fearing

Electrical Engineering and Computer
Sciences

University of California, Berkeley

(slides courtesy of Prof. John Wawrzynek)

<http://www-inst.eecs.berkeley.edu/~cs150>


Fall 2013

EECS150 - Lec20-Timing


Page 1

Recap and Outline

NAND gate:

 


Tri-state buffer

 

transmission gate
useful in
implementation

Latch Implementation:

 


Outline for Today

- Transmission gate, Latch
- CMOS delay


2

CMOS Logic Gates in General

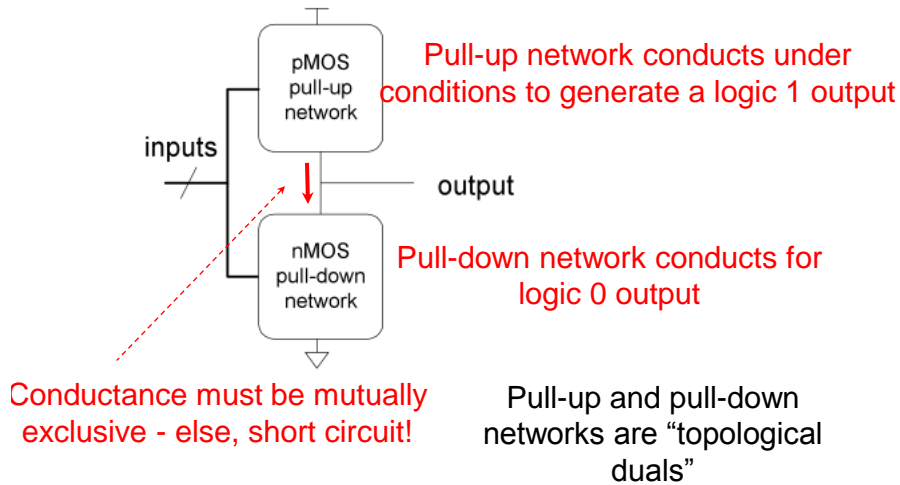

Transmission Gate

 
- Transmission gates are the way to build "switches" in CMOS.
- In general, both transistor types are needed:
 - nFET to pass zeros.
 - pFET to pass ones.
- The transmission gate is bi-directional (unlike logic gates).





- Does not directly connect to Vdd and GND, but can be combined with logic gates or buffers to simplify many logic structures.

Transmission-gate Multiplexor

2-to-multiplexor:
 $C = sa + s'b$

 


Switches simplify the implementation:

  

Compare the cost to logic gate implementation.


4-to-1 Transmission-gate Mux

 

- The series connection of pass-transistors in each branch effectively forms the AND of s1 and s0 (or their complement).
- Compare cost to logic gate implementation

Alternative 4-to-1 Multiplexor

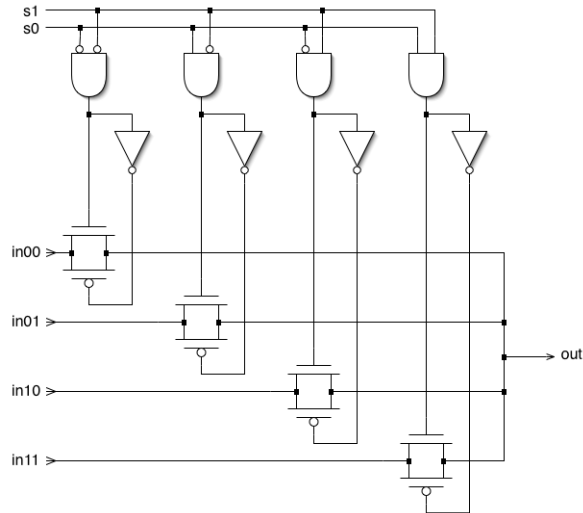- This version has less delay from in to out.
- In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).




Tri-state Buffers

Tri-state Buffer:


OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1

"high impedance" (output disconnected)


Variations:

 

Inverting buffer

 


Inverted enable

 


transmission gate useful in implementation

Tri-state Buffers

 


Tri-state buffers enable "bidirectional" connections.

 Tri-state buffers are used when multiple circuits all connect to a common wire. Only one circuit at a time is allowed to drive the bus. All others "disconnect" their outputs, but can "listen".





Tri-state Based Multiplexor


Multiplexor

 

If $s=1$ then $c=a'$


 
 


 Transistor Circuit for inverting multiplexor:




Latches and Flip-flops

Positive level-sensitive latch:

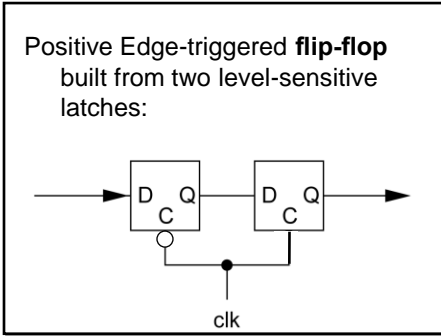  



Latch Implementation:

 



CMOS Delay: Transistors as water valves

If electrons are water molecules,
and a capacitor a bucket ...

  A "on" p-FET fills up the capacitor with charge.




A "on" n-FET empties the bucket.

  

This model is often good enough




Transistors as Conductors

- Improved Transistor Model: **nFET**

 

- We refer to transistor "strength" as the amount of current that flows for a given V_{ds} and V_{gs} .
- The strength is linearly proportional to the ratio of W/L .

pFET

   


Fall 2013

EECS150 - Lec20-timing1


Page₁₃

Gate Delay is the Result of Cascading

- Cascaded gates:

 

"transfer curve" for inverter.

 


In general:
prop. delay = sum of individual prop. delays of gates in series.

Fall 2013


EECS150 - Lec20-timing1

Page₁₄



Delay in Flip-flops

 

 - Setup time results from delay through *first* latch.



Clock to Q delay results from delay through *second* latch.

  


Fall 2013

EECS150 - Lec20-timing

Page 15

Wire Delay

 

- Ideally, wires behave as “transmission lines”:
 - signal wave-front moves close to the speed of light
 - $\sim 1\text{ft/ns}$
 - Time from source to destination is called the “transit time”.
 - In ICs most wires are short, and the transit times are relatively short compared to the clock period and can be ignored.
 - Not so on PC boards.

Fall 2013


EECS150 - Lec20-timing

Page 16

Wire Delay

- Even in those cases where the transmission line effect is negligible:

 - Wires possess distributed resistance and capacitance



- Time constant associated with distributed RC is proportional to the *square* of the length

- For **short wires** on ICs, resistance is insignificant (relative to effective R of transistors), but C is important.



- Typically around half of C of gate load is in the wires.

- For **long wires** on ICs:

- busses, clock lines, global control signal, etc.

- Resistance is significant, therefore distributed RC effect dominates.

- signals are typically “rebuffered” to reduce delay:

  


Fall 2013

EECS150 - Lec20-timing1

Page17

Delay and “Fan-out”

 


- The delay of a gate is proportional to its output capacitance. Connecting the output of a gate to more than one other gate increases its output capacitance. It takes increasingly longer for the output of a gate to reach the switching threshold of the gates it drives as we add more output connections.
- Driving wires also contributes to fan-out delay.
- What can be done to remedy this problem in large fan-out situations?

Fall 2013

EECS150 - Lec20-timing1

Page18

Components of Path Delay

 

1. # of levels of logic
2. Internal cell delay
3. wire delay
4. cell input capacitance
5. cell fanout
6. cell output drive strength

Fall 2013

EECS150 - Lec20-timing1

Page₁₉

Who controls the delay?

got here


	Silicon foundry engineer	Cell Library Developer, FPGA-chip designer	CAD Tools (logic synthesis, place and route	Designer (you)
1. # of levels			synthesis	RTL
2. Internal cell delay	physical parameters	cell topology, trans sizing	cell selection	
3. Wire delay	physical parameters		place & route	layout generator
4. Cell input capacitance	physical parameters	cell topology, trans sizing	cell selection	
5. Cell fanout			synthesis	RTL
6. Cell drive strength	physical parameters	transistor sizing	cell selection	instantiation (ASIC)

Fall 2013

EECS150 - Lec20-timing1

Page₂₀

Searching for processor critical path

 

Must consider all connected register pairs, paths from input to register, register to output. Don't forget the controller.

- Design tools help in the search.
- Synthesis tools report delays on paths,
- Special static timing analyzers accept a design netlist and report path delays,
- and, of course, simulators can be used to determine timing performance.

Tools that are expected to do something about the timing behavior (such as synthesizers), also include provisions for specifying input arrival times (relative to the clock), and output requirements (set-up times of next stage).

Fall 2013


EECS150 - Lec20-timing1

Page21

Real Stuff: Timing Analysis

The critical path

 Most paths have hundreds of picoseconds to spare.




From "The circuit and physical design of the POWER4 microprocessor", IBM J Res and Dev, 46:1, Jan 2002, J.D. Warnock et al.

Fall 2013

EECS150 - Lec20-timing1

Page22

Clock Skew

 


- Unequal delay in distribution of the clock signal to various parts of a circuit:
 - if not accounted for, can lead to erroneous behavior.
 - Comes about if:
 - clock wires have different delay,
 - circuit is designed with a different number of clock buffers from the clock source to the various clock loads, or
 - buffers have unequal delay.
 - All synchronous circuits experience some clock skew:
 - more of an issue for high-performance designs operating with very little extra time per clock cycle.

Fall 2013

EECS150 - Lec20-timing1

Page23

Clock Skew (cont.)

 


- If clock period $T = T_{CL} + T_{setup} + T_{clk \rightarrow Q}$, circuit will fail.
- Therefore:
 1. Control clock skew
 - a) Careful clock distribution. Equalize path delay from clock source to all clock loads by controlling wires delay and buffer delay.
 - b) don't "gate" clocks in a non-uniform way.
 2. $T \geq T_{CL} + T_{setup} + T_{clk \rightarrow Q} + \text{worst case skew. (setup time violation)}$
 3. Watch out for hold time violation (inputs from NSD change before clock)
- Most modern large high-performance chips (microprocessors) control end to end clock skew to a small fraction of the clock period.

Fall 2013

EECS150 - Lec20-timing1

Page24

Clock Skew (cont.)

 

- **Note reversed buffer.**
- In this case, clock skew actually provides *extra time* (adds to the effective clock period).
- **Watch out for hold time violation!** WB
- This effect has been used to help run circuits as higher clock rates. Risky business!


Fall 2013

EECS150 - Lec20-timing1


Page25

Real Stuff: Floorplanning Intel XScale

80200

 

Fall 2013

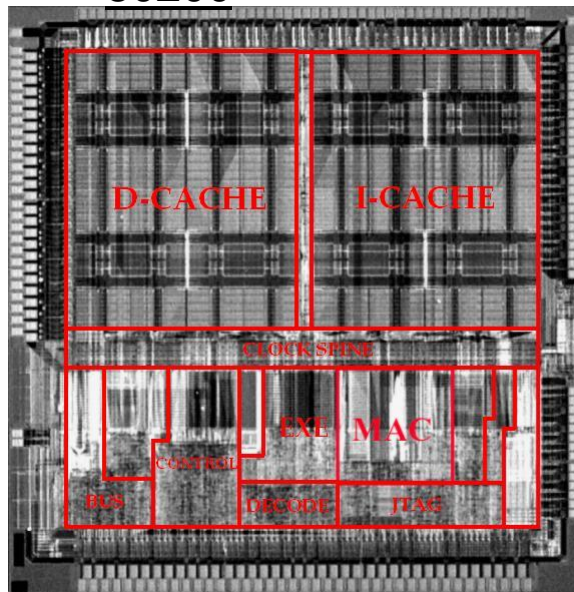

e26

Conclusions

- CMOS details – transmission gate, latch
- timing
- PLL